

G G 161190
BRENTFORD SQ
NEWS 878-1882
1 \$4.30

OCTOBER 1990

EVERYDAY ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY

£1.50

FREQUENCY METER/TACHO

Measures from 10Hz to 100kHz
plus rotating speed

FRIDGE ALERT

Keep your food at a safe
temperature

GHOST WAKER

A fun project for Halloween

ISSN 0262-3617



9 770262 361010

The No.1 Magazine for Electronic & Computer Projects



ONE POUND PACKS

All packs are £1 each. Note the figure on the extreme left of the pack ref number and the next figure is the quantity of items in the pack, finally a short description.

- BD2 5 13A spurs provide a fused outlet to a ring main where devices such as a clock must not be switched off.
- BD9 2 6V 1A mains transformers upright mounting with fixing clamps.
- BD13 12 30 watt reed switches, it's surprising what you can make with these—burglar alarms, secret switches, relay, etc., etc.
- BD22 2 25 watt loudspeaker two unit crossovers.
- BD30 2 Nicad constant current chargers adapt to charge almost any nicad battery.
- BD32 2 Humidity switches, as the air becomes damper the membrane stretches and operates a microswitch.
- BD42 5 13A rocker switch three tags so on/off, or change over with centre off.
- BD45 1 24hr time switch, ex-Electricity Board, automatically adjust for lengthening and shortening day, original cost £40 each.
- BD49 5 Neon valves, with series resistor, these make good night lights.
- BD56 1 Mini uniselector, one use is for an electric jigsaw puzzle, we give circuit diagram for this. One pulse into motor, moves switch through one pole.
- BD67 1 Suck or blow operated pressure switch, or it can be operated by any low pressure variation such as water level in water tanks.
- BD103A 1 6V 750mA power supply, nicely cased with mains input and 6V output leads.
- BD120 2 Stripper boards, each contains a 400V 2A bridge rectifier and 14 other diodes and rectifiers as well as dozens of condensers, etc.
- BD132 2 Plastic boxes approx 3in cube with square hole through top so ideal for interrupted beam switch.
- BD134 10 Motors for model aeroplanes, spin to start so needs no switch.
- BD137 1 6 1/2 inch 4 ohm speaker 10W rating.
- BD139 6 Microphone inserts—magnetic 400 ohm also act as speakers.
- BD148 4 Reed relay kits, you get 16 reed switches and 4 coil sets with notes on making c/o relays and other gadgets.
- BD149 6 Safety cover for 13A sockets—prevent those inquisitive little fingers getting nasty shocks.
- BD180 6 Neon indicators in panel mounting holders with lens.
- BD193 6 5 amp 3 pin flush mounting sockets make a low cost disco panel.
- BD199 1 Mains solenoid, very powerful, has 1in pull or could push if modified.
- BD201 8 Keyboard switches—made for computers but have many other applications.
- BD211 1 Electric clock, mains operated, put this in a box and you need never be late.
- BD221 5 12V alarms, make a noise about as loud as a car horn. Slightly soiled but OK.
- BD252 1 Panostat, controls output of boiling ring from simmer up boil.
- BD259 50 Leads with push-on 1/4in tags—a must for hook-ups—mains connections etc.
- BD263 2 Oblong push switches for bell or chimes, these can mains up to 5 amps so could be foot switch if fitted into pattress.
- BD268 1 Mini 1 watt amp for record player. Will also change speed of record player motor.
- BD305 1 Tubular dynamic mic with optional table rest.
- BD653 2 Miniature driver transformers. Ref. LT44. 20k to 1k centre tapped.
- BD548 2 3.5V relays each with 2 pairs changeover contacts.
- BD667 2 4.7 µF non-polarised block capacitors, pcb mounting.

There are over 1,000 items in our Catalogue. If you want a complete copy please request this when ordering.

METAL PROJECT BOX Ideal for battery charger, power supply etc. Sprayed grey size 8" x 4" x 4 1/2". Louvered for ventilation. Price £3.00. Ref. 3P75.

FLOPPY DISCS 5 1/4" pack of 10 £5.00. Ref. 168. 3 1/2" pack of 15 £10.00. Ref. 10P88.

PERSONAL STEREOS Again customer returns but complete and with stereo head phones. A bargain at only £3.00 each. Our ref. 3P83.

MICROWAVE CONTROL PANEL Mains operated, with touch switches. This unit has a 4 digit display with a built in clock and 2 relay outputs—one for power and one for pulsed power level. Could be used for all sorts of timer control applications. Only £6.00. Our ref. 6P18.

EQUIPMENT WALL MOUNT Multi adjustable metal bracket ideal for speakers, lights, etc. 2 for £5.00. Our ref. 5P152.

NEW MAINS MOTORS 25 watt 3000 rpm made by Franco. Approx 6" x 3" x 4". Priced at only £4.00 each. Our ref. 4P54.

SHADED POLE MOTORS Approx 3" square. Available in 24V and 240V AC. Both with threaded output shaft and 2 fixing bolts. Price is £2.00 each. 24V Ref. 2P65, 240V Ref. 2P66.

SUB-MIN TOGGLE SWITCH Body size 8mm x 4mm x 7mm. SBDT with chrome dolly fixing nuts. 3 for £1. Order ref. BD649.

COPPER CLAD PANEL for making PCB. Size approx 12in long x 8 1/2in wide. Double-sided on fireproof middle which is quite thick (about 1 1/2in) so this would support quite heavy components and could even form a chassis to hold a mains transformer, etc. Price £1 each. Our ref. BD683.

POWERFUL IONISER

Generates approx. 10 times more IONS than the ETI and similar circuits. Will refresh your home, office, workshop etc. Makes you feel better and work harder—a complete mains operated kit, case included. £18. Our ref. 18P2.

2KV 500 WATT MAINS TRANSFORMERS. Suitable for high voltage experiments or as a spare for a microwave oven etc. £10.00. Ref. 10P93.

REAL POWER AMPLIFIER for your car, it has 150 watts output. Frequency response 20hz to 20Khz and signal to noise ratio better than 60dB. Has built in short circuit protection and adjustable input level to suit your existing car stereo, so needs no pre-amp. Works into speakers ref. 30P7 described below. A real bargain at only £57.00. Order ref: 57P1.

REAL POWER CAR SPEAKERS. Stereo pair output 100W each. 40hm impedance and consisting of 6 1/2" woofer, 2" mid range and 1" tweeter. Ideal to work with the amplifier described above. Price per pair £30.00. Order ref: 30P7.

VIDEO TAPES These are three hour tapes of superior quality, made under licence from the famous JVC company. Offered at only £3 each. Our ref. 3P63. Or 5 for £11. Our ref. 11P3. Or for the really big user 10 for £20. Our ref. 20P20.



ELECTRONIC SPACESHIP.

Sound and impact controlled, responds to claps and shouts and reverses when it hits anything. Kit with really detailed instructions. Ideal present for budding young electrician. A youngster should be able to assemble but you may have to help with the soldering of the components on the pcb. Complete kit £10. Our ref. 10P81.

COMPUTER KEYBOARDS Brand new, uncased. £3.00 each. ref. 3P89.

12" HIGH RESOLUTION MONITOR. Amber screen, beautifully cased for free standing, needs only 12V 1.5 amp supply. TTL input separate syncs. Brand new in makers cartons. Price £22.00. Order ref. 22P2.

SINCLAIR C5 WHEELS

Including inner tubes and tyres. 13" and 16" diameter spoked poly carbonate wheels. Finished in black. Only £6.00 each. 13" Ref. 6P10, 16" Ref. 6P11.

COMPOSITE VIDEO KITS These convert composite video into separate H sync, V sync and video. Price £8.00. Our ref. 8P39.

LINEAR POWER SUPPLY Brand new +5 3A, +/-12V 1A. Complete with circuit diagram. Short circuit protected. Our price £12.00. Ref. 12P21.

3 1/2in FLOPPY DRIVES We still have two models in stock: Single sided, 80 track, by Chicon. This is in the manufacturers metal case with leads and IDC connectors. Price £40, reference 40P1. Also a double sided, 80 track, by NEC. This is uncased. Price £60.00, reference 60P2. Both are brand new.

10 MEMORY PUSHBUTTON TELEPHONES These are customer returns and "sold as seen". They are complete and may need slight attention. Price £6.00. Ref. 6P16 or 2 for £10.00. Ref. 10P77. BT approved.

INDUCTIVE PROXIMITY SWITCHES These will detect ferrous or nonferrous metals at approx. 10mm and are 10-36V operation. Ideal for alarms position sensors, etc. RS price is £64.00 each! Ours £12.00. Ref. 12P19.

BOSCHERT SWITCHED MODE POWER SUPPLIES -5V at 15A, -12V at 3A, -12V at 2A +24V at 2A, 220V or 110V input. Brand new and guaranteed. Retail price is £180! Ours £20. Ref. 20P30.

TV SOUND DECODER. Nicely cased, mains powered with 8 channels. Will drive a small speaker directly or could be fed into HI FI system etc. £12.00 each. Ref. 12P22.

PC POWER SUPPLIES Brand new with built in fan and power switch on the back -5, -5, -12, -12V. 150 watt made by AZTEC £25.00 each. Ref. 25P18.

VERY POWERFUL 12 VOLT MOTORS. 1/2d Horsepower. Made to drive the Sinclair C5 electric car but adaptable to power a go-kart, a mower, a rail car, model railway, etc. Brand new. Price £20. Our ref. 20P22.

AS ABOVE with gearbox. Phone for price and availability.

PHILIPS LASER

This is helium-neon and has a power rating of 2mW. Completely safe as long as you do not look directly into the beam when eye damage could result. Brand new, full spec. £35. Our ref. 35P1. Mains operated power supply for this tube gives 8kV striking and 1.25kV at 5mA running. Complete kit with case £15.

PANEL METERS 270 deg movement. New, £3.00 each. Our ref. 3P87.

SURFACE MOUNT KIT Makes a super high gain snooping amplifier on a PCB less than an inch square! £7.00. Our ref. 7P15.

CB CONVERTERS Converts a car radio into an AM CB receiver. £4.00. Our ref. 4P48.

GEIGER COUNTER KIT Includes PCB, tube, loudspeaker, and all components to build a 9v battery operated geiger counter. Only £39. Our ref. 39P1.

12V TO 220V INVERTER KIT This kit will convert 12V DC to 220V AC. It will supply up to 130 watts by using a larger transformer. As supplied it will handle about 15 watts. Price is £12. Our ref. 12P17.


SPECTRUM AND COMMODORE SOFTWARE Pack of 5 different tapes only £3.00. Ref. 3P96 for Spectrum and 3P97 for Commodore 64.

HIGH RESOLUTION MONITOR 9in black and white, used Philips tube M24/360W. Made up in a lacquered frame and has open sides. Made for use with OPD computer but suitable for most others. Brand new. £20. Our ref. 20P26.

12 VOLT BRUSHLESS FAN. Japanese made. The popular square shape (4 1/2in x 4 1/2in x 1 1/4in). The electronically run fans not only consume very little current but also they do not cause interference as the brush type motors do. Ideal for cooling computers, etc., or for a caravan. £8 each. Our ref. 8P26.

MINI MONO AMP on p.c.b. size 4" x 2" (app.)

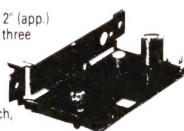Fitted Volume control. The amplifier has three transistors and we estimate the output to be 2W rms. More technical data will be included with the amp. Brand new, perfect condition, offered at the very low price of £1.15 each, or 13 for £12.00.



BULL ELECTRICAL

Dept. EE 250 PORTLAND ROAD, HOVE, BRIGHTON, SUSSEX BN3 5OT.



MAIL ORDER TERMS: Cash, PO or cheque with order. Monthly account orders accepted from schools and public companies. Please add £2.50 postage to orders. Minimum order £5. Phone (0273) 203500. Fax No. (0273) 23077.

POPULAR ITEMS

— MANY NEW THIS MONTH

MAINS FANS Snail type construction. Approx. 5" x 4" mounted on a metal plate for easy fixing. New. £5.00 each. Our ref. 5P166.

MICROWAVE TURNABLE MOTOR Complete with weight sensing electronics that would have varied the cooking time. Ideal for window displays, etc. Only £5.00. Our ref. 5P165.

JOYSTICKS for BBC, Atari, Dragon, Commodore, C64 only. All £5.00 each. All brand new, state which required.

PC STYLE CASES 18" X 18" X 6" Complete with fan and grill illuminated power switch and IEC filtered power input plug. Priced at only £15.00. Ref. 15P38.

SUB-MIN PUSH SWITCHES Not much bigger than a plastic transistor but double pole PCB mounting. 3 for £1.00. Our ref. BD688.

AA CELLS Probably the most popular of the rechargeable NICAD types. 4 for £4.00. Our ref. 4P44.

20 WATT 4 OHM SPEAKER With built in tweeter. Really well made unit which has the power and the quality for hifi 6 1/2". Price £5.00. Our ref. 5P155 or 10 for £40.00 ref. 40P7.

MINI RADIO MODULE Only 2in square with ferrite aerial and solid dia. tuner with own knob. It is superhet and operates from a P3 battery and would drive a crystal headphone. Price £1.00. Our ref. BD716.

BULGIN MAINS PLUG AND SOCKET The old and faithful 3 pin with screw terminals. The plug is panel mounted and the socket is cable mounted. 2 pairs for £1.00 or 4 plugs or 4 sockets for £1.00. Our ref. BD715, BD715P, or BD715S.

MICROPHONE Low cost hand held dynamic microphone with on/off switch in handle. Lead terminates in 1.5mm and 1.25mm plug. Only £1.00. Ref. BD711.

MOSFETS FOR POWER AMPLIFIERS AND HIGH CURRENT DEVICES 140V 100 watt pair made by Hitachi. Ref. 2SJ99 and its complement 2SK343. Only £4.00 a pair. Our ref. 4P51.

TIME AND TEMPERATURE LCD MODULE A 12 hour clock a Celsius and Fahrenheit thermometer a too hot alarm and a too cold alarm. Approx 50x20mm with 12.7mm digits. Requires 1AA battery and a few switches. Comes with full data and diagram. Price £9.00. Our ref. 9P5.

REMOTE TEMPERATURE PROBE FOR ABOVE. £3.00. Our ref. 3P60. PAPST fan 80 x 80mm 230V. Our ref. 9P7. Price £9.

PAPST fan 120 x 120mm 230V. Our ref. 6P6. Price £6.

600 WATT AIR OR LIQUID MAINS HEATER Small coil heater made for heating air or liquids. Will not corrode, lasts for years. Coil size 3" x 2" mounted on a metal plate for easy fixing. 4" dia. Price £P78 or 4 for £10.00. Our ref. 10P76.

EX-EQUIPMENT POWER SUPPLIES Various makes and specs, ideal bench supply. Only £8.00. Our ref. 8P36.

ACORN DATA RECORDER Made for the Electron or BBC computer but suitable for others. Includes mains adaptor, leads and book. £12.00. Ref. 12P15.

PTFE COATED SILVER PLATED CABLE 19 strands of .45mm copper will carry up to 30A and is virtually indestructible. Available in red or black. Regular price is over £120 per reel. Our price only £20.00 for 100m reel. Ref. 20P21 or 1 of each for £35.00. Ref. 35P2. Makes absolutely superb speaker cable!

NEW PIR SENSORS Infra red movement sensors will switch up to 1000W mains. UK made, 12 months manufacturers warranty, 15-20m range with a 0-10min timer, adjustable wall bracket. Our ref. 25P16. Price £25.

GEARBOX KITS Ideal for models, etc. Contains 18 gears (2 of each size), 4 x 50mm axles and a powerful adjustable speed motor. 9-12V operation. All the gears, etc. are 2mm push fit. £3.00 for the complete kit. Ref. 3P93.

MINI HIFI SPEAKERS Made for televisions, etc. Two sizes available. 70mm x 57mm 3W 8 ohm, 2 for £3.00. Ref. 3P99. 127mm x 57mm 5W 8 ohm, 2 for £3.00. Ref. 3P100.

BBC JOYSTICK INTERFACE Converts a BBC joystick port to an Atari type port. Price £2.00. Our ref. 2P261.

TELEPHONE EXTENSION LEAD 5m phone extension lead with plug on one end, socket on the other. White. Price £3.00. Our ref. 3P70 or 10 leads for only £19.00! Ref. 19P2.

LCD DISPLAY 4 1/2" digits supplied with connection data £3.00. Ref. 3P77 or 5 for £10. Ref. 10P78.

CROSS OVER NETWORK 8 Ohm 3 way for tweeter midrange and woofer nicely cased with connections marked. Only £2.00. Our ref. 2P255 or 10 for £15.00. Ref. 15P32.

BASE STATION MICROPHONE Top quality uni-directional electret condenser mic 600 impedance sensitivity 16-18KHz - 68db built in chime complete with mic stand bracket. £15.00. Ref. 15P28.

MICROPHONE STAND Very heavy chrome mic stand, magnetic base 4" high. £3.00 if ordered with above mic. Our ref. 3P80.

SOLAR POWERED NICAD CHARGER 4 Nicad AA battery charger. Charges 4 batteries in 8 hours. Price £6.00. Our ref. 6P3.

YUASHA SEALED LEAD ACID BATTERIES. 6V 10AH only £9.00 each or 2 for £15.00. Ref. 15P37.

STC SWITCHED MODE POWER SUPPLY. 220V or 110V operation giving 5V at 2A +24V at 0.25A -12V at 0.15A and +90V at 0.4A £12.00 each. Ref. 12P27.

SOLDERING IRON STAND Price £3.00. Our ref. 3P66.

INCAR GRAPHIC EQUALIZER/BOOSTER Sillimline 7 band with built in 30 watts per channel amplifier. 12V operation, twin 5 LED power indicators, 20-21KHz with front and rear fader plus headphone output! Brand new and guaranteed. Only £25.00. Ref. 25P14.

CENTRONICS ADAPTER KIT Converts plotter/printer to Centronics compatible. Price £4.00. Our ref. 4P57.

CAR IONIZER KIT Improve the air in your car, clears smoke and helps prevent fatigue. Case req. Price £12.00. Our ref. 12P8.

NEW FM BUG KIT New design with PCB embedded coil 9v operation. Priced at £5.00. Our ref. 5P158.

NEW PANEL METERS 500A movement with three different scales that are brought into view with a lever. Price only £3.00. Ref. 3P81.

STROBE LIGHTS Fit a standard edison screw light fitting 240V 40/min. flash rate available in yellow, blue, green and red. Complete with socket. Price £10 each. Ref. 10P80 (state colour required).

ELECTRONIC SPEED CONTROL KIT Suitable for controlling our powerful 12v motors. Price £17.00. Ref. 17P3 (heatsink required).

EXTENSION CABLE WITH A DIFFERENCE It is flat on one side making it easy to fix and look tidy. 4 core, suitable for alarms, phones etc. Our price only £5.00 for 50m reel. Ref. 5P153.

1990 CATALOGUE NOW AVAILABLE PLEASE SEND 6" X 9" SAE FOR FREE COPY

EVERYDAY ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY

ABC




MEMBER OF THE ASSOCIATION OF ELECTRONIC PUBLISHERS

VOL. 19 No. 10 OCTOBER 1990

The No 1 Magazine for Electronic & Computer Projects

ISBN 0262 3617

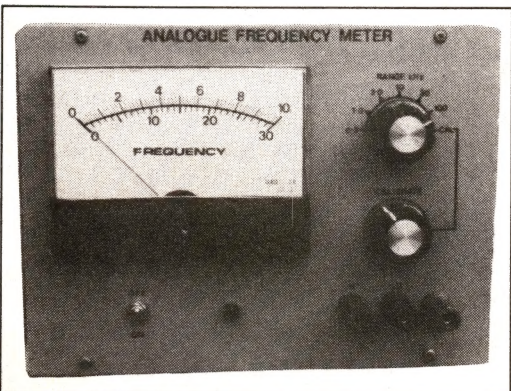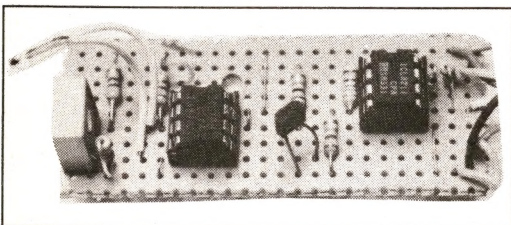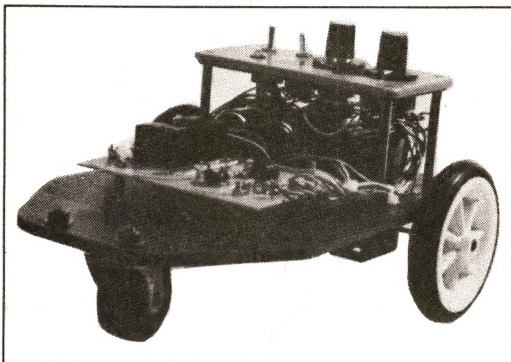PROJECTS... THEORY... NEWS...
COMMENT... POPULAR FEATURES...



Projects

- FREQUENCY METER/TACHOMETER** by Steve Knight **636**
Measures from 10Hz to 100kHz, inexpensive and accurate
- GHOST WAKER** by Max Horsey **642**
Even the "Ghost Busters" will be impressed
- MOBILE LINE TRACKER** by Chris Walker **659**
Keep on the straight and narrow or drive right around the bend
- FRIDGE ALERT** by T. R. de Vaux Balbirnie **670**
Ensure the correct environment for your food, not germs
- CAR HEATER THERMOSTAT** by T. R. de Vaux-Balbirnie **680**
You will never get hot under the collar if you install this unit!

Series

- ON SPEC** by Mike Tooley **647**
The last of the series for Spectrum owners
- MICRO IN CONTROL - 11** by John Hughes **652**
Software development
- BBC MICRO** by Robert Penfold **664**
Object Counting - Infra-Red Detector
- AMATEUR RADIO** by Tony Smith G4FA1 **668**
Novice Licence Update; WW2 Amateur Operations; Introduction to VHF/UHF; Scanners
- INTERFACING THE RML NIMBUS - 2**
by Andrew Channerley **674**
We take a look at the Nimbus and its BBC-type parallel card
- ROBOT ROUNDUP** by Nigel Clark **684**
Annual review of the products available for robotics enthusiasts

Features

- EDITORIAL** **635**
- FOR YOUR ENTERTAINMENT** by Barry Fox **650**
Musical Notes; Play Time; Power Cut; Off-Side, Divine Act
- SHOP TALK** with David Barrington **665**
Product news and component buying for projects
- ACTUALLY DOING IT** by Robert Penfold **666**
Project wiring
- FIBRES AND OPTOELECTRONICS** by Mike Tooley **686**
Review of an Open Learning package
- DIRECT BOOK SERVICE** **688**
Selected technical books by mail order
- PRINTED CIRCUIT BOARD SERVICE** **692**
P.C.B.s for EE projects
- ADVERTISER'S INDEX** **696**

FREE WITH THIS ISSUE

Marco Trading 1991 catalogue, banded to all copies

© Wimborne Publishing Ltd 1990. Copyright in all drawings, photographs and articles published in **EVERYDAY ELECTRONICS** is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our November '90 issue will be published on Friday, 5 October 1990. See page 627 for details.

Readers Service • Editorial and Advertisement Departments **635**

FINAL CLEARANCE

OUR SALE IS

ALMOST OVER – BUT YOU'VE JUST ONE MORE
CHANCE TO BUY AT UNBELIEVABLE PRICES!
ALL ITEMS LISTED BELOW ARE FINAL REDUCTIONS!
FROM PREVIOUS SALE PRICES!! SALE MUST END
28TH SEPT!! ALL GOODS SHOWN IN DETAIL IN OUR 16-PAGE
SALE SUPPLEMENT – FREE ON REQUEST!!

**KEYBOARD
PARCEL 1**
ANY 5 FOR
£25.00

**KEYBOARD
PARCEL 2**
OUR SELECTION OF
10 ASSTD.
£30.00

**DUAL
SHEET
FEEDER**
3 FOR
£25.00

DATABOXES
ANY 5 OF
RD 13.3, 14.3, 31.4, 32.3,
32.4, 41.2, 51.2
(Give alternatives, nearest available
will be supplied)
£25.00

SWITCH MODE PSU.
ASTEC AA12531
PARCEL OF 5
FOR JUST
£20.00

**SOUNDER
PARCEL**
PACK OF 10
NOW REDUCED TO
£6.00

BURGLAR ALARM
SB17 (page 110 of cat)
ORIGINALLY £2.50
TO CLEAR:

5 FOR £5

**BBC 'B' MUSIC
SOFTWARE**
1 Each of Music Master,
Mupados Recorder Tutor
& Micro Maestro
ORIGINALLY £101.00!!

NOW ONLY £9.00
FOR ALL THREE!!

**SWITCH MODE
PSU'S**
1) 5V 6A 2) 5V 10A
3) ASTEC AA12531
ALL 3 FOR £15!
JUST ARRIVED! – Big parcel
of Semi's – LS from 4p,
T's 1½p, 5V 5A Regs £1.50.
ASK FOR FREE LIST!!

**FREE EASIWIRE KIT WITH ALL SALE
ORDERS OVER**

GREENWELD

**ELECTRONIC
COMPONENTS**

**27D PARK ROAD
SOUTHAMPTON SO1 3TB**

**Tel: (0703) 236363
Fax: (0703) 236307**

£20
MIN ORDER
£10 + P&P
£3 per order
(UK/BFPO ONLY)
ALL PRICES INCLUDE VAT

THE EE MUSKETEER

"One for all and all for one"

A complete home entertainment controller in ONE handheld unit!

If you own a television set, video cassette recorder, midi hi-fi unit, graphic equaliser, satellite TV decoder etc., then you probably have a small arsenal of remote control units as well! What would you say to a single device which could replace up to four separate controllers whilst retaining all the commands of each one?

The EE Musketeer will do this, so you only need one controller on the armchair.



FREE WITH THIS
1990 GREENWELD ISSUE OF EE
ELECTRONIC COMPONENTS CATALOGUE
132 PAGES OF **WORTH £1.50**
BARGAINS

A special
FREE EASIWIRE
offer is included for
EE readers

IN-LINE DIMMER

As well as adding a touch of luxury, a dimmer saves energy and greatly extends the life of the bulb. This circuit acts as an in-line switch as fitted to many types of table lamp. Built in a small plastic box it provides full-power operation plus three levels of dimming using two rocker switches. The In-Line Dimmer may be used to control all filament bulbs up to 250 watts rating used on a.c. mains supplies.

CYCLE REAR LIGHT MONITOR

Riding a bicycle at night is a hazard especially if the lights are not working properly. This circuit monitors the efficiency of the rear light and signals the rider with a pulsed high-pitched tone if a fault develops.

EVERYDAY ELECTRONICS

NOVEMBER ISSUE ON SALE FRIDAY 5TH OCTOBER 1990

We deliver from stock - The fastest way to order is a fax !


ULTRASONIC CAR ALARM



Complete kit including case
44.367BKL £ 30.40

This system is specially designed to protect your car and its contents against potential thieves. Low current consumption and high noise immunity are just two of its distinguishing features. In addition the system has a voltage sensing device i.e. the alarm is also triggered if appliances are switched on by an unauthorised person (e.g. the interior lighting when the door is opened).

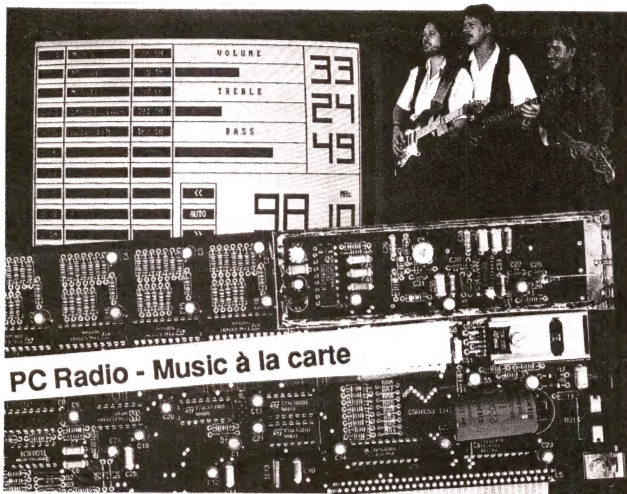PC Radio (Elektor Electronics February 1990)



Specification

Input sensitivity:

Input 1 : 2 mV
Input 2 : 200 mV

Dealy Time:

variable from 60 ms to 1 s

Bandwidth :

100 Hz to 12 kHz

Additional features:

- inputs mixable
- single and multiple echo
- adjustable delay level
- switchable vibrator
- switch-controlled noise suppression

This FM radio consists of an insertion card for IBM PC-XTs, ATs and compatibles and is available as a kit or a ready-built and aligned unit. The radio has an on-board AF power amplifier for driving a loudspeaker or a headphone set, and is powered by the computer. A menu-driven program is supplied to control the radio settings.

Complete kit
44.544BKL £ 82.75

Ready assembled module
44.544F £ 137.30

VM 1000 Video-Modulator

(Elektor Electronics March 90)



Many inexpensive or older TV sets lack a SCART or other composite video input, and can only be connected to a video recorder or other equipment via an RF modulator. The modulator operates at a UHF TV channel between 30 and 40. Use is made of a single-chip RF modulator that couples low cost to excellent sound and picture quality.

Complete kit
44.546BKL £ 36.90

Ordering and payment:

- all prices excluding V.A.T. (French customers add 18.6%T.V.A.)
- send Euro-cheque, Bank Draft or Visa card number with order. Please add £ 3.00 for p & p (up to 2 kg total weight)
- postage charged at cost at higher weight Air/Surface -
- we deliver worldwide except USA and Canada
- dealer inquiries welcome

RFK 700 RGB-CVBS Converter

(Elektor Electronics October 89)

Nearly all computers supply as an output signal for colour monitors RGB signals. With the help of the RFK 7000 it is possible to record this signals with a videorecorder or to give them onto a colour TV (This is only possible, if the

computer delivers a vertical sync. of 50 Hz and a horizontal sync. of 15.625 Hz). The voltage supply is gained from a 12V/300mA-DC voltage mains adaptor.

Complete kit
44.525BKL £ 66.50


Ready assembled module
44.525F £ 119.50

FRK 7000 CVBS-RGB Converter

With the help of the FRK 7000 e.g. it is possible to use a cheap clour monitor with RGB input on a video recorder. The voltage supply is gained from a 12V/300mA-DC voltage mains adaptor.


Complete kit
44.509BKL £ 66.50

Ready assembled module
44.509F £ 119.50

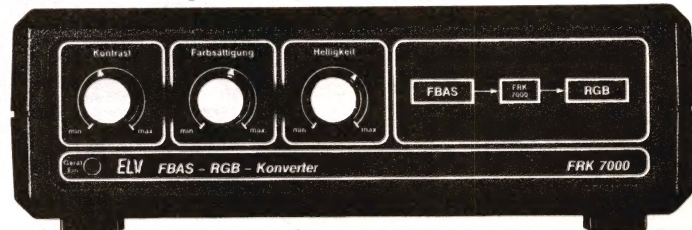

LPS 8000 / LC 7000 Low Cost Show Laser

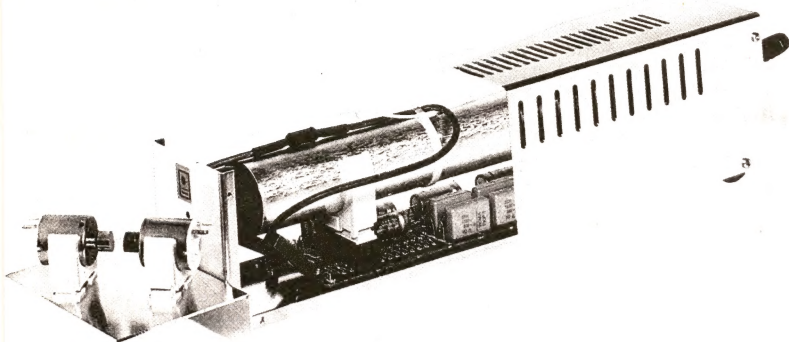(Electronics The Maplin Magazine Dec 88 + Feb-Mar 90)



An almost infinite number of circular patterns can be projected onto a wall or ceiling with this super laser show equipment.

The complete project includes a laser tube and accompanying power supply, housed in a metal case, and a laser controller, LC 7000. The laser controller drives the accompanying deflection unit, fixed onto the laser power supply case, which produces the numerous configurations.

Naturally the laser tube, together with the power supply, can produce beams without the laser controller and the controller can be used with other, similar lasers.

LPS 8000 Laser Power Supply, complete kit

Version 240 Volts AC	
44.428BKL220	£ 86.90
Version 220 Volts AC	
44.428BKL240	£ 86.90

LC 7000 Laser Controller, complete kit

Version 12 Volts DC	
44.427BKL	£ 60.80

H-N Laser Tube 2 mW

44.428LR	£ 60.80
----------------	---------

LPS 8000 Laser Power Supply, ready assembled module

Version 240 Volts AC	
44.428F240	£ 156.50
Version 220 Volts AC	
44.428F220	£ 156.50

LC 7000 Laser Controller, ready assembled module

Version 12 Volts DC	
44.427F	£ 104.30

Laser Motor-Mirror Set, complete kit


44.506M	£ 22.95
---------------	---------

VIDEO RECORDING AMPLIFIER

(Elektor Electronics April 89)

Losses can easily occur when copying video tapes resulting in a distinct reduction in quality. By using this video recording amplifier, with no less than four (!) outputs, the modulation range is enlarged and the contrast range of the copy increases.

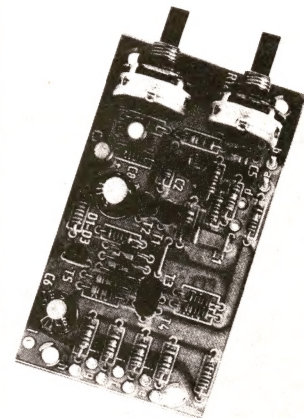Two level controllers for edge definition (contour) and amplification (contrast range) allow individual and precise adaptation.



Complete Kit


(including Box, PCB and all parts)

44.324BKL	£ 14.75
-----------------	---------

IBM PC Service Card

(Elektor Electronics May 1990)

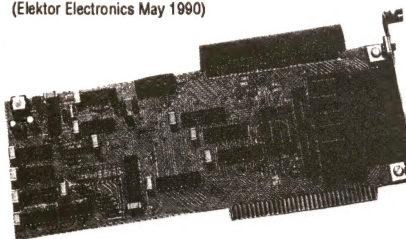This card was developed for assistance in the field of service, development and test. The card is used as a bus-extension to reach the measurement points very easy. It is also possible to change cards without having a "hanging computer".



Complete kit

44.517BKL	£ 77.95
-----------------	---------

Ready assembled module

44.517F	£ 137.95
---------------	----------

TA 1000 Telephone Answering Unit

(Elektor Electronics January 1990)


This automatical telephone answering unit uses a 256-kbit voice recording circuit to store and replay your spoken message of up to 15 seconds. Noteworthy features are that it is available as a complete kit, provides a battery back-up facility and does not require alignment. No provision is made, however, to record incoming calls.

Complete kit

44.433BKL	£ 45.65
-----------------	---------

Ready assembled module

44.433F	£ 87.25
---------------	---------

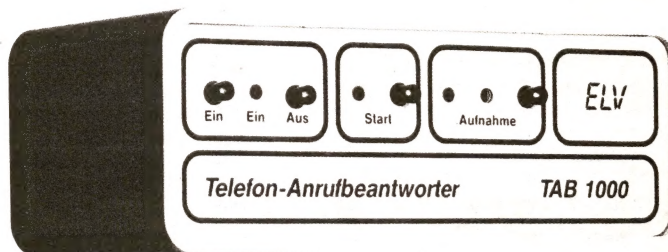


IC TESTER for IBM-PC-XT/AT

(Electronics The Maplin Magazine Jun-Jul 89 +

Elektor Electronics December 89)

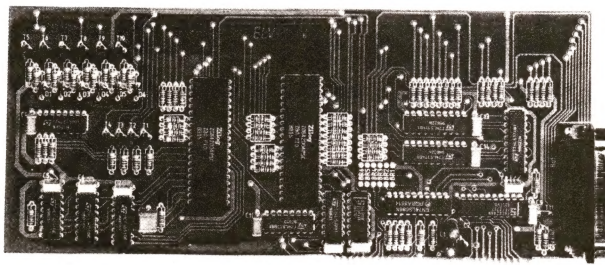With the ELV IC tester logic function tests can be carried out on nearly all CMOS and TTL standard components, accommodated in DIL packages up to 20 pin. The tester is designed as an insertion card for IBM-PC-XT/AT and compatibles. A small ZIF test socket PCB is connected via a flat band cable. Over 500 standard components can be tested using the accompanying comprehensive test software.



Complete Kit including Textool socket, connectors, sockets, Flat band cable, PCB, Software

44.474BKL	£ 60.85
-----------------	---------

Ready Assembled Module

4.474F	£ 113.00
--------------	----------

Software, single

44.474SW	£ 17.85
----------------	---------

HIGH GRADE COMPONENT PARCELS

**EVERYTHING
MUST
GO!**

SEMI CONDUCTORS

What a selection! Every single parcel will contain: ICs, signal diodes, rectifiers, zeners, semiconductor VDRs, transistors, FETs, high voltage transistors, power transistors, triacs, voltage regulators, and a good deal more. Did I mention the varicap tuning diodes? The VHF transistors? The Schottky rectifiers? All the semiconductors you've ever wanted, but could never afford. This has to be one of the finest parcels we have ever offered. Don't miss it!

PARCEL 9A:
200 SEMICONDUCTORS
for £10! + VAT

PARCEL 9B:
1000 SEMICONDUCTORS
for £40! + VAT

PRESETS

An attractive and very functional pack of preset pots. The parcels contain a high proportion of top quality cermet, both single and multi-turn. In fact they outnumber the carbon types! All styles and types are represented: open, enclosed, vertical, horizontal, square, round, 3/4" and 1 1/4" multi-turns, and so on. All values from a few ohms to several megs.

PARCEL 11A:
200 PRESETS for £6 + VAT

PARCEL 11B:
1000 PRESETS for £25 + VAT

SWITCHES

Take a rocker switch in one hand, a roller microswitch in the other, and have yourself a rock 'n' roll party! OK, the the jokes aren't up to much, but the switches are superb. Lots of rocker switches – ideal as spares for household gadgets. Some, so I'm told, fit the dashboard cut-outs on Ford cars, so just think of the extra lights and stuff you could fit! Then there are the toggles, the push switches, the rotaries and the sliders. All tucked up snugly, bless their cotton socks, in our switch parcels. And all for 10p each or less – it's enough to make you explode with joy. Well, nearly enough.

**PARCEL 14A: 100 ASSORTED
SWITCHES for £10! + VAT**

**PARCEL 14B: 300
ASSORTED
SWITCHES
for £25! +
VAT**

MONSTER OPTO PARCELS

If it has anything to do with light, it's in here. There are LEDs of all shapes, sizes and colours, seven segment displays, infra-red senders and receivers, bar graph assemblies, opto switches, and who knows what else. The larger parcels have LCDs too. An excellent selection of top quality devices.

PARCEL 12A:
100 OPTO DEVICES for £10 + VAT

PARCEL 12B:
300 OPTO DEVICES
for £25 + VAT

H.V. POLYESTERS

Above 100n or so the price of non-electrolytic caps starts to rise steeply. To get one above 1µF will cost the earth, or at least a major planet. And not even an asteroid for change. These parcels contain caps to at least 4µF. Replace those nasty non-polar electrolytics in your speaker crossovers, connect them across electrolytic smoothing and coupling caps in your hi-fi, stop using back-to-back tants in your projects. The larger caps will easily cost several ££s each from normal suppliers. We've got too many, so...

PARCEL 15A:
200 HV POLYESTERS
for £10 + VAT

PARCEL 15B:
600 HV POLYESTERS
for £25 + VAT

Unless otherwise stated, all the clearance parcels we offer contain brand new, top grade components. If some of the offers look too good to be true, all I can say is that the optimists will get some stunning bargains, the cynics will never know what they've missed, so everybody will be happy! All offers apply only while current stocks last – watch out for next month's parcels or, better still, be the first to hear about any new offers by putting your name on our mailing list.

CONNECTORS

If you ever again need to connect anything to anything else, the chances are you'll find the plugs and sockets for it in this parcel. Computers?

There are D connectors, printer connectors, RS232 connectors, and so on. PCBs? There are edge connectors and pin connectors. RF connectors?

No problem. Audio? There are speaker plugs and sockets, DIN connectors and much more. And all for 10p or less apiece! How can you resist it?

PARCEL 10A:
100 ASSORTED CONNECTORS for £10! + VAT

PARCEL 10B:
300 ASSORTED CONNECTORS
for £25! + VAT

RESISTORS

Supplied to you as they arrive with us: some bagged, some bandoliered, some reeled, some loose. The mixture has 1/4W resistors in every single E12 value, with some E24 and an assortment of E96 precision types. Then there are 1/2W

resistors and a nice selection of power types to 5W and above. The proportions vary from parcel to parcel, but you'll certainly have an excellent range of types and values.

I have absolutely no intention of counting out tens of thousands of resistors, so these are sold by weight. As a rough guide 1000 1/4W resistors weigh about 240g, so there are over 4000 of these to the Kg.

PARCEL 13A:
10Kg RESISTOR
PARCEL £30
+ VAT

JUNK!

Bits of equipment, PCBs, components, hardware, mags, books, data, everything electronic turns up at some time or other in our legendary JUNK parcels.

There's so much unsorted stuff around the place we hardly know what goes in there ourselves! The components won't be neatly packed – once we've combed their hair and dressed them in their Sunday best, they go onto one of lists. In the JUNK parcel you see them in the raw state.

The first 10Kg is yours for £18 + VAT. After that, the price is £1 per Kg, so 11Kg will be £19 + VAT, 12Kg will be £20 + VAT, and so on. Have as much as you like!

JUNK SPECIAL:
1 cwt for £50!
+ VAT

UK Orders:

Please add £2.50 towards postage and packing and 15% VAT to the total

Europe and Eire:

Please add £6.00 carriage and insurance. No VAT

Outside Europe:

Please add £12.00 carriage and insurance. No VAT

HIGHGRADE COMPONENTS LTD

Unit 111, 8 Woburn Road, Eastville, Bristol BS5 6TT
Tel: 0600 3715 Fax: 0600 72262

H5

RTVC HAVE DONE IT AGAIN!

We have secured all stocks of nearly new factory refurbished car stereos, manufacturer approved, at unrepeatable prices. We also offer a 6 month guarantee with all units (this only applies to products marked ★ on this page)



Alba digital auto reverse push button AM/FM / LW car stereo with separate bass/treble control APPSS on tape. 25 watts per channel output, with line output for car components use.

★£79.40 + £2.30 pp



Sparkomatic Phoenix Digital auto reverse AM/FM/LW car stereo, with tape volume and balance control. 9 watts output per channel


★£52.40 + £2.80 pp



Sparkomatic Auto reverse AM/FM car stereo with tone, volume and balance control

★£44.20 + £2.80 pp

IN-CAR STEREO BOOSTERS

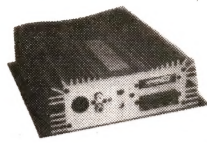

In-Car Stereo Hi-power booster amplifiers. 300W output. 150W x 2 inputs for low power car stereos and phono inputs short circuit protection

£94.95 + £2 pp



150W output 75 x 2 inputs above

£43.00

+ £2.00 pp

IN CAR WOOFERS

6 1/2" 40W Nominal, 60W Max, 4 ohm Goodman's woofer.

£9.95 + £1.90 pp

8" 60W Nom. 90W Max, 4-5 ohm Richard Allen woofer

£33.80 + £3.50 pp

10" 100W Nom. 150W Max 4-5, ohm Richard Allen woofer

£41.50 + £3.50 pp

12" 100W Nom. 250W Max, 4-5 ohm Richard Allen woofer

£43.50 + £4 pp

15" 100W Nom. 250W Max, 4-5 ohm Richard Allen woofer

£79.35 + £5 pp

TWEETERS AND MID RANGE FOR IN-CAR USE

4 1/2" 100W 4-5 ohm sealed back mid range. Goodman

£5.50 + £1.50 pp

2 1/4" 65W 4-5 ohm Ferro fluid cooled dome tweeter with housing. Audax

£5.00 + £1.20 pp

3 1/2" 100W 8 ohm Ferro fluid cooled dome tweeter for 4-8 ohm use

£8.95 + £1.20 pp

ACOUSTIC REAR PARCEL SHELF

To get the best sound from your car woofers, replace your rear hatchback parcel shelf with one of these 18mm thick fibreboard units, tailor made for your car, supplied with grille cloth and fixings. When ordering please state make, model, and year of reg.

£39.80 + £6 pp

ROSS PUSH BUTTON RADIO

Mains and battery operated.

High quality VHF/FM,

Medium and Long Wave reception.

6 pushbutton selected

preset stations

Fully retractable telescopic

aerial.

Headphone/earphone

jack socket.

Size 230H x 150W x 65D

Ref RE-5500

Brand new.

Listed price over £30.00

£14.95 + £2.80 pp



MAIL ORDER £1 BARGAIN PACKS BUY 20 GET 1 FREE

Please state pack(s) required

No.	Qty.	per pack
BP015B	1	30W dome tweeter. Size 90x66mil JAPAN made
BP016	6	2200µf can type Electrolytic 25V d.c. computer grade made in UK by PHILIPS
BP017	3	33000µf 16V d.c. electrolytic high quality computer grade UK made
BP019	20	20 ceramic trimmers
BP020	4	Tuning capacitors. 2 gang dielectric a.m. type
BP021	10	3 position, 8 tag slide switch 3 amp rated 125V a.c. made in USA
BP022	5	Push-button switches, push on push off, 2 pole change over. PC mount JAPAN made
BP023	6	2 pole 2 way rotary switch
BP024	2	Right angle, PCB mounting rotary switch, 4 pole, 3 way rotary switch UK made by LORLIN
BP025	4	3 pole, 3 way miniature rotary switch with one extra position off (open frame YAXLEY type)
BP026	4	4 pole, 2 way rotary switch UK made by LORLIN
BP027	30	Mixed control knobs
BP029	6	Stereo rotary potentiometers
BP030	2	10k wire wound double precision potentiometers UK made
BP031	6	Single 100k multitune pots, ideal for varicap tuners UK made by PHILIPS
BP032	4	UHF varicap tuner heads, unboxed and untested UK made by PHILIPS
BP033	2	FM stereo decoder modules with diagram UK made by PHILIPS
BP033A	4	6"x3/4" High grade Ferrite rod. UK made
BP034	3	AM IF modules with diagram PHILIPS UK made
BP034A	2	AM-FM tuner head modules. UK made by Mullard
BP034B	1	Hi-Fi stereo pre-amp module inputs for CD, tuner tape, magnetic cartridge with diagram.
BP035	6	All metal co-axial aerial plugs
BP036	6	Fuse holders, panel mounting 20mm type
BP037	6	In line fuse holders 20mm type UK made by BULGIN
BP038	20	5 pin din, 180° chassis socket
BP039	6	Double phono sockets, Paxolin mounted
BP041	3	2.8m lengths of 3 core 5 amp mains flex
BP042	2	Large VU meters JAPAN made
BP043	30	4V miniature bulbs, wire ended, new untested
BP044	2	Sonotone stereo crystal cartridge with 78 and LP styli JAPAN made
BP045A	2	Mono Cassette Record and play heads
BP046A	2	606 Mains transformers, PCB mounting. Size 42x33x35
BP047	1	24V 0.3VA mains power supply. Brand new boxed UK made by MULLARD
BP047A	1	25V DC 150mA mains adaptor in black plastic case with flying input and output leads new units made for famous sound mixer manufacturer. Size 80x55x47
BP049	10	OC44 transistors. Remove paint from top and it becomes a photo-electric cell (ORP 12) UK made by MULLARD
BP050	30	Low signal transistors n.p.n., p.n.p. types
BP051	6	14 watt output transistors. 3 complimentary pairs in T066 case (ideal replacement for AD161 and 162s)
BP052A	1	Tape deck pre-amp IC with record/replay switching No LM1818 with diagram
BP053	5	5 watt audio ICs. No TBA800 (ATEZ)
BP054	10	Motor speed control ICs, as used with most cassette and record player motors
BP055	1	Digital DVM meter I.C. made by PLESSEY as used by THANDAR with diagram
BP056	4	7 segment 0.3 LED display (red)
BP057	8	Bridge rectifiers, 1 amp, 24V
BP058	200	Assorted carbon resistors
BP059	1	Power supply PCB with 30V 4VIA transformer. MC7818CT IC & bridge rectifier. Size 4"x2 3/4"
BP061	5	6.35mm Mono jack plugs
BP063	5	6.35mm stereo switched jack sockets
BP064	12	Coax chassis mount sockets
BP065	1	3mtr Euro-mains lead with chassis socket

MULTIBAND RADIO

VHF 54-176 MHz + AM CB BANDS 1-80

Listen to: AIR TRAFFIC CONTROL,

AIRCRAFT, RADAR

PUBLIC UTILITIES

RADIO AMATEURS AND

MANY MANY MORE

£17.95

POSTAGE


£2.85

SQUELCH CONTROL

"RUBBER DUCK AERIAL"



HAND HELD WALKIE TALKIES

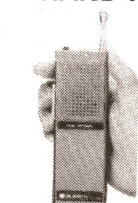

Ideal for sports or any outdoor activities. Built-in call button and separate volume control. Range 1.2km maximum. 49MHz crystal control superhet circuit with built-in condenser mic. and speaker. Unit supplied with vinyl carrying case and personal earphone.

£32.90 a pair

+ £2.60 P&P

RADIO AND TV COMPONENTS ACTON LTD
21 HIGH STREET, ACTON, LONDON W3 6NG

MAIL ORDER TERMS. POSTAL ORDERS and/or CHEQUES with orders. Orders under £20 add £3.00 service charge. Net monthly accounts to Schools, Colleges and P.L.C. only. ACCESS VISA Phone orders between 9.30 & 12pm please. Overseas readers write for quote on delivery.

Phone: 071-723 8432 or 081-992 8430
Callers 323 Edgware Road, London W2. Closed Sun.
21 High St., Acton, London W3 closed Sun, Mon & Wed

30+30 WATT AMPLIFIER KIT



An easy to build amplifier with a good specification. All the components are mounted on the single P.C.B. which is already punched and backprinted.

■ 30W x 2 (DIN 4 ohm)

■ CD/Aux, tape I, tape II, tuner and phono inputs.

■ Separate treble and bass

■ Headphone jack

Size (H.W.D.) 75x400x195mm

Kit enclosed: case, P.C.B., all components, scale and knobs £36.80, post £3.50

(Featured project in *Everyday Electronics* April 1989 issue). Reprint Free with kit.

AMPHONIC 125+125 POWER AMPLIFIER



125 watt per channel stereo power amplifier with independent volume controls, professional 19" rack mount and silent running cooling fan for extra reliability.

Output power 125W RMS max. per channel

Output impedance 4 to 16 ohms

(max. power into 4 ohms)

Sensitivity 450V at 22K ohms


Protection Electronic short-circuit and fuses

Power 220-240V a.c. 50Hz

Chassis dim 435x125x280mm

£142 + £7.00 p&p

STEREO MIXER

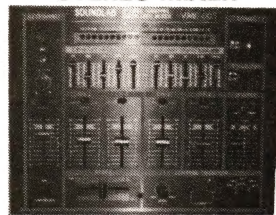

5-channel stereo disco mixer in racking case which can handle up to a total of 10 phono, line and mic inputs, switchable on front panel. Twin 5-band graphic equalizer with insert/bypass switch. Cross fader between channels 1 and 2. Mic channel with low cut filter and talkover switch. Separate L and R master controls.

Output for amp, tape and headphones.

Input Mic 0.3mV 600 ohms

Phono 2.5mV 50K ohms

Outputs: Amp & Tape 50mV @ 75ohms

Headphone 1.2V

Equalizer control frequencies 60, 250, 1k, 3.5k, 12kHz

Equalizer control range ±12dB boost or cut

Size 350 x 280 x 90mm

£118.90 + £5.80 P&P

BELT-DRIVE QUICKSTART VARISPEED DISCO TURNTABLE

★ Quick start ideal for scratching

★ Pitch control

★ Pop-up target lamp

★ Strobe lamp

★ Counterweighted tubular tone arm with plug-in headshell

★ Full manual control

★ Remote start/stop

★ 7.5kg



£112.00

+ £7.00 P&P

28.0.28V 4 AMP MAINS TRANSFORMERS

With a 5.5V at 0.5A mains input 110-240. Size 90 x 105 x 75 fitted with copper screening band; made for famous HIFI Co. £6.50 each. Postage £2.80. It's weight is 2.7kg! Brand new and unused condition.

MAGENTA

ELECTRONICS LTD

MAIL ORDER AND SHOP
EE93 135 Hunter Street
Burton-on-Trent
Staffs, DE14 2ST
Tel: 0283 65435
Fax: 0283 46932



All prices include VAT
Shop open 9-5 Mon-Fri;
9-2 Saturday
Official orders welcome

Add £2
p&p to
all orders

SUPERHET BROADCAST RECEIVER


EE MAR '90

At last, an easy to build SUPERHET A.M. radio kit. Covers Long and medium Wave bands. built in loudspeaker with 1 watt output. Excellent sensitivity and selectivity provided by ceramic I.F. filter. Simple alignment and tuning without special equipment. Kit available less case, or with pre-cut and drilled transparent plastic panels and dial for a striking see-through effect.

KIT REF 835

£16.79

D.C. MOTOR GEARBOXES

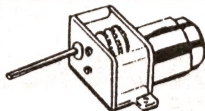

Ideal for Robots and Buggies. A miniature plastic reduction gearbox coupled with a 1.5-4.5 Volt mini motor. Variable gearbox reduction ratios are obtained by fitting from 1 to 6 gearwheels (supplied). Two types available:

SMALL UNIT TYPE MGS £3.99

Speed range 3-2200 rpm. Size 37x43x25mm

LARGE UNIT TYPE MGL £4.55

Speed range 2-1150 rpm. Size 57x43x29mm

Supplying Electronics for Education, Robotics, Music, Computing and much, much more!

NEW CATALOGUE OUT
OCTOBER. SEE FUTURE
ISSUES OF EVERYDAY
ELECTRONICS FOR
DETAILS

STEPPING MOTORS

A range of top quality stepping motors suitable for driving a wide range of mechanisms under computer control using simple interfacing techniques.

ID35 PERMANENT MAGNET MOTOR — 48 steps per rev. £16.50

MD200 HYBRID MOTOR — 200 steps per rev. £16.80

MD35 1/4 PERMANENT MAGNET MOTOR — 48 steps per rev. £12.70

MD38 PERMANENT MAGNET MOTOR — 48 steps per rev. £8.95

HAMEG HM 203-7 OSCILLOSCOPE

New model just arrived. Special summer discount price. Full two year parts and labour warranty.

£309

20MHz-2 channels 1mV sensitivity.
Easy to operate and high performance + £46.35 VAT
Next Day Delivery £8.50

EDUCATIONAL BOOKS & BOOK PROJECTS

ADVENTURES WITH ELECTRONICS

The classic Easy to Follow book suitable for all ages. Ideal for beginners. No soldering, uses an S-DEC breadboard. Gives clear instructions with lots of pictures. 16 projects — including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-DEC breadboard and all the components for the series.

ADVENTURES WITH ELECTRONICS COMPONENT PACK (less book)

£5.25
£23.49

FUN WITH ELECTRONICS

From the USBORNE Pocket Scientist series — An enjoyable introduction to electronics. Full of very clear full colour pictures accompanied by easy to follow text. Ideal for all beginners — children and adults. Only basic tools are needed. 64 full colour pages cover all aspects — soldering — fault finding — components (identification & how they work). Also full details of how to build 6 projects — burglar alarm, radio, game, etc. Requires soldering — 4 pages clearly show you how.

The components supplied in our pack allows all the projects to be built and kept. The book is available separately.

FUN WITH ELECTRONICS Book COMPONENT PACK (less book)

£2.50
£18.45

30 SOLDERLESS BREADBOARD PROJECTS

A book of projects by R. A. Penfold covering a wide range of interests. All projects are built on a Verobloc breadboard. Full layout drawings and component identification diagrams enable the projects to be built by beginners. Each circuit can be dismantled and rebuilt several times using the same components. The component pack allows all projects in the book to be built one at a time. Projects covered include amplifiers, light actuated switches, timers, metronome, touch switch, sound activated switch, moisture detector, M.W. Radio, Fuzz unit, etc.

30 SOLDERLESS BREADBOARD PROJECTS Book 1 COMPONENT PACK

£2.95
£28.50

ENJOYING ELECTRONICS

A more advanced book which introduces some arithmetic and calculations to electronic circuits. 48 chapters covering elements of electronics such as current, transistor switches, flip-flops, oscillators, charge, pulses, etc. An excellent follow-up to Teach-in or any other of our series. Extremely well explained by Owen Bishop who has written many excellent beginners' articles in numerous electronics magazines.

ENJOYING ELECTRONICS Book COMPONENT PACK

£3.60
£15.05

Note — A simple multimeter is needed to fully follow this book. The M102 BZ is ideal.

£13.98

A FIRST ELECTRONICS COURSE

A copiously illustrated book that explains the principles of electronics by relating them to everyday objects. At the end of each chapter a set of questions and word puzzles allow progress to be checked in an entertaining way. An S-DEC breadboard is used for this series — soldering is not required.

A FIRST ELECTRONIC COURSE BOOK PACK

£3.75
£23.47

EVERYDAY ELECTRONICS KIT PROJECTS

ALL KITS HERE HAVE BEEN FEATURED IN EE. IF YOU DO NOT HAVE THE MAGAZINE WITH THE ORIGINAL ARTICLE, YOU WILL NEED TO ORDER THE REPRINT FOR 80p EXTRA. REPRINTS ALSO AVAILABLE SEPARATELY. KITS INCLUDE CASES, PCB's, HARDWARE AND ALL COMPONENTS (UNLESS STATED OTHERWISE) CASES ARE NOT DRILLED, LABELS ARE NOT SUPPLIED.

Ref	Price	Ref	Price
835	SUPERHET BROADCAST RECEIVER Mar 90	542	PERSONAL RADIO June 86
	With drilled panels and dial	528	PA AMPLIFIER May 86
	Without above	523	STEREO REVERB Apr 86
834	QUICK CAP TESTER Feb 90	513	BBC MIDI INTERFACE Mar 86
833	EE 4 CHANNEL LIGHT CHASER Jan 90	512	MAINS TESTER & FUSE FINDER Mar 86
815	EE TREASURE HUNTER Aug 89	497	MUSICAL DOOR BELL Jan 86
814	BAT DETECTOR June 89	493	DIGITAL CAPACITANCE METER Dec 85
812	ULTRASONIC PET SCARER May 89	481	SOLDERING IRON CONTROLLER Oct 85
800	SPECTRUM EPROM PROGRAMMER Dec 88	464	STEPPER MOTOR INTERFACE FOR THE BBC
796	SEASHELL SYNTHESIZER Nov 88		COMPUTER less case Aug 85
790	EPROM ERASER Oct 88		1D35 STEPPER MOTOR EXTRA
769	VARIABLE 25V-2A BENCH POWER SUPPLY		OPTIONAL POWER SUPPLY PARTS
	Feb 88	461	CONTINUITY TESTER July 85
763	AUDIO SIGNAL GENERATOR Dec 87	455	ELECTRONIC DOORBELL June 85
739	ACCENTED BEAT METRONOME Nov 87	453	GRAPHIC EQUALISER June 85
740	ACOUSTIC PROBE Nov 87 (less bolt & probe)	444	INSULATION TESTER Apr 85
744	VIDEO CONTROLLER Oct 87	392	BBC MICRO AUDIO STORAGE SCOPE
734	AUTOMATIC PORCH LIGHT Oct 87		INTERFACE Nov 84
728	PERSONAL STEREO AMP Sep 87	387	MAINS CABLE DETECTOR Oct 84
730	BURST-FIRE MAINS CONTROLLER Sep 87	386	DRILL SPEED CONTROLLER Oct 84
724	SUPER SOUND ADAPTOR Aug 87	362	VARICAP AM RADIO May 84
718	3-BAND 1.6-30MHz RADIO Aug 87	337	BIOLOGICAL AMPLIFIER Jan 84
719	BUCCANEER I.B. METAL DETECTOR July 87	263	BUZZ OFF Mar 83
	Inc coils, and case, less handle and hardware	242	INTERCOM no case July 82
722	FERMOSTAT July 87	240	EGG TIMER June 82
715	MINI DISCO LIGHTS June 87	108	IN SITU TRANSISTOR TESTER June 78
707	EQUALIZER (IONISER) May 87	106	WIERD SOUND EFFECTS GEN Mar 78
700	ACTIVE I/R BURGLAR ALARM Mar 87	101	ELECTRONIC DICE Mar 77
581	VIDEO GUARD Feb 87		
584	SPECTRUM SPEECH SYNTH (no case) Feb 87		
578	SPECTRUM I/O PORT less case Feb 87		
569	CAR ALARM Dec 86		
563	200MHz DIG. FREQUENCY METER Nov 86		
561	LIGHT RIDER LAPEL BADGE Oct 86		
560	LIGHT RIDER DISCO VERSION		
559	LIGHT RIDER 16 LED VERSION		
556	INFRA-RED BEAM ALARM Sep 86		
544	TILT ALARM July 86		

TEACH-IN 1 PROJECTS

591	REGULATOR UNIT & SAFE POWER SUPPLY	£29.95
592	UNIVERSAL LCR BRIDGE	£28.89
593	DIODE/TRANSISTOR TESTER	£21.22
594	AUDIO SIGNAL TRACER	£18.73
595	AUDIO SIGNAL GENERATOR	£29.31
596	R.F. SIGNAL GENERATOR	£27.37
597	FET VOLTMEETER	£24.02
598	DIGITAL PULSE GENERATOR	£18.65

INSULATION TESTER

EE APRIL 85



A reliable electronic tester which checks insulation resistance of wiring appliances etc., at 500 volts. The unit is battery powered simple and safe to operate. Leakage resistance of up to 100 Megohms can be read easily. One of our own designs and extremely popular.

KIT REF 444

£21.89

3 BAND SHORT WAVE RADIO

EE AUG 87

Covers 1.6-30 MHz in 3 bands using modern miniature coils. Audio output is via a built-in loudspeaker. Advanced design gives excellent stability, sensitivity and selectivity. Simple to build.

KIT REF 718

£29.66

MINI STROBE

EE MAY '86

A hand held stroboscope which uses 6 "ultra bright" LEDs as the light source. Designed to demonstrate the principles of stroboscope examination, the unit is also suitable for measuring the speed of moving shafts etc. The flash rate control covers 170-20,000 RPM in two ranges.

KIT REF 529

£15.50

EE EQUALISER

EE MAY '87

A mains powered ioniser with an output of negative ions that give a refreshing feeling to the surrounding atmosphere. Negligible current consumption and all-insulated construction ensure that the unit is safe and economical in use. Easy to build on a simple PCB.

KIT REF 707

£17.37

LIGHT RIDERS

EE OCT '86

Three projects under one title - all simulations of the Knight Rider lights from the TV series. The three are a lapel badge using six LEDs, a larger LED unit with 16 LEDs and a mains version capable of driving six main lamps totalling over 500 watts.

KIT REF 559 CHASER LIGHT

£15.25

KIT REF 560 DISCO LIGHTS

£21.93

KIT REF 561 LAPEL BADGE

£11.40

PET SCARER

EE MAY 89

Produces high power ultrasound pulses. L.E.D. flashes to indicate power output and level. Battery powered (9V-12V or via Mains Adaptor).

KIT REF 812

Mains Adaptor £1.98

£14.49

DIGITAL FREQUENCY 200 MHz METER

EE NOV 86

An 8 digit meter reading from AF up to 200 MHz in two ranges. Large 0.5" Red LED display. Ideal for AF and RF measurements. Amateur and C.B. frequencies.

KIT REF 563

£69.95

ACOUSTIC PROBE

EE NOV '87

A very popular project which picks up vibrations by means of a contact probe and passes them on to a pair of headphones or an amplifier. Sounds from engines, watches and speech travelling through walls can be amplified and heard clearly. Useful for mechanics, instrument engineers and nosey parkers!

KIT REF 740

£19.58

MUSICAL DOORBELL

EE JAN '86

This project uses a special I.C. pre-programmed with 25 tunes and 3 chimes. A Magenta design, the circuit is battery powered and only draws current whilst producing sounds. Two rotary switches select the tune required. Provision is made for three bell pushes, each of which sounds a different tune, so that three points of entry can be identified.

KIT REF 497

£20.95

EE TREASURE HUNTER

EE AUG '89

A sensitive pulse induction Metal Detector. Picks up coins and rings etc., up to 20cms deep. Low "ground effect". Can be used with search-head underwater. Easy to use and build, kit includes search-head, handle, case, PCB and all parts as shown.

KIT REF 815

Headphones

£41.95

£1.99

DIGITAL CAPACITANCE METER

EE DEC 85

Simple and accurate (1%) measurement of capacitors from a few pF up to 1,000 μ F. Clear 5-digit LED display indicates exact value. Three ranges - pF, nF, and μ F. Just connect the capacitor, press the button and read the value.

KIT REF 493

£46.46

MOSFET VARIABLE BENCH 25V 2.5A POWER SUPPLY

EE FEB 88

A superb design giving 0.25V and 0-2.5A. Twin panel meters indicate Voltage and Current. Voltage is variable from zero to 25V. A Toroidal transformer MOSFET power output device, and Quad op-amp IC design give excellent performance.

KIT REF 769

£55.61

4 CHANNEL LIGHT CHASER

EE Jan '90

A 1000W per channel chaser with zero volt switching, hard drive, inductive load capability, mic sound sensor and sophisticated 'beat' detector. Chase steps to music or auto when quiet. Variable speed and mic. sens. LED mimic on front panel. Switchable for 3 or 4 channels. P552 output. Ideal for rope lights, pin spots, disco and display lighting.

KIT REF 833

£31.45

EPROM ERASER

EE OCT '88

Safe low-cost unit capable of erasing up to four EPROM's simultaneously in less than twenty minutes. Operates from a 12V supply. Safety interlock. Convenient and simple to build and use.

KIT REF 790

£27.90

STEPPING MOTOR INTERFACE

EE AUG '85

This interface enables 4 phase unipolar stepping motors to be driven from four output lines of any computer user port. The circuit is especially suitable for the ID35 motor and our MD200 which are commonly used in buggies and robot arms. Supplied complete with ribbon cable and connector for the BBC user port.

KIT REF 464

£9.40

TK FOR KITS

GUARD DOG KIT




One of the best burglar deterrents is a guard dog and this kit provides the barking without the bite! Can be connected to a doorbell, pressure mat or any other intruder detector and produces random threatening barks. Includes mains supply and horn speaker.

XK125

£21.95

DISCO LIGHTING KITS

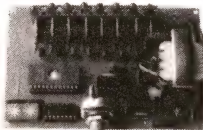

DL8000K 8-way sequencer kit with built-in opto-isolated sound to light input. Only requires a box and control knob to complete**£39.95**
DL1000K 4-way chaser features bi-directional sequence and dimming 1kW per channel...**£23.95**
DLA/1 (for DZ1000K)
 Optional op-to input allowing audio beat/light response.....**95p**
DL3000K 3-channel sound to light kit, zero voltage switching, automatic level control and built-in mic. 1kW per channel**£19.55**
XK139 Uni-directional chaser. Zero switching and built-in audio input.....**£12.95**


POWER STROBE KIT

Produces an intense light pulse at a variable frequency of 1 to 15Hz. Includes high quality PCB, components, connectors, 5Ws strobe tube and assembly instructions. Supply: 240V ac. Size: 80x50x45.

XK124 STROBOSCOPE KIT. £17.25



PROGRAMMABLE ELECTRONIC LOCK KIT

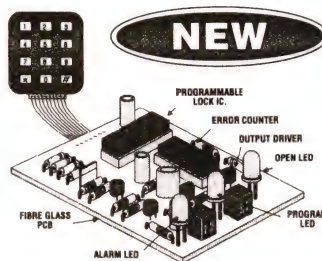

Keys could be a thing of the past with this new high security lock. Secure doors to sheds, garages, even your home or prevent the unauthorised use of computers, burglar alarms or cars. One 4-digit sequence will operate the lock while incorrect entries will sound an alarm. The number of incorrect entries triggered before the alarm is triggered is selected by you. Further entries will be ignored for a time also set by you. Only the correct sequence will open the lock and switch off the alarm. The sequence may easily be changed by entering a special number and code on the supplied keyboard. Kit includes; keyboard, alarm buzzer, high quality PCB and all electronic components. Supply 5-15V DC. Will drive our Latch Mechanism (701 150 @ £18.98) or relay directly.

XK131


£19.95

SIMPLE KITS FOR BEGINNERS


Especially aimed at the beginner. Have fun with your project even after you have built it and also learn a little from building it. These kits include high quality solder resist printed circuit boards, all electronic components (including speaker where used) and full construction instructions with circuit description.



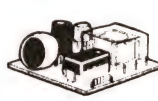SK1 DOOR CHIME plays a tune when activated by a pushbutton **£4.50**



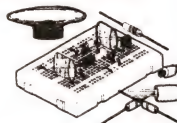SK2 WHISTLE SWITCH switches a relay on and off in response to whistle command **£4.50**



SK3 SOUND GENERATOR produces FOUR different sounds, including police/ambulance/fire-engine siren and machine gun **£4.50**

XK118 TEN EXCITING PROJECTS FOR BEGINNERS this kit contains a solderless breadboard, components and a booklet with instructions to enable the absolute novice to build ten fascinating projects including a light operated switch, intercom, burglar alarm and electronic lock. Each project includes a circuit diagram, description of operation and an easy to follow layout diagram. A section component identification and function is included, enabling the beginner to build the circuits with confidence**£17.25**

ELECTRONIC WEIGHING SCALE




Kit contains a single chip microprocessor. PCB, displays and all electronics to produce a digital LED readout of weight in Kgs or Sts/Lbs. A PCB link selects the scale-bathroom/two types of kitchen scales. A low cost digital ruler could also be made.

ES1

£8.25

VOICE RECORD/PLAYBACK KIT

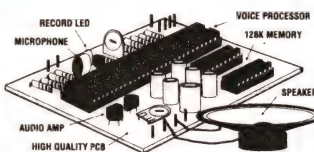


This simple to construct and even simpler to operate kit will record and playback short messages or tunes. It has many uses - seatbelt or light reminder in the car, welcome messages to visitors at home or at work, warning messages in factories and public places. In fact anywhere where a spoken message is announced and which needs to be changed from time to time. Also suitable for toys - why not convert your daughter's £8 doll to an £80 taking doll!!

Size 76 x 60 x 15mm
 Message time 1-5 secs normal speed, 2-10 secs slow speed

XK129

£25.95

SUPER-SENSITIVE MICROBUG

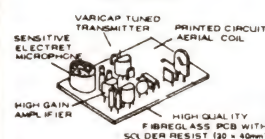

Only 45x25x15mm, including built-in mic. 88-100MHz (standard FM radio). Range approx. 300m depending on terrain. Powered by 9V PP3 (7mA). Ideal for surveillance, baby alarm etc. **XK128**

£6.35

NEW

REMOTE CONTROL DIMMER KIT

Imagine controlling the brightness of your lights or switching them on or off from the comfort of your armchair! This kit contains all the components from front panel to the last screw to enable you to do just that and fit the shallowest wall boxes. Max power 300W (not fluorescents).

XK132**£19.95**

IR TRANSMITTER KIT

Designed for use with the XK132 and comes complete with a pre-drilled box. A PP3 9 volt battery is required.

MK 6**£4.95**


XK136 TOUCH DIMMER KIT**£12.95**

VERSATILE REMOTE CONTROL SYSTEM

These kits can switch up to 16 pieces of equipment on and off or control 16 functions depending on the keyboard selected for the MK18 transmitter. MK12 receiver has 16 logic outputs and operates from 12 to 24V d.c. or 240V a.c. via the transformer supplied. The MK18 requires a 9V battery and keyboard. Great for controlling lights, TVs, garage doors etc.

MK12 IR Receiver**£19.55**
MK18 Transmitter**£8.95**
MK 9 4-way Keyboard**£2.75**
MK10 16-way Keyboard**£7.95**
601 133 Box for transmitter**£2.95**

PROPORTIONAL TEMPERATURE CONTROLLER KIT

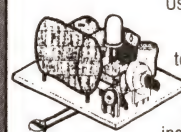

Uses "burst fire" technique to maintain temperature to within 0.5°C. Ideal for photography, incubators, wine making, etc.

Maximum load 3kW (240V AC). Temperature range up to 60°C. Size 50x40x25mm. **XK140****£8.95**

TK

ELECTRONICS

TK ELECTRONICS

**13 Boston Road
 London W7 3SJ
 Tel: 081-579 9794
 Fax: 081-566 1916**

ORDERING INFORMATION All prices INCLUDE VAT. Free P & P on orders over £60 (UK only), otherwise add £1.15. Overseas Customers divide total order by 1.15 then add P & P: Europe £3.50, elsewhere £10.00. Send cheque/PO/Visa/Access No. with order. Giro No. 529314002. Local Authority and educational institutions orders welcome. Shop Open: Tuesday-Thursday 10 am - 5 pm. Saturday 10 am - 4 pm.



ORDERS: 081-567 8910 24 HOURS

EVERYDAY ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY

The Magazine for Electronic & Computer Projects

VOL. 19 No. 10

October '90

Editorial Offices:

EVERYDAY ELECTRONICS EDITORIAL,
6 CHURCH STREET, WIMBORNE,
DORSET BH21 1JH

Phone: Wimborne (0202) 881749

Fax: (0202) 841692. DX: Wimborne 45314.

See notes on **Readers' Enquiries** below – we regret that lengthy technical enquiries cannot be answered over the telephone.

Advertisement Offices:

EVERYDAY ELECTRONICS ADVERTISEMENTS,
HOLLAND WOOD HOUSE, CHURCH LANE,
GREAT HOLLAND, ESSEX CO13 0JS.

Phone (0255) 850596

DESIGN

With our popular *Micro In Control* series coming to an end next month, it is time to look at what will follow. We are often asked to tell readers how to design an XYZ for their next project, as many readers are aware it is not quite that simple! However, our new *Circuit Design Teach-In* series starting in the December issue, will do just that. The series has been written for us by Mike Tooley, who should be well known to most readers, and Mike's words describe the series very well:

"This ten part series is designed for the beginner. It not only aims to dispel some of the perceived mystery of electronic circuits but it also shows how even the relative newcomer to electronics can, with the right approach, design and realise quite complex circuits.

Each part will incorporate a design problem together with a complete practical project. The practical project will stand on its own and thus may appeal to those who may not necessarily be following the series, whilst the design problem has been designed to give readers some scope for experimentation.

The series will employ an absolute minimum of mathematics. Furthermore, the traditional analytical approach (based on circuit theorems) will largely be replaced by experiential learning. The overall aim being that of fostering an intuitive approach."

TEACH-IN FOUR

While on the subject of Teach-Ins our new publication *Teach-In No. 4. Introducing Digital Electronics*, will be on sale on 21st September so watch out for that too. It is a complete course for City & Guilds 726/301 (Introductory Digital Electronics) and will be invaluable to anyone taking up the hobby or getting involved in study for C&G or other qualifications, including G.C.S.E. courses.

PRICE

No doubt you will have noticed that from this issue EE will cost you £1.50. It has been 18 months since our last price rise and our costs – particularly paper prices – continue to rise. I believe EE is no more expensive than any of our rivals (cheaper than some) and still offers the best value for money of any of the monthly electronic hobby magazines. **You can avoid this price rise for a year if you are quick!** See page 667.



SUBSCRIPTIONS

Annual subscriptions for delivery direct to any address in the UK: £16.00. Overseas: £19.50 (£37 airmail). Cheques or bank drafts (in £ sterling only) payable to Everyday Electronics and sent to EE Subscriptions Dept., 6 Church Street, Wimborne, Dorset BH21 1JH. **Subscriptions can only start**

with the next available issue. For back numbers see below.

BACK ISSUES

Certain back issues of EVERYDAY ELECTRONICS are available price £1.50 (£2.00 overseas surface mail) – **£ sterling only please** – inclusive of postage and packing per copy. Enquiries with remittance, made payable to Everyday Electronics, should be sent to Post Sales Department, Everyday Electronics, 6 Church Street, Wimborne, Dorset BH21 1JH. In the event of non-availability one article can be photostatted for the same price. *Normally sent within seven days but please allow 28 days for delivery.* We have sold out of Sept., Oct. & Dec. 85, April, May, Oct. & Dec. 86, Jan., April, May & Nov. 87, Jan., March, April, June & Oct. 88, & March 90.

BINDERS

Binders to hold one volume (12 issues) are available from the above address for £4.95 (£6.95 to European countries and £9.00 to other countries, surface mail) inclusive of post and packing. *Normally sent within seven days but please allow 28 days for delivery.* **Payment in £ sterling only please.**

Editor: MIKE KENWARD

Secretary: PAMELA BROWN

Deputy Editor: DAVID BARRINGTON

Business Manager: DAVID J. LEAVER

Editorial: WIMBORNE (0202) 881749

Advertisement Manager:

PETER J. MEW, Frinton (0255) 850596

Classified Advertisements:

Wimborne (0202) 881749

READERS' ENQUIRIES

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years old. Letters requiring a personal reply must be accompanied by a **stamped self-addressed envelope** or a **self addressed envelope and international reply coupons.**

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot however guarantee it and we cannot accept legal responsibility for it.

COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers.

We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

We regret that **we cannot provide data or answer queries on projects that are more than five years old.**

ADVERTISEMENTS

Although the proprietors and staff of EVERYDAY ELECTRONICS take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are *bona fide*, the magazine and its Publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or are in the form of inserts.

The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture. Legal remedies are available in respect of some of these circumstances, and readers who have complaints should first address them to the advertiser.


TRANSMITTER/BUGS/TELEPHONE EQUIPMENT

We would like to advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the U.K. Readers should check the law before using any transmitting or telephone equipment as a fine, confiscation of equipment and/or imprisonment can result from illegal use. The laws vary from country to country; overseas readers should check local laws.



FREQUENCY METER/TACHOMETER

STEVE KNIGHT

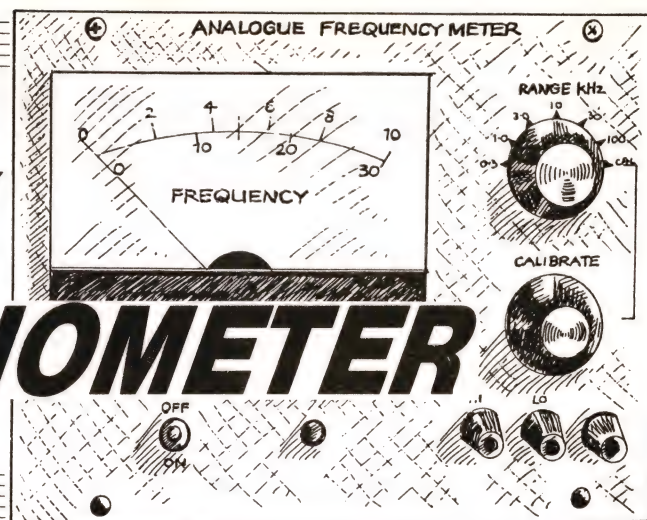

A straightforward, inexpensive but accurate frequency meter. Measures from 10Hz to 100kHz.

A SHORT while ago a colleague who operated a small engineering plant, knowing I dabbled in things electronic, asked me if I could make up for him a box of tricks (as he put it) which would measure the speed of rotating shafts. The design criteria, apart from a reasonable accuracy, simplicity of operation and cheapness, being that no mechanical contact was to be made to any of the shafting under investigation, neither was any mechanical switching to be involved.

Well, a few weeks work produced a unit which did the job adequately and had an accuracy of well within one per cent. What turned up was basically a photodiode sensor with a self-contained light source, which illuminated and then detected by reflection the passage of black and white stripes painted on to part of the shafting being looked at.

This gave a square wave output corresponding to the transitions between the light and dark areas on the shaft. The output was then fed into a simple frequency counter which provided a direct indication on the scale of an analogue meter, of the number of square wave cycles per second and hence (knowing the number of stripes painted on the shaft) the rotational speed of the shaft.

This original instrument had a single frequency measuring range of 1kHz and when used for the purpose for which it was designed, that is, a Tachometer, it was useful for measuring the speeds of rotating mechanisms well beyond 10,000 revolutions per minute.

On thinking this project over afterwards, it seemed logical that since the end effect was the measurement of frequency, then a design could be made up of two separate units: A Frequency Meter part, which could be extended in frequency to at least 100kHz to make it into a self-contained addition to the home experimenters' laboratory instruments. A useful optical sensor unit which could be used with the frequency meter to form a Tachometer, or used in its own right as a beam-break detector, or as a tape or punch card reader, to name just a couple of applications.

As such, either or both designs might be of interest to home constructors, so the extended and modified forms of both the original frequency meter (this month) and the optical Sensor/Tachometer will be described over the next two issues.

FREQUENCY MEASUREMENT

An analogue frequency meter may seem rather like a restricted or even antiquated piece of equipment in this age of digital devices but there is a maxim I have always followed over very many years in the electronics game: *"never make a thing more complicated than it has to be to do the work you want it to do."*

That way, a lot of expense and frustration is avoided and egos are less likely to get dented. If a piece of equipment does a particular job, who cares whether there are just a couple of transistors inside the box or fifty integrated circuits?

So, although the Frequency Meter we are talking about here has an upper frequency limit of 100kHz (this can be extended by frequency division as it is in a digital meter)

and an accuracy of two per cent, we mustn't dismiss it as old hat. What it does have, and this is important for most of us, is cheapness and simplicity and a usefulness in the fact that most home workshop measurements are needed over the audio range where an accuracy of one or two per cent is perfectly adequate. With an upper limit of, say, 100kHz, it will cover ninety-five per cent of everything a home experimenter gets up to.

This simple part of the project, which of course can be used in its own right, will give you a frequency measuring range from about 10Hz up to 100kHz with an accuracy, with care, of better than ± 2 per cent. With the meter scale being linear, the accuracy is unaffected by the input wave shape and input amplitudes down to 0.2V can be measured. There are six switched frequency ranges and a built-in calibration system which enables the circuit to be set up to the correct operating conditions every time it is used.

Protection is provided against excessive input levels and against d.c. voltages which might be inadvertently applied. The input "LO" terminal SK2 is also isolated from the case of the instrument (if a metal box is used) which is a useful feature in conditions where earthed input levels "ain't necessarily so".

The use of the frequency meter as a tachometer is accomplished by the attachment of the second unit which is a photodiode and light source, plus amplifier, and this will be discussed in due course.

CIRCUIT PRINCIPLES

The principle on which the Frequency Meter is based is shown in Fig. 1. The input waveform is first converted to a rectangular pulse train by a two-stage saturating amplifier.

This waveform is then used to switch transistor TR3 on and off on each of the alternate half cycles appearing at its base. For convenience, the component numbering is the same as that used in the full circuit diagram of Fig. 2, given later.

During the negative half cycle of input, TR3 is turned off and capacitor C charges by way of resistor R8 and diode D4. The cathode (k) of diode D6 is held at a reference potential determined by the

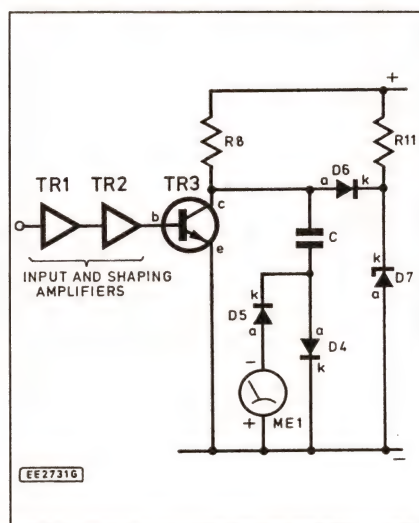


Fig. 1. Basic operation of the Frequency Meter.

Zener diode D7 (9.1V) and any attempt by the collector of TR3 (and hence the potential on the upper plate of C) to rise above about 9.3V causes D6 to conduct and clamp the collector at that level. The capacitor consequently charges always to the same level irrespective of signal amplitudes elsewhere in the circuit.

On the following half cycle, TR3 switches hard on and capacitor C discharges through the transistor, diode D5 and the meter movement ME1. For a given value of C, the mean current through the meter will be a function of the extent to which C is discharged and this will be directly related to the input frequency. Hence the meter reading is proportional to frequency.

CIRCUIT DESCRIPTION

The complete circuit diagram of the Frequency Meter is given in Fig. 2. The input transistor TR1 is a junction-gate f.e.t. preceded by a voltage limiter. This arrangement provides a high input impedance to the instrument (of the order of one megohm) and overload protection.

Switch bank S1b merely keeps the positive terminal of the meter ME1 "earthed" for the six range positions selected on S1a and so provides the discharge path for the appropriate range capacitor as detailed in the notes to Fig. 1. On the seventh position however, the meter and a preset resistance, VR1, are switched across the Zener reference diode D7.

This preset is adjusted during setting-up to give full scale deflection of the meter which is then correctly calibrated for that reference level. This is necessary as Zener diodes themselves have a five per cent tolerance. Once set, this calibration is thereafter controlled from a front panel potentiometer VR2 and holds for all frequency ranges.

The power supply source is quite conventional. A bi-phase rectifier, diodes D8 and D9, provide a d.c. output of about 24V across reservoir capacitor C13 from a 15V-0-15V, 250mA miniature mains transformer, and this is further smoothed and filtered by resistor R12 and capacitor C12. Resistor R11 is the Zener protection resistor and transistors TR1 and TR2 are further decoupled by the R5, C3 combination.

PRINTED BOARD

All components except the meter, the range switch and the calibration control are mounted on a single printed circuit board which itself is screwed directly on to the rear of the meter, using the meter terminals as the fixing points. This board is available through the *EE PCB Service*, quote code EE704.

The board measures 137mm by 103mm (5 $\frac{3}{8}$ in by 4in) and should preferably be of the fibreglass form as the mains transformer is also mounted on it. The brittle bakelite-based board can be used but is best avoided.

The component layout and full size copper foil master pattern is shown in Fig. 3. The two meter fixing holes at points M+ and M- suit the *specified* meter; if you use an alternative meter these positions may need to be adjusted accordingly.

You may have to adjust the hole positions to suit or, in the event of extreme variation, run two leads from the board to the meter and mount the board in some other fashion. A note should also be made of the polarity of the terminals of any alter-

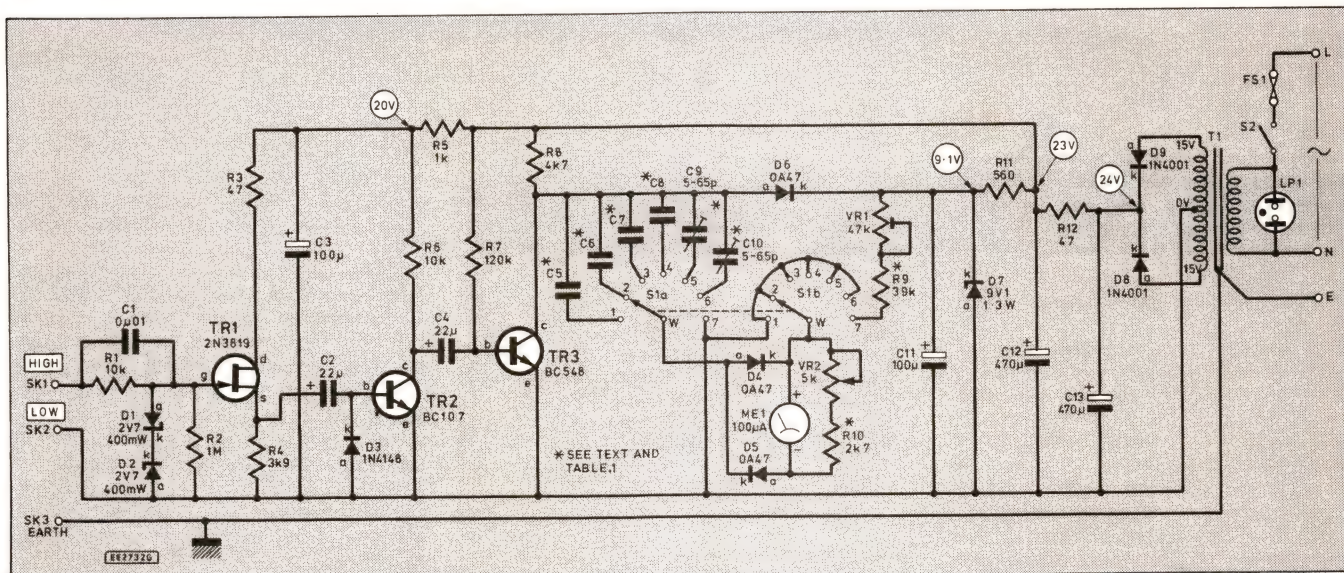


Fig. 2. Circuit diagram of the Frequency Meter.

The maximum amplitude of the signal applied to the gate of the f.e.t. is limited to about $\pm 2.7V$ by the action of Zener diodes D1 and D2 together with resistor R1. If the signal exceeds this level in either polarity, the appropriate Zener will break down and the excess voltage will be developed across R1. Capacitor C1 provides some high frequency compensation.

The f.e.t. itself is used as a source follower and the output across the source load R4 is an in-phase version of the input signal. Transistor TR2 is a simple squaring amplifier whose output switches TR3 on and off in accordance with the description already given.

The charging capacitors for each of the six frequency ranges are selected by the switch bank S1a. These capacitors have to be highly stable and of close tolerance, and although shown as single components in the diagram, are mostly made up from two paralleled components. Capacitor C5, for example, is made up from a 39n and an 8n2, a total capacity of 47n2, while C10 is made up from 100p and a 5-65p trimmer. We will return to this matter in the alignment details later.


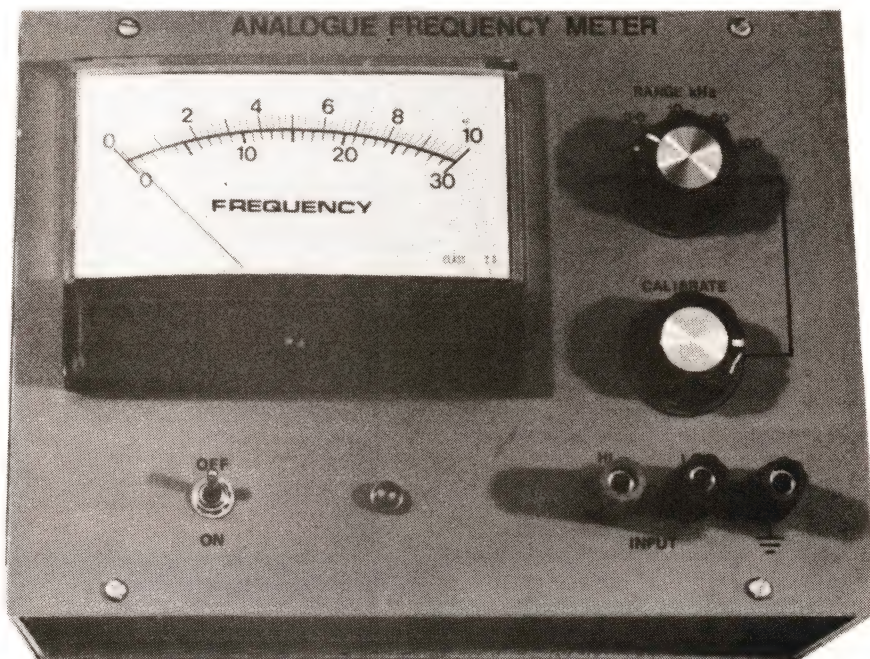


Fig. 3. P.C.B. pattern - shown full size - and (opposite) the component layout and wiring.

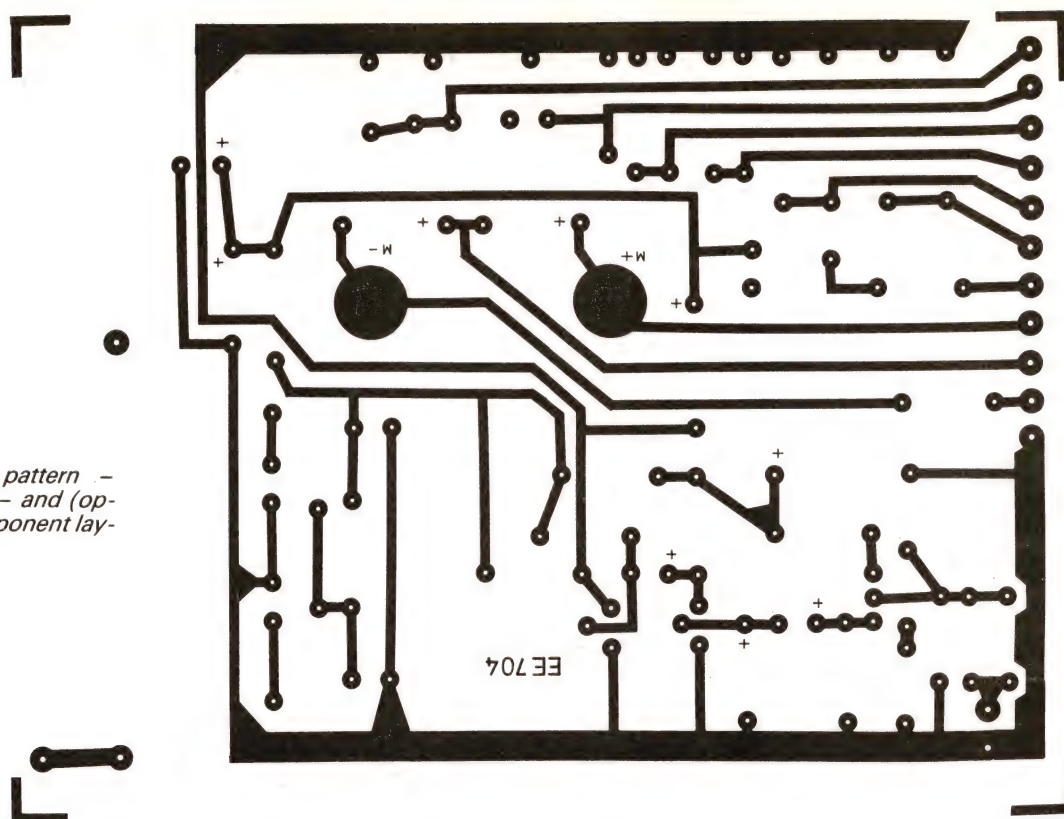

COMPONENTS

Resistors

R1, R6	10k (2 off)
R2	1M
R3, R12	47 (2 off)
R4	3k9
R5	1k
R7	120k
R8	4k7
*R9	39k
*R10	2k7
R11	560

All ½W 5% carbon or better

Potentiometers

VR1	47k min. preset, horiz
VR2	5k rotary carbon, lin.

Semiconductors

D1, D2	2.7V Zener, 400mW (2 off)
D3	1N4148 signal diode
D4, D5, D6	0A47 germanium diode (3 off)
D7	9.1V Zener, 1.3W
D8, D9	1N4001 1A 50V rec. diode (2 off)
TR1	2N3819 <i>n</i> -channel field effect transistor
TR2	BC107 <i>n</i> pn silicon, signal
TR3	BC548 <i>n</i> pn silicon, signal

Miscellaneous

ME1	100µA 4in. moving coil panel meter
S1	Two-pole 12-way wafer switch (2 wafers)
S2	Mains On/Off toggle or slide switch
T1	Mains 10VA min. transformer; 0V-15V, 0V-15V 330mA sec.
LP1	250V neon indicator lamp
FS1	500mA fuse, with panel mounting fuseholder

Printed circuit board available from *EE PCB Service*, code EE704; metal case, approx. 203mm x 152mm x 100mm (see text); 4mm screw/socket terminal (3 off - red, black, green); control knobs (2 off); mains cable; plastic sleeving; connecting wire; mains cable clamp/grommet; solder tags (4 off); solder; nuts, bolts and washers etc.

*Resistors R9 and R10 may need modification if an alternative meter is used.

Capacitors C5 to C10 are paralleled pairs. All values above (and including) 1000p (1n) are 1 per cent tolerance, high stability types. Capacitors below 1n may be nominal 2½ per cent polystyrene.

Capacitors

C1	0µ01 polyester
C2, C4	22µ tantalum bead 25V (2 off)
C3	100µ axial elec. 25V
*C5-C10	See text (Table 1)
C11	100µ radial elec. 25V
C12, C13	470µ radial elec. 25V (2 off)
*C9, C10	5-65p trimmer (2 off)

See
SHOP
TALK
Page

nate meter even if the terminal spacing is identical. Viewed from the rear of the meter, the positive terminal must be on the left.

There is little to say about mounting the components on to the board. There are a number of diodes and electrolytic capacitors and the polarities of these must be carefully observed, particularly capacitors C2 and C4 which are tantalum beads and the markings on some of these are notoriously indistinct. Make doubly sure you get them the right way round.

Diodes D4, D5 and D6 are germanium types, preferably 0A47s although 0A91s may be used. The miniature transformer is bolted directly to the board using 6BA screws and the connections from the secondary winding made with short wires down to the appropriate copper pads.

When mounting the transformer T1, put a thin washer *between* the transformer and the board as Fig. 4. shows. This prevents the slight deformation of the board which might occur as the transformer screws are tightened up. *Do not overtighten them in any event.*

FREQUENCY SELECTION


The frequency range capacitor selection, C5 to C10, are positioned along the top edge of the board. These enable the range 10Hz to 100kHz to be covered in six switched stages.

Frequencies below 10Hz are seen as rapid vibrations of the meter pointer and are not accurately readable; the upper limit is determined by the smallest value of capacitor which adequately swamps out the effect of circuit strays. It is possible to get up to about 250kHz with care, but above some 150kHz the reading is not entirely reliable, hence the decision to make the upper limit 100kHz for this design.

As the board diagram shows, provision is made for each capacitor position to accept a paralleled arrangement of two com-

Approx cost
guidance only

£25
plus case

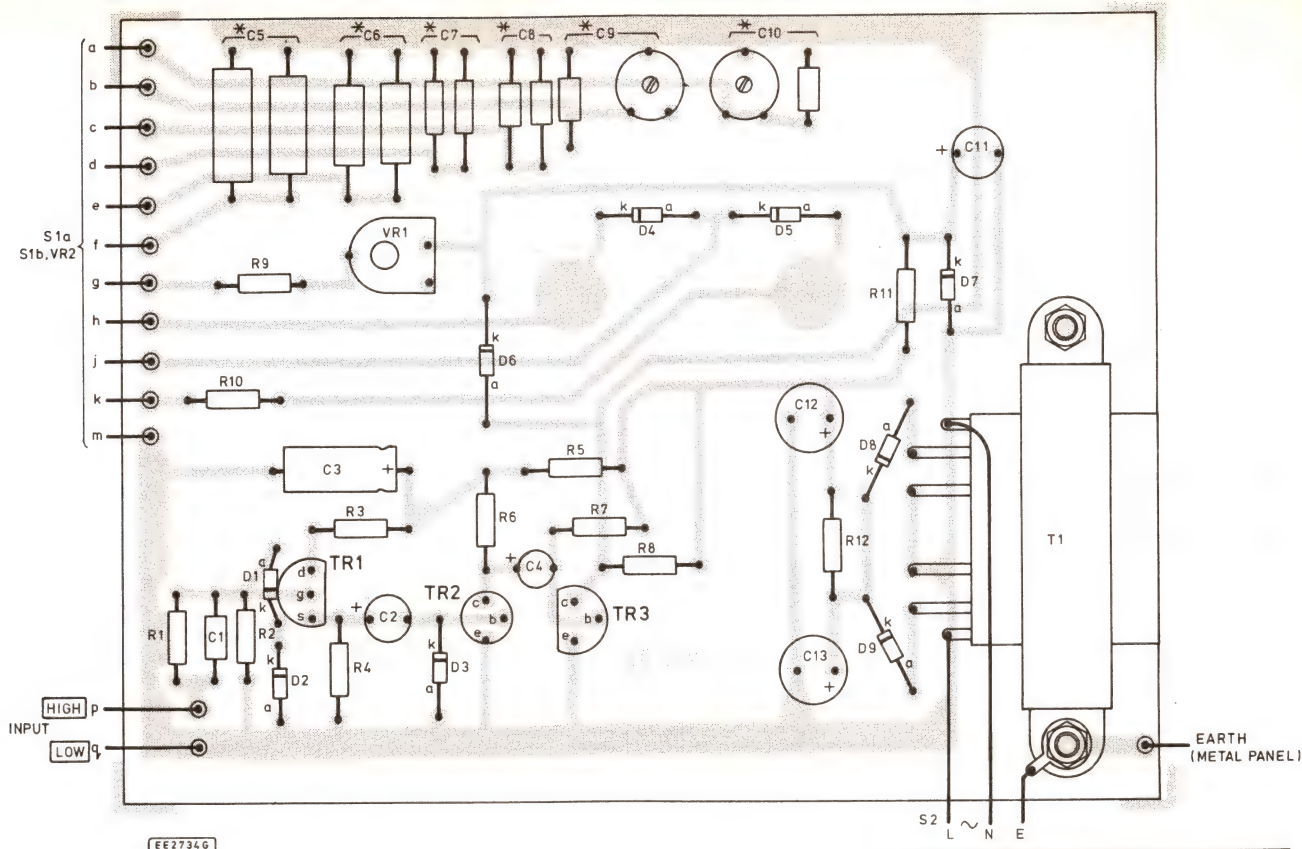

ponents; this makes the final adjustments very much easier.

Table 1. shows the capacitor combinations used in the prototype and these gave an accuracy within ± 2 per cent. However, because of circuit tolerances and variations, some slight adjustments may well be needed in copy models and this is where the idea of using paralleled capacitors comes in.

The C5 position may be a single 47n ± 1 per cent component or a 39n in parallel with an 8n2. No adjustment is needed on this frequency range (0-300Hz) as it is set up against the calibration circuit; and for capacitors C9 and C10 the addition of a 5-65p trimmer capacitor makes the final adjustment on the two upper ranges (0-30kHz and 0-100kHz) very easy.

To start off, then, solder *all* the capacitors for the C5, C9 and C10 positions into place, but use solder pins into the positions for C6, C7 and C8 and solder only the *larger* valued capacitor of each pair to these for the time being; that is, the 10n for C6, the 3n9 for C7 and the 1n for C8. The additional paralleled capacitors to each of these will be connected to the unused pins during alignment later on.

When you have reached this stage in the board assembly, double check on the polarities of the electrolytics and the diodes and go over your soldering to make certain

that there are no bridges across tracks or poor joints. Now solder 75mm (3in) lengths of insulated wire, preferably of different colours to avoid later confusion, to the points along the left-hand side of the board which will connect to the switch S1 and calibration control VR2 (points a through m) and two similar lengths to the input pads (points p and q). Finally, don't forget to bridge the tags on the mains transformer primary winding which connect the separate parts of this winding together.

RESCALING THE METER

The specified meter is scaled 0-100 μ A and this needs to be changed. This is because we are effectually measuring frequency and not microamps and the ranges go up in

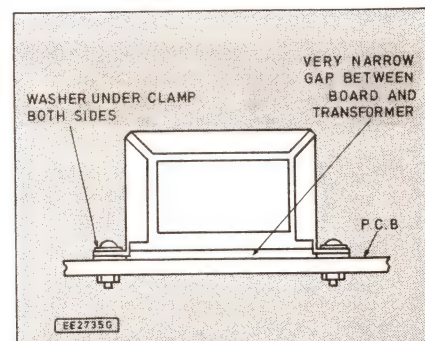



Fig. 4. Transformer mounting.

steps of 3 and 10 units i.e. 300Hz, 1000Hz, 3000Hz etc. So we need to add a 0-30 scale on to the existing 0-100 one and put the word "Frequency" somewhere.

The readjusted scale is shown in Fig. 5. and anyone with an artistic bent and a

TABLE 1

Cap.	Main capacitance	Parallel capacitance
C5	39n	8n2
C6	10n	3n9
C7	3n9	250p
C8	1n0	330p
C9	390	5-65p trimmer
C10	100p	5-65p trimmer

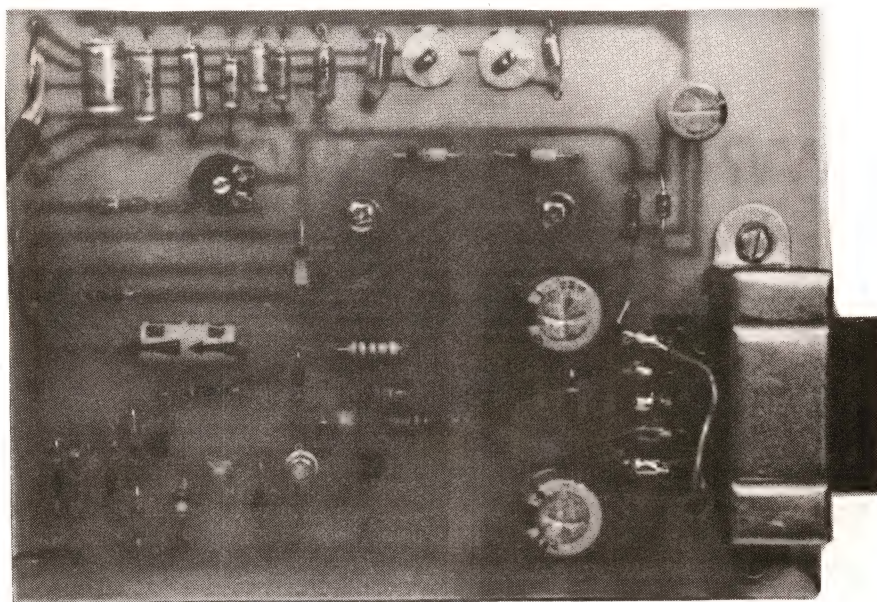

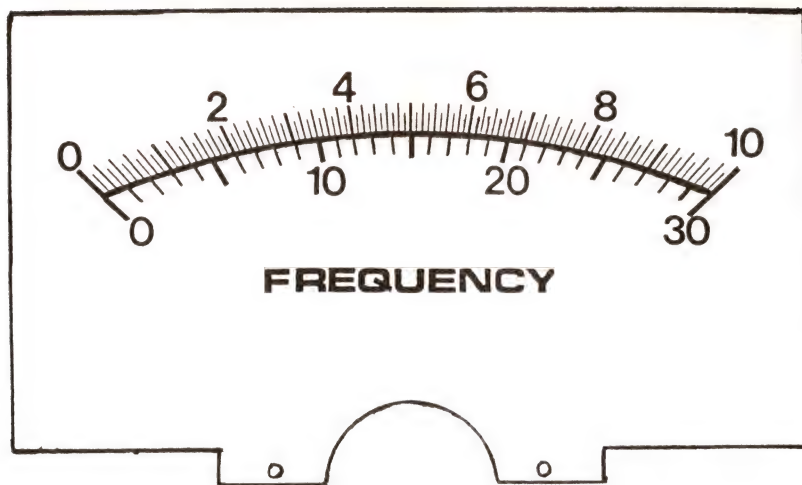


Fig. 5. The required meter scale.

steady hand can use rub-on lettering and Indian ink to fabricate the scale for himself. However, many of us do not have either the steady hand or the bent; so to make life not altogether discouraging, the scale has been reproduced full size and a photocopied scale can be cut out and glued to the existing scale.

To fit the scale, first gently prise off the transparent plastic cover from the meter, using only your fingers and thumbs, *not* screwdrivers or the like, or the plastic may be damaged. And make sure the surroundings are clean and dust free. Remove the existing scale by unscrewing the two fixing screws and *slide* it out from beneath the pointer.

Cut out the photocopied scale to the outline, apply a suitable adhesive thinly to the back of the metal scale and by aligning

the top edges of metal and paper carefully you will be able to stick the paper scale accurately and smoothly to the metal. Slide the scale back into place and screw into position, then snap the cover back on, starting by engaging it at the bottom edge. Check the pointer zeroing adjustment by turning the button adjuster.

PREPARING THE FRONT PANEL

At this point I have a confession to make. The case I used for this project was one I had had collecting dust on the workshop shelf for a number of years. It was a one-off case in the first place and so is not to be had from anywhere else.

However, as the whole assembly of board, meter and the other parts go on to a

single front panel, it might be worth looking round for a box having a minimum panel size 203mm by 152mm (8in by 6in) as this carries the component parts quite comfortably. A minimum depth of about 100mm (4in) for the box is adequate.

Perhaps it might not be unreasonable to suggest using a panel size of 203mm by 152mm cut from a piece of 16swg aluminium and then making a case up in the form of a simple wooden box measuring 203mm by 152mm by 100mm deep. The sides could be made from plywood and the back a piece of hardboard. This would save the trouble of hunting around for a suitable case and would be a lot cheaper.

Details for the panel cut-outs, assuming a size of 203mm by 152mm, are shown in Fig. 6. The four fixing holes on the top and bottom edges are not shown as the positions of these are not critical and have to suit whatever form of box the front panel will finally screw to.

The way the front panel is legended, using rub down lettering, is shown in the photographs. The actual size of the circular marked scales for the Range and Calibrate controls should suit the size of the knobs used; 25mm (1in) diameter are about right.

The four fixing holes for the meter are always a problem to position, but in the box which comes with the specified meter you will find a cardboard packing piece which serves excellently as a template for marking out the fixing holes relative to the large centre hole. Cut out the large circle *first* and then mark and drill the fixing holes.

A fretsaw is useful for cutting the meter hold if you haven't a punch. If you use a drop of paraffin or turps as a lubricant, you will find a fretsaw cuts 16swg aluminium with no great difficulty at all.

The input terminals SK1-SK3 are 4mm screw/socket types and are coloured red (HI), black (LO) and green (earth). You can if you wish go your own way here and use a BNC connector although this does not isolate the "earthy" input SK2 (LO) from the metal panel. With the socket terminals, don't forget the locating spigot on the terminal moulding.

ASSEMBLY

Once the front panel is ready, the meter, range switch, calibration potentiometer, input terminals and the mains switch and indicator can be mounted. The range switch is a two-wafer assembly and uses a pair of 1-pole 12-way wafers with the stop mechanism adjusted so that only the first seven positions are used.

Although standard size wafers and mechanism were used on the prototype, there is no reason why miniature wafers cannot be used, and this would in fact allow a little more room between switch and board. The switch mechanism has a projection on its front face which acts as an anti-rotation feature; a hole should be drilled in the panel so that this projection engages in it when the switch fixing nut is tightened up.

Put a tag under one of the lower fixing nuts of the meter and run a wire from this to the Earth terminal on the input grouping; also leave a few inches floating from this same tag to make connection to the transformer frame after the board has been fitted.

When the above points have been seen to, the board itself should be screwed to the meter terminals at positions M+ and M-.

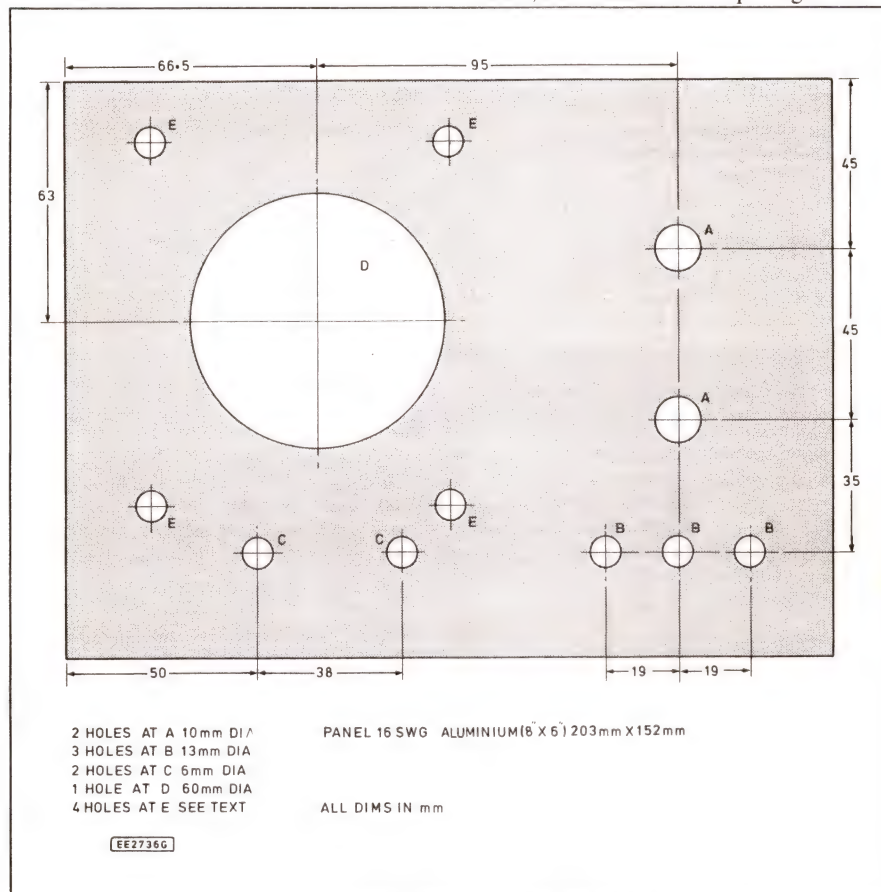


Fig. 6. Front panel drilling details.

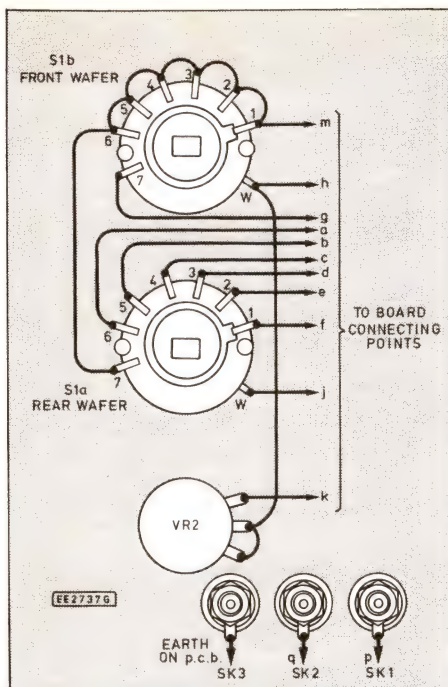


Fig. 7. Control and socket wiring.

The screws supplied with the meter can be used but they are a bit on the short side particularly if you put a washer under each head (as you should); if you can find two others with an extra eighth-inch of thread, use them.

INTERWIRING

Now wire up the range switches and the calibration potentiometer as detailed in Fig. 7. Contacts not used on the switch wafers are not shown. The actual position of the sliding contact on the wafers may differ from that illustrated, depending upon whether you use standard or miniature wafers, or other makes of switch. Loop the wires from the board to the switch contacts neatly and do not make them so short that they are tight anywhere.


Now wire up the transformer T1 primary via the on-off switch, not forgetting the neon indicator. You must stick some tape over the primary terminals and the switch tags, so that they are insulated and out of harms way while you carry out the calibration.

CALIBRATION

To get the best possible accuracy from the project, you need a Signal Generator covering the range 300Hz to 100kHz; failing that, if you can get hold of a 300Hz source of good accuracy, plus an oscillator which will go up to 100kHz even if it is not calibrated or particularly accurate, the work is not difficult.

First of all, set the front panel Calibrate control fully anticlockwise and the preset potentiometer (VR1) on the p.c.b. to about mid-position. Switch on the Frequency Meter and turn the Range switch to CAL.

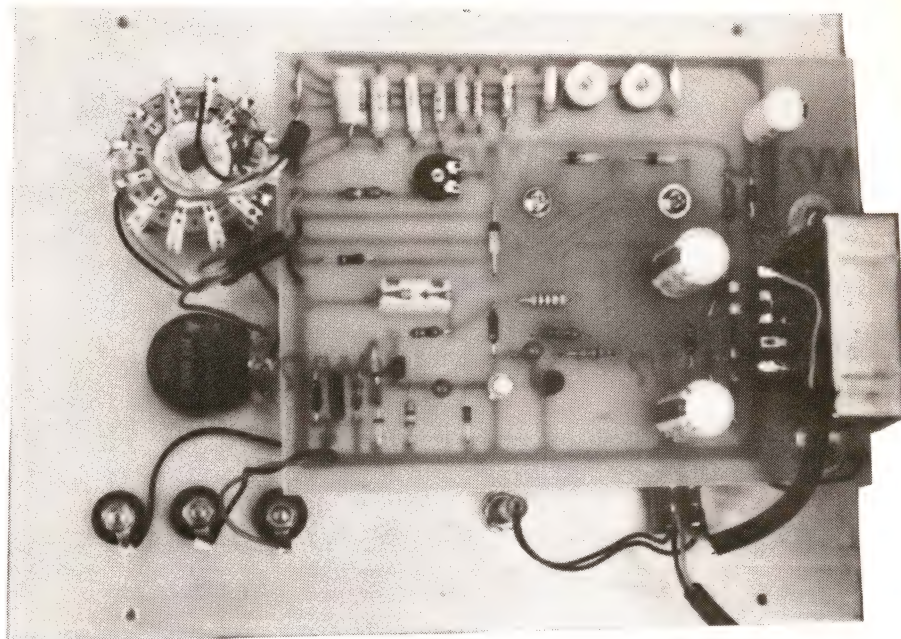The meter should not indicate anything on the frequency range positions of the switch but on the CAL position it should give a reading which should be adjustable over a small range by the Calibration control. The exact variation and its value is unimportant. If it does this and there are no other signs of circuit discontent, things are probably working out correctly.



Assuming now that you have or can lay your hands on a known source of frequency in the range 300Hz to 100kHz, proceed as follows: connect the signal source to the frequency meter input HI and LO terminals and set the output of the source to 300Hz at a level of a volt or so.

Turn the Range switch on the project to 0.3kHz and adjust the front panel Calibration control for full scale deflection (f.s.d.) of the meter. This should occur somewhere about the centre position of the control.

Now, *without* disturbing the Calibrate setting, switch the Range selector to CAL and adjust the preset potentiometer on the p.c.b. (VR1) to again provide f.s.d. on the meter. Switch back to the 0.3kHz position and check that the f.s.d. is unaffected.

This frequency range is now correctly set up. Check the range and operation by progressively reducing the input frequency from 300Hz down to 15Hz or so; the meter reading should accurately follow this variation.

What we now have to do on the next *three* ranges is to find the appropriate capacitor to parallel with those already mounted on the board to give us a correct frequency reading in each case. This might sound as though things are going to get difficult and tedious, but in practice the job is done fairly quickly and is well worth a bit of patience.

Here is the drill for the 1kHz range, and the rest follow similarly:

Temporarily connect a 3n9 capacitor (you can leave the leads full length at this stage) in parallel with the 10n already mounted in the C5 combination on the

board, using the appropriate solder pins. This value is in accordance with Table. 1. of values given earlier.

Switch the Range selector to 1kHz and set the signal source to 1kHz output; if you are lucky the meter will read full scale (equal to an input of 1kHz in frequency). If the reading is worse than ± 2 per cent or whatever accuracy you are settling for, you will need to make some adjustments.

If the reading is too low *add* a further capacitor in parallel with the 3n9; until you get about two per cent change in the reading per 100p added. If the reading is too *high*, replace the 3n9 with a 3n3 and add, say, a 470p so that you get an equivalent which is a little below the first 3n9 value.

When you get things right, solder the added capacitor(s) securely to the pins. None of these additional capacitors need be more accurate than five per cent.

Carry on in the same way for the 3kHz and 10kHz ranges, starting off with the added capacitor value as that indicated in Table. 1. and making any necessary adjustments to get the correct frequency reading. On the top two ranges, simply adjust the trimmer capacitors to bring the meter reading to the correct f.s.d. of 30kHz and 100kHz respectively.

Everything hinges on getting the 300Hz range right; after that, if you have no means of calibrating otherwise, the capacitor values given in Table. 1. should give you a not unreasonable overall accuracy to the other ranges.

The 50Hz mains supply can be used as a stop-gap measure in aligning the 300Hz range; put a bridge rectifier across the secondary of a low voltage transformer, 2V or 3V being enough, see Fig. 8. The output from this bridge will then be a 100Hz waveform which when connected to the frequency meter will indicate 100Hz on the 300Hz range. Do your initial calibration, then, at this point instead of at the f.s.d. point.

Whenever the instrument is used, the initial setting up simply consists of switching to CAL and adjusting the Calibrate control (if necessary) to f.s.d. before making any frequency measurements.

Next Month: Add-on Optical Sensor Tachometer.

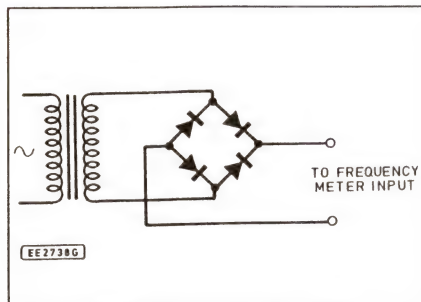


Fig. 8. Basic calibration circuit.

GHOST WAKER

MAX HORSEY



Create your own surprise on the night of Halloween. Even the "Ghost Busters" will be impressed

THIS is an ideal project for Halloween, but sound operated devices also have many other applications. The circuit employs a miniature microphone which causes a pair of eyes inside a mask to flick open for a short time. A pair of green l.e.d.s in the nostrils add to the eerie effect, particularly in subdued lighting.

PRINCIPLE OF OPERATION

Sound is picked up by the microphone (Fig. 1), and amplified by a simple op-amp pre-amplifier. The output from the op-amp is rectified (i.e. changed from a.c. to d.c.) and used to control a Darlington power amplifier. When the power amplifier switches on, a large current flows through the solenoid and l.e.d.s.

CIRCUIT DESCRIPTION

The microphone is an electret type, which is small, inexpensive, and particularly sensitive. Unlike ordinary dynamic types it requires a d.c. supply, and this is provided via R1 - see Fig. 2. The small alternating current from the microphone is fed via C1 to the non inverting input of IC1.

Capacitor C1 is necessary in order to isolate the d.c. voltage level at the lower end of R1, from the voltage at the junction between R2 and R3. This latter voltage is set at half the supply voltage.

and since the audio signal produced by the microphone is alternating, the signal can flow through C1 and into the non-inverting input pin 3. This causes a similar, but amplified alternating signal at output pin 6. In other words, the previously steady d.c. level is now fluctuating at the same frequency as the original sound wave.

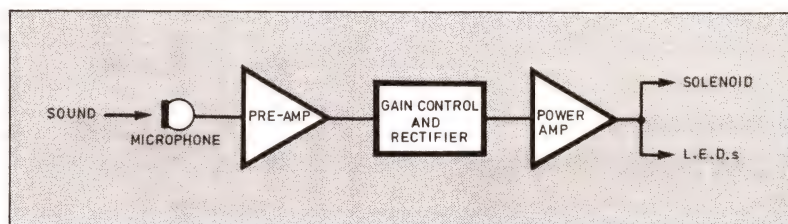


Fig. 1. System block diagram for the sound-operated "Mask".

The d.c. voltage at output pin 6 should equal the voltage at pin 3, and this is ensured by means of negative feedback, where R4 couples pin 6 to the inverting input pin 2. If the d.c. output voltage changes slightly, the change is inverted via pin 2, causing the output voltage to return to its correct value. Capacitor C3 blocks any flow of d.c. and therefore has no effect on these d.c. voltage levels. Capacitor C4 also blocks the flow of d.c. to the 0V rail.

Alternating currents are - in general terms - able to flow through capacitors,

Since resistor R4 connects the output back to the inverting input, the a.c. output would be cancelled out. However, capacitor C3 provides an a.c. path to 0V via R5. Now only part of the a.c. output arrives at pin 2, and the output is therefore only partially reduced. The ratio of R4 to R5 sets the approximate maximum a.c. gain achieved by the circuit.


POWER AMPLIFIER

The a.c. signal passes via C4 to VR1. The position of the slider on VR1 determines the signal level passed to the next stage. Diodes D1 and D2 act as a voltage doubler and rectifier, charging capacitor C7 to a d.c. voltage level which depends upon the amplitude (size) of the a.c. signal flowing via C5.

The value of C7 determines the time for which the eyes remain open after the sound has stopped. Resistor R7 regulates the discharge of C7 into the transistors (TR1 and TR2), which are connected as a Darlington pair. The gain achieved is determined by multiplying the gain of TR1 by the gain of TR2.

When the Darlington pair turns on, current flows via the solenoid, through TR2 to 0V. The l.e.d. D3 is wired in series with D4 and current limiting resistor R8. Diode D5 prevents damage caused to the transistors by back e.m.f. produced by the solenoid.

Fig. 2. Complete circuit diagram for the Ghost Waker mask.

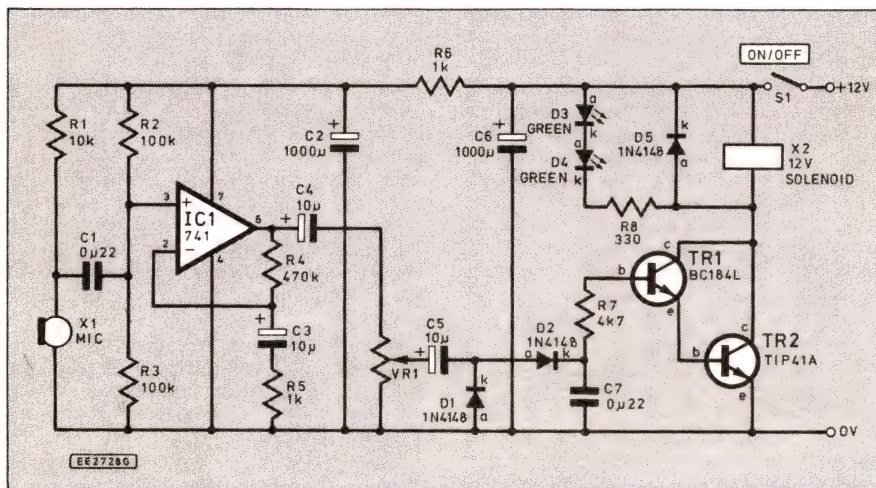

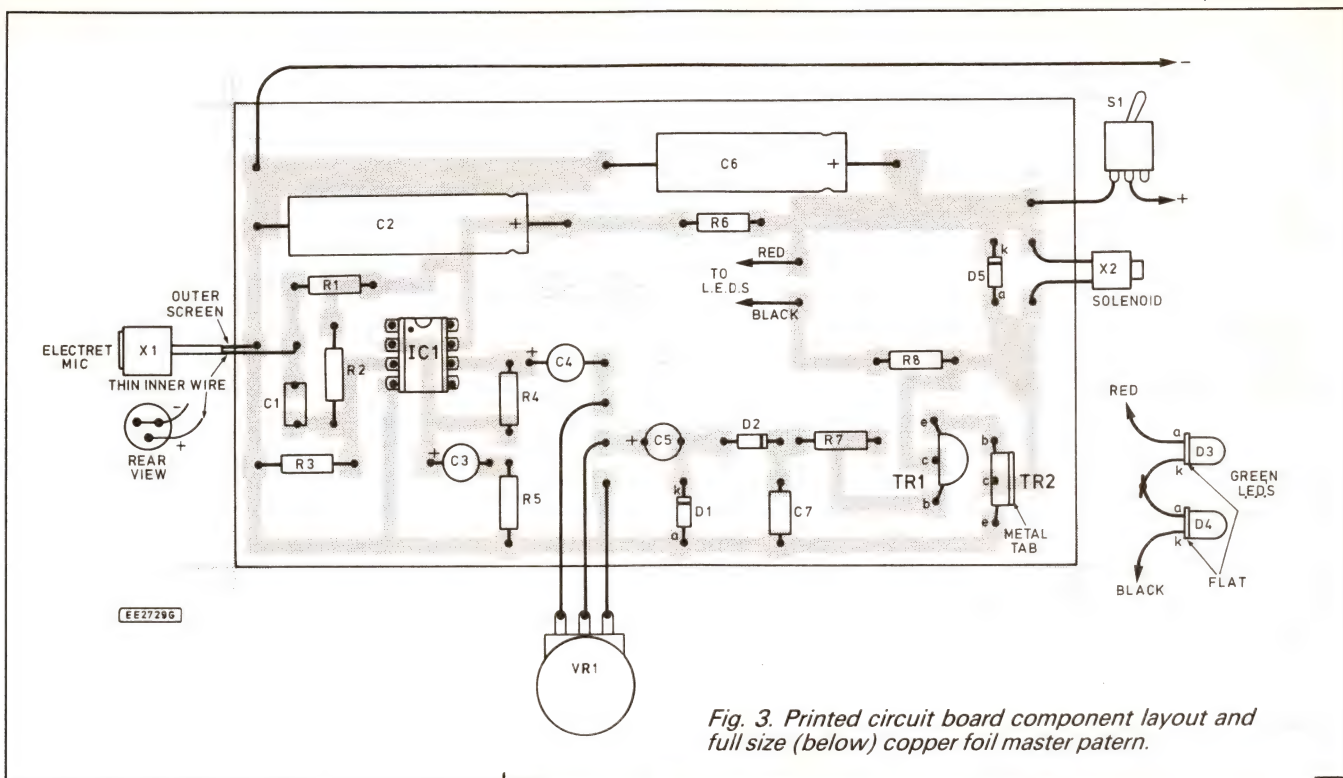


Fig. 3. Printed circuit board component layout and full size (below) copper foil master pattern.

DECOUPLING

The solenoid requires quite a large current, and this can cause voltage fluctuations which would upset the operation of the sensitive pre-amplifier. Resistor R6 is provided to partly isolate the power rails between the pre-amplifier, and power

COMPONENTS

Resistors

R1	10k
R2, R3	100k (2 off)
R4	470k
R5, R6	1k (2 off)
R7	4k7
R8	330

All 0.25W $\pm$ 5% carbon

Potentiometer

VR1	47k lin
-----	---------

Capacitors

C1, C7	0 μ 22 polyester (2 off)
C2, C6	1000 μ axial elect. 25V (2 off)
C3 to C5	10 μ radial elect. 25V (3 off)

Semiconductors

D1, D2,	
D5	1N4148 diode (3 off)
TR1	BC184L <i>n</i> p <i>n</i> transistor
TR2	TIP41A <i>n</i> p <i>n</i> transistor
D3, D4	I.e.d. green standard (2 off)


Miscellaneous

X1	microphone, electret type
X2	solenoid (small 12V type)
S1	on/off toggle switch
Printed circuit board, available from the EE PCB Service, order code EE703; case; screw for solenoid; Meccano or Fishertechnik type axle; Meccano supports, nylon thread, elastic thread, table tennis balls (2 off); thin cardboard; mask; beard, etc.; connecting wire; battery holder or main adaptor (see text); fixings etc.	

See
**SHOP
TALK**
Page

Approx cost
guidance only

£20

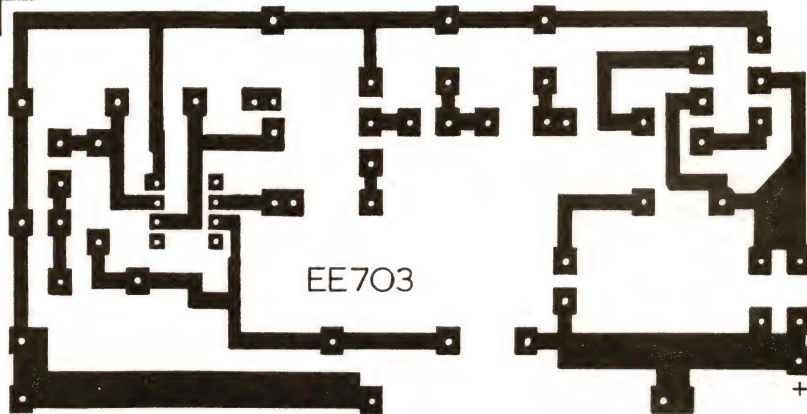

amplifier stages. Capacitor C2 helps to ensure a steady supply voltage for the pre-amp, and C6 provides general decoupling for the circuit.

CONSTRUCTION

The circuit is constructed on a p.c.b. shown in Fig. 3. Begin by soldering in the smallest components and i.c. socket. Check that the diodes and transistors are fitted the correct way round, and that a BC184L is used for TR1, and not a BC184 which has leads in a different order. Capacitors C2 and C6 are axial types, which lie flat against the p.c.b. Ensure that capacitors C2, C3, C4 and C6 are fitted the correct way round.

Connect wire leads for the microphone, i.e.d.s, solenoid and power supply. Switch S1 may be omitted if the circuit is to be powered from a mains power unit. Finally push the 741 i.c. into its socket, ensuring that pin one is in the correct corner. This i.c. is not sensitive to static electricity, and can be handled without precautions.

THE CASE

Any type of housing may be employed; some constructors may prefer to mount the circuit on a block of wood, with the



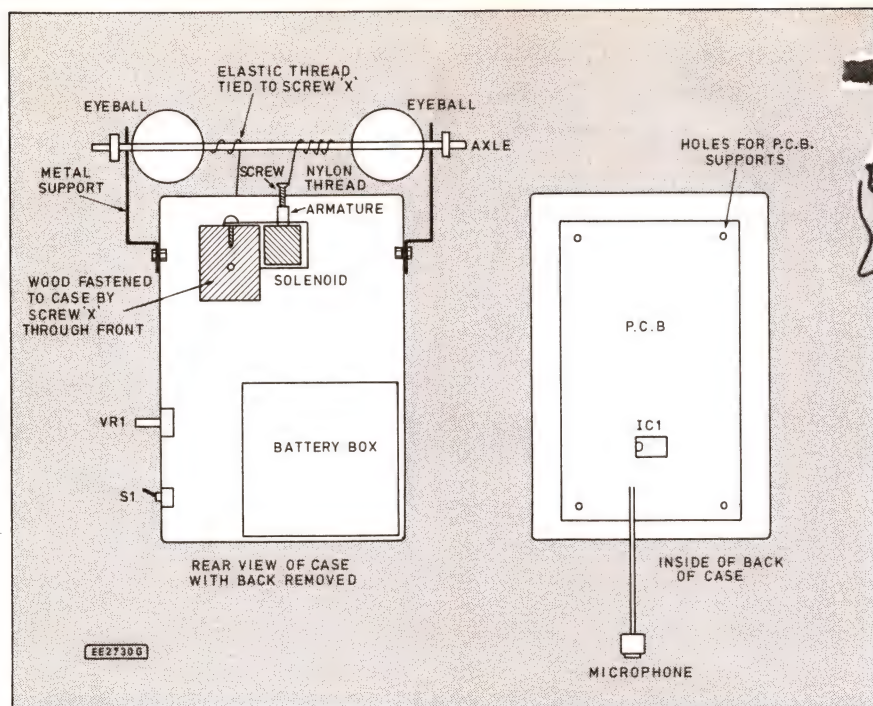


Fig. 4. Method of mounting the solenoid and p.c.b. inside the case. The "eyes" are held in position by strips of metal on the side of the case.

mask fully covering the circuit. However, the prototype was based around a standard plastic case, which houses the circuit, solenoid and batteries. All the awkward mechanical parts were then secured, enabling the mask to be fitted later. Begin by drilling holes for the solenoid armature screw, solenoid mounting block, axle supports, VR1, S1, and the leads for the l.e.d.s and microphone, see Fig. 4. The p.c.b. may be fastened by means of self adhesive p.c.b. supports.



Most solenoids allow a screw (e.g. size M6) to be inserted into the soft iron armature. Strong nylon thread is then used to link the screw to the axle which houses the table tennis ball "eyes". The solenoid must be positioned very carefully, using a small block of wood as shown. It should then be connected to the circuit, with the wires either way round.

EYES

The eyeballs are made using table tennis balls arranged as shown in Fig. 4. Holes should be made in the table tennis balls (a veroboard track cutter is ideal for this purpose), so that they make a tight fit on the axle. The prototype axle was a standard Meccano or Fischertechnik type.

The thread attached to the solenoid armature causes the balls to rotate one way, and the elastic thread pulls them back. Sticky tape may be used to fix the threads to the axle. The eye movement is limited by the armature resting against the top surface of the case when the eyes are closed, and by the armature being pulled fully into the solenoid coil when the eyes are open. Long eyelashes made from thin cardboard are fastened to the eyeballs using double sided sticky tape, or glue, AFTER the mask has been fitted.

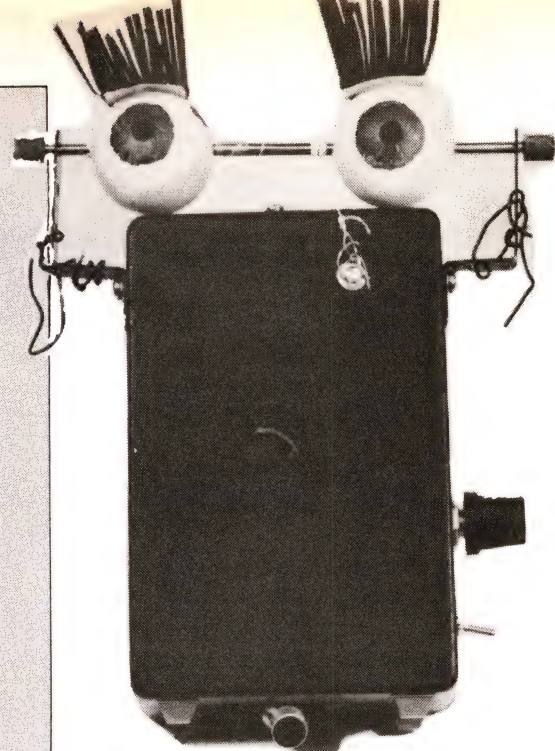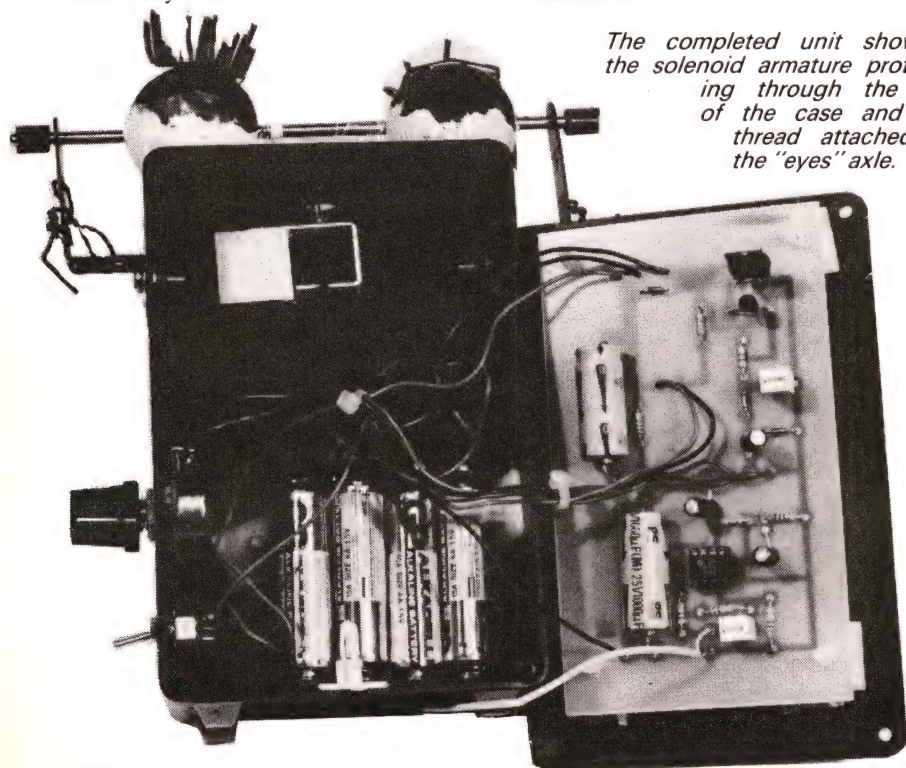The completed unit showing the solenoid armature protruding through the top of the case and the thread attached to the "eyes" axle.



The screw on the top right anchors the elastic thread and also holds the solenoid in position. The two leads from the centre go to the "nostril" l.e.d.s.

Long insulated leads should be fitted to the p.c.b., and inserted through the hole in the case BEFORE the l.e.d.s are connected. Ensure that the l.e.d.s are connected the correct way round - colour coding the wires will help avoid mistakes. The l.e.d.s may then be pushed into holes made in the mask, just before the mask is put in position.

MICROPHONE

The microphone may be positioned inside the case, however there is a danger that it may pick up noise from the solenoid. The best position is probably below the project case, just behind what will become the beard of the ghost. In this case screened wire should be used to connect the microphone to the circuit.

Certain suppliers provide microphones with screened cable already fitted, but otherwise follow the diagram (Fig. 3.) very closely to ensure that the microphone is connected the correct way round.

POWER SUPPLY

A set of eight 1.5V (AA type) batteries is suggested. However, for long term use a mains adaptor could be employed; these cost little more than a couple of sets of batteries, but be sure to select an adaptor which can supply enough CURRENT to drive the solenoid, about 500mA in the prototype.

The adaptor need not be regulated, since any voltage between 12V and 20V is satisfactory. However, voltage fluctuations may cause the circuit to become unstable, resulting in the eyes continually opening and closing! This may be cured by using either a proper voltage regulator, a power supply with a larger current output, or a very large capacitor across the supply rails. Experiment for the best results!

TESTING

If a voltmeter is available, it is helpful to check the voltage across the supply rails immediately the power is applied. Any drop much below 12V indicates a serious fault, and the supply can be switched off

before damaging the circuit, or running down the batteries.

Assuming that S1 is switched on, and all is well, wait a few seconds for C3 to charge, and the pre-amp to begin to operate. Turn VR1 to full gain (fully clockwise if wired correctly), and make a sound. The l.e.d.s should light and the solenoid operate for a short time. If nothing happens, try turning VR1 fully anti-clockwise in case it is connected incorrectly.


FAULT FINDING

Common mistakes include connecting the microphone the wrong way round, and connecting the l.e.d.s, diodes, transistors and capacitors the wrong way. Check all these items, then check for poor soldered joints, or bridged connections, particularly around the i.c. Note that the spare pins, 1, 5, and 8 must NOT be connected to any other part of the circuit.

Check the voltage across pins 7 and 4 of IC1. You should obtain a reading of about 12V. Now connect the negative lead of the voltmeter to 0V on the circuit, and use the positive lead as a probe. You should obtain the following readings to within about a volt:

Pin 7 of IC1	: 12V
Pin 3 of IC1	: 6V
Pin 6 of IC1	: 6V
Junction between R1 and microphone	: 3V to 10V

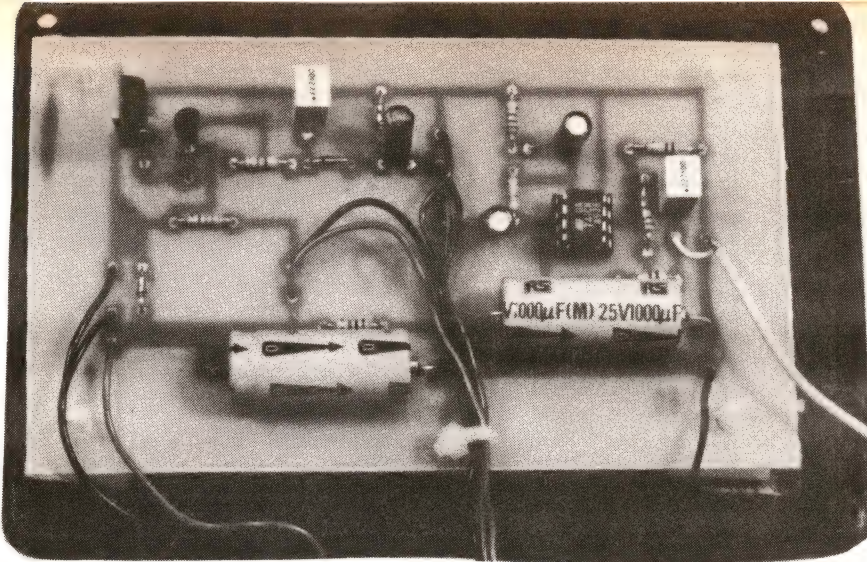The failure of any test indicates a fault in that area – perhaps a wrong resistor value, or a poor connection.



Layout of components on the completed printed circuit board. The screened lead on the right-hand edge of the board connects to the microphone.

The junction between D2, R7 and C7 provides a useful test point. The voltage at this point should be below 1.2V when the solenoid is off, and above 1.4V when the solenoid is on. A further crude, but helpful test is to join this point directly to positive, using a piece of wire. The l.e.d.s and solenoid should operate. If this fails, the power amplifier section is at fault.

Beyond this, an oscilloscope will determine whether the microphone is providing an alternating signal at pin 3 of IC1. An amplified signal should be present at pin 6. Note that the output signal may be distorted (clipped), but this is of no consequence in this type of circuit.

Masks vary so much that only a general guide is possible. It will probably be necessary to enlarge the eyes to accommodate the table tennis eyeballs. The mask may be fitted to the supports holding the axle, using stiff wire. Any gaps around the eyeballs can be filled with hair, eyebrows etc. A beard will conceal the bottom of the case and microphone, and long eyelashes are fitted as described earlier. Any further refinements can be left to the imagination of the constructor.

The overall effect is quite eerie, and may alarm unsuspecting visitors. At any rate, it will provide an amusing talking point, and help get the party going!



HART AUDIO KITS – YOUR VALUE FOR MONEY ROUTE TO ULTIMATE HI-FI

HART KITS give you the opportunity to build the very best engineered hi-fi equipment there is, designed by the leaders in their field, using the best components that are available. With a HART KIT you have direct access to the friendly HART service, you are not dealing through, or paying for, any middlemen. Every HART KIT is not just a new equipment acquisition but a valuable investment in knowledge, giving you guided hands-on experience of modern electronic techniques. Telephone or write for your FREE LISTS giving full details of all our Kits, components and special offers. Here are a few selected items: –

AUDIO DESIGN 80 WATT POWER AMPLIFIER



This fantastic John Linsley Hood designed amplifier is the flagship of our range, and the ideal powerhouse for your ultimate hi-fi system. This kit is your way to get E.K. performance for a few tenths of the cost! Featured on the front cover of "Electronics Today International" this complete stereo power amplifier offers World Class performance allied to the famous HART quality and ease of construction. John Linsley Hood's comments on seeing a complete unit were enthusiastic: – "The external view is that of a thoroughly professional piece of audio gear, neat, elegant and functional. This impression is greatly reinforced by the internal appearance, which is redolent of quality, both in components and in layout."

The standard amplifier comes with the option of a stereo LED power meter and a versatile passive front end giving switched inputs, and ALPS precision, low-noise volume and balance controls. A new relay switched front end option also gives a tape input and output facility. This means that for use with tuners, tape and CD players, or indeed any other 'flat' inputs the power amplifier may be used on its own, without the need for any external signal handling stages. 'Slave' and 'monobloc' versions without the passive input stage and power meter are also available.

All versions fit within our standard 420 x 260 x 75mm case to match our 400 Series Tuner range. ALL six power supply rails are fully stabilised and the complete power supply, using a toroidal transformer, is contained within a heavy gauge aluminium chassis/heat-sink fitted with IEC mains input and output sockets. All the circuitry is on a proper printed circuit with low-resistance blade connectors for the six stabilised DC outputs.

HART KITS don't leave you to fasten a few capacitors to the floor of the main chassis and wire the power supply the hard way! HART wiring is even pre-terminated, ready for instant use! Remember with a HART KIT you get the performance you want at the price quoted through proper engineering design and the right components. We do not insult your intelligence by offering a kit at what seems a fair price and then tell you that you have to spend three times as much to get an

upgraded model!
RLH Reprints of latest 'Audio Design Amplifier' articles.....£2.70
K1100CM HART Construction Manual with full parts list.....£4.50
Why not buy the reprints and construction manual to see how easy it is to build your own equipment the HART way. The FULL cost can be credited against your subsequent kit purchase.

SPECIAL OFFERS FOR THE NEXT MONTH

All orders for complete kits will get the ALPS Precision Pots in the Passive Input Stage included FREE. We can also include the new Relay Switched Input Stage, normally £57.28, for only £30!

ALPS PRECISION LOW-NOISE STEREO POTS



Now back in stock, the last batch sold out months ago! Exciting range of precision audio pots in values to cover most quality amplifier applications. All are in 2-gang stereo format, with 20mm long 6mm dia. steel shafts, smooth rotation type with no indents.

Now you can throw out those noisy ill-matched carbon pots and replace with the real hi-fi components only used selectively in the very top flight of World Class amplifiers, and HART Kits! The improvement in track accuracy and matching really is incredible giving better tonal balance between channels and rock solid image stability. Values available are 10K and 100K Log, 100K Lin and 10K Special Balance. (Zero loss in centre position). Our prices are incredibly low for pots of this quality due to large purchases for our quality kits.

2-Gang Lin.....	£8.67
2-Gang Log.....	£8.67
2-Gang Special Balance, zero crosstalk and zero centre loss.....	£9.40

LINSLEY HOOD 400 SERIES SUPER HIGH QUALITY AM/FM TUNER SYSTEM

This ultra high quality analogue tuner system is the ideal companion to the 80W Audio Design Amplifier in any ultimate hi-fi setup, with case size, front plate layout and even control pitches unified for stacking. Like the 80W Audio Design Amplifier this is your route to ultimate performance at incredibly low cost! Two designs by John Linsley Hood make up this combination of his ultra high quality FM tuner and stereo decoder and the Synchrodyne AM receiver. Novel circuit features in the FM section include ready built pre-aligned front end, phase locked loop demodulator with a response down to DC and advanced sample and hold stereo decoder together making a tuner which sounds better than the best of the high-priced exotica but, thanks to HART engineering, remains very easy to build and set up. The Synchrodyne AM section with its selectable bandwidth provides the best possible results from Long and Medium wave channels, so necessary in these days of split programming. If you want the very best in real hi-fi listening then this is the tuner for you. Since all components are selected by the designer to give the very best sound this tuner is

not cheap, but in terms of its sheer sound quality it is incredible value for money. To cater for all needs AM only and FM only versions are available as well as the full AM/FM model, with any unit being upgradeable at any time. For further details see our fully illustrated lists.

RLH7 Reprints of articles describing the 'Synchrodyne' Section.....£2.60
INS450 Construction Manual for 'Synchrodyne' AM Section.....£2.90
RLH8 Reprints of 3 articles covering the FM Tuner Section.....£2.70
INS400 Construction Manual for FM Section.....£4.90
Don't forget you can buy the construction manual and reprints to see how easy it is and the cost will be credited IN FULL when you buy your kit.

HIGH QUALITY REPLACEMENT CASSETTE HEADS



Do your tapes lack treble? A worn head could be the problem. Fitting one of our replacement heads could restore performance to better than new! Standard inductances and mountings make fitting easy on nearly all machines and our TC1 Test Cassette helps you set the azimuth spot on. As we are the actual suppliers you get prime parts at lower prices, compare our prices with other suppliers and see! All our heads are suitable for use with any Dolby system and are normally available ex stock. We also stock a wide range of special heads for home construction and industrial users.

HS16 Sendust Alloy Stereo Head, high quality head with excellent frequency response and hyperbolic face for good tape contact.....£17.86
HC40 NEW RANGE High Beta Permalloy Stereo Head. Modern space saver design gives excellent high-frequency response with easy fitting and lower cost. Suitable for chrome, metal and ferric tapes, truly a universal replacement head, with ample quality for hi-fi decks and cheap enough for car players!.....£6.86

HS100 Special Offer Stereo Permalloy Head.....	£2.86
HRP373 Downstream Monitor Stereo Combination Head.....	£44.39
HQ551 4-Track Record & Play Permalloy Head for auto-reverse car players or quadraphonic recording.....	£16.79
H524 Standard Erase Head.....	£2.59
HQ751E 4/4 AC Erase Head, tracks compatible with HQ551.....	£57.06
REEL TO REEL HEADS	
S99R 2/4 Record/Play 110mH.....	£13.34
S99E 2/4 Erase Head 1mH, Universal Mount.....	£11.96

TAPE RECORDER CARE PRODUCTS
HART TC1 TEST CASSETTE. Our famous triple purpose test cassette. Sets tape azimuth, VU level and tape speed.....£5.36
DEM1 Mains Powered Tape Head Demagnetizer, prevents noise on playback due to residual head magnetisation.....£4.08
DEM115 Electronic, Cassette Type, demagnetizer.....£8.61

Our new Summer '90 price list is FREE. Send for your copy now. Overseas customers welcome, please send 2 IRCs to cover surface post or 5 for Airmail. We now accept inland and overseas order by post or telephone on all Access, Master and Visa Credit Cards.

Please add part cost of carriage and insurance as follows:
INLAND: Orders up to £20 – £1, Orders over £20 – £2.50;
Next day – £9. OVERSEAS: Please see the ordering information with our lists.

QUALITY AUDIO KITS

24hr SALES LINE
(0691) 652894

ALL PRICES INCLUDE VAT



TRANSISTORS		COMPUTER IC'S	
AA132	9p	2114	200p
AC107	40p	2532	330p
AC125	25p	2536	200p
AC126	25p	2537	200p
AC127	21p	2538	200p
AC128	21p	2539	200p
AC128K	26p	2540	200p
AC141K	30p	2541	200p
AC142K	30p	2542	200p
AC176	28p	2543	200p
AC176K	28p	2544	200p
AC187	21p	2545	200p
AC187K	28p	2546	200p
AC188	21p	2547	200p
AC188K	28p	2548	200p
AC189	48p	2549	200p
AC191	48p	2550	200p
AD149	60p	2551	200p
AF124	50p	2552	200p
AF125	50p	2553	200p
AF126	50p	2554	200p
AF127	50p	2555	200p
AF139	30p	2556	200p
AF239	30p	2557	200p
AF379	45p	2558	200p
BA145	10p	2559	200p
BA148	10p	2560	200p
BA154	8p	2561	200p
BA157	8p	2562	200p
BB105B	18p	2563	200p
BB205B	24p	2564	200p
BC107	8p	2565	200p
BC108	8p	2566	200p
BC109	8p	2567	200p
BC109C	8p	2568	200p
BC115	10p	2569	200p
BC118	11p	2570	200p
BC140	20p	2571	200p
BC141	20p	2572	200p
BC142	20p	2573	200p
BC143	20p	2574	200p
BC147	8p	2575	200p
BC148	8p	2576	200p
BC149	8p	2577	200p
BC157	8p	2578	200p
BC159	8p	2579	200p
BC160	8p	2580	200p
BC171	10p	2581	200p
BC172	10p	2582	200p
BC177	14p	2583	200p
BC178	14p	2584	200p
BC179	14p	2585	200p
BC182	7p	2586	200p
BC183	7p	2587	200p
BC183L	7p	2588	200p
BC184	7p	2589	200p
BC184L	7p	2590	200p
BC212	7p	2591	200p
BC212L	7p	2592	200p
BC213	7p	2593	200p
BC213L	7p	2594	200p
BC214	7p	2595	200p
BC214L	7p	2596	200p
BC237	7p	2597	200p
BC238	7p	2598	200p
BC239	7p	2599	200p
BC300	20p	2600	200p
BC301	20p	2601	200p
BC302	20p	2602	200p
BC303	20p	2603	200p
BC304	20p	2604	200p
BC308	10p	2605	200p
BC327	7p	2606	200p
BC328	7p	2607	200p
BC337	7p	2608	200p
BC338	7p	2609	200p
BC441	28p	2610	200p
BC446	8p	2611	200p
BC449	15p	2612	200p
BC461	28p	2613	200p
BC477	18p	2614	200p
BC478	18p	2615	200p
BC479	18p	2616	200p
BC489	20p	2617	200p
BC490	18p	2618	200p
BC516	22p	2619	200p
BC528	22p	2620	200p
BC537	8p	2621	200p
BC546	8p	2622	200p
BC547	8p	2623	200p
BC548	8p	2624	200p
BC549	8p	2625	200p
BC560	8p	2626	200p
BC566	8p	2627	200p
BC567	8p	2628	200p
BC568	8p	2629	200p
BC777	8p	2838	200p
BC778	8p	2839	



*a regular
feature for
the Spectrum
Owner...*

by Mike Tooley BA

LAST MONTH we described some applications for our SAM Coupé S-Channel ADC. This month, in our sixty-eighth and last *On Spec*, we shall be rounding off the series by dealing with a number of odds and ends, hints and tips, and queries sent in by readers.

We shall begin, however, by indulging in a little nostalgia as we look back over the past six years at some of the milestones in the development of the Spectrum and SAM computers.

Swan Song

Sir Clive Sinclair's vision of low-cost computing for the masses astonished many of the pundits a decade ago. Until the advent of the ZX-81 (and later the Spectrum) computers suitable for "home use" were either "bottom-of-the-range" (but nevertheless expensive) CP/M machines or were systems which were put together as kits (remember the UK-101?) by those having already gained some expertise in electronics.

In 1982, the idea that a colour computer with 16 or 48K of RAM could be available at less than £100 was nothing short of amazing! Nevertheless, it was Sir Clive's foresight and imagination that took this concept into reality and a whole new generation of computer users was borne overnight.

Furthermore, the Spectrum went from strength to strength. Improvements to the basic 16K machine included the Spectrum 48K, Spectrum Plus, 128K, Plus Two, and later the Amstrad/Sinclair Plus Three machine.

During this time a large number of software houses and third party hardware suppliers were busy climbing onto an unstoppable rolling bandwagon. Not surprisingly, some of these companies failed but others went on to become major international concerns employing hundreds of hardware and software engineers. One such company (which was involved at the beginning) was Miles Gordon Technology. It was their bold decision to further develop the Spectrum line with a revolutionary new home computer, the Sam Coupé.

Owners of the Coupé (me included) can be justifiably proud of this machine. It

corrects many of the shortcomings of the Plus Two and Plus Three machines and provides a performance which rivals many of today's 16-bit home computers. One can only hope that the development of this machine continues and that further support will be forthcoming from software developers eager to take advantage of the power of this machine.

On Spec Awards

Whilst the Spectrum was a bold new concept, it is undeniably true that the machine would not have gained so much popularity without the enthusiastic support of a great many third party hardware and software developers. In such a small space, it is unfortunately impossible to mention all of those concerned: so, with tongue in cheek, I have drawn up my own personal list of *On Spec Awards* for excellence in support of the Spectrum.

Regrettably, many of today's computer products (both software and hardware) get "hyped" into the market by over-enthusiastic sales promotion. For this reason, my personal accolade is based on innovation rather than commercial success. Here are the "winners":

ON SPEC AWARDS

Best peripheral hardware: MGT's **Disciple** interface.

Best productivity software: Joint winners, Kemsoft's **PCB Designer** and Besoft's **Electrodraw**.

Best software development tool: Ocean's **Laser Genius** machine code development system. *Laser Genius* was written by Chris Smith, Andrew Foord and Kevin Hambleton.

Best Spectrum programming language: Betasoft's **BETA BASIC**.

Best Spectrum book: **Understanding your Spectrum - BASIC and Machine Code Programming** by Dr Ian Logan (published by Melbourne House ISBN 0 86161 111 X).

Points from the post

H. De Groot writes from Pretoria South Africa with a useful snippet for owners of early versions of the Spectrum. Mr de Groot writes:

"Recently I have had two Spectrum Issue Two for repair. Both had the same fault: R56 (56 ohm) resistors in the - supply circuit burnt out. This voltage is only used in the 16K RAM. The question was, which chip had failed?"

Your articles in On Spec May and December 1989 were very helpful. Somebody told me that the 4116 are very unreliable and they can be replaced with 4164 after making a few on-board modifications as follows:

- Leave pin-1 of each RAM disconnected (I bend the pin upwards)*
- Pin-8 should be connected to VCC (+5V not +12V)*
- Pin-9 should be connected to ground.*

Mr de Groot suggests that a large number of RAM problems can be eliminated with this modification. The modification effectively uses half of the available memory capacity of the 4164 (the upper half is unused as the A7 input on pin-9 is held permanently low by grounding).

The 4164 employs only a single +5V supply rail, rather than the three rails (-, +5 and +12V) required by the 4116. I am uncertain as to whether the 4116 is any

less reliable than the 4164 however, since the latter device uses only a single supply rail, the equipment has to be very much more reliable since it will be very much less susceptible to faults which arise from the power supply rails!

Also on the topic of 4116 RAMs, **Walter Wirth** writes from Colombo Sri Lanka to describe a fault which recently occurred to his Spectrum Plus. Walter writes:

"I write with reference to your On Spec column in the December issue of Everyday Electronics. The day after this issue arrived, my Spectrum Plus went faulty from mains fluctuation. On power-up the computer partially initialised and locked up. I was left with a yellow screen, some randomly distributed 'set' pixels and, instead of the Sinclair copyright message, some gibberish consisting of partially formed and garbled letters.

After much testing, I traced the fault to 'open' 4116 DRAM chips IC9 and IC13. These are in the lower 16K RAM. Because this area holds the System Variables and screen display data, a fault in lower RAM can cause all sorts of problems. 'Open' chips do not overheat so can be a great pain to troubleshoot. The fault was finally detected by 'piggyback' substitution of good RAM chips.

For your readers' reference Television magazine ran an excellent series of articles by Ken Taylor on servicing Sinclair computers in the May to October 1986 issues.

Walter Wirth is trying to make contact with several UK based manufacturers of peripherals, including RAM Electronics and Quasar Software. If any reader can provide an up to date address, fax or telephone number for either of these firms please drop me a line so that I can pass on the information.

High Price

Chris West has sent me a very interesting letter from Canterbury in which he bemoans the relatively high price of non-games software for the Spectrum. Chris writes:

"I was pleased to read your recent reviews of some of the electronic CAD packages available for the Speccy. Unfortunately, these are somewhat expensive compared to the games software which I normally buy. Can you explain why this is? How easy would it be for me to write my own CAD program and would I have to use machine code?"

Well, Chris, I must confess that I just don't agree with you concerning the price of the CAD packages recently reviewed in *On Spec*. Both Kemsoft's **PCB Designer** and Besoft's **Electrodraw** are first class packages offered at a fraction of the cost of similar offerings designed to run on a PC.

Furthermore, just because these programs run on a humble Spectrum they should not be regarded as in any way inferior. For the enthusiast working at home, they both provide an affordable route into electronic CAD!

As regards writing your own package. I certainly hope that you have plenty of time available! Spectrum BASIC would almost certainly be far too slow for the time critical routines associated with manipulation of screen images and thus a good starting point would be the acquisition of a good book on machine code, an assembler and monitor, and a disk drive (and interface) to remove some of the tedium associated with software development in a cassette based environment. All of this will

cost many times more than a ready made electronic CAD package even without considering the hundreds of hours needed to perfect the software!

MGT

Several readers have asked for further information concerning the demise of MGT and, in particular, for details of where to go for support for the Sam Copé. I am, therefore, very happy to report that, by the time that you read this, the "Sam Coupé Hotline" should be up and running. This service will provide all the latest news, hints and tips for Sam owners updated every week.

The material will be produced by Alan Miles and Bruce Gordon (creators of the Coupé) and should certainly prove invaluable to users. The service is available on ☎ 0898 299380 and calls are charged at 25p per minute at the "cheap rate" and 38p per minute at other times. For further information contact Bruce Everiss on ☎ 0926 640137.

And finally...

In closing this series, I would like to extend a very sincere thank you to all those readers who have taken the time and trouble to write with hints, tips, and queries.

When I started writing the first *On Spec* (some six years ago) I little thought that the series would run for so long. At the time, I recall suggesting to Mike Kenward that the series would stand or fall on the level of interest from readers (without a regular in-

jection of ideas and material I certainly did not think I could keep *On Spec* going for very long!)

In reality, the support from readers has been truly amazing, indeed in the early years each day's post seemed to bring in something new from an *On Spec* reader. It is this, more than anything else, that has made the series worthwhile for me.

Finally, if you have any suggestions for inclusion in a possible future series, please don't hesitate to drop me a line at the address below. I regret that I cannot answer letters on an individual basis but rest assured that your comments will be noted and passed on to the Editor.

Mike Tooley, Faculty of Technology, Brooklands College, Heath Road, Weybridge, Surrey KT13 8TT.

C.E.S.N.W. FOR ELECTRONIC COMPONENTS

TEST EQUIPMENT REPAIRS IBM PC ACCESSORIES AT DISCOUNT PRICES

Let us source that difficult to find component for your kit or project

Send for details of all our services.

**Appt. 2, No 8 Meirion Gardens
Colwyn Bay, Clwyd
North Wales LL29 7PR**

Tel: 0492 533083 Fax: 0492 534716

CAMBRIDGE COMPUTER SCIENCE LIMITED

☆ 10MByte Winchester, used 3 months Wty.	£42.00 each
☆ 5.25" Disk Drives, 80 Tk. DSD	£34.00 each
☆ 5.25" Disk Drives, 80 Tk. DSD, used, no Wty (Sold on a strictly "as is" basis)	£15.00 each
☆ 5.25" Disks, DSD, 48tpi boxes of 10	£3.00 box
☆ 40W PSU 5V 3.75A, 12V 1.5A, 12V 0.4A, cased with on/off switch	£10.00 each
☆ Bare switch mode PSU 5V 2.5A, 12V 2A, 12V 0.1A	£7.00 each
☆ 8086 CPU chips	£2.00 each
☆ 280A CPU, CTC, PIO	£1.20 each; DMA £2.00
☆ 74LS TTL, pick and mix, buy 10 or more for	£4.50 all 4
Types available: 00 02 04 08 11 12 13 15 20 21 26 27 30 32 33 38 42 74 83 96 107 109 122	
☆ 132 136 139 145 151 153 157 158 162 163 164 165 174 191 193 253 257 298 353 365 670	
☆ 2764 EPROMS (Ex-equipment)	£1.00 each or £5.00/5
☆ 27128 EPROMS	£2.50 each
☆ 27C256-25 EPROMS	£3.50 each
☆ 256K Byte DRAM Modules, removed from equipment	£6.00 each
☆ 6116 2K Byte SRAM	£1.10 each
☆ 6264 8K Byte SRAM	£3.80 each
☆ 65256 32K Byte RAMS	£7.00 each
☆ 8K Byte NV RAM chips	£3.00 each
☆ 20-pin dill low profile IC sockets	£0.50/10
☆ 40-pin dill low profile IC sockets	£0.60/10
☆ DEC LS111 (23 CPU cards used but working)	£50.00 each
☆ CPU cards (Newbrain) 280 CPU, 3 EPROMS & 60+ mostly 74LS ICs	£2.00 each
☆ LCD graphics module 240 by 64 pixel with drive chips	£13.00 each
☆ Circuit tester, finds faults in TTL & CMOS logic circuits, inc. leads	£8.00 each
☆ Keyboard, 100 keys on board LCD & micro i/f	£8.00 each

Prices include postage. Add 50p (plus VAT) to orders below £5.00. All items new unless stated. Add 15% VAT to all prices. Send an SAE for our latest list or for more info.
Dept EE, 374 Milton Road, Cambridge CB4 1SU
Tel: 0223 424602 or 0831 430496 (Please note mail order only)

GEM TECH Ideal Learning Projects for All

Putting you on the
Diamond Road
to Electronics

Kits for
all
abilities
Step-by-Step
Instructions

plus
Tutorials
Books
and
Features

Projects
for
Motoring
Audio
Lighting
Metering
Effects
etc.

plus
PCB
Making
Materials
and equipment

Catalogue
only
50p

plus
Assembly
Tools

plus Test Gear

Plus this month's
Special Offers!

GEM-TECH
Dept EE10, Unit J
8 Finucane Drive,
Orpington,
Kent BR5 4ED

MAIL ORDER

VARIABLE VOLTAGE TRANSFORMERS

INPUT 220/240V AC 50/60 OUTPUT 0-260V	Price	P&P
0.5KVA 2.5 amp max	£29.00	£3.75 (£37.65 inc VAT)
1KVA 5 amp max	£37.40	£4.25 (£41.65 inc VAT)
2KVA 10 amp max	£54.00	£5.48 (£59.48 inc VAT)
3KVA 15 amp max	£71.50	£6.24 (£77.74 inc VAT)
5KVA 25 amp max	£128.50	(Carriage on request)

VOLTAGE CHANGING TRANSFORMER
1250 Watt auto. Tapped 0-90V, 100, 110, 115, 120 twice to obtain voltages between 90 and 240V. Fitted in heavy duty louvered metal case. Fused input. Price incl VAT & p&p £39.50.

COMPREHENSIVE RANGE OF TRANSFORMERS-LT-ISOLATION & AUTO (110-240V Auto transfer either cased with American socket and mains lead or open frame type. Available for immediate delivery.

ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES
4ft 40 watt £10.44 (£12.00 inc VAT) **Caller only**
2ft 20 watt £7.44 + £1.25 p&p (£8.69 inc VAT)
13in 10 watt £5.80 + 75p p&p (£6.55 inc VAT)
12in 8 watt £4.80 + 75p p&p (£5.55 inc VAT)
9in 6 watt £3.96 + 50p p&p (£4.46 inc VAT)
6in 4 watt £3.96 + 50p p&p (£4.46 inc VAT)
230V AC BALLAST KIT for either 6in, 9in or 12in tubes £5.50 + 55p p&p (£6.05 inc VAT)
For 13in tubes £6.00 + 75p p&p (£6.75 inc VAT)

400 WATT UV LAMP

Only £34.00 + £2.50 p&p (£41.98 inc VAT)
175 WATT SELF BALLASTED BLACK LIGHT MERCURY BULBS Available with BC or ES fitting. Price incl VAT & p&p £19.84.

12 VOLT BILGE PUMPS

Buy direct from the importers
500 GPH 15ft head 3 amp
£16.00 inc.
1750 GPH 15ft head 9 amp
£20.18 + £2.00 p&p (£25.50 inc VAT)

EPROM ERASURE KIT

Build your own EPROM ERASURE for a fraction of the price of a made-up unit kit of parts less case includes 12in 8 watt 2537 Angstrom Tube Ballast unit pair of bi-pin leads neon indicator on/off switch safety microswitch and circuit £14.00 + £2.00 p&p (£18.40 inc VAT)

SUPER HY-LIGHT STROBE KIT

Designed for Disco, Theatrical users etc.
Approx 16 joules. Adjustable speed £48.00 + £2.00 p&p (£57.50 inc VAT)
Case and reflector £22.00 + £2.00 p&p (£27.60 inc VAT)
SAE for further details including Hy-Light and Industrial Strobe Kits.

WIDE RANGE OF XENON FLASHTUBES

Write/Phone your enquiries
EXTENSIVE RANGE OF DIFFERENT TYPES OF GEARED MOTORS AVAILABLE FROM STOCK

WASHING MACHINE WATER PUMP
Brand new 240V AC fan cooled can be used for a variety of purposes. Inlets 1 1/2 ins. Outlet 1 inch. Price including p&p and VAT — £10.95 and £2 for £20 including p&p and VAT.

12V DC 20 RPM REVERSIBLE MOTOR

Swiss precision built. Ideal for robotics. Size: length inc. shaft 90mm. Diameter front fixing 38mm square. Currently advertised by well known supplier at £27.00 plus p&p & VAT. Our Price **£14.95 inc. p&p & VAT**

GIANT BLOWER EXTRACTOR UNIT

Twin output centrifugal blower 1HP 240V AC motor, output approx. 3800 c.f.m. Size: Length 100cm; Height 27cm; Depth 26cm; Fixing plate 106 x 33cm. Price **£125 + VAT**. Ex warehouse.

TORIN CENTRIFUGAL BLOWER

230V ac 2.800 RPM 0.9amp 130mm diameter impeller outlet 63 x 37mm overall size 195 x 160 x 150mm long. Price **£17.50 + £2.50 p&p** (£23 inc VAT)

SHADED POLE GEAR MOTORS

In the following sizes:
9 RPM 12 RPM 80 RPM 160 RPM 110V AC or 240V AC with capacitors (supplied). Price incl VAT & p&p **£12.65**

GEARED MOTORS

71 RPM 20lb inch torque reversible 115V AC input including capacitor and transformer for 240V AC operation. Price incl VAT & p&p **£23.00**.

SOLID STATE EHT UNIT

Input 230/240V AC. Output approx. 15KV. Producing 10mm spark. Built-in 10 sec timer. Easily modified for 20 sec. 30 sec to continuous. Designed for boiler ignition. Dozens of uses in the field of physics and electronics. eg supplying neon or argon tubes etc. Price less case **£8.50 + £1.00 p&p** (£10.93 inc VAT) NMS

HEAVY DUTY MOTOR

Crouzet 115V/230V A.C. heavy duty 1RPM motor. Anticlockwise type 82/015. Size 68mm diameter x 55mm long. Shaft 6mm diameter x 20mm long. Price inc. VAT & p&p **£18.40**.

RHEOSTAT

50W 2ohm 5amp ceramic power rheostat. Price inc. VAT & p&p **£10.25**.

MICROSWITCH

Pye 15amp changeover lever microswitch, type S171. Brand new. Price **£5 for £6.90 inc. VAT & p&p**.

NMS = NEW MANUF SURPLUS
R&T = RECONDITIONED AND TESTED

SERVICE TRADING CO
57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB
081-995 1560
Showroom open Monday/Friday
ACCOUNT CUSTOMERS MIN. ORDER £10



Hobby Kit Electronics

JUST A SMALL SELECTION OF KITS FROM OUR EVER INCREASING RANGE

Kit No	Description	Price (each) £ (Incl. VAT)
1001	0.2 WATT FM TRANSMITTER.....	4.16
1004	LIGHT SWITCH.....	5.83
1006	800 WATT MUSIC-TO-LIGHT.....	4.99
1009	1 WATT FM TRANSMITTER.....	5.42
1013	AM-FM-VHF RECEIVER.....	13.33
1018	GUITAR TREMOLO.....	7.08
1020	0-5 MINUTE TIMER.....	5.42
1022	METAL DETECTOR.....	4.16
1026	RUNNING LIGHTS.....	8.33
1027	Ni CAD BATTERY CHARGER.....	7.08
1029	4 SOUNDS ELECTRIC SIREN.....	4.99
1034	CAR BATTERY CHECKER.....	2.92
1036	TRANSISTOR TESTER.....	3.75
1038	AM-FM AERIAL AMPLIFIER.....	2.92
1044	GRAPHIC EQUALIZER.....	12.91
1045	SOUND EFFECT GENERATOR.....	6.66
1047	SOUND SWITCH.....	9.58
1055	FM RECEIVER USING TDA 7000.....	12.49
1059	TELEPHONE AMPLIFIER.....	8.33
1065	INVERTER 12V D.C. TO 220V A.C.....	20.82
1069	12V D.C. FLUORESCENT TUBE UNIT.....	5.42
1073	VOX ACTIVATED SWITCH.....	6.24
1075	ELECTRONIC DICE WITH L.E.D.'s.....	6.66
1091	GUITAR PRE-AMPLIFIER.....	7.50
1098	DIGITAL THERMOMETER WITH L.C.D. DISPLAY.....	20.82
1114	ELECTRONIC LOCK.....	7.50
1117	TV PATTERN GENERATOR.....	9.17
1119	TELEPHONE LINE RECORDING.....	4.16
1122	TELEPHONE CALL RELAY.....	6.66
1124	ELECTRONIC BELL.....	4.99
1125	TELEPHONE LOCK.....	6.66
1129	NEGATIVE ION GENERATOR.....	14.16
1131	ROBOT VOICE.....	6.66
1133	STEREO SOUND-TO-LIGHT.....	9.52
1203	MINI FM TRANSMITTER WITH MICROPHONE.....	4.16

*All kits are supplied complete including
Silk-Screened p.c.b., Components, Solder,
Wire and full instruction sheet.*

*Purpose-built boxes with silk-screened front
panels are available for some of the above.
Please consult our catalogue.*



CREDIT CARD HOTLINE
081-205 7485

VISA

LARGE STOCKS OF IC's, SEMI's,
OPTO ELECTRONICS, CAPACITORS,
RESISTORS AND SWITCHES.

**NEW ARRIVALS NOW INCLUDES
TEST EQUIPMENT AND TOOLS**

Hobbykit Ltd.



CREDIT CARD HOTLINE
081-205 7485

VISA

UNIT 19, CAPITOL INDUSTRIAL PARK
CAPITOL WAY,
LONDON NW9 0EQ
FAX NO: 01-205 0603

HENRY'S

ELECTRONICS

DISTRIBUTORS

**ELECTRONICS DISTRIBUTORS FOR TRADE,
INDUSTRY, EXPORT, EDUCATION AND HOBBYISTS**

**BIG DISCOUNTS
FOR EDUCATION
AND QUANTITY**

- Tools/Service Aids
- Test Instruments
(UK's largest in-stock Range)
- Communications
- Public Address/Disco
Equipment
- Security/CCTV/
Doorphones/Alarm Systems
- TV, Video Distribution
- Speakers for Hi-Fi, in car, PA
and Disco
- Components, Audio, TV,
Video, Telephone and
Computer Accessories


SPECIAL OFFERS

Dmm was (£18.95) **£13.95**
(30 models stocked)
1 kw outdoor PIR Lights con-
troller was (£32.95) **£19.95**
VHF/UHF TV/FM Amplifier
was (£11.95) **£9.95**
Analogue MM 27 Ranges
CAP/Hfe/Temp/10A AC/DC
etc. was (£39.95) **£29.95**
ALL PRICES INCLUDE VAT

FREE CAR PARKING

Two Car Parks (Bell and Church Streets).
Present your ticket when purchasing and
get one hour as discount.

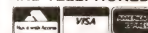OPEN 6 DAYS A WEEK FOR CALLERS
AND TELEPHONED ORDERS



HENRY'S AUDIO ELECTRONICS

404 Edgware Road, London W2 1ED
Instruments/Audio 071-724 3564
Security/Communications/CCTV 071-724 0323
Components 071-723 1008 Fax: 071-724 0322
Trade/Education/Export 071-258 1831
Account facilities available.

**CATALOGUES
IN COLOUR**

- Instruments
 - Security
 - Supplements
 - Components
- Ask Henry's first
£1 for callers: large
SAE £2 stamp UK
by post: Export
£5.00 Free to
Education with
Trade Prices

OMNI ELECTRONICS

174 Dalkeith Road, Edinburgh EH16 5DX · 031 667 2611

A COMPREHENSIVE RANGE WITH SERVICE SECOND TO NONE



OUR MUCH EXPANDED, BETTER
ILLUSTRATED CATALOGUE
WILL COST £1.50 - TO
INCLUDE VOUCHERS
TO USE AGAINST
FUTURE PURCHASES.
TO RECEIVE A COPY
AS SOON AS THEY
ARE READY, PLEASE
SEND YOUR REMITTANCE
WITH THE VOUCHER BELOW.

Please send me a copy of the 1990/91 OMNI catalogue as soon as it is ready.
Payment of £1.50 enclosed.

NAME:
ADDRESS:
TELEPHONE:



**Open: Monday-Friday 9.00-6.00
Saturday 9.00-5.00**

VISA

FOR YOUR ENTERTAINMENT

by Barry Fox



Musical Notes

The music you hear from around 50 per cent of British radio stations is now selected by a computer. The market leader, called Selector, was on demonstration at the *Radio Academy Festival* held in Glasgow earlier in July.

Selector is a program that runs on a desk-top PC. It stores a list of all the records in common use, along with tell-tale information on each, such as the length of each tune, whether it is vocal or instrumental, the tempo in beats per minute, how long the musical introduction runs before anyone sings, whether there is a fade-out at the end and so on.

The station then enters its own set of "rules", largely derived from market research amongst listeners. These dictate what mood of music can be played at each hour of the day, on each day of the week.

The computer then juggles all the information and rules to jigsaw tunes of the right mood and right length to fill up each hour of programming. It takes five minutes to programme a full day's selection. At the same time the computer spews out play lists for the payment of fees to the various copyright agencies.

I watched it in action, and asked about some of the short-hand codes used for the rules displayed on screen.

What does BW stand for? we asked innocently. "B stands for Black and W stands for Wimpy", we were told.

So BW means wimpy music played by a black artist. "B two in a row" means that the station audience is happy to have two tunes by black artists played in a row. White Wimpy is far less popular.

I particularly liked the rule for A Capella music, a vocal ramble without musical accompaniment much favoured by pretentious pop stars. This is ruled as "no more than one every 900 minutes."

Play Time

I review jazz compact discs for a hifi magazine, and recently had the National Youth Jazz Orchestra's recording "*Big Band Christmas*" (NYJ CD 009).

NYJO is best described as the unofficial university of non-classical music in Britain. Over the last quarter century many musicians have started successful careers with NYJO.

The Big Band Christmas recording came out of a concert tour, for which NYJO founder and leader Bill Ashton pulled in arrangements of Christmas standards from well known arrangers.

When reviewing I routinely check the playing time. You would be surprised how many CDs short change the listener with well under the hour that has become the ballpark time for a CD.

The CD player read out the playing time as 76 minutes 35 seconds. Surely this is longer than the theoretical maximum playing time available from a CD? Microsoft's tome on CD and CD-ROM technology "The new Papyrus" quotes maximum playing time for an audio CD as 74 mins 33 secs, derived from a maximum of 335,475 data frames running at the standard rate of 75 per second.

I checked the disc on another player

Power Cut

The Inland Revenue and Customs and Excise have legendary Draconian powers. But so, I recently discovered, do the Electricity Boards.

Earlier this year a video and TV shop in North London closed suddenly. Post piled up inside the door, with no one moving it. Some were obviously bills. There was unsold stock inside too, including prestige TV sets from a major manufacturer.

Eventually a notice appeared on the

door saying that the LEB had moved in and changed the locks. The shop's owner could call at the LEB's office, with proof of identity, to collect the keys—after paying all unpaid bills, of course.

So far the locks remain and the post continues to pile up.

This raises an interesting question. How does a manufacturer retrieve unsold stock on which payment is due, if the LEB has changed the locks on the premises? It's something for suppliers to think about.

Off-Side

Although the 1990 football World Cup is now over (to the undisguised relief of those who are bored with endless talk of soccer) the run-up to the next World Cup, to be held in the US in 1994, has already begun. And already storm clouds are gathering.

TV is the cause. Although North Americans play soccer at high school, they soon forget about it and spend the rest of their lives watching American football or baseball. These two games have one thing in common, interrupted action. The interruptions are filled by advertising commercials on TV.

The referee is in radio contact with the TV crew during the game to synchronize screens. Live in the stadium, giant TV screens display action replays, close-ups of the players, endless statistics about the teams and digital clock count-downs of the time remaining in the game.

By a string of good fortunes, I sat with some American visitors in the Olympic Stadium in Rome watching the World Cup final, and they were very soon predicting doom for 1994. Although FIFA (Federation Internationale de Football Association) allows two large video screens in the stadium to show close-ups of the teams before and after the game, it prohibits any video coverage during the game. Match time is shown by an old-fashioned analogue clock, which gives no clue to how much time is left on the referee's stop watch, after extensions for injury etc.

What really shook the Americans, was

the non-stop play, 45 minutes each half, with absolutely no time for commercial breaks in a live TV transmission. If all the commercials are crammed into the 15 minute half time interval, viewers will simply switch stations, go to the toilet and make coffee.

The US TV networks now want FIFA to change the rules of soccer to suit TV sponsors, by breaking the game down into four quarters instead of two halves. FIFA is confidently expected to tell the Americans to get lost.

Divine Act

Incidentally there was one delightful incident at the end of the World Cup match which the TV cameras never covered. Official sponsors, such as Canon, Coca-Cola, Fuji, JVC and Philips pay FIFA a small fortune to have their names displayed round the pitch and thus be seen on TV.

As the match drew to a close a hot air balloon emblazoned with advertising for non-sponsors Hitachi floated into the Roman night sky from a hill a couple of kilometres away and for a while looked as if it would drift into the open top of the stadium, just as the Cup was being awarded. This would have grabbed Hitachi free world TV coverage.

Instead the balloon stopped dead at a religious statue on the hill, apparently snagged on the figure's outstretched arm. There it hung, until the crowd had gone home, out of sight of the TV cameras and seen only by a few spectators restless with the presentation ceremony.

MARCO TRADING

ELECTRONIC COMPONENTS



& EQUIPMENT

MAIL ORDERS • WHOLESALE
RETAIL



SEND ORDERS TO - DEPT 10
MARCO TRADING
THE MALTINGS, HIGH STREET, WEM
SHROPSHIRE SY4 5EN
Tel: (0939) 32763 Telex: 35565
Fax: (0939) 33800
ELECTRICAL & ELECTRONIC
COMPONENT SUPPLIERS
24HR ANSAPHONE

LATEST 1991
132 Page
CATALOGUE
ONLY
£1.50

OCTOBER SPECIAL OFFER

SWITCH MODE P.S.U. SPECIAL

WEIR - HIGH PERFORMANCE SWITCHED MODE POWER SUPPLY TYPE: HSS 100/11

Probably the highest quality switched mode power supply on the market!

The unit is operable on 110V or 240V a.c. and capable of 100W output if convection cooled or 150W with forced air cooling. (Minimum air-flow rate 20CFM). Overvoltage protection is provided on output 1 by a latch circuit. Full spec. sheets available upon request.

WEIR MODEL: HSS 100/11

REMEMBER ALL BRAND NEW.
THIS MODEL STILL IN PRODUCTION!

- ★ **Input** 110-240V a.c. 50-60Hz
- ★ **Output** 1 +5V at 12A
- ★ 2 -12V at 1.3A
- ★ 3 +12V at 3.5A
- ★ 150 Watt Max (forced air cooled)
- ★ **Size** 214 x 117 x 60mm
- ★ **Weight** 1.2Kg
- ★ BT Approved
- ★ Fully enclosed with mains terminal shroud.

Normal list price is £121.00 each!!!

ORDER CODE:

PRICE **£35.00**

SO/WEIR (HURRY, HURRY, only a few hundred available)



POST PACKING £1.75
ALL PRICES INCLUDE 15% VAT

LOOK OUT FOR NEW SPECIAL
OFFER EVERY MONTH WITH
EVERYDAY ELECTRONICS

FM TRANSMITTER

Very High Quality "MINI-BUG" - Ideal for baby alarms etc!! reception on any FM radio. Frequency: 105-109MHz FM power: PP3 9V battery (not included). Dimensions: 4.25" x 2.25" x 0.76" Code SO.004

£9.99

TDK CASSETTES

AD 90, used once. Bulk erased, good as new, fully guaranteed.

£7.50 for 10

£60.00 for 100

ANTEX IRONS

C-15W IRON.....	£8.37
CS-17W IRON.....	£8.48
XS-25W IRON.....	£8.59
XS-KIT 25W.....	£11.98
CS-KIT 17W.....	£11.87
C-KIT 15W.....	£11.98

ALL BITS FOR IRONS - £1.62
ELEMENTS £4.10 STANDS £3.24

MARCO KITS

Ceramic 50V (125)	£3.99
Electrolytics Red (100)	£8.50
Fuse 20mm Q.B. (80)	£4.75
Fuse 20mm A.S. (80)	£8.50
Pre-set Pots Horiz. (120)	£7.75
Pre-set Pots Vert. (120)	£7.75

RESISTORS


0.25W Popular (1000)	£6.99
0.25W 5 off (305)	£3.75
0.25W 10 off (610)	£5.10
0.5W Popular (1000)	£10.75
0.5W 5 off (365)	£5.40
0.5W 10 off (730)	£8.75
1W 5 off (365)	£15.25
2W 5 off (365)	£25.00
Zener Diodes 5 off (55)	£3.99

NI-CAD CHARGER

Charges AA, AAA, C, D & PP3
Ni-Cads
240V AC **£4.99**

12V TWIN FLUORESCENT
LAMP 12" DOUBLE TUBES

ONLY **£5.99**

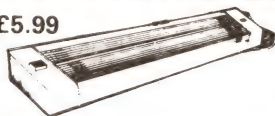

22SWG RESIN SOLDER

500gm. REEL. 1+ 10+

£4.99 £4.75

ALSO 18SWG at £4.95 500gm

Orders of 5 or more reels please add a further 75p P&P

NI-CAD RECHARGEABLE BATTERIES


	PRICE	EACH
1+		10+
AAA	£1.50	£1.30
AA	95p	85p
C	£1.95	£1.80
D	£2.00	£1.85
PP3	£3.90	£3.75

SAVE
£ 30 TO £ 60

ACTICON OFFERS MORE SCOPE...

... THAN ANY OTHER OSCILLOSCOPE

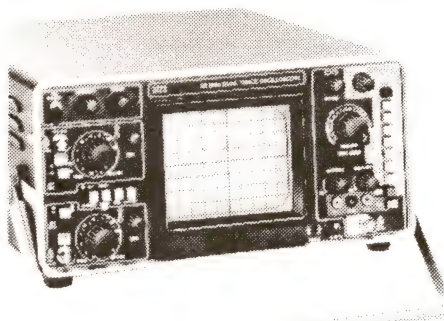HIGH QUALITY • MAXIMUM PERFORMANCE • BEST VALUE FOR MONEY




PRICE EXCLUDES VAT & DELIVERY

3123

£ 299

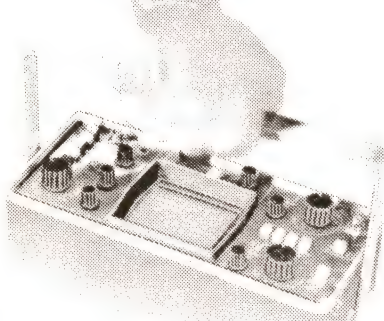25MHz DUAL TRACE
5" OSCILLOSCOPE
2mV SENSITIVITY, VARIABLE
HOLD, DUAL COMPONENT TESTER




PRICE EXCLUDES VAT & DELIVERY

3044

£ 595

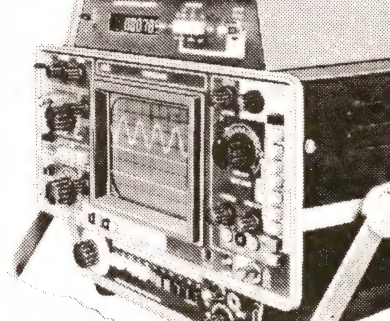20MHz DUAL TRACE
BATTERY MINISCOPE
1mV SENSITIVITY, 2 HOURS OPERATION
BUILT-IN CHARGER



PRICE EXCLUDES VAT & DELIVERY

4445

£ 595

5 in 1 TESTATION
25 MHz DUAL TRACE SCOPE, 35 MHz
8 DIGIT FREQ. COUNTER, 100 KHz FUNCTION GENERATOR, TRIPLE OUTPUT, DC SUPPLY, DUAL COMPONENT TESTER

ACTICON LTD., P.O. BOX 145, NEWBURY, BERKS RG13 2JA

THIS CARD IS YOUR INSTANT SAVING CERTIFICATE (VALID TILL 15th DEC'90)

Mail this back with your order to save £ 30 on 3123 & £ 60 on 3044 & 4445

MICRO IN CONTROL



JOHN HUGHES Part Eleven

Starting from very basic principles this series quickly builds through logic to simple microprocessor control.

Outward Bound!

T We've learnt how to make our system detect the operation of a switch, so we could detect the closure of any contacts, such as a reed switch. Now we should consider how to send out signals as well as receive them.

S The VIA will do this, I assume.

T Yes. As we mentioned previously, the eight pins of Port A can be programmed to be either inputs or outputs as we wish. The 6522 has a second register associated with Port A. It's called the Data Direction Register for the Port. We can refer to it as DDRA. Its address is C003 (two up on the Port itself).

S Why TWO up?

T Well, the VIA chip has two ports, A and B, and two direction registers, DDRA and DDRB. They are located next to each other, like this:

Location 0 . . . Port B
Location 1 . . . Port A
Location 2 . . . DDRB
Location 3 . . . DDRA

Don't ask me why this is the order, but so it is. The chip also has a dozen more registers which make it so very versatile, as we'll see.

Now, the trick in using a DDR is to remember that a logic 1 in any bit will make the CORRESPONDING bit in the Port into an OUTPUT, while a 0 in a DDR bit makes the Port bit an INPUT. After a RESET, all bits are inputs. This makes for safety, as an unexpected output from a controller could have some alarming effects!

S If we wanted some outputs, then, we'd write a 1 into each required bit of the data direction register?

T Exactly. Let's say we wished to have pin 0 (the right-hand one) of the eight to act as an output pin; to drive a relay circuit, for instance. What value would we put in location C003 (DDRA)?

S 0000 0001/01 in hex.

T Right. If we proceed to write a routine

which, say, causes a switching signal to be sent to it, we could check that the signal was there, using a voltmeter, or an indicator from our logic kit. Let's try:

Exercise 19 Spot the flasher!

There is a sub-routine at FB9E which is just a delay routine. In other words, it slows things down for an appreciable second or so, to give us a chance, for without such delays, our micro rips through its instructions in literally millionths of a second. The delay uses the value (22 hex, remember) stored at 0006. It also includes the display subroutine within itself.

Our program can first set up the port to have one output, then switch over this output by simply adding 1 to it. If we then call "delay and display" and loop back to start again, that should do it. Care to try to write it out before looking at my version of it?

S Give us a few minutes, then.

T Well, just a few. I'll use 0200 as my start address. It has to be in RAM, remember. (after a pause) Here goes:

START	0200	A9	01	LDA	01	I	Set up DDRA with 01.
	0202	8D	03	STA	C003		
SWITCH	0205	EE	01	INC	C003		switch bit 0, Port A.
	0208	20	9E	JSR	FB9E		use delay/display s/r.
	020B	4C	05	JMP	0205		Back to switch again.

S I see, the adding "one" in the third line ALWAYS switches from 0 to 1 or from 1 to 0.

T Yes. There are many quaint little tricks like that. You could use the ADC instruction instead to add one.

S I did!

T You may now like to study, or even try out, if you rig up the necessary hardware, some of the control examples in ROM. There's one, you may have noticed, for a model train control, if you add the sensors (reed switches) and use the outputs to control relays for stop/go, forward/reverse, and slow/fast. You'll find it uses pins 6 and 7 as inputs, and 0, 1 and 2 as outputs. The others are unused. (Fig. 11.1)

Less hardware is needed for some of the other programs in ROM, worth studying because the techniques they use can be applied to many control systems.

Exercise 20 Analogue and Digital - Again

Early in our discussions, we moved from analogue circuits, such as amplifiers, whose output signal is proportional (we hope) to the input signal, and concentrated on digital (logic) signals which are always ON or OFF (5V or 0V). However, the real world is more akin to an analogue system, isn't it, in the way things vary?

S Yes, it gets warmer or colder gradually, not in a step / and daylight dawns slowly, and it gets dark gradually.

T Exactly. For some control applications we need to deal with signals which follow such a variable pattern. Can you think of an example?

S The output of an electronic thermometer / or a car speedo / or a light dimmer control.

T Good. And no doubt you can think of others. Well, as with all control systems, there are INPUTS and there are OUTPUTS, from sensors and into drivers, with the processing circuit between (Fig.11.2). We've already rigged up such systems using all analogue circuits with a transistor as an amplifier (doing the "processing"). An LDR as input sensor, with a milliammeter as output device would form a light-level meter, wouldn't it (Fig. 11.3)?

S Or our light "dimmer", with a variable resistor in the base circuit of the transistor driving the lamp (Fig. 11.4).

T Right. In fact, most radios and tape recorders are based on analogue signals,

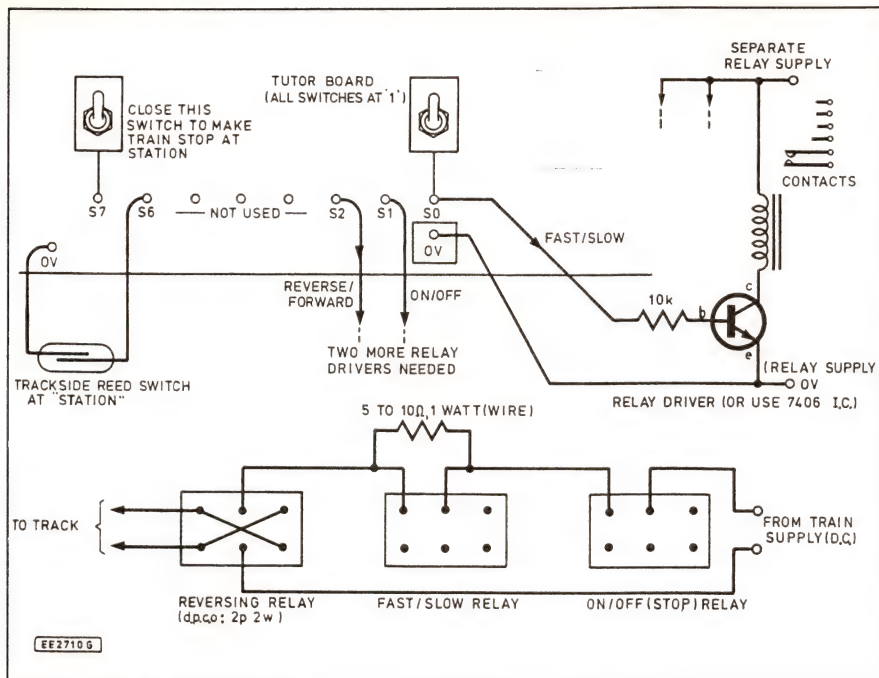


Fig. 11.1. Control of model train. Example in ROM:

It may be possible to lay one's hands on a toy electric train set, and the hardware shown here can be added to a very basic layout with a single loop of track having one model train running on it. The diagram shows a circuit for a relay linked to an output from the micro. Three such circuits are needed, as indicated, using PA0, PA1 and PA2.

The three transistors could be replaced by an open-collector driver chip such as the 7406, which has six such drivers in it. No inputs are essential for the demonstration program, but it can take account of inputs to PA7 and PA6, if a trackside reed switch, operated by a magnet on the train, is linked as shown to PA6. Then, during the run, if switch 7 (or an external switch linked to PA7) is closed, the train will stop at the reed switch position (station?). Remember to leave board switches at logic 1. The sample ROM program (START ADDRESS FF40) sends out a series of "action" codes, each lasting for a certain "duration". There are eight of them here, but the program allows for changes, which will be discussed later.

(The program can, of course, be tried out without any hardware other than three indicators for the outputs, but it is strongly recommended that some external circuitry be built and tested. THIS IS THE WAY TO LEARN HOW A REAL CONTROL SYSTEM WORKS.) A separate relay supply is best.

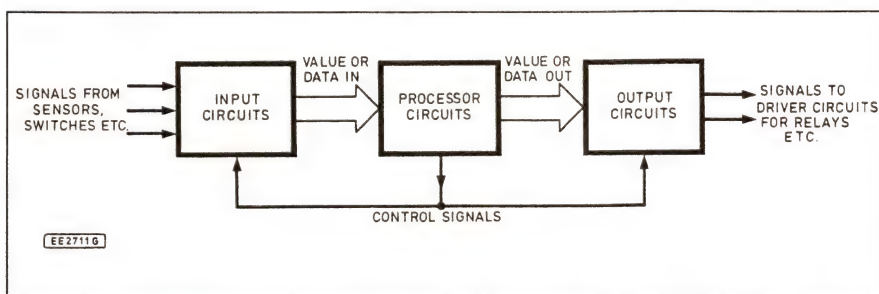


Fig. 11.2. Arrangement for control system. (In this case no feedback is shown.) It could represent a digital or an analogue system

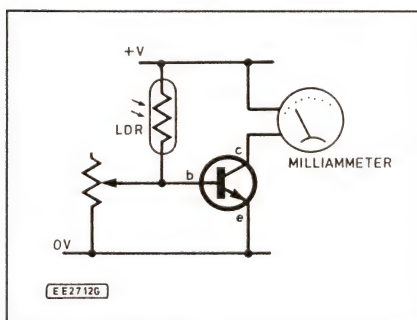


Fig. 11.3. A very simple "light meter" arrangement (analogue).

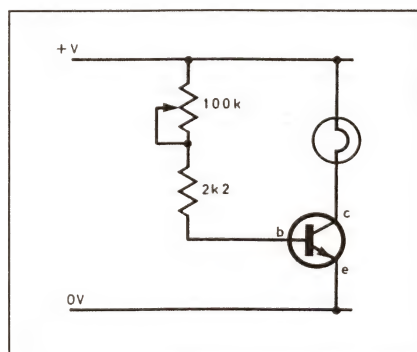


Fig. 11.4. A "dimmer" for a small lamp.

though digital techniques are well on the way to taking over nowadays.

S How can the two be linked?

S (another) There are conversion circuits, aren't there? Probably in the form of i.c.s.

T There are. In fact, that's what we shall have to look at for our control systems if we wish to use microprocessor control of analogue signals ("computer control", in other words). Here's an example with the 6502 system:

Exercise 21 Swinging the LED...

At first sight, it may seem that, while analogue signals can change gradually from one value to another, our digital signals cannot; however, we can arrange a series of digital signals to cause changes in tiny steps, becoming very like an analogue signal. As you guessed, there are chips to do just this; we'll meet them in due course.

S Won't we notice the steps?

T If we only have a few big steps, yes, though this may not matter in some cases. But if we use a large number of very tiny steps, it's virtually impossible to distinguish them from a steady change.

S Doesn't the quantum theory mean that all changes take place in infinitesimally small steps, anyway?

S (others) What's he on about? He's right / etc...

T I agree. If you think about any measurement, quite apart from theory, it's impossible to carry it out to more than a limited precision. So... a lot of small steps, OK?

S But how many, though?

T With eight bits, we can have...

S 256 steps, as there are 256 different values possible.

T That's right, values from 0 to 255 are available. This can give quite a smooth change.

S How can we make a suitable circuit?

T We must distinguish between inputs, which require a conversion from analogue to digital signals (A to D), and outputs, which need the opposite, D to A conversion. Let's consider the latter to start with, as there are a couple of programs in the Tutor ROM to demonstrate it immediately. At least, they demonstrate one easy way to do the conversion. Consider an output signal from a digital line. It can have two values. What are they?

S (chorus) 0 volts and 5 volts, or thereabouts.

T Of course. Now suppose we use such a signal to drive a l.e.d. and cause the signal to be switched ON for half the time, OFF for half the time, at a fast frequency.

S Like in the "organ" multivibrator we made.

T Exactly. How will the l.e.d. appear?

S Dimmer / it'll be getting half the full signal / on average, that is.

T Right again. Now suppose we could alter the "mark to space" ratio, so that it's ON longer than OFF, or vice versa.

S It would be brighter / or dimmer / we could make it as bright or dim as we like / between zero and maximum.

S (others) IF we can arrange the switching patterns.

T Good. Well, with a suitable program we can do just that. The start address of the first program is at FDC0, but FIRSTLY, you will need to enter two numbers into locations 0001 and 0002, to set the desired ratio. Right?

S So, first, we go to location 0001, that's: 0000 0000 0000 0001 and enter a number as its DATA. Any number?

T I suggest you enter FF into BOTH locations to start with (enter the first, use INC, and enter the second). Then go to the start FDC0 (1111 1101 1100 0000) and press GO to see the display l.e.d. flashing.

S This will be the slowest speed.

T Right. Use RST to stop it, then change ONE of the values (the one in 0001 for ON, the other for OFF) to see the effect when you run it again. Then try two equal but SMALL values to make the flashing so rapid that the l.e.d. will appear to be lit steadily. Try a few more combinations of small but unequal values to "adjust" the l.e.d. to any brightness you wish.

S (later) It takes a lot of entering! / not too bad with the keypad.

T It does, so let's make the micro do the changing of the values. There are two programs which you can just RUN and watch: The first is at FDEA, so go to this start address and GO.

S (after watching for a few moments) The l.e.d. starts off flashing slowly and gradually speeds up / then repeats it.

T Yes. The program makes the ON time shorter, the OFF time longer, in steps, then jumps back to start again. The other program starts at FE0D, and does the same, but at a higher speed, so the l.e.d. appears to dim smoothly.

S Could we make it come on gradually, too?

T Of course, with some more programming. If you wish to try, you could study the ROM routine for this one and see how it might be altered or extended. The earlier mark/space setting program, and both the slow and fast D/A examples use another "delay and display" subroutine (a shorter one) at FDDDB. We could learn a little more by studying this subroutine, so here it is, labelled D/D:

FDDDB	D/D	A5	00	LDA	00	Take value at 0000
FDDD		85	10	STA	10	Into 0010 as timer
FDDF	LOOP	20	87	JSR	F887	Call display s/r
FDE2		C6	10	DEC	10	Count down timer
FDE4		D0	F9	BNE	FDDF	Until zero, then
FDE6		60		RTS		Return to main prog.

Note the backwards branch, to LOOP, which occurs each time until the timer value at 0010 (whatever it was as copied from 0000) has dropped to zero as a result of the decrement at each loop. The branch value F9 is a negative number and means "branch back seven places".

S That is, FF, FE, FD, FC, FB, FA, F9.

T Right. So it goes back from where it is, at FDE4 (containing the F9), to FDDF. Then it moves on, as usual, to the next location, FDDF, and carries out the instruction (JSR in this case) which it finds there. On zero result, it drops through in the normal way to the next instruction at FDE6.

We can also note that this subroutine, like many others, calls another subroutine ("Display") within itself. They are said to be "nested subroutines" and there is a limit (quite a high one, fortunately) upon how many can be nested within each other. It is the job of the STACK POINTER register in the 6502 (refer back to the "programmer's model" if you've forgotten about it) to keep track of the moves in and out of the various sub-routines. Luckily, most of this "housekeeping" is done automatically by the CPU, but we may, later, meet some instructions which allow us to

put our oar in as well. For now, we can let the 6502 get on with it.

S Could we look at one of the main programs as well?

T Of course. Here is the ROM version of the fast D/A demonstration we just used. Notice how it starts with small timer values so as to avoid flicker effects in the l.e.d.:

FE0D	Fast D/A	A9	00	LDA	00	Start with l.e.d. OFF for
FE0F		85	F0	STA	F0	short, On for longer,
FE11		85	01	STA	01	still shortish, time,
FE13		A9	20	LDA	20	by putting 0 in 01 (and
FE15		85	02	STA	02	in display), 20 in 02.
FE17	LOOP	A5	01	LDA	01	Give OFF value from 01
FE19		85	00	STA	00	into 00 for timer, and
FE1B		20	DB	JSR	FDDDB	call D/D subroutine.
FE1E		C6	F0	DEC	F0	Now switch bit 1 . . .
FE20		A5	02	LDA	02	copy ON time from 02
FE22		85	00	STA	00	into 00 (for s/r)
FE24		20	DB	JSR	FDDDB	and call s/r again
FE27		C6	02	DEC	02	Decrement ON value,
FE29		F0	E2	BEQ	FE0D	if zero, back to start.
FE2B		E6	01	INC	10	Increment OFF value.
FE2D		EA		NOP		These are "pass" codes
FE2E		EA		NOP		used by the programmer
FE2F		EA		NOP		to fill up space, or
FE30		EA		NOP		to adjust timing loops.
FE31		C6	F0	DEC	F0	Switch bit 1 again . . .
FE33		F0	E2	BEQ	FE17	and use it to loop round again.

So the program alternately loops round the ON and the OFF states, one time being lengthened, the other shortened, at each loop. It will continue indefinitely until stopped with the RESET key. The NOP codes here suggest that, as often may happen, the program was altered during de-bugging. The empty spaces were just filled in to avoid re-writing the final instructions into new locations. An assembler would do this automatically. Sometimes, however, NOPs are used for fine adjustment of the time taken by a loop in, for example, a clock program.

S It means "No Operation" other than to move on, then?

T That's it. Take no action, but carry on with the next instruction. As it's difficult to make space in our programs (with no assembler at present to do it for us) it's not a bad idea to sprinkle a few bunches of two or three NOPs here and there, just in case we may need to insert an extra instruction when we test our work. But don't go mad, as they do slow things down a little.

S And use up memory space.

T Yes. Next, we should look at ways of deriving digital signals from analogue ones.

S The opposite of what we've been doing.

T Yes, and don't forget that the conversion, either way, can be carried out by ready-made chips. We have been using a "software solution" to our problem. A "hardware solution" may sometimes be preferable. In all control projects, a balance has to be struck between hardware and software. It's sometimes called the "hardware/software trade-off", and applies, as we've seen, to many aspects of logic control, not just to A/D and D/A conversions. That's why, ideally, a design engineer should know a good deal both about electronic circuitry and also about

programming techniques, so as to be able to select appropriately.

S Hardware solutions are faster, aren't they?

T As a rule, yes. Software solutions are much more flexible and sometimes less expensive. But not if you have to buy a micro just to, say, dim a lamp!

Exercise 22 Soft(ware)- Centred?

In this Exercise we shall build an A/D converter circuit, but, as we are using a micro anyway, we'll not use too much hardware, though we can meet a very useful type of chip. The LM339 (not a member of the 74 series) contains a type of circuit called an op-amp (operational amplifier), a type originally developed for performing the mathematical operations of an "analogue computer". This works, as its name implies, along quite different lines from our digital system, and merits close study (another time!) in its own right. The LM339 is designed to be used as a "comparator", which, as this implies, compares two input signals (analogue signals) and gives an output which is suitable for using as a digital input.

S Like the outputs from the 74 series chips.

T Just so. In fact, the 74 series and all other logic chips, really contain such op-amp circuits, but used with switched signals not slowly changing ones.

S We saw the same transistor circuit doing both in our very first Exercises.

T Good. Now the LM339 will work quite well with our 5V supply, so set up the circuit shown here (Fig. 11.5) using a bread-board linked to the Tutor sockets. The value of R2 can be altered slightly to give bigger or smaller voltage steps, but the maximum input signal cannot exceed about 4V.

Resistor R1 may not be needed if a low impedance source is being used, and it could form part of an input divider for use with higher voltages.

S Will the circuit act as a sort of digital voltmeter?

T It will, with suitable software, though the display we are using is more akin to an analogue display! The measurement is made digitally, anyway, so that you can see how it may be done.

S Analogue displays (I mean pointers) are often easier to read, I think. / Such as a car speedometer / or clock.

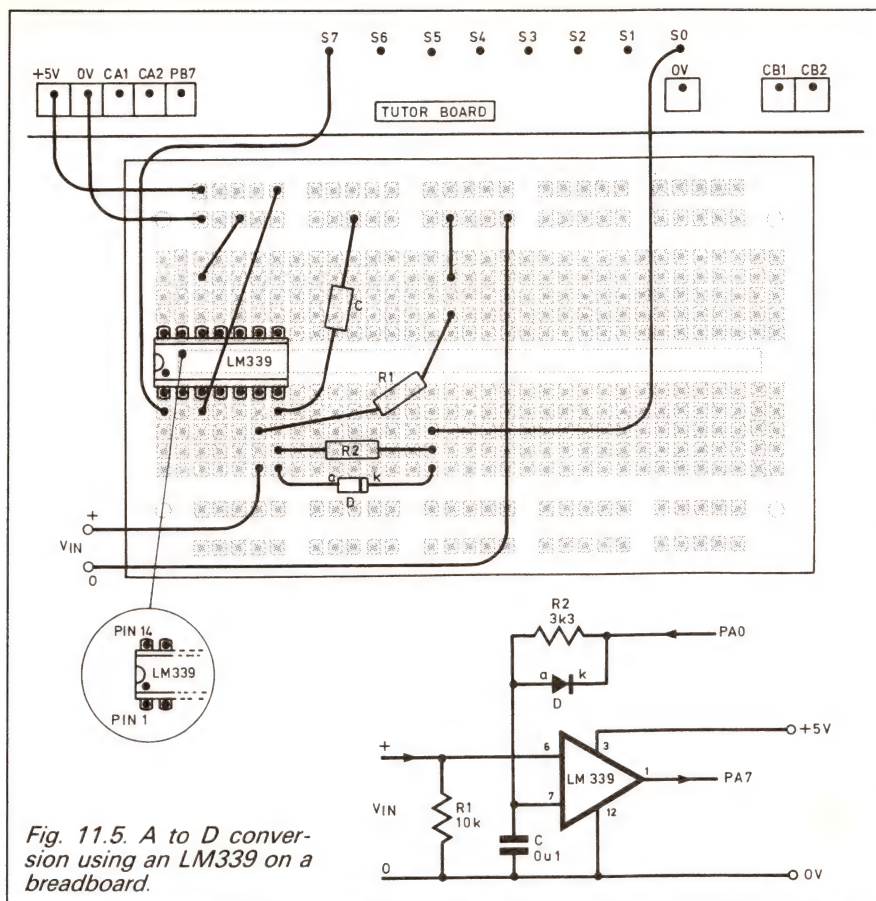


Fig. 11.5. A to D conversion using an LM339 on a breadboard.

Table 11.1. Second part of 6502 Instruction Set.
(There are 56 mnemonics in all, with 13 possible modes)

MNEM	Description (Total bytes)	MODES:						
		IMM 2	ACC 1	ABS. 3	Z/P 2	IMP. 1	ABS,X 3	ZP,X 2
ASL	Arith. Shift LEFT		0A	0E	06		1E	16
BIT	Test bits 6 and 7			2C	24			
CPX	Compare X value	E0		EC	E4			
CPY	Compare Y value	C0		CC	C4			
DEX	Decrement X					CA		
DEY	Decrement Y					88		
INX	Increment X					E8		
INY	Increment Y					C8		
LDA	(additional codes)			AD	A5		BD	B5
LDX	Load into X register			AE	A6			
LDY	Load into Y register	A9		AC	A4		BC	B4
LSR	Logic Shift RIGHT	A2	4A	4E	46		5E	56
NOP	No operation	A0				EA		
ROL	Rotate LEFT		2A	2E	26		3E	36
ROR	Rotate RIGHT		6A	6E	66		7E	76
STA	(additional codes)			8D	85		9D	95
STX	Store from X register			8E	86			
STY	Store from Y register			8C	84			94
TAX	Copy (Transfer) Acc. to X reg.					AA		
TAY	Copy Acc. into Y reg.					A8		
TSX	Copy Status into X reg.					BA		
TXA	Copy X value into Acc.					8A		
TXS	Copy X value into Status					9A		
TYA	Copy Y value into Acc.					98		

The modes are, (altogether) immediate, absolute, zero-page, accumulator, implied, (indirect, X), (indirect), Y, zero-page, X, absolute, X, absolute, Y, relative, absolute-indirect, and zero-page, Y.

T Agreed, on the whole. Changing values are easier to follow, aren't they? But each has its uses. Let's carry on.

S What about the program? I expect it's in the ROM.

T Yes it is. It's part of the system "firmware" remember? That is the programs (software) permanently fixed. What do you need to know?

S Its START ADDRESS/Any preparation before running it/How to interpret the outcome.

T OK. It starts at FA93, and you can use Card 4 as a sort of scale for it. The idea is that, if you apply a small d.c. voltage (say from a small cell) between the 0V line and the lead to pin 6 of the chip, one l.e.d. lights up and "runs" along the scale to indicate the voltage. Again, use RST to stop the program. But note, to run it again, you will have to re-enter the START ADDRESS, as it will have been cleared.

S (after setting up) My l.e.d. can't decide where to stop.

T It's quite sensitive and fast acting. There may be a poor contact in the input leads. Or it may be "between" two values. A more elaborate program could prevent this, but it has its uses, for instance in following a "sound" signal from a microphone amplifier.

S Can we try that?

T Yes. There are some suggestions here (Fig. 11.6).

S (later still) How does it work?

T I was waiting for that, for it allows us to study some further 6502 instructions, of a very important kind. Remember the IN-DEX REGISTERS in the Programmers' Model?

S There were two, X and Y, weren't there?

T Yes. They are similar, but can play slightly different roles. For our purpose we could use either, but we shall use the X register for now. Our program will, in fact, include just three new instructions involving the X index register. here they are:

LDX, which we shall use in immediate mode. It copies from the following location, a value into X just as LDA copies into the accumulator. The op-code for immediate LDX is A2.

S Does it have other modes?

T Yes, you can see them in the full instruction set, but here's an extension to our earlier version. (Table 11.1.)

Then there's DEX, which, of course, decrements the X value and thirdly, one of a range of "indexed instructions" for which the registers are mainly intended. It is STA,X although we don't write it quite like that in a program, as you'll see. The idea to grasp is that, when it receives and indexed op-code, the micro goes, not to the address in the data byte(s), but to the address X places further along in memory.

S So, if we alter X, it will use different locations?

T It will, and we can make it move up or down a table of values, as we shall see when we analyse this program later.

S And there seems to be a LDA,X instruction, too.

T Plus a few more using X and Y in this way. Can you see why they can be so useful?

S Because the X value can be changed by the program.

T Good thinking. Yes, it enables the programmer to send the micro, as it were, to different locations (to STORE or to LOAD) using the SAME sequence of instructions, by changing the value in the X register for each occasion the sequence is used.

S It might be a subroutine / or affected by a key press / or an input signal from a sensor.

T Exactly. All good examples. In our case, we shall use the INDEXED mode of STA to send logic 1 to the LEFTMOST bit of each display register (that's F3, F2, F1 and F0) in turn, so that our "voltmeter" program starts with only the extreme left-hand l.e.d. lit, and makes the "lit" l.e.d. move along to the right as the input voltage is increased.

S I can imagine how it might change from one register to the next, by changing X, but how can we make it move along each individual display register?

T Good question. Well, one more new instruction needed. It's one of several which use the "shift register" function we saw with our row of bistables. Remember?

S When a pattern can be shifted by each clock pulse along the row of flip-flops?

Fig. 11.6. Extensions to Circuit using "voltmeter".

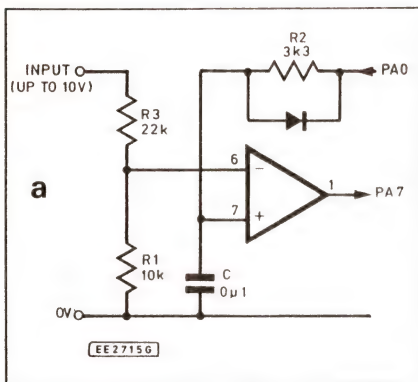


Fig. 11.6 (a) Measuring Higher voltages. A "potential divider" circuit, using two fixed resistors R3 and R1 (already connected) allows a high voltage to be applied to the new input terminals, because only a fraction $R1/(R1+R3)$ of the total voltage is actually applied to the converter input. Thus, to extend the range to say 10V, R3 would need to be about twice R1, i.e. 22K. By using a variable resistor, we could, within limits, measure any higher voltage we wished.

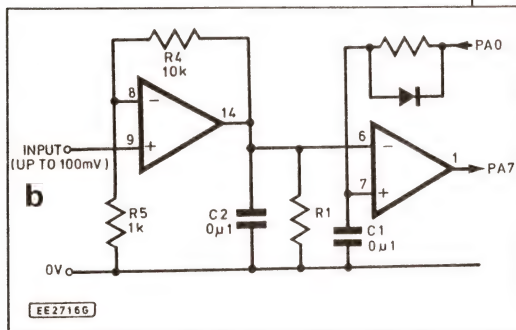


Fig. 11.6 (b) Measuring Lower voltages. An operational amplifier (op-amp) is needed to increase the small input voltage to our 3V range; a section of the LM339 might be used, though not primarily designed for this purpose. The suggested circuit shown here uses the standard method of setting the gain to the ratio $R4/R5$; with the values

shown, signals of up to 0.1V (100mV) could be indicated. The same gain, if preferred, could be obtained by using 100k and 10k respectively, as long as the ratio is ten to one. A much higher ratio is suggested in example (d) to give a far more sensitive amplifier for tiny signals.

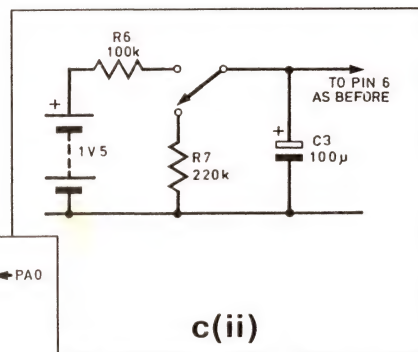
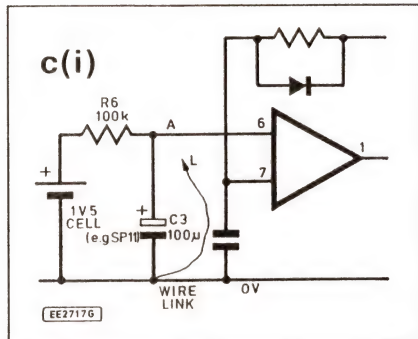


Fig. 11.6 (c) Demonstrating the action of a capacitor. In (i) the voltage across the capacitor is displayed as the capacitor is charged up through a high value resistor R6 (try 100k to start with, and use a 100 microfarad electrolytic capacitor for C3). It will be necessary to short-circuit the capacitor with a wire link L to repeat the demonstration. In (ii) the charge and discharge can both be observed by using a two-way switch. As well as C3, the values of both R6 and R7 can be changed, and their effect on the "time constant" observed.

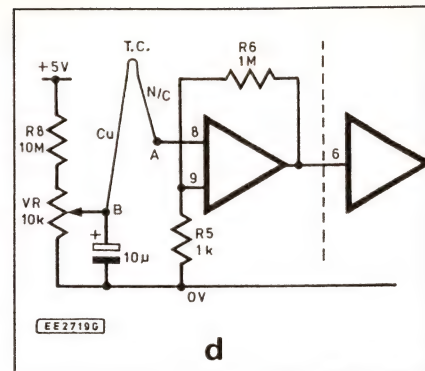


Fig. 11.6 (d) A "thermometer". By using higher sensitivity in the op-amp section of the LM339, the temperature of a simple thermocouple can be shown. The thermojunction is made by twisting together tightly 15cm lengths of bare copper wire and nichrome wire, with a length of sleeving slipped over it for insulation.

A potentiometer P (10k or so) allows "zero" setting; the flame of a match held under the junction will send the light quickly along the l.e.d.s!

Note that the COPPER end is connected to point B in the circuit to give a positive input voltage.

As an alternative, the thermocouple can be removed and a small loudspeaker (or microphone, if one is available) connected in its stead between A and B; it should then be possible to detect sounds as in a VU meter! (despite the a.c. nature of the output).

T That's it. The instruction we'll use is: LSR, which means Logical Shift Right. (Op-code for indexed zero-page mode is 56.)

S So if we've lit up the left-hand l.e.d. only, this instruction will "shift" the light along, one place at a time.

T Just the job. In fact, in our program, it too is indexed, so there are really four instructions involving X.

S Are there any more new instructions in the program?

T Just one. And we don't really need this one. It's to test the comparator (the LM339) output. We COULD use the CMP instruction from our original set (followed by a branch), but the 6502 has a special instruction for testing a register.

BIT is its mnemonic, op-code for z-p is 24.

It saves having to tell the micro what to compare with, or having to load the accumulator (which, of course, overwrites

what's already there - it may matter). BIT has also to be followed by a suitable branch instruction.

S Does this program use any subroutines?

S (another) It'll have to use the DISPLAY s/r, and perhaps a delay timer.

T Right you are. It uses yet another delay and display subroutine, which has a fixed delay, but which also saves the value of X, so that it isn't lost during the subroutine itself (which also uses the X index register). Here's the subroutine, labelled DDX. You'll notice that, as you suspected, it too calls the display s/r.

FA28	DDX s/r	86	DC	STX	DC	Save X value (in 00DC)
FA2A		A9	50	LDA	50	set fixed speed, using
FA2C		85	DF	STA	DF	00DF as timer location
FA2E	LOOP	20	87 F8	JSR	F887	Include display s/r in
FA31		C6	DF	DEC	DF	timing loop, branch to
FA33		D0	F9	BNE		FA2E until zero, then
FA35		A6	DC	LDX	DC	restore X value and
FA37		60		RTS		return.

List 11.1. A/D conversion "voltmeter" programme: (Hardware required as described in text)

FA93	START	A9	00	LDA	00	Clear Port A
FA95		8D	01	C0	STA	C001
FA98		A9	0F	LDA	0F	Set up DDRA
FA9A		8D	03	C0	STA	C003
FA9D		A9	00	LDA	00	Clear all displays
FA9F		85	F0	STA	F0	
FAA1		85	F1	STA	F1	
FAA3		85	F2	STA	F2	
FAA5		85	F3	STA	F3	
FAA7		A9	01	LDA	01	Send charging signal
FAA9		8D	01	C0	STA	C001
FAAC		EA		NOP		to capacitor circuit
FAAD	LHBYTE	A2	03	LDX	03	and comparator input.
FAAF	LHBIT	A9	80	LDA	80	Set X = 3 for LH disp.
FAB1		95	F0	STA	F0,X	(starting at F0 + X = F3)
FAB3	TEST	2C	01	C0	BIT	C001
FAB6		30	05	BMI	FAC2	Is comp. output 1 yet?
FAB8		EA		NOP		If so, display l.e.d., if
FAB9		56	F0	LSR	F0	not, shift to l.e.d. one
FABB		D0	F6	BNE	FAB3	place to the right.
FABD		CA		DEX		Repeat until byte done
FABE		10	EF	BPL	FAAF	then reduce X for next
FAC0		D0	D1	BNE	FA93	Repeat for all bytes,
FAC2	DISP	20	28	FA	JSR	four in this case.
FAC5		4C	93	FA	JMP	Call DDX display s/r,
						and do it all again.

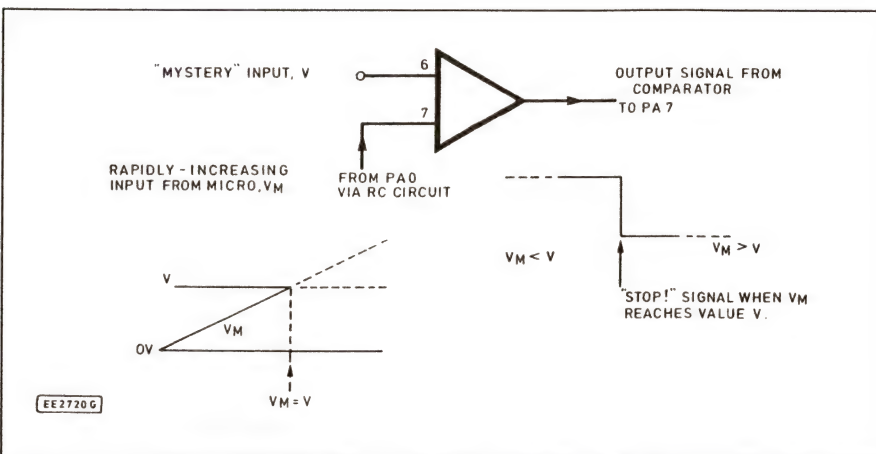


Fig. 11.7. How comparator output switches when both inputs become equal.

T That's right, though it's too slow for some jobs, believe it or not.

Have you spotted the new instruction types in the program? Notice how index X is first loaded with 3, then the value 80 (in hex, remember) is loaded into the accumulator. Anyone care to carry on with the tale?

S The next instruction STA,X F0 puts this value, which is 1000 0000 in binary, into location F0 plus X (which is 3) that is, into F3 (00F3), the left-hand display register.

T Very well put. This is how the extreme left-hand l.e.d. is lit to start with. Can anyone else take up the story?

S (others) The BIT instruction tests PA7 / if it's a 1 the value is negative and the BMI instruction causes a branch / to the DDX subroutine / then the whole thing is repeated by the JMP back to the start.

T This will give a steady "reading" won't it?

S Yes, so this must be when the signals are equal / the output from the comparator must be zero to start with / so the BMI branch

WON'T happen / and the LSR instruction will make the next l.e.d. light up.

T Good. Any questions?

S Yes. I can't see how the program makes the digital voltage increase while the l.e.d. gallops along the scale.

T That's the key question. In fact, the steady increase in "digital" voltage isn't provided by the program. It could be, and in some more elaborate (and expensive) chips, a real digital to analogue conversion is carried out. We may have time to study a typical purpose-built chip later. Here, we have used the gradual charging of a capacitor to provide the growing signal.

S So it's not a digital one at all / a cheat!

T Well, not entirely. In the program you'll see that the signal out from PA0 is switched to zero at the start of the program (and thus at each rapid loop). But, starting at location FAA7, two instructions switch it ON (to about 5V or so, right?), whereupon the capacitor starts to charge via resistor R2. The values are chosen to suit the speed at which the l.e.d. bit races along the scale

(which is pretty fast). The diode allows a quick discharge at the start of each program loop.

S In other words, the scale shows the TIME the capacitor took to reach the "mystery" voltage value?

T That's it. It's a fairly simple way to arrange to measure an analogue voltage with a digital system. Agreed?

S Well, OK. But you should show us the specialised chips soon / but these simple circuits can keep costs down when strict accuracy isn't vital.

T The dedicated chips are very useful, but they require little or no programming as they do the conversions with their own "hardware solutions". We've used very strongly software-oriented solutions, to gain the practice.

I'd like to dwell for a while on this business of indexed instruction modes, as they can be useful in several ways. For example, the monitor "knows" which key has been pressed because each has its own "key value" when depressed (because of the way they are wired to Port B, the one we can't use, as the CPU monopolises it!). To cut a long story short, what we need to know, to make use of this, is that, if NO KEY is being pressed, the key value is 08

GO gives value 00 A/S gives 04
DA gives value 01 X/Y gives 05
AH gives value 02 INC gives 06
AL gives value 03 SHIFT gives 07

S There's bound to be a subroutine to read the keys!

T You're right. It's at FC60, but remember, like all subroutines, IT CAN'T BE USED ON ITS OWN. But it can be demonstrated with a short program starting at FCAA (or you could write your own).

Exercise 25 Now hear this!

First, use the demonstration routine just mentioned, starting at FCAA, to confirm the above values. Just run the program, see 08 in the status display l.e.d.s, then press each key in turn and hold it while you check the value on the l.e.d.s. In binary of course, as usual.

We can use these values to make the keys act in whatever way we wish.

S Wasn't this done in the "Thief?" game we saw earlier?

T It was; you could now follow the design of that game if you wished to, or make up your own. What I suggest, though, is that we try to make the keys act as the keys of a sort of primitive "organ"; not unlike the digital equivalent of the "cheapo" version we looked at when we discussed multi-vibrators. The "mini-wurlitzer", right?

S That used a variable resistor pitch control, with graphite as the resistor.

T Yes. Now we'll look at a program to make the keys set the pitch. It will bring to our notice the use of a "look-up table", a very useful technique to add to our bag of tricks. In fact it's also used, as you can imagine, in the "Train Control" program we described earlier.

S You said the train program could be modified. Can we try?

T OK. We'll look at it after we've done the tune player program, which is a little simpler to start with.

Next month: The final part deals with the "tune player" and a three floor lift program

QUALITY MULTIMETERS AT LOW COST.

QI9001



- LOW COST 10A DIGITAL MULTIMETER**
- 3.5 digit, 0.7% basic accuracy
 - Low cost, excellent value
 - Pocket size, 10A rating
 - Diode check (28V/1mA)
 - Battery included
 - Safe - meets UL12444 and VDE0411

SPECIFICATION

DC VOLTAGE	
5 ranges: 200mV, 2V, 20V, 200V, 1000V	
Resolution: From 0.1mV to 1V	
Accuracy: $\pm 0.7\%$ of reading + 2D	
DC CURRENT	
5 ranges: Covering 200 μ A, 2mA, 20mA, 200mA, 2A (10A separate terminal)	
Resolution: From 0.1 μ A to 10mA	
Accuracy: ± 1.0 to $\pm 1.5\%$ of reading + 2D	
Maximum full-scale voltage drop: 0.25V	
AC VOLTAGE	
2 ranges: 200V, 750V	
Resolution: From 100mV to 1V	
Accuracy: $\pm 1.2\%$ of reading + 10D	
Frequency range: 45 to 450Hz	
RESISTANCE	
5 ranges: 200, 2k, 20k, 200, 2M Ω hm	
Resolution: From 100 Ω hm to 1k Ω hm	
Accuracy: From ± 0.7 to $\pm 1\%$ of reading	
SIZE	
75x130x25mm	

EXCELLENT VALUE LARGE DISPLAY ANALOGUE MULTIMETER

- Large 3.5 inch, 90° mirrored meter, pivot and jewel
- Polarity reverse
- Safe - meets UL12444 and VDE0411
- dB range
- 10A scale
- TR test (good or bad and NPN or PNP)
- Desk stand
- Battery included

SPECIFICATION

DC VOLTAGE	
6 ranges: 0.1, 2.5, 10, 50, 250, 1000V	
Sensitivity: 20,000 ohms per volt	
Rated Accuracy: Within $\pm 3\%$ DC of full scale	
DC CURRENT	
5 ranges: 50 μ A, 2.5, 25, 250mA, 10A, 10A on separate jack	
Potential Drop: 0.25V on all ranges	
Rated Accuracy: Within $\pm 3\%$ full scale, all ranges	
AC VOLTAGE	
4 ranges: 10, 50, 250, 1000V	
Sensitivity: 8,000 Ohms per volt	
Indication: Full wave average responding, calibrated in RMS for sinusoidal waveforms	
Frequency Response: Rated accuracy to 50,000 Hz on all ranges through 10V to 1kHz on 50V range	
Rated Accuracy: Within $\pm 4\%$ AC of full scale	
RESISTANCE	
4 ranges: 2k, 20k, 2M, 20M Ω hm	
dB	
4 ranges: -20 to +62dB	
SIZE	
102x150x45mm	

QI9003



- COMPACT, HIGH-QUALITY DIGITAL MULTIMETER WITH BARGRAPH**
- Easy and accurate
 - Autoranging or manual
 - 10A current range
 - Extended 20M Ω hm ranges
 - Comprehensive displays
 - Transistor test
 - Continuity buzzer (4kHz)
 - Hold/memory feature
 - Desk stand
 - Battery included

SPECIFICATION

RESISTANCE	
5 ranges (low power): 2k, 20k, 200k, 2M, 20M Ω hm	
6 ranges (high power): 200, 2k, 20k, 200k, 2M, 20M Ω hm	
Accuracy: ± 0.75 to 2% of reading (+1D to +5D)	
Resolution: Low 10 Ω hm, high 0.10 Ω hm	
DC VOLTAGE	
5 ranges: 200mV, 2V, 20V, 200V, 1000V	
Accuracy: $\pm 0.5\%$ of reading + 1D	
Resolution: 100 μ V	
DC CURRENT	
2 ranges: 200mA, 10A	
Accuracy: ± 0.75 to 1.5% of reading (+1D to +5D)	
Resolution: 100 μ A	
AC VOLTAGE	
4 ranges: 2V, 20V, 200V, 750V	
Accuracy: $\pm 0.75\%$ of reading + 5D	
Resolution: 1mV	
AC CURRENT	
2 ranges: 200mA, 10A	
Accuracy: ± 1 to 2% of reading + 5D	
Resolution: 100 μ A	
SIZE	
74x149x30mm	

QI9002



- ANALOGUE INSULATION TESTER**
- Large 3.5 inch, 90° mirrored meter, pivot and jewel
 - Rugged design
 - Safe - meets UL12444 and VDE0411
 - 300VAC measurement
 - Push to test and continuity test voltage modes
 - Desk stand
 - Battery included

SPECIFICATION

MEGA OHM	
Scale range: 0-200M Ω hm	
Effective measuring range: 1-100M Ω hm (Primary effective scale range)	
Accuracy: Within $\pm 7\%$ of the value indicated in the primary effective scale range	
Other - within $\pm 3\%$ of scale length	
Test voltage: 500V	
AC VOLTAGE	
Scale range: 0-300V	
Accuracy: Within $\pm 5\%$ of max. scale value	
SIZE	
102x150x45mm	

HIGH QUALITY ANALOGUE DESK INSTRUMENT (30k Ω hm/V)

- Extra large 4 inch, 90° mirrored meter
- Pivot and jewel mechanism
- Safe - meets UL12444 and VDE0411
- dB range and 10A range
- Polarity reverse
- TR test (good or bad and NPN or PNP)
- Battery test
- Desk stand
- Battery included

SPECIFICATION

AC/DC VOLTAGE	
11 ranges: DC 3V/AC, DC 10/30/100/300/1000V	
Sensitivity DC: 30,000 Ohms per volt DC	
Sensitivity AC: 10,000 Ohms per volt AC	
Rated Accuracy: Within $\pm 3\%$ DC and $\pm 4\%$ AC of full scale on all ranges	
Indication: Full wave average responding; Calibrated in RMS for sinusoidal waveforms	
DC CURRENT	
5 ranges: 100 μ A/3m/30m/300mA, 10A, 10A on separate jack	
Potential Drop: 0.3V on all ranges	
Rated Accuracy: Within $\pm 3\%$ full scale on all ranges	
RESISTANCE	
4 ranges: 1k Ω hm, 10k Ω hm, 1M Ω hm, 10M Ω hm	
dB	
5 ranges: -20 to +62dB	
SIZE	
112x162x50mm	

QI9004



POWERFUL AND RUGGED MULTI-PURPOSE DIGITAL MULTIMETER

- Buzzer continuity test
- 20A and extended 20M Ω hm ranges
- Ultra-rugged design
- Temp., Cap., Freq., Diode test, etc.
- Desk stand
- Battery included

SPECIFICATION

DC VOLTAGE	
4 ranges: 200mV, 20V, 200V, 1000V	
Accuracy: $\pm 0.5\%$ of reading + 2D	
DC CURRENT	
3 ranges: 2mA, 200mA, 20A	
Accuracy: 0.5 to 1.5% of reading + 1D	
AC VOLTAGE	
4 ranges: 200mV, 20V, 200V, 750V	
Accuracy: 0.5 to 1% of reading + 5D	
FREQUENCY COUNTER	
2 ranges: 200kHz, 20MHz	
Accuracy: $\pm 2\%$ of reading + 5D	
RESISTANCE	
6 ranges: 200, 2k, 20k, 200k, 2M, 20M Ω hm and continuity buzzer	
Accuracy: 0.5 to 2% of reading (+2D to +5D)	
CAPACITANCE	
3 ranges: 2000pF, 2nF, 20 μ F	
Accuracy: $\pm 2\%$ of reading + 5D	
TEMPERATURE	
2 ranges: -20 to 1200°C, 0 to 2000°F	
SIZE	
95x200x55mm	

QI9005



- COMPACT, HIGH-QUALITY DIGITAL MULTIMETER WITH BARGRAPH**
- Easy and accurate
 - Autoranging or manual
 - 10A current range
 - Extended 20M Ω hm ranges
 - Comprehensive displays
 - Transistor test
 - Continuity buzzer (4kHz)
 - Hold/memory feature
 - Desk stand
 - Battery included

SPECIFICATION

RESISTANCE	
5 ranges (low power): 2k, 20k, 200k, 2M, 20M Ω hm	
6 ranges (high power): 200, 2k, 20k, 200k, 2M, 20M Ω hm	
Accuracy: ± 0.75 to 2% of reading (+1D to +5D)	
Resolution: Low 10 Ω hm, high 0.10 Ω hm	
DC VOLTAGE	
5 ranges: 200mV, 2V, 20V, 200V, 1000V	
Accuracy: $\pm 0.5\%$ of reading + 1D	
Resolution: 100 μ V	
DC CURRENT	
2 ranges: 200mA, 10A	
Accuracy: ± 0.75 to 1.5% of reading (+1D to +5D)	
Resolution: 100 μ A	
AC VOLTAGE	
4 ranges: 2V, 20V, 200V, 750V	
Accuracy: $\pm 0.75\%$ of reading + 5D	
Resolution: 1mV	
AC CURRENT	
2 ranges: 200mA, 10A	
Accuracy: ± 1 to 2% of reading + 5D	
Resolution: 100 μ A	
SIZE	
74x149x30mm	

QI9006



POWERFUL AND RUGGED MULTI-PURPOSE DIGITAL MULTIMETER

- Buzzer continuity test
- 20A and extended 20M Ω hm ranges
- Ultra-rugged design
- Temp., Cap., Freq., Diode test, etc.
- Desk stand
- Battery included

SPECIFICATION

DC VOLTAGE	
4 ranges: 200mV, 20V, 200V, 1000V	
Accuracy: $\pm 0.5\%$ of reading + 2D	
DC CURRENT	
3 ranges: 2mA, 200mA, 20A	
Accuracy: 0.5 to 1.5% of reading + 1D	
AC VOLTAGE	
4 ranges: 200mV, 20V, 200V, 750V	
Accuracy: 0.5 to 1% of reading + 5D	
FREQUENCY COUNTER	
2 ranges: 200kHz, 20MHz	
Accuracy: $\pm 2\%$ of reading + 5D	
RESISTANCE	
6 ranges: 200, 2k, 20k, 200k, 2M, 20M Ω hm and continuity buzzer	
Accuracy: 0.5 to 2% of reading (+2D to +5D)	
CAPACITANCE	
3 ranges: 2000pF, 2nF, 20 μ F	
Accuracy: $\pm 2\%$ of reading + 5D	
TEMPERATURE	
2 ranges: -20 to 1200°C, 0 to 2000°F	
SIZE	
95x200x55mm	

SEND ORDER FORM WITH CHEQUE OR POSTAL ORDER TO QUILLER LTD.

METER	QUANTITY	PRICE	METER	QUANTITY	PRICE	COST	£
QI9001		£15	QI9004		£29	1st class post -	
QI9002		£45	QI9005		£48	(1.50 per item)	£
QI9003		£19	QI9006		£68	VAT at 15%	£
						TOTAL	£

Name _____ Company _____

Address _____

Tel. _____

Phone now for details of your nearest stockist
(0202) 417744

...or simply complete the order form
and send it to Quiller at the address below.

QUILLER


QUILLER LIMITED, 2 PAISLEY ROAD, BOURNEMOUTH, BH6 5EU.
TELEPHONE: (0202) 417744. FAX: (0202) 421255. TELEX: 41832 QUILL G.

ALL SPECIFICATIONS ARE SUBJECT TO CHANGE WITHOUT PRIOR NOTICE.

MOBILE LINE TRACKER

CHRIS WALKER

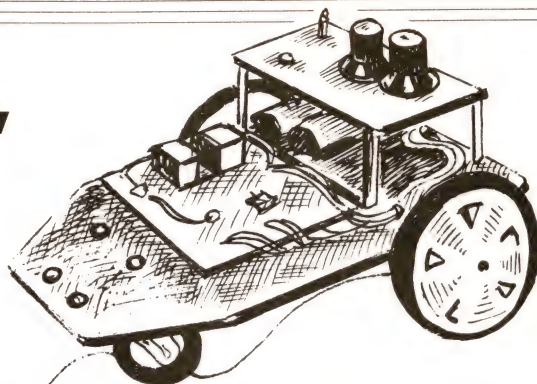There is no likelihood of a fuel crisis with this vehicle, and it will keep to the route you set out for it!



ROBOTICS is a fascinating branch of electronics for the home constructor as it adds that extra dimension of *motion* to his or her projects. Flashing lights and tuneful bleeps are always popular but if the thing actually moves and does something, well that will attract attention!

The Mobile Line-Tracker described here is a simple reflex action robot which will optically follow a meandering line on the floor. A control is provided to enable the unit to cope with a wide range of contrasts between floor and line. In addition, it can choose between following a white or black line and can handle quite severe bends.

This experimental project illustrates some basic "sense-and-control" concepts which form important building blocks in a robot system. The Mobile Line-Tracker can be built as described to produce a fully independent "buggy" which will provide hours of fun and fascination. Alternatively, readers may rather incorporate the sense-and-control system into part of a larger robot assembly.

ON THE LINE

Line-following robots are being used more and more to carry goods around warehouses and factories and to deliver mail within an office building. Unlike a train, these robots are not restricted to rails

so they can follow the same routes used by the human workers. Home users might employ one to carry drinks to their guests, and act as a sort of butler!

The industrial versions of these "trolleys" usually follow a line of magnetic material embedded into the floor. Optical line followers which actually "look" at a visible line are more prone to interference from ambient lighting (with the resultant risk of losing the line), but they offer much more scope for experimentation for the home enthusiast.

In practice, suitable lines can be easily and cheaply laid using masking tape or something similar. This method also ensures quick removal at the end of the day. The prototype model will even successfully follow a line chalked onto concrete, and when you stop to look closely at all the gaps and breaks in the line, you realise what an achievement this is!

IN GEAR

The problem with many automated and robotic projects is that they require some degree of skill to construct drive units such as gearboxes, bearings and wheels etc. It is often difficult for the average constructor to manufacture a small gearbox with reliably-meshing gears, as the author knows too well. Ready built drive assemblies are available on a limited market

but, since they are often aimed at the radio-controlled model builder, they can be expensive.

The Mobile Line-Tracker was built using easily available combined motor/gearboxes and popular electronic components. Little difficulty should be found in reproducing a similar unit.

SYSTEM OPERATION

How the two side-by-side optical sensors view the "tracker line" from above is illustrated in Fig. 1. A small lamp is used to illuminate the line in the area of the sensors. For the sake of argument, let's assume that the vehicle is following a white line on a dark coloured floor.

If both sensors are over the line as in Fig. 1a then both receive similar amounts of light reflected off the line and the vehicle proceeds straight ahead. If the tracker veers left (or if the line bends to the right) then the right-hand sensor receives more light than the left, since the latter has now moved off the white line (Fig. 1b.).

If this light level difference is above a level set by the Contrast control then the *right* hand drive motor is switched *off* and the left motor steers the vehicle towards the right and back onto the line. Excessive movement to the right (Fig. 1c.) causes the *left* hand motor to stop and the vehicle is steered back onto the line until both sensors receive a similar level of reflected light once more.

Thus a simple feedback loop is established whereby the control of the drive motors is continuously adjusted to try and maintain even illumination of both light sensors, i.e. the vehicle follows the white line.

In order to follow a *black* line drawn on a light coloured surface it is necessary only to interchange the control signals to each motor. If, for example, the vehicle moves left off the black line then the left hand sensor receives more light from the pale floor. Rather than switching off the left motor, the *right* hand motor is arrested and this swings the buggy towards the right and back onto the black line.

A changeover switch is used to select whether the vehicle follows a black or white line.

SENSORS

The complete circuit diagram for the Mobile Line-Tracker is given in Fig. 2. Two TIL78 phototransistors, TR1 and TR2, form the "eyes" of the robot, each one being mounted in a length of tubing so

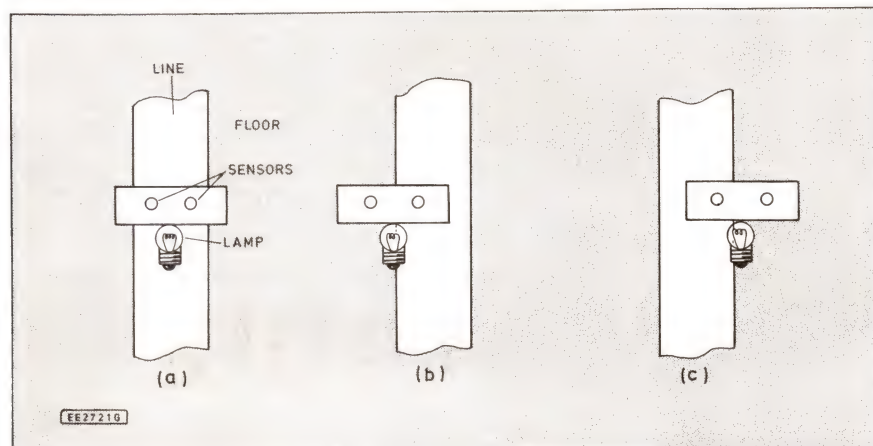


Fig. 1. How the optical sensors view the "illuminated" line from above.

that they have a narrowed-down field of view and only receive light reflected from the floor.

Phototransistors are used in preference to light dependent resistors (l.d.r.s) for this application because they are generally smaller, cheaper and faster to respond to changes in dim light. The latter being one important feature if the robot is not to lose the line on a sharp bend.

The npn phototransistors TR1, TR2 pass a current from collector to emitter which is proportional to the light intensity falling on their semiconductor junction. This "photocurrent" flows through resistors R1 and R2 which develop a potential difference across them which is proportional to this current. Therefore, the voltage at the emitter of each phototransistor rises as more light is detected.

by an amount dependent on the setting of VR2. The gain is adjustable from zero to 100.

The op-amp IC1 is run from a split-rail power supply of +9V and -9V relative to the zero volt (0V) line. Therefore, the output of the op-amp (pin 6) can swing *positive* and *negative*.

A positive output voltage (greater than about 2V) will light one half of the bi-colour l.e.d. D1, whilst a negative output will light the complimentary colour. Two separate l.e.d.'s connected "back-to-back" would achieve the same effect.

Thus the magnitude of the output voltage from IC1 depends on the illumination *difference* between TR1 and TR2 and also on the setting of the Contrast control VR2. If the contrast between the line and floor is high (e.g. a white line on a black floor) then

RELAYS

A *positive* output from IC1 signifies that TR1 is illuminated more than TR2. Current flows into the base of the transistor TR3 which switches on and energises the coil of relay RLA.

Similarly a *negative* output indicates that TR2 is receiving more light than TR1 and this switches on the transistor TR4 which energises relay RLB. Each relay coil operates a single changeover contact, RLA1 or RLB1.

However, in order to stop the relays from continuously operating for small illumination imbalances, Zener diodes D2 and D5 ensure that no base current flows into transistors TR3 or TR4 until the amplifier output rises above about $\pm 4.7V$. Signal diodes D3 and D6 prevent the base/emitter

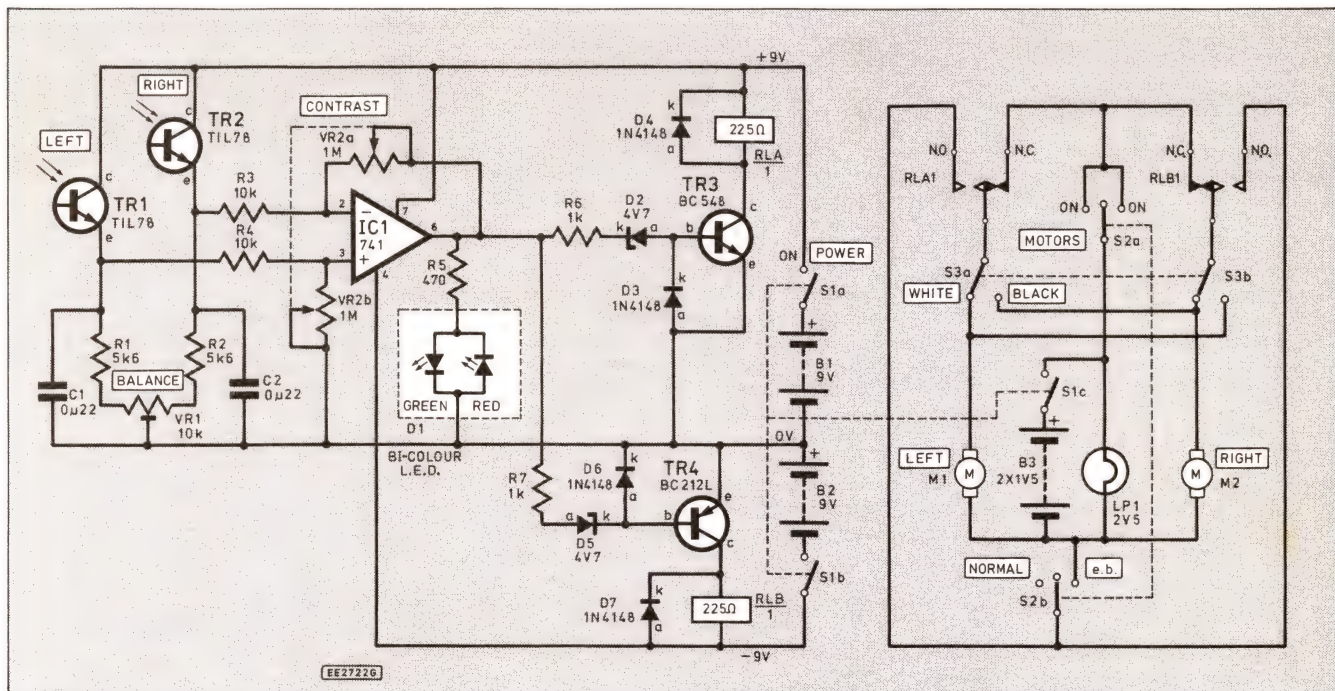


Fig. 2. Complete circuit diagram for the Mobile Line-Tracker. The phototransistors TR1 and TR2 are mounted on the underside of the vehicle and form the sensor "eyes".

Present potentiometer VR1 is used to "balance" the sensory circuit and compensate for component tolerances so that the emitter voltages can be made equal when both phototransistors are positioned over a white surface. Capacitors C1 and C2 help to remove electrical noise picked up by the wires running to each phototransistor, especially noise generated by the drive motors. It is worth noting that the TIL78 phototransistor has a peak response in the infra-red region but it is sufficiently sensitive to visible light to be of use in this application.


DIFFERENTIAL AMPLIFIER

The good old 741 operational amplifier is put to good use in this circuit. It is cheap, easily obtainable and performs its job admirably making the use of a more "up-market" chip pointless!


Resistors R3 and R4, together with the double-ganged Contrast control potentiometer VR2, develop the op-amp into a differential amplifier which subtracts the voltage at TR2 emitter from the voltage at TR1 emitter and amplifies this difference

VR2 would be set to a low resistance to reduce the gain of the differential amplifier.

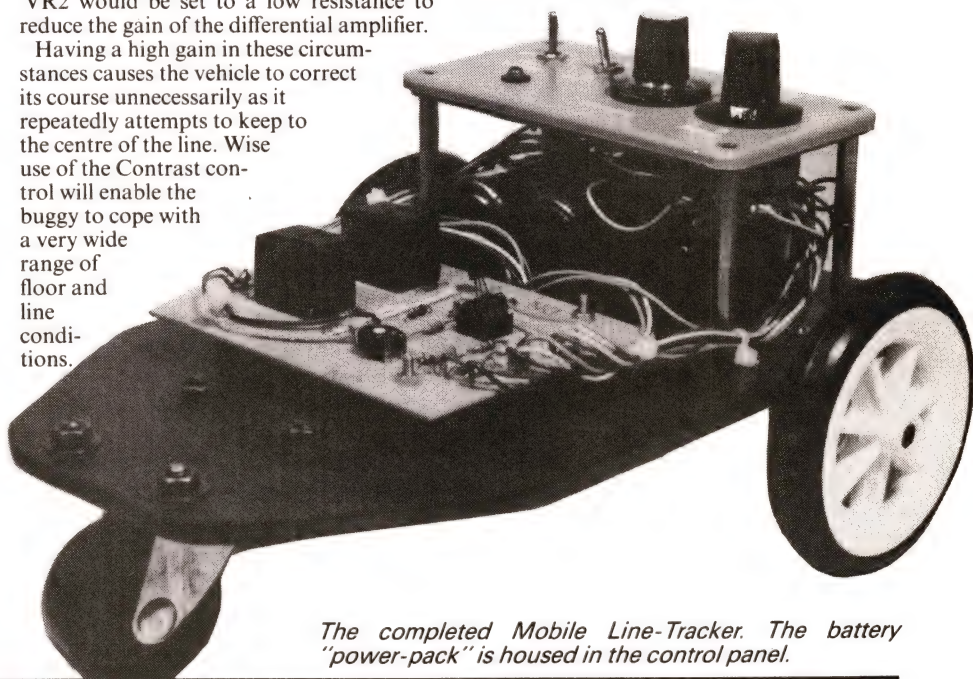Having a high gain in these circumstances causes the vehicle to correct its course unnecessarily as it repeatedly attempts to keep to the centre of the line. Wise use of the Contrast control will enable the buggy to cope with a very wide range of floor and line conditions.



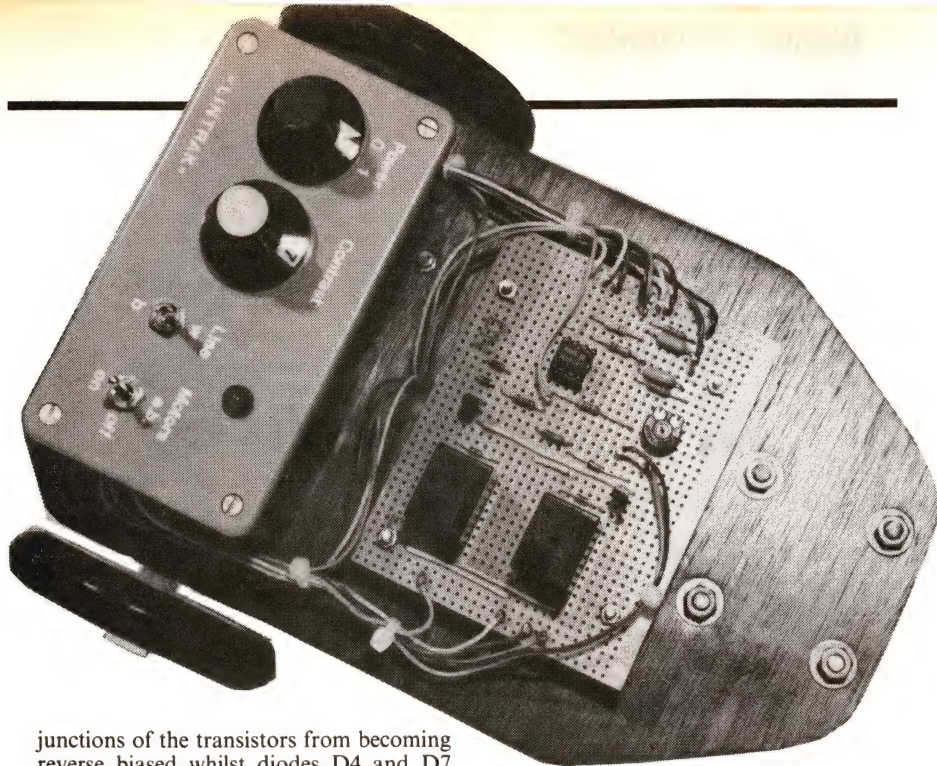The completed Mobile Line-Tracker. The battery "power-pack" is housed in the control panel.



junctions of the transistors from becoming reverse biased whilst diodes D4 and D7 quench the "back-emf" generated when the relay coils are switched off.

Switch S1 is a 3-pole ON/OFF switch. S1a and S1b switch the +9V and -9V power from batteries B1 and B2 whilst S1c controls power to the motors. When the relays are not energised, current consumption is about 1mA from each 9V battery but this rises to about 50mA as the relays switch on.

Obtaining relays with a reasonably high coil resistance (in order to reduce the operating current and prolong battery life) proved a difficult task. Eventually a 9V 225 ohm coil type was found and worked successfully. A more easily obtainable 6V 100 ohm coil could be used but the drain on the PP3 batteries would be substantially higher and it may be economical to consider using rechargeable Ni-Cad types.

DRIVE MOTOR CONTROL CIRCUIT

Battery B3, consisting of two 1.5V cells in series, supplies power via switch S1c to the line-illuminating filament lamp LP1 and the drive motors M1 and M2. Switch S2 is a 3-position ON/OFF/ON type which enables the motors to be switched off independently of the power to the sensory circuit. In either ON position S2a links the positive terminal of battery B3 to the normally closed contacts of the relays.

Providing the relays are not energised, current is fed to the motors via switch S3a and S3b. The position of S3 determines which motor is controlled by which relay,

i.e. this switch provides the option of "Black line" or "White line" tracking.

If, due to an illumination imbalance between the phototransistors, one of the relay coils switches on the normally closed contact opens and power to the relevant motor is interrupted. Thus the motor stops and the vehicle is steered back onto the line.

One problem that robot designers frequently encounter is that of "overshooting". If the phototransistors sense that the tracker is veering off the line and switches off one motor, that motor will not stop instantly but its inertia causes it to run on for a short time (about 0.5 seconds in the prototype). This slow response may cause the vehicle to lose the line, depending on the severity of the bend.

However, if the motor terminals are short circuited whilst the motor is turning then the induced e.m.f., generated by the motor coil rotating in its magnetic field, will cause a current to flow in the coil which tries to oppose the movement (remember Lenz's law?). In a nutshell, the motor is rapidly brought to rest, its kinetic energy dissipated as heat in the coil and shorting wires. A similar arrangement is often used on electric trains and heavy road vehicles to assist braking; the technique is known as electromagnetic braking (e.b.).

If switch S2b is closed, then as each relay contact changes-over the appropriate motor is electromagnetically braked because the motor terminals are shorted via the normally open relay contacts.

It is useful to provide the option of having the motors running with or without electromagnetic braking because the latter inherently makes the "buggy" follow a jerky path, since the motors switch on and off very rapidly. Electromagnetic braking will be needed if the vehicle is to encounter sharp bends at high speeds.

CHASSIS CONSTRUCTION

A detailed description of the chassis layout is not given because exact positioning of wheels etc. is unimportant. A look at the photographs should give some ideas for a starting point.

The prototype model was constructed on a piece of 5mm plywood cut to a size of 150mm x 240mm. The motor/gearboxes, sensors and lamp are mounted on the underside of this chassis together with a single front castor to allow the buggy to steer left and right.

On the top side goes the circuit board, batteries and control panel. 4BA and 6BA nuts, bolts and washers are used extensively to anchor various components to the chassis. The prototype was left uncased to allow spectators to marvel at the workings!

The motor/gearboxes are purchased as a single unit and are available in a large (MGL) and a small (MGS) version. The large type is recommended for longer life. Two such units will be required.



Instructions for assembling are supplied but only four of the possible six gear wheels are used (*plus* the output gear). When the motor is run from a 3V supply this results in an output shaft speed of 30r.p.m. Using 8cm (3 1/8 in.) diameter wheels gives a forward speed of about 12 centimetres per second.


These gearboxes are quite robust but simply placing a drive wheel on the output shaft and allowing the soft plastic shaft bearings to support the weight of the vehicle would soon cause distortion. A very effective bearing can be fashioned from a 12.5mm (0.5in.) long 6BA brass spacer as shown in Fig. 3.

The spacer should be held in a vice and drilled through with a 1/8 in. bit so that the output shaft is a close fit through the tube. The spacer is then mounted through a 20mm steel L-bracket (from the hardware shop) as shown. The screw hole in the bracket may need enlarging to accommodate the spacer but make it a tight fit and further anchor it with epoxy-resin (Araldite).

A little jiggling may be required to match the heights of the bearing and shaft, use packing washers as needed. A *little* oil should periodically be applied to bearings and gears.

Fig. 3. Details of the motor/gearbox and drive shaft bearing mounting. A close-up of the underside chassis and drive motors is shown in the photograph below.

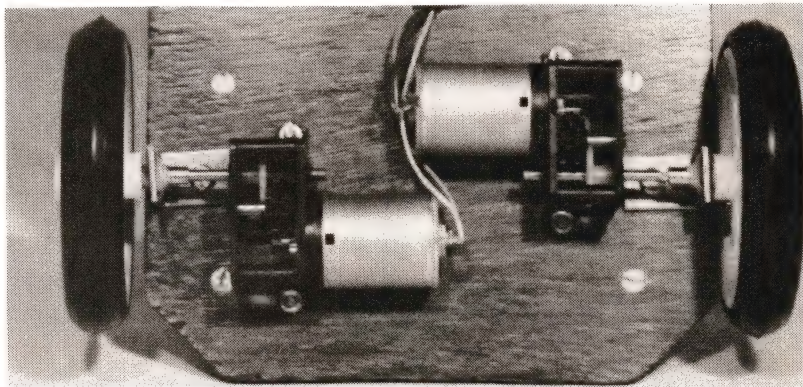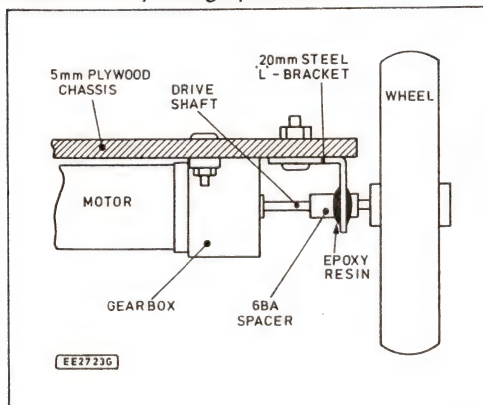

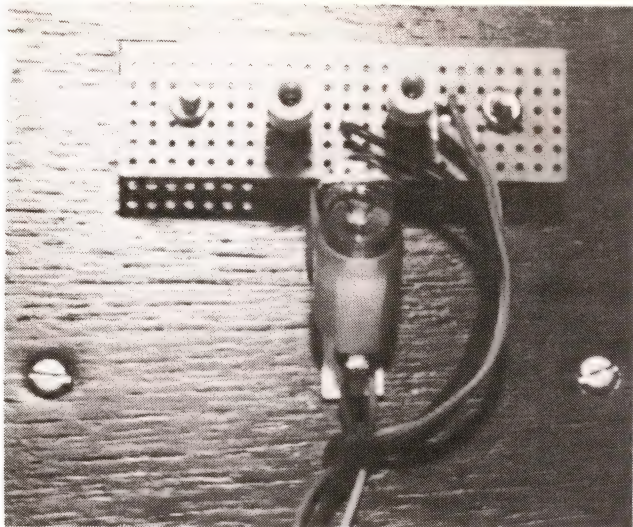

The completed sensor assembly showing the positioning of the lamp.

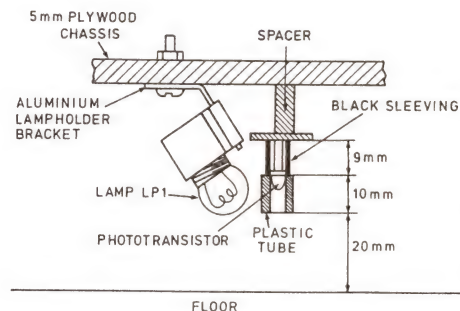
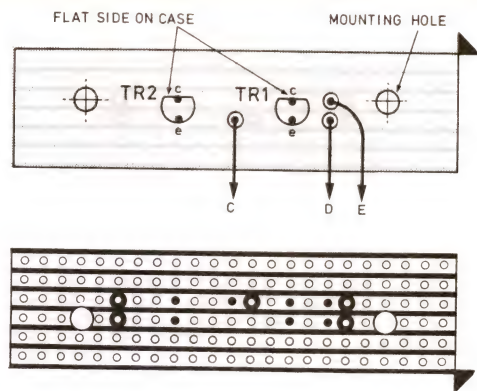


Fig. 4. (right). Details of the line sensor assembly. The sensor is mounted beneath the vehicle – see text.

COMPONENTS

Resistors

R1, R2	5k6 (2 off)
R3, R4	10k (2 off)
R5	470
R6, R7	1k (2 off)

See
**SHOP
TALK**
Page

Potentiometers

VR1	10k miniature preset, horiz.
VR2	1M double-ganged rotary lin.

Capacitors

C1, C2	0μ22 polyester (2 off)
--------	------------------------

Semiconductors

D1	Bi-colour l.e.d.
D2, D5	4V7 Zener (2 off)
D3, D4	
D6, D7	1N4148 signal diode (4 off)
TR1, TR2	TIL78 phototransistor (2 off)
TR3	BC548 npn silicon
TR4	BC212L pnp silicon
IC1	741 op.amp.

Miscellaneous

RLA, RLB	9V 225ohm coil relay, contacts: single-pole changeover, rated at least 1A (see text) (2 off)
----------	--

S1	3-pole 4-way rotary switch
S2	d.p.d.t. toggle switch, with centre-off position
S3	d.p.d.t. toggle switch
M1, M2	combined motor and gearbox, type MGL
LP1	2V5 200mA MES type torch bulb

Stripboard (two pieces) 0.1in matrix, size 29 strips x 39 holes and 6 strips x 23 holes; 8cm diameter wheels (2 off); 5mm plywood 150mm x 240mm; 20mm steel L-brackets and 6BA brass spacers (2 off each); 8-pin d.i.l. socket; terminal pins; clip-on MES bulb holder; plastic tube and sleeving for sensors; knobs (2 off); material for control panel; battery holder for B3 (2 x C-size); PP3 battery clips (3 off); batteries, PP3 (2 off) and C-size (2 off); flexible connecting wire; 4BA and 6BA nuts, bolts, washers and spacers; small furniture castor.

Approx cost
guidance only

£25

SENSOR ASSEMBLY


The relative position of the wheels and sensors and the height of the latter above the line has an important influence on the behaviour of the vehicle. Feel free to experiment, but start by placing the sensors at a distance in front of the rear axles which is roughly equal to half the distance between the rear wheels.

The phototransistors are each mounted in one end of a 10mm length of opaque plastic tube. The open end of this tube should be mounted about 20mm above the ground. A suggested method is shown in Fig. 4..

the sensors are soldered to a piece of stripboard, size 6 strips by 23 holes.

Black sleeving placed over the phototransistor leads between the stripboard and plastic tube prevents light entering through the back of the transistor case, this is important. Remember that the TIL78 is sensitive to infra-red and some apparently opaque plastic tubes are actually quite transparent to IR. A layer of self-adhesive foil tape wrapped around the tube will make it completely "light-proof".

Lamp LP1 is positioned just behind the sensors using a clip-on type MES bulb holder. Avoid light shining directly into the ends of the tubes.

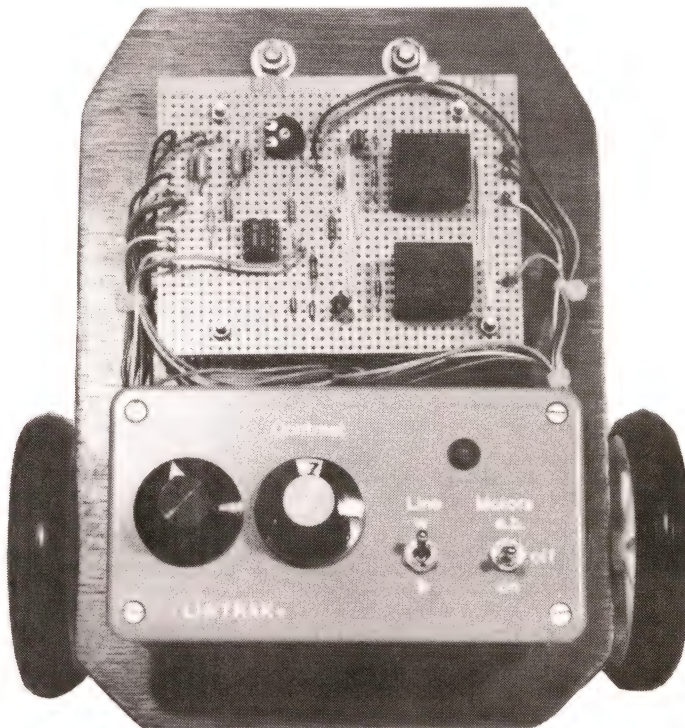

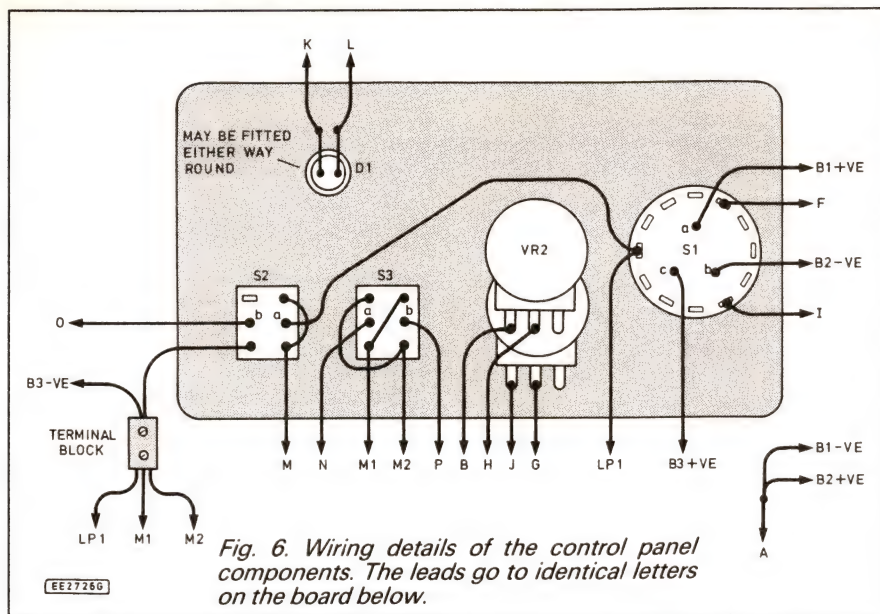


Fig. 6. Wiring details of the control panel components. The leads go to identical letters on the board below.

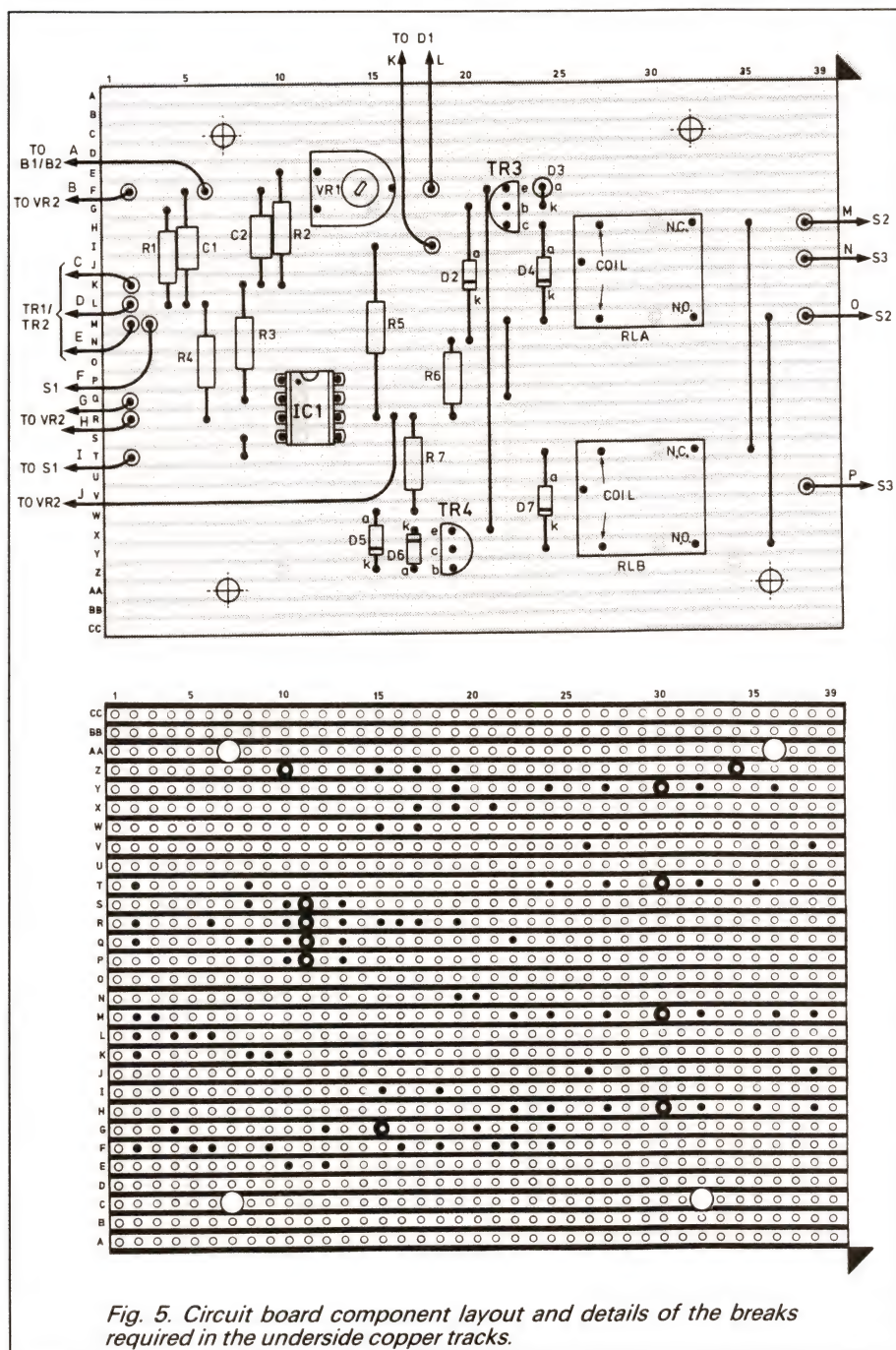


Fig. 5. Circuit board component layout and details of the breaks required in the underside copper tracks.

CIRCUIT BOARD

The three switches, potentiometer VR2 and l.e.d. D1 are mounted on a control panel which can be supported on four 50mm pillars above the batteries, the latter being held on the chassis by double-sided sticky pads.

The remainder of the electronic components are mounted on a piece of 0.1in. matrix stripboard, size 29 strips by 39 holes. Prepare this board by drilling the four mounting holes and then making the 11 breaks in the copper tracks as shown in Fig. 5.

Solder in the five wire links and then fit the remainder of the components as shown in Fig. 5, taking care not to overheat the semiconductors when soldering. Also, take care not to confuse the Zener diodes (D2 and D5) with the 1N4148 signal diodes.

All diodes and transistors on this board need to be inserted the correct way around. Use an 8-pin d.i.l. socket for IC1, do not solder it directly to the board.

The relays used in the prototype had pins which were not spaced on the usual 0.1in. grid and these required careful bending before they would fit on the stripboard. The use of terminal pins for all flying lead connections makes point-to-point wiring easier later on.

Once the board is completed the interconnections between motors, sensors, lamp, circuit board, batteries and control panel can be made according to Fig. 6. Do not make these flying leads unnecessarily long or else interference pickup from the motors may be a problem.

SETTING-UP

Turn the Contrast control VR2 fully clockwise (minimum resistance) and switch on S1. Lamp LP1 should light. Switching the motor switch S2 to either "ON" position should cause both motors to run. If either wheel turns backwards, reverse the connections to that motor.

Now switch S2 OFF, turn the Contrast control to about mid-position and place the Mobile Line-Tracker on a large white surface, e.g. a large sheet of paper. Make sure that the ambient lighting is even and then adjust preset VR1 until the l.e.d. D1 is NOT lit.

Turning the preset VR1 either way from this "null point" should make D1 light up either green or red. With careful adjustment, it should be possible to null the circuit even with the Contrast control turned fully anticlockwise (maximum resistance).

If it is not possible to extinguish the l.e.d. by this method then first double check that the phototransistors have been orientated correctly, the flat side of the device indicates the collector (C). If you are convinced that there are no errors in construction then try moving the position of LP1 to gain a more even illumination under each sensor.

USE

The Mobile Line-Tracker should now happily follow a line which, as mentioned previously, can be laid using masking-tape, insulating-tape or chalk, for example. Find out by experiment what is the best setting for the Contrast control under a certain set of conditions and whether or not electromagnetic braking of the motors is required to prevent the vehicle overshooting on corners. □

BEEB MICROBEEB

... Counting ... Infra-Red Detector ... Counting ...

TWO subjects that seems to crop up in readers' letters from time to time are those of batch counting, and what might be termed "people detecting". In the first case you have objects passing by on a conveyor belt, and some means of counting them is required. Things are not always in quite this form, and the objects to be counted might actually be something like people passing into an entrance or out of an exit.

The object of the exercise might not be to count people at all, and it might simply be necessary to detect their presence in order to activate a security system. Thus, although these two subjects may seem to have little in common, they are really much the same. Many methods of detecting objects work equally well with people, for use in security systems, or whatever.

For any form of batch counting a computer makes a good basis for the equipment. Apart from simply keeping a running count, it can be programmed to sound an audible warning when a certain number is reached, or it could perhaps be used to switch off a process once a certain count had been reached. Sometimes circuitry is needed in order to avoid spurious counts, but with a computer based system it may well be possible to use software deglitching, thus enabling simpler detector circuitry to be used.

Computers are also good as the basis of security systems. They permit sophisticated features to be included at low cost, since these features can often be implemented simply by making some additions to the software.

Count On It

There are various ways of detecting objects or people, but the most simple and universally applicable are the optoelectronic systems. These consist basically of *broken beam* circuits and *reflected beam* circuits.

With the former, a light beam is shone from one side of the conveyor belt (or whatever) to a photocell on the opposite side. As objects pass by on the conveyor belt they briefly break the light beam, producing pulses from the photocell that can be counted.

With reflected beam systems there is again a beam of light shone across the conveyor belt, but the photocell is alongside the light source, "looking" in the same direction. It picks up the light reflected from the objects passing along the conveyor belt, again producing pulses that can be counted.

This second method is more convenient in that it keeps all the electronics in one box rather than having two units on opposite sides of the conveyor belt. It is more difficult to implement in practice though, as the amount of light reflected from the objects being counted may not be very great.

It is also something that might be inconsistent, depending on just what is being counted. The broken beam circuits are generally more simple and give better reliability.

Broken light beam units can be based on simple torch bulb and photo-resistor circuits, but these are often unreliable. The

main problem is that of the ambient lighting tending to hold the unit in the "off" state.

Infra-red circuits give greater reliability, but simple d.c. systems do not provide very great range. For some applications very short range operation is all that is needed, and a simple d.c. infra-red system is then likely to be the best choice.

There are actually "slotted" opto switches available, which consist of a l.e.d. and a photo-detector in one unit with a slot between the two. These are mainly intended for operation in r.p.m. counters and a few other specialised applications. As the slot is only a few millimetres wide, they would seem to be unsuitable for most batch counting etc.

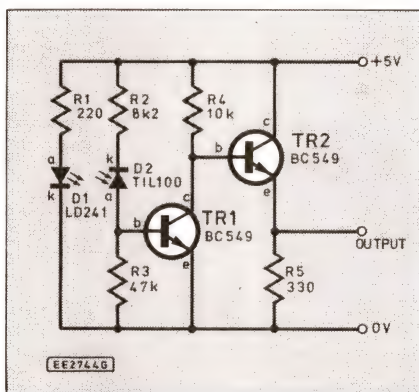


Fig. 1. The circuit diagram for a simple infra-red beam detector.

Infra Red Detector

Making a discrete version having longer operating range is not difficult, and a suitable circuit appears in Fig. 1. Diode D1 is an infra-red l.e.d. which generates the beam, and resistor R1 is its current limiting resistor. The specified value of R1 sets the l.e.d. current at about 15 milliamps, but a higher current can be used in order to boost the range of the unit. Do not use a value lower than 56 ohms (which gives a 50 milliamp l.e.d. current).

D2 is an infra-red detector diode, and like any diode it has a high reverse resistance under normal conditions. The infra-red radiation from D1 causes its leakage level to rise to a much higher level than normal, causing transistor TR1 to switch on. Transistor TR2 simply acts as an emitter follower buffer stage at the output, and this enables the circuit to drive normal five volt logic inputs.

With TR2 normally switched on, the output is at logic 0. If the beam from D1 is interrupted, D2 reverts to a high leakage level, TR1 switches off, and the output goes to logic 1. The circuit therefore produces a low output under standby conditions, and a high output level when it is activated.

Although I have specified an LD241 for D1 and a TIL100 for D2, any similar five millimetre diameter infra-red l.e.d. and large infra-red photo-diode should work in the circuit. Some suppliers simply sell these components as large infra-red l.e.d.s and

photo-diodes, rather than selling them under particular part numbers. For optimum range it is best to use a l.e.d. which has a narrow beam, but getting the optics lined up correctly is easier if a wider beam type is utilized.

The value specified for resistor R3 (47k) will probably give good results, but a slightly lower value can be used if the ambient light level is sufficient to activate the unit when the beam is blocked. Infra-red systems are less prone to problems with ambient light than are visible light systems, but they are not totally free from them. There is a certain amount of infra-red light in a normal environment, and tungsten lighting is quite a good generator of infra-red.

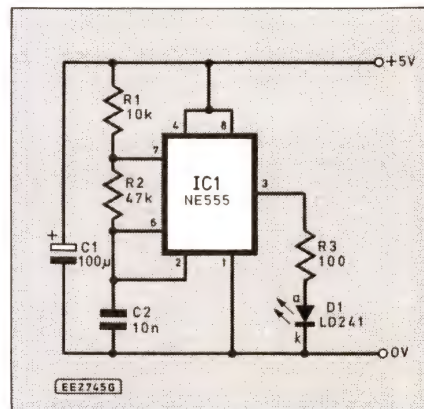


Fig. 2. The pulsed transmitter. This is basically just a standard 555 astable.

Pulsing

A simple d.c. circuit of this type will not provide a particularly large maximum operating range. A range of up to about 150 millimetres should be possible, or with everything carefully set up and a higher l.e.d. current about double this might be achievable.

This is sufficient for some applications, but for others a range of a metre or two is required. Ranges of this order are easily achieved using pulsed infra-red circuits.

The point of using a pulsed transmitter is that the receiver can be an a.c. coupled amplifier. The d.c. output level from the photo-diode is unimportant, and can vary widely without any ill effects being apparent.

The use of coupling capacitors is to block the d.c. signal, but allow the pulses to pass. This permits large amounts of amplification to be used, with the pulses (or lack of them) being detected using a rectifier, a smoothing circuit, and a level detector circuit.

There can still be problems with the ambient infra-red level, but this is relatively unlikely. The normal infra-red background level varies only slowly, and is not pulsed. The exception is mains powered tungsten lighting, which produces significant amounts of infra-red pulsed at 100Hz (i.e. once per mains half cycle). However, this can normally be blocked from the photo-diode, and the receiver will

be insensitive to it anyway due to the relatively low pulse frequency.

The circuit diagrams for the pulsed infra-red transmitter and receiver are shown in Fig. 2 and Fig. 3 respectively. The transmitter is basically just a standard 555 astable circuit operating at around 1kHz. Resistor R3 sets the l.e.d. current, and can be reduced somewhat in value if greater range is required.

In the receiver, Fig. 3, diode D2 detects the infra-red pulses and produces electrical pulses that are fed to the input of a simple two stage amplifier. The low values of the coupling capacitor roll-off the low frequency response of the circuit and combat potential problems with mains "hum".

Capacitor C7 rolls-off the very high frequency response of the amplifier, and is needed in order to combat instability. The output of the amplifier is fed to a conventional two diode rectifier and smoothing circuit.

circuit drops to zero and the output of the unit goes to the high state.

The maximum range of this circuit is a metre or so, but this can be extended a little by using a higher l.e.d. current. A better way of boosting the unit's range is to use a lens in front of the receiving diode.

This does not need to be a good quality type, and the inexpensive Maplin 30mm diameter plastic lens is perfectly satisfactory. The lens must be mounted ahead of the photocell at a distance that is equal to the focal length of the lens (80 millimetres in the case of the Maplin lens).

The effect of the lens is to gather up the infra-red energy over a relatively large area and concentrate it onto the smaller area of the photo-diode. This will often boost the range of the system by a factor of five or more, but the increase obtained obviously depends on the characteristics of the lens used.

A side effect of adding the lens is that it gives the receiver a very narrow angle of

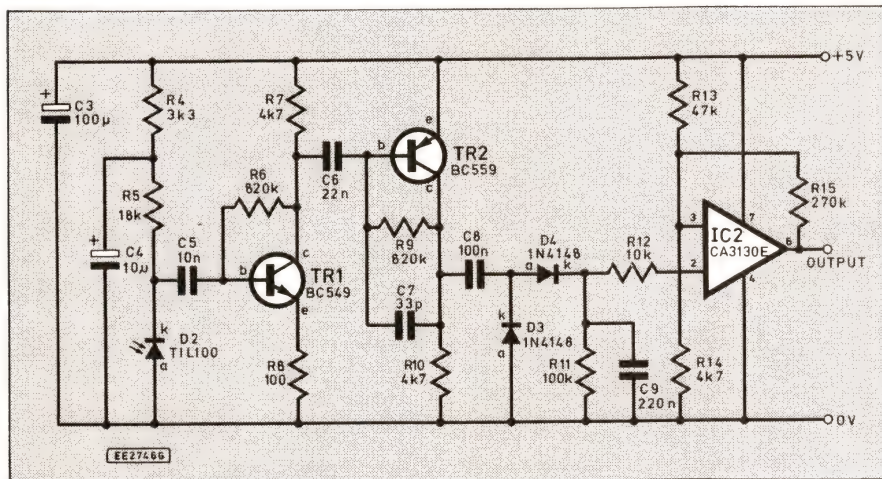


Fig. 3. The circuit diagram for the infra-red pulsed receiver.

IC2 acts as an inverting trigger circuit, and its output triggers to the high state when the input voltage falls below a certain threshold level. Normally the unit is receiving infra-red pulses, and the output from the smoothing circuit is above the threshold level. However, when the beam is blocked, the voltage from the smoothing

view. The unit must therefore be accurately aimed at the transmitter if the system is to function properly.

The range can be further boosted by adding a lens in front of the transmitting l.e.d. as well. Quite long operating ranges can be obtained in this way, but optical alignment of the system becomes very critical

Interfacing

The user port of the BBC computer permits several interfacing options. For a counting application the obvious one is the 6522 VIA in the mode where it counts pulses from an external source.

This may not be the best choice though, since the detector circuit is quite likely to generate a few spurious pulses. This would result in grossly inflated counts. If this method is used, it will almost certainly be necessary to add a monostable at the output of the detector circuit in order to provide "debouncing".

Using an ordinary digital input to monitor the output of the detector, and a loop to repeatedly read the output level in order to detect a change to the high state, there is a slight risk of pulses being missed. In reality this is probably not a very great risk, since the pulses from the detector would normally be fairly long, and the loop would presumably monitor the detector's output a few hundred times per second. However, this possibility can be removed altogether by using a "handshake" input set to respond to low-to-high transitions.

If "deglitching" is required in order to prevent spurious counts, this can be provided by the software. For the sake of this example, assume that the count rate will never exceed two per second.

The routine that detects pulses from the detector could include a delay loop to ensure that something close to 0.5 seconds elapses after one pulse is detected, before the output is monitored again. Any spurious pulses after an initial transition will then not be counted, because the software will be idling when they occur, and will ignore them.

There can sometimes be problems with false counts due to something like a moth flying through the beam, or electrical interference from lighting etc. These "false alarms" will usually provide very short output pulses, and can be detected by suitable software routines.

After the initial detection of the pulse, it is just a matter of having a loop routine to provide a suitable delay before checking the output level from the detector again. If it is still high, then the output pulse is a proper type. If not, then it is a spurious pulse.

SHOP TALK

with David Barrington

Please Note

The diodes used in the power supply bridge arrangement in the *Valve Distortion Unit* should be 1N4007's. The 4001's are underrated and should NOT be used.

Car Heater Thermostat

We have been unable to find any source for the rod thermistor VA1067S used in the *Car Heater Thermostat*. According to our information this device is rated at 150k at 25°C and 2k5 at 150°C.

An alternative suggestion is to use a bead type thermistor, which seems to be more readily available, and adapt the water sensor assembly to suit. A suitable bead thermistor is stocked by Maplin, order code FX43W.

Most advertisers should stock a suitable 12V 16A relay. These are listed for automobile applications and the most popular ones have a coil resistance of about 200 ohms.

Ghost Waker

A suitable mask for the *Ghost Waker* project should be stocked by "high street" joke shops or from a theatrical costume supplier.

The microphone used in the prototype model was purchased from Maplin, code QY62S. Miniature 12V solenoids are reasonably expensive and it may be worth "shopping around". One similar to the type used is the 12V 48 ohm coil from Maplin (YR88V).

The small printed circuit board is available from the *EE PCB Service*, code EE703 (see page 692).

Mobile Line-Tracker

The only items that could cause local purchasing problems for constructors undertaking the *Mobile Line-Tracker* are the motor/gearbox and possibly phototransistor.

The combine low voltage d.c. motor/gearbox unit is listed by Magenta (☎ 0283 65435)

and the larger MGL (£4.55) unit should be purchased. They are also able to supply the TL78 phototransistor and the 3in dia. wheels.

The front wheel "castor" and the plywood chassis should be available from DIY stores. Most component suppliers should be able to offer suitable p.c.b. relays, but check the contact pin arrangement before wiring onto the circuit board and adapt as necessary.

Frequency Meter

The meter used in the *Frequency Meter* is the 4in. 100µA moving coil panel mounting type from Maplin, code YJ96E. The trimmer capacitors (code WL72P) and the mains transformer (code LY03D) were also purchased from the same company.

The printed circuit board is available from the *EE PCB Service*, code EE704 (see page 692).

Fridge Alert

The only component called for in the *Fridge Alert* that is likely to cause some local difficulties is the glass bead thermistor GL16.

The glass types are fairly expensive, but most of our advertisers should be able to offer a suitable equivalent. The GL16 is rated at one megohm at 20°C and has a minimum resistance of 170 ohm.

In case of difficulty in purchasing the i.c.s, the ICL7611 is currently listed by Cricklewood and the ICL8211 by Maplin.

ACTUALLY DOING IT!

by Robert Penfold

THE TREND in modern commercial electronics is to have as many of the components as possible on the main circuit board. Along with the resistors, semiconductors, capacitors, etc., there are printed circuit mounted controls, sockets, and even larger items such as mains transformers.

In the commercial electronics world this method of construction has the advantage of keeping down production costs. Designs for the amateur electronics enthusiast make relatively little use of printed circuit mounting controls, sockets, and the like.

Using these components generally simplifies the electronics side of construction, as well as reducing the risk of errors. It is rather restrictive though, in that it usually ties you down to using the particular case that the circuit board was designed to fit. Making even a few minor modifications to the project, such as repositioning a few controls slightly, might be impossible.

Actually this is not quite true, since in most cases there is no difficulty in having ordinary potentiometers, sockets, or whatever, mounted off-board, and wiring them to the circuit board. For the absolute beginner it is probably best not to do this, as it increases the risks of errors.

However, for the complete beginner there is a lot to be said in favour of reasonably simple projects that have all or virtually all the components mounted on a (ready made) custom printed circuit board. This method of construction leaves a minimal amount of scope for errors! For the slightly more experienced constructor though, using off-board controls and sockets should not give too many problems, and gives you plenty of scope to do your own thing.

The hobby of electronic project construction need not consist of producing exact clones of published designs. Customising projects, or simply adapting them slightly to suit the particular components to hand are well established practices. Eventually you might start "borrowing" sections of published designs in order to put together your own designs, perhaps ultimately progressing to projects that are genuinely all your own work.

HARD WIRING

The wiring from controls etc. to a printed circuit board is known by such names as "point-to-point", "hard", and "spaghetti" wiring. I think it is true to say that most constructors find that this

point-to-point wiring helps to make building a project more interesting.

Mounting components on a printed circuit board is generally easier and more "foolproof", but can lack interest as a result of this. Wiring up controls etc. takes a little more time and concentration, but is a more rewarding task as a result of this.

In component catalogues you will usually find a variety of wires for use in projects. For most hard wiring a medium thickness multi-strand p.v.c. insulated wire is the most popular type. A 7/0.2 type (which has seven strands of 0.2 millimetre diameter wire) is the usual choice.

In the larger catalogues you may find thinner types, such as 7/0.1 wire, but these are just a bit too thin for general use. They are actually capable of taking the currents in most projects, where the maximum current flow is often only a few milliamps. However, their thinness make them a bit difficult to deal with, and the 7/0.2 type is much easier to use.

Most electronic component catalogues list at least one thickness of single strand connecting wire. The advantage of the single strand variety is that it can easily be formed into the desired shape so that it can be neatly and easily routed around a project. It tends not to be very popular as it has a tendency to break.

The whole point of multi-strand wire is that by having a number of very thin wires it is flexible and has good resistance to breaking due to metal fatigue. Also, if when stripping the insulation from a multi-strand wire it should be accidentally nicked slightly, it is likely that only one or two of the strands will be damaged and break, leaving five or six strands intact. This is less than ideal, but the five or six unbroken strands of wire should be sufficient to do the job properly.

If a single strand wire should be nicked slightly when the insulation is being stripped, it will be rendered very vulnerable to breaking at that point, and will probably snap before too long. In my experience single strand connecting wire has always been more trouble than it is worth, and I would certainly not recommend it for general project wiring.

In some component catalogues you may find some thicker connecting wires listed. These are only required for projects such as large power supplies and high power audio amplifiers where large currents are involved in certain parts of the circuit.

The resistance in thinner wires could cause a reduction in the performance of the circuit, and in an extreme case there would be the risk of the wire burning out (possibly causing a fire in the process). If a heavy duty connecting wire is needed, this should be pointed out in the book or article in which the project is featured.

Wires of this type should only be used when they are really necessary. Apart from their relatively high cost, they are a bit large and cumbersome to use.

PROJECT WIRING

Project wiring mainly consists of small groups of wires running from an off-board component to a set of solder pins on the circuit board. This type of wiring can be added in as several totally separate wires, but this is not likely to give particularly neat results.

Neatness of the wiring is not just a matter of making the interior of the project look pretty so that you can impress your friends. With a tangle of wires it is very difficult to sort out any errors, and the risk of making errors in the first place probably increases. If the project should require servicing at some later date, this is likely to prove easier if the wiring is neat, tidy, and easy to follow.

The traditional method of handling groups of wires is to use separate wires, but to route them side-by-side into neat collections of wires. The wires in each group can be tied together using thin cord, but this is not as easy as you might think. I have seen some very neat looking cableforms of this type in ready-made equipment, but have never managed to produce passably neat cables myself! A much easier and quite neat alternative is to use a few bands of insulating tape.

My preferred method these days is to use ribbon cable. As its name suggests, it is a flat ribbon-like cable that is effectively a number of pieces of thin multi-strand connecting wire laid side-by-side and moulded together. It is generally only sold as cables having ten or more leads, but it is easily pulled apart so that a piece having the required number of leads can be removed.

The grey type is a bit cheaper than the multi-coloured "rainbow" type. However, the latter is much better as it makes it more difficult to misidentify wires and get connections accidentally swapped over. For this application the multi-coloured type is probably well worth the extra expense. The thin ribbon cable intended for use with IDC connectors is the most widely available, but for present purposes the slightly thicker types are a bit better.

STRIPPING

As already pointed out, nicking a wire when stripping the insulation from it is likely to seriously weaken the wire. Using multi-strand wire minimises the problem, but it is important to strip insulation without damaging the wire if maximum reliability is to be obtained.

I make no apologies for giving the much repeated advice not to use knives or scissors as wire strippers. Even if we ignore the very real danger of cutting yourself when using these methods, there is still the problem of the wire getting damaged. Proper wire strippers do not cost a great deal, are very quick and easy to use, and provided they are set correctly there is little risk of damaging the wire.

In practice it is not usually possible to get everything adjusted quite as precisely as this, and the wire strippers are adjusted so that they do not quite cut right through the insulation. If you close the blades over a wire and then pull it away from the strippers, the insulation will invariably break, with the unwanted piece coming away with the strippers. This invariably leaves the wire totally undamaged.

TINNING

The ease with which the vast majority of components can be soldered onto a printed circuit board can give you a false sense of security when carrying out the hard wiring. In order to avoid problems with "dry" joints it is essential to "tin" both surfaces to be joined with a generous amount of solder. In order to do this, first apply the iron to the tag, end of a lead, or whatever, and then apply some solder.

From time to time you will encounter an awkward tag or lead that will not tin properly. This happens when the surface is contaminated with oxide, grease, or dirt of some other kind. The solder will go into blobs which run straight off the tags or lead.

Instead of leaving a shiny and nicely tinned surface that will solder easily, the result is usually a blackened surface covered with burnt flux from the solder. Producing good soldered joints with one or both surfaces like this is impossible.

The cure for this problem is to clean the lead or tag by scraping it with some very fine sandpaper, a small file, or the blade of a pen knife. Once the shiny metal is showing through nicely, there should be no difficulty in tinning the lead or tag.

If a component shows obvious signs

of corrosion, or any contamination that is likely to prevent it being tinned properly, it makes sense to clean away the contamination before trying to tin the component, rather than waiting until problems have arisen. Even if you should manage to tin a doubtful looking component, you might find that it has not taken the solder very well, and that a weak soldered joint will be produced as a consequence.

With both surfaces properly tinned, actually completing the soldered joints should not be at all difficult. The ends of leads are hooked around tags of the type that have holes, or wrapped a few times around the type that do not.

This second method is also used when making connections to solder pins in printed circuit boards. I would strongly urge the use of solder pins rather than making off-board connections direct to the pads of the board.

Using pins will give a finished assembly that is very much tougher. It usually makes wiring up a project very much easier as well.

Run plenty of solder onto the joints. Very little solder will give a good electrical connection, but a more generous amount will produce a joint that is also physically strong.

SCREENING

A slight complication with some projects (mainly audio types and test equipment) is the need for some of the wiring to be of the screened variety. A screened lead consists basically of an inner conductor, a layer of plastic insulation around that, a layer of braided wire around that, and then finally an overall layer of insulation, see Fig. 1.

The idea is for the outer conductor to be connected to the earth rail of the circuit. The inner conductor is then screened, and will not pick up mains "hum" or other electrical interference. Screening can be used in much the same way to prevent a wire from radiating a signal.

There are multiple screened leads, and the type you are most likely to use is a twin type for stereo equipment. The over-

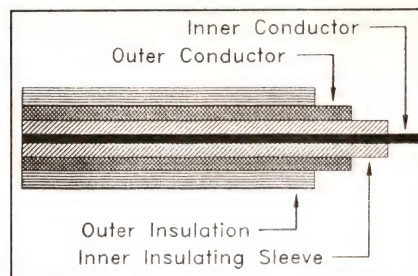


Fig. 1. Cross section through a screened cable. The outer conductor screens the inner one.

all screened leads have two insulated leads sharing a common outer conductor. These tend to give significant amounts of stray coupling from one lead to the other, rendering them considerably less than ideal for many applications. The other type is so-called "figure of 8" style cable, which is effectively just two single screened leads laid side-by-side and fixed together.

Screened leads can be a bit awkward to deal with. Unless a particular type is specified, it is probably best to opt for one of the thinner cables. The outer insulation of these can easily be removed with the aid of most wire strippers.

The thicker screened cables defeat most wire strippers, and the outer cladding has to be removed by carefully cutting through it using a modelling knife. Go as slowly and carefully as necessary to avoid any serious damage to the braiding. If you should damage the braiding, cut off the end section of the cable and try again.

You should find that the braiding can be combed out with the aid of a fingernail, and then it is tightly twisted together to form a lead. Next it is heavily tinned with solder to prevent it from unwinding. If any little bits of wire are missed and left sticking out, cut them off so that they cannot accidentally short circuit to something.

Finally, a small piece of insulation is removed from the inner conductor, and the exposed lead is tinned with solder. The lead is then ready for connection.

Note: Subs price held until October 1st -
ORDER NOW!

ELECTRONICS

SUBSCRIPTION ORDER FORM
Annual subscription rates (1990): UK £16. Overseas
£19.50 (surface mail) £37 (air mail)
To: Everyday Electronics, Subs. Dept., 6 Church Street,
Wimborne, Dorset BH21 1JH.

Name.....

Address

I enclose payment of £..... (cheque/PO in **£ sterling**
only payable to Everyday Electronics)  
 Access or Barclaycard/Visa No. _____

[illegible]

Signature..... Card Ex. Date.....

Please supply name and address of card-holder if different from the subscription address shown above.

Subscriptions can only start with the next available issue. For back numbers see the Editorial page.

EVERYDAY ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY

NEWSAGENT ORDER FORM

Please reserve/deliver a copy of **Everyday Electronics** for me each month.

Signed

Name and Address
(BLOCK CAPITALS PLEASE)

Everyday Electronics is published on the first Friday of each month and distributed by Seymour.

Make sure of your copy of EE each month—cut out this form, fill it in and hand it to your newsagent.

REPORTING AMATEUR RADIO



Tony Smith G4FA1

NOVICE LICENCE UPDATE

The RSGB reports good progress on the proposed Novice Licence. The basic idea is that those wishing to obtain the new licence will have to attend a course given by an RSGB registered Instructor. Normally Instructors will deal with just four students at a time although special arrangements can be made for disabled or geographically isolated students.

During the 30-hour course all the basics will be taught, including etiquette and operating disciplines. On satisfactory completion of a course a student can take the 90 minute Novice multiple choice examination which will be held every three months. This will have 10 questions on licensing conditions and a further 35 covering other aspects included in the course.

A Novice Training Manual has been prepared and during the next few months all proposed books for students should be completed. Everything seems on course to introduce the new licence within the DTI's target date of early 1991.

ISRAEL RESTRICTIONS LIFTED

Last month I mentioned a 1987 broadcast by Ko1 Israel, the *Voice of Israel*, which referred to the fact that except for Egypt, there were no amateur exchanges allowed between Israel and the surrounding countries in the Middle East.

Circumstances have now changed dramatically and, according to the W5YI REPORT of July 1, Israeli operators may now freely contact amateurs in Algeria, United Arab Emirates, Bahrain, Tunisia, Jordan, Kuwait, Lebanon, Libya, Mauritania, Morocco, Sudan, Syria, Oman, Iraq, Saudi Arabia, Qatar, and both Yemens.

WW2 AMATEUR OPERATIONS

In wartime, restrictions on possible means of communication with the enemy are inevitable and amateur radio operation is closed down. Nevertheless some German amateur stations remained on the air throughout WW2, and were "worked" by a number of mysterious British stations towards the end of the war. According to an article in *Morsum Magnificat*, winter 1989, by Michael Ockenden, G3MHF, some 150 German amateur stations operated mainly on the 80 and 40 metre bands trying to persuade the outside world that life in Germany was continuing normally!

Contacts with American stations continued until 1940 when the "Ws" were forbidden to work stations operating from the war zone. A few licences were issued for stations in Hungary and Czechoslovakia, and German amateurs with D-calls operated from France, Greece, North Africa, Norway, and Spain. It was naturally suspected that these stations were set up for political or intelligence purposes but, according to the author, despite their

propaganda purposes there was nothing sinister about the operators or the QSOs (contacts) which passed between them.

In 1945, a number of British stations using G7 calls appeared on the bands. The Germans thought these stations were on the east coast of England and contacts with them were prolonged in the hope of identifying them. The QSOs were conducted in a polite and correct manner and all logs were sent to the authorities in Berlin.

No official explanation has ever been given about these G7 stations although they must have been specially authorised to operate, possibly for intelligence purposes. Pirate stations using G4 and G9 calls were also heard by the Germans around this time so another possibility is that the G7s were set up to help track down the pirates. Perhaps, one of these days, someone will reveal what was really going on!

Incidentally, *Morsum Magnificat*, "which records the story of Morse telegraphy right back to the time when Samuel F. B. Morse first dreamed of communication by means of dots and dashes," has a new editor. He is Geoff Arnold, G3GSR, who publishes *Radio Bygones* and who was previously editor of *Practical Wireless*.

Further details can be obtained from *Morsum Magnificat*, 8A Corfe View Road, Corfe Mullen, Wimborne, Dorset BH21 3LZ.

INTRODUCTION TO VHF/UHF

"Amateur radio is often associated with the HF bands below 30MHz ... However, the area where there is probably more activity and growth is actually in the VHF (very high frequency) and UHF (ultra high frequency) portions of the spectrum which lie between 30MHz and 3000MHz."

So begins the introduction to a new book, *An Introduction to VHF/UHF for Radio Amateurs*, by Ian Poole, G3YWX. Intended to be of use to both newcomers and experienced radio operators it provides a general survey of the amateur bands in this wide range of spectrum and the variety of characteristics and activities within these bands.

For most people entering amateur radio via the full Radio Amateurs' examination or for those coming in via the new Novice Examination, the 2 metre VHF band, will probably provide their first experience on the air. This small (94 pages) book will tell them most of what they need to know to get started and will help them to extend their activities to additional modes and bands in due course.

It covers such matters as propagation; bands and bandplans; receivers and transmitters; aerials; mobile and repeater operation; Dxing; data communications; and scanners, and there is a short but useful appendix containing abbreviations and

codes. Its size prevents it from going to deeply into any particular aspect, but that is exactly what is required from an "Introduction" to any subject. My sole reservation is that a bibliography for the benefit of those wishing to read further would have been helpful.

If one tunes around the VHF bands at present, the book reference to "activity and growth" might be doubted as there is currently an apparent decline in activity. The present excellent conditions on the HF bands around the peak of the sunspot cycle have resulted in thousands of class A licensees deserting VHF to enjoy themselves on HF Dx bands below 30MHz.

These operators will return in force when HF conditions deteriorate and long-term growth in VHF and UHF will then continue. It is often claimed that the one remaining area left for true amateur experimentation and development is at UHF – but this type of activity is still in the future for those at the stage where they have a need for this introductory book!

SCANNERS

Although scanners and scanning are not strictly part of amateur radio, the book includes an interesting chapter on this subject because it is an "aspect of the VHF/UHF arena which is becoming increasingly popular." It points out, however, that the law about receiving different transmissions varies widely from country to country and that it is wise to investigate the current position.

In the UK, the Wireless Telegraphy Act states that the public may only listen to broadcast stations, standard frequency transmissions and licensed radio amateurs, although "it is quite easy to obtain a license to pick up transmissions from weather satellites." In spite of these restrictions, "scanners are widely available and are on sale quite openly ... it is necessary to be aware of the restrictions because people have been prosecuted for listening to police transmissions."


The book describes the development of scanners from the earliest models, which used crystal controlled local oscillators (needing one crystal per channel), which could only monitor ten or fifteen channels. In contrast, it discusses today's models, using frequency synthesisers, which cover large numbers of channels and incorporate large banks of memories and other features.

A section on operation describes the functions of the various controls found on a typical scanner, and the wide range of services to be found throughout the spectrum including a list of the major frequency allocations between 30 and 1000MHz.

An Introduction to VHF/UHF for Radio Amateurs, by I. D. Poole, is published by Bernard Babani (publishing) Ltd, price £3.50. Available from *EE Direct Book Service*.

REALISTIC®

Walkie talkies

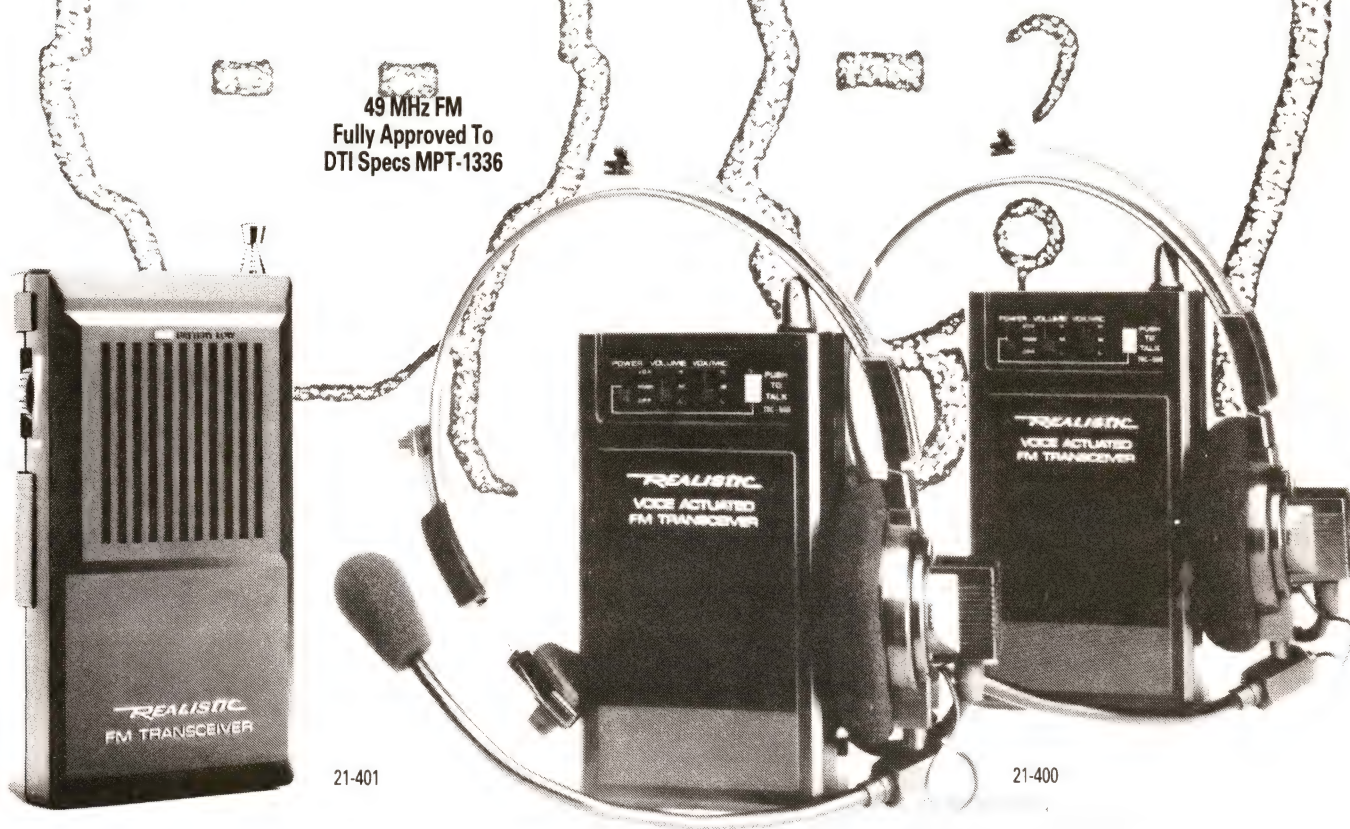

£24⁹⁵ EACH

• Licence Not Required

Realistic TRC-501. Only 1 inch thick and five ounces light! Call button transmits a tone signal. Low-battery indicator, push-to-talk button, telescopic aerial. Includes belt clip. Requires one 9v battery.

£59⁹⁵ PAIR

• Licence Not Required

Realistic TRC-500. Voice-actuation gives you hands free communication. Dual-conversion superhets for high sensitivity and clear 2-way communication. Volume switch. With belt clips. Each headset requires 9v battery.

Tandy®


Over 400 Tandy Stores And Dealerships Nationwide. See Yellow Pages For Address Of Store Nearest You.

InterTAN U.K. Ltd., Tandy Centre, Leamore Lane, Walsall, West Midlands. WS2 7PS
Tel: 0922 710000

5°C FRIDGE ALERT

T. R. de VAUX-BALBIRNIE

Keeps harmful germs at bay

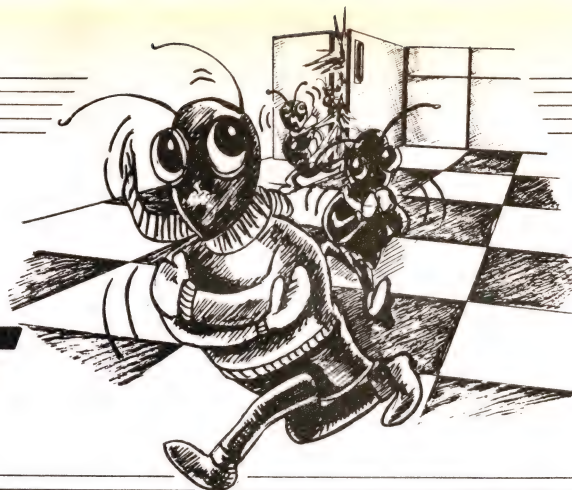

RECENT statistics reveal that only 1 in 10 people ever check the temperature of their fridge. This is unfortunate since, unless it is cool enough, bacteria multiply rapidly and can cause food poisoning. This is true for everyone, but especially so where babies and elderly people are involved due to their limited resistance to infection.

It is generally agreed that the temperature of a fridge should be kept below 5°C. However, human nature being what it is, regular checking with a thermometer will soon be abandoned after an initial burst of enthusiasm. During warm weather, the cabinet temperature often rises and can reach a dangerous level unless the thermostat is re-adjusted.

FRIDGE ALERT

The circuit to be described here gives a continuous check and warns the user of a rise in temperature for whatever reason. In use, the 5°C alert is placed inside the fridge – perhaps in a door compartment where it will be seen each time the fridge is opened. A red l.e.d. (TEMP!) will flash if the temperature rises above a preset level.

The circuit is self-contained with everything, including battery and sensor housed inside a small plastic case. You will need a mercury thermometer for setting-up purposes but this can probably be borrowed.

Since the circuit is switched on continuously, it is important to minimise the standby current requirement. Care over design has kept this to less than

5µA. The specified lithium battery should provide years of service providing the l.e.d.'s are not called upon to light very often.

There is a battery check facility – it is suggested, however, that the battery be replaced as a matter of course every 2 years. Using the specified battery is important for, although other types are cheaper, they will perform less satisfactorily.

Not only do lithium batteries have a very long life and high capacity for their size, they maintain a fairly steady terminal voltage over a long period of time and this helps in providing precise operation. However, in tests on the prototype, operation remained within one degree for any battery voltage between 6 and 10 volts.

CIRCUIT DESCRIPTION

The complete circuit diagram for the 5°C Fridge Alert is shown in Fig. 1. This comprises two sections. The first centres on IC1 and forms the temperature sensor. The other consists of IC2 and associated components and is the battery condition warning.

This latter section is only called into play when push-to-test switch S1 (BATTERY TEST), is operated. This keeps current drain to a minimum. There was thought to be no point in providing an on-off switch for the circuit as a whole.

The temperature-sensing section operates in the following way. IC1 is a CMOS operational amplifier which, under

quiescent conditions, requires only 12µA approximately. This makes it ideal for the present purpose.

The non-inverting input, pin three, receives a voltage whose value depends on the potential divider action of preset, VR1, in conjunction with resistors, R3 and R4. With the values specified VR1 will allow voltage adjustment between nominal limits of 2.5V and 3.6V.

The inverting input, pin two, also receives a voltage from the potential divider consisting of resistor R1 in the upper section and the thermistor R2 in the lower one. The thermistor is a miniature "bead" type whose resistance falls as its temperature rises.

At 5°C the voltage at pin two will be approximately 3V and VR1 will be adjusted at the setting-up stage so that the voltage at pin three is just less than this. The op-amp will then be off with the output, pin six,

COMPONENTS

Resistors

- R1, R3 4M7
- R2 *GL16 min bead thermistor
- R4 2M2 (see text)
- R5 56k
- R6 12k
- R7 10k
- R8 270

All 0.6W 1% metal film

*1M at approx. 20°C

See
SHOP
TALK
Page

Potentiometer

- VR1 1M sub-miniature vertical preset

Semiconductors

- D1 5mm flashing red l.e.d. (3.5V to 12V operation with no series resistor required)
- D2 5mm green l.e.d.
- TR1 ZTX300 npn silicon
- IC1 ICL7611 CMOS op-amp
- IC2 ICL8211 voltage indicator


Miscellaneous

- B1 Lithium battery (PP3), with connector
- S1 Miniature push-to-make switch
- Stripboard 0.1in, matrix, size 9 strips x 24 holes; plastic case, size 107mm x 53mm x 18mm (internal); 8-pin d.i.l. socket (2 off); connecting wire; solder etc.

Approx cost
guidance only

£12
excl. Bat.

Fig. 1. Complete circuit diagram for the 5°C Fridge Alert.

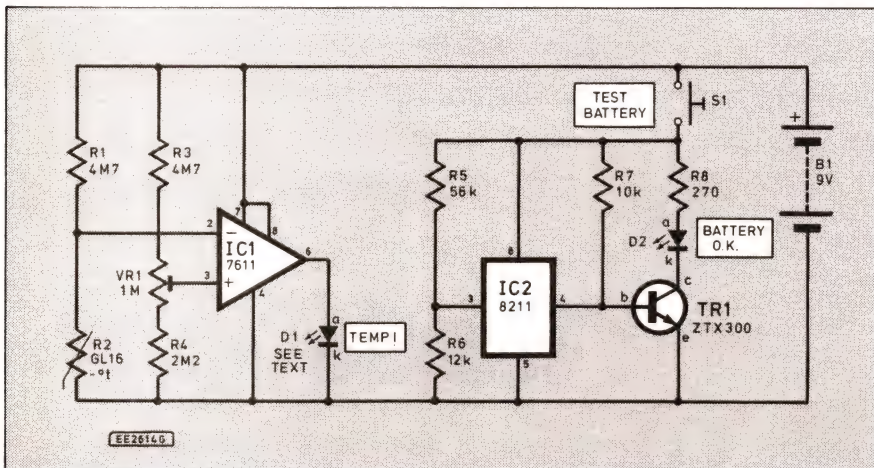

low (negative supply voltage). The flashing l.e.d, D1, will therefore be off.

When the temperature of R2 rises, its resistance falls and so does the voltage across it. The voltage at the inverting input is now less than the non-inverting one and the output, pin six, goes high (positive supply voltage). This operates D1, the flashing l.e.d. (see components list). An ordinary (non-flashing) one could be used, but the effect would not be so eye-catching and it would require a series current-limiting resistor of 390 ohms.

BATTERY CHECK

The battery checking section, operates in the following way. IC2 is a voltage detector integrated circuit which responds to the voltage applied to the threshold input, pin three. If this is less than the internal reference voltage of 1.15V, the output pin four, can "sink" current from the positive line. This current is limited to 7mA by on-chip circuitry.

When Battery Test switch, S1, is pressed, IC2 receives power from the supply, B1, to pin eight. The potential divider consisting of resistors R5 and R6 are connected directly across the supply.

With the specified values and a battery voltage of 7V approximately and above, the voltage applied to pin three will exceed 1.15V. Current then flows through resistor, R7 and turns on transistor, TR1. Thus the green l.e.d. (Battery OK) operates through current-limiting resistor, R8. When the battery voltage is less than 7V, the voltage at IC2 pin three is less than 1.15V and TR1/D2 will be off.

This method gives positive indication that the battery is sound. This is thought to be better than the l.e.d. lighting when the battery is low since general failure – even a very discharged battery – would do this as well. A further advantage of the present system is that the l.e.d. imposes a current drain and the terminal voltage of the battery is measured "on-load".

CONSTRUCTION

Most of the components are fitted on a piece of 0.1in matrix stripboard, size 9 strips x 24 holes. Details of the component layout on the board is shown in Fig. 2.

Cut a piece of board to size and make all track breaks and inter-strip links as indicated. Drill the single mounting hole. Solder all on-board components into position.

Note that the full length of the thermistor (R2) wires should be used. Sleeve them using insulation removed from scrap connecting wire and solder this component into position quickly to avoid heat damage. Do not insert the i.c.s into their holders until the end of construction.

The reason for the bead thermistor being board-mounted is to make it relatively slow at responding to the fridge temperature. If it protruded through a hole in the case, it would respond rapidly to a rise in temperature when the door was opened. This would cause unnecessary on-off switching and waste the battery life.

Solder 5cm pieces of light-duty stranded connecting wire to strips A, B, E, G, H and I along the right-hand side of the completed circuit panel as indicated. Solder the battery connector to strip A (positive) and strip I (negative).

Prepare the box by drilling holes for D1, D2 and switch S1 as shown in the photograph. The l.e.d's may be a tight

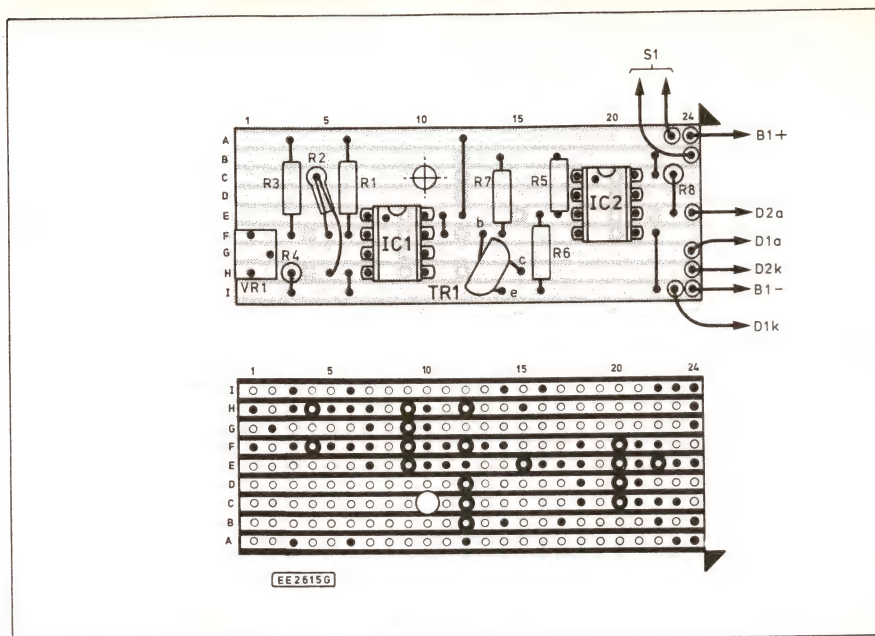


Fig. 2. Stripboard component layout and details of breaks required in the under-side copper tracks.




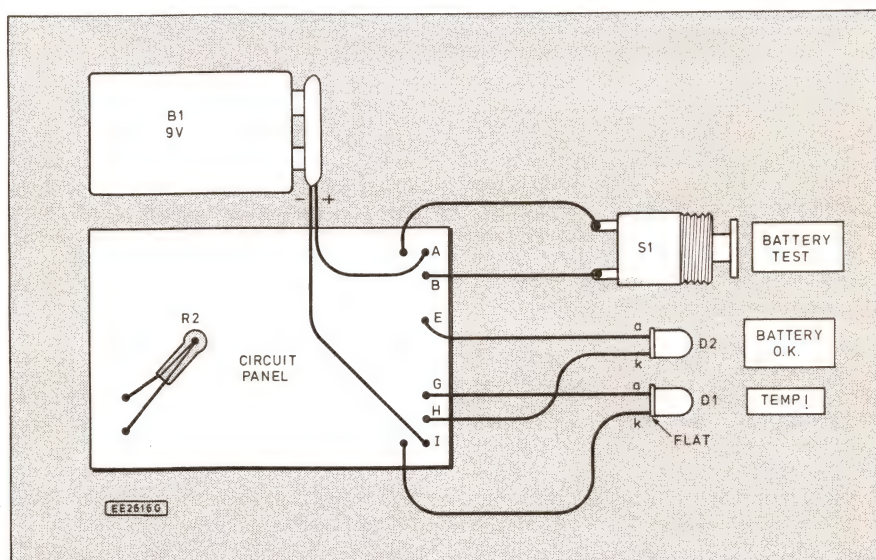


Fig. 3. Interwiring from the circuit board to the battery, test switch and the two "condition" l.e.d.s. (below) The completed alert placed on a shelf inside the fridge.

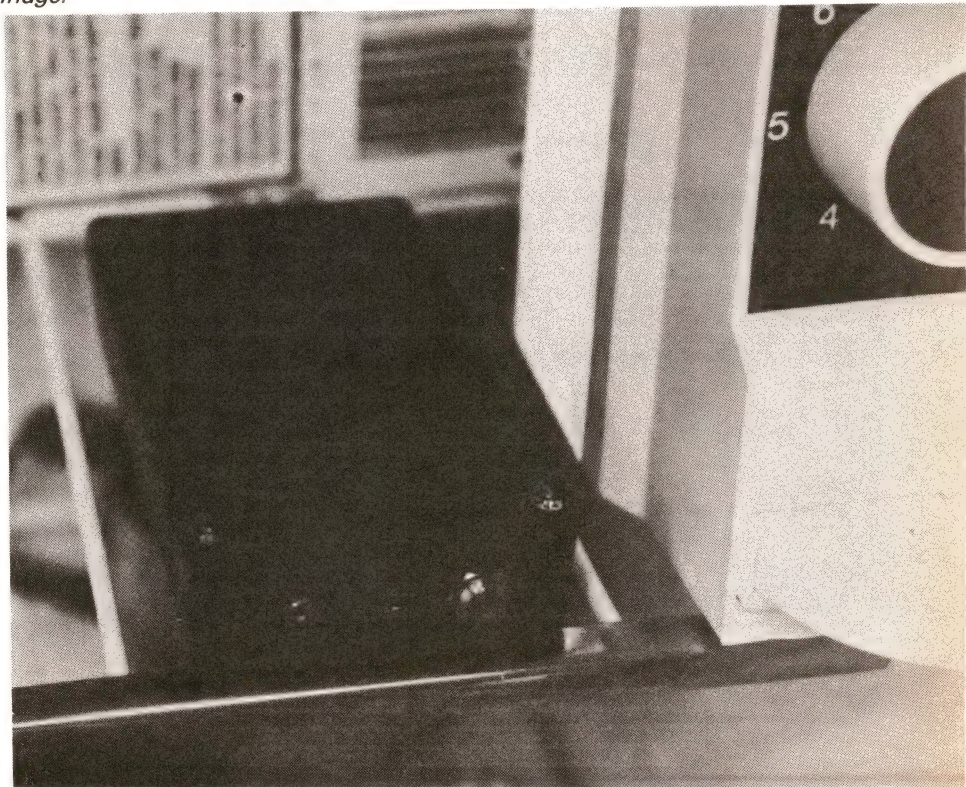

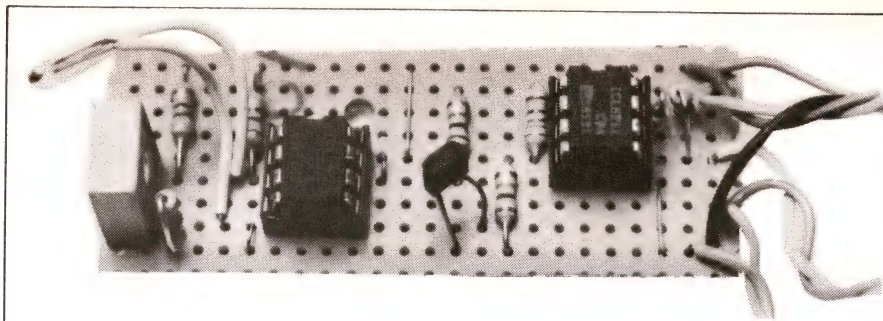

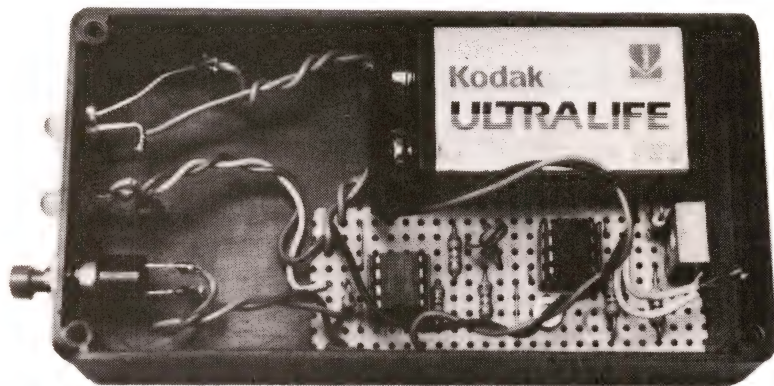The completed circuit board, with thermistor, is shown above and the layout of components inside the case, below.



push fit in the holes or l.e.d. clips could be used. In the prototype, the l.e.d.'s and switch S1 were mounted on a short side of the box. However, the positions could be altered to suit the application.

Drill the hole for circuit panel mounting and a further small hole to align with preset VR1 so that this component may be adjusted using a small screwdriver with the lid in position. Mount all remaining components and, referring to Fig. 3, complete the wiring. Solder the l.e.d. wires quickly to prevent possible heat damage.

Insert both i.c.'s into their holders, observing the orientation. Do this without touching the pins since these are CMOS devices and could be damaged by static electricity which may exist on the body. Adjust preset VR1 to approximately mid-track position.

TESTING

With the circuit panel removed from the case, connect the battery – D1 (TEMP!)

should flash – this is because it is signalling a relatively high temperature. Make a basic test by touching the tip of R2 with something cold – a packet of frozen food, for example. Do not allow water to get on the connecting leads or drip onto the circuit panel or operation will be disturbed.

The l.e.d. should stop flashing. If it continues to flash, rotate VR1 sliding contact until it does stop.

If the circuit behaves correctly, accurate setting of preset VR1 will be required to give operation at 5°C. This is done with the circuit panel in position and adjustment made through the hole in the box. If the l.e.d. fails to flash at all, check that it has been connected with the correct polarity and reverse the connections if necessary.

Attach the circuit panel to the base of the case using a small fixing through the hole drilled for the purpose. Secure the battery using an adhesive fixing pad. Fit the lid, checking for trapped wires and short-circuits – especially between the l.e.d. connections.

Place the box inside the fridge near the centre of the cabinet. For setting-up use a mercury thermometer. The best type will cover a narrow range, zero to 50°C for example, but the more usual –10° to 110° one will do.

Adjust the fridge thermostat over a period to provide a cabinet temperature of between four and five degrees. This cannot be done quickly, you will need to wait for the temperature to stabilize after each adjustment.

The temperature inside the refrigerator varies. A higher temperature is found on the top shelf compared with the base, typically four degrees. It is important to realize this when adjusting the operating temperature since it will affect the positions where various kinds of food are stored.

Adjust preset VR1 so that l.e.d. D1 is just off. Clockwise rotation (as viewed from the edge of the circuit panel) raises the switching temperature. The lid of the case may be left off to speed up the response time between adjustments. Each adjustment must be made quickly so that R2 does not rise in temperature significantly while the door is open. Check that the correct setting has been obtained and make minor adjustments as necessary.

If l.e.d. D1 either remains on or off despite VR1 adjustment, it will be necessary to alter the value of resistor R4. If D1 remains on despite total clockwise rotation of VR1, reduce the value from 2.2M to 1M. If the opposite is the case, that is, if the l.e.d. remains off despite complete anti-clockwise rotation of VR1 sliding contact, increase R4 to 3.3M.

BATTERY CHECK

The battery check facility should now be tested. The easiest way to do this is to use any PP3 battery known to be in poor condition but still serviceable. When this is connected and switch S1 pressed, the green l.e.d., D2, (Battery OK) should fail to light. With a new battery in place it should light up. An alternative method is to use a 6V supply (4 off AA cells, for example) – this will be too low to operate D2. If the l.e.d. fails to light, check its polarity and reverse the connections if necessary.

There were no problems in the prototype unit due to moisture, from the "fridge", condensing on the circuit panel tracks. This would cause erratic behaviour. A light spray of water-repellent silicone grease would cure this. □

MAKE YOUR INTERESTS PAY!

Over the past 100 years more than 9 million students throughout the world have found it worth their while! An ICS home-study course can help you get a better job, make more money and have more fun out of life! ICS has over 90 years experience in home-study courses and is the largest correspondence school in the world. You learn at your own pace, when and where you want under the guidance of expert 'personal' tutors. Find out how we can help YOU. Post or phone today for your **FREE INFORMATION PACK** on the course of your choice. (Tick one box only!)

Electronics	☐	TV, Video & Hi-Fi Servicing	☐
Basic Electronic Engineering (City & Guilds)	☐	Refrigeration & Air Conditioning	☐
Electrical Engineering	☐	Car Mechanics	☐
Electrical Contracting/Installation	☐	Computer Programming	☐
GCSE/GCE/SCE over 40 examination subjects to choose from			

Name _____ Address _____

ICS International Correspondence Schools Dept ECS A0
Telephone 081-643 9568 or 041-221 2926 (24 hours)
312/314 High Street, Sutton, Surrey SM1 1PR

VELLEMAN KITS

Over 100 Project Kits in stock
Send 50p for 1990 Catalogue + Price List
RETAILERS WANTED

Why not be one of our many retailers who carry our top range of high quality kits (Discounts to be arranged)
Send Details and Letterhead to:

HIGH-Q-ELECTRONICS
PO BOX 1481 LONDON NW7 4RF

TEL: **0707 263562**



FAX: **081-209 1231**


SCHOOLS AND COLLEGES WELCOME



TRANSFORMERS FROM JAYTEE

The UK Distributor for Standard Toroidal Transformers

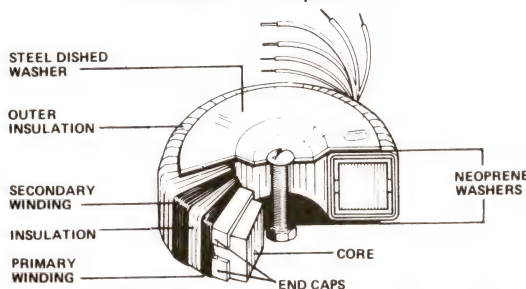- * 106 types available from stock
- * Sizes from 15VA to 625VA
- * Dual 120v primaries allowing 110/120v or 220/240v operation



TYPE	SERIES NO.	SEC VOLTS	RMS CURRENT	TYPE	SERIES NO.	SEC VOLTS	RMS CURRENT
15VA £9.80	03010	6+6	1.25	160VA £17.70	53011	9+9	8.89
	03011	9+9	0.83		53012	12+12	6.66
	03012	12+12	0.63		53013	15+15	5.33
	03013	15+15	0.50		53014	18+18	4.44
	03014	18+18	0.42		53015	22+22	3.63
	03015	22+22	0.34		53016	25+25	3.20
	03016	25+25	0.30		53017	30+30	2.66
30VA £11.20	03017	30+30	0.25		53018	35+35	2.28
	13010	6+6	2.50		53026	40+40	2.00
	13011	9+9	1.66		53028	110	1.45
	13012	12+12	1.25		53029	220	0.72
	13013	15+15	1.00		53030	240	0.66
	13014	18+18	0.83	225VA £19.35	63012	12+12	9.38
	13015	22+22	0.68		63013	15+15	7.50
50VA £12.75	13016	25+25	0.60		63014	18+18	6.25
	13017	30+30	0.50		63015	22+22	5.11
	23010	6+6	4.16		63016	25+25	4.50
	23011	9+9	2.77		63017	30+30	3.75
	23012	12+12	2.08		63018	35+35	3.21
	23013	15+15	1.66		63026	40+40	2.81
	23014	18+18	1.38		63025	45+45	2.50
80VA £14.10	23015	22+22	1.13		63033	50+50	2.25
	23016	25+25	1.00		63028	110	2.04
	23017	30+30	0.83		63029	220	1.02
	23028	110	0.45		63030	240	0.93
	23029	220	0.22	300VA £21.10	73013	15+15	10.0
	23030	240	0.20		73014	18+18	8.33
120VA £15.00	43010	6+6	6.66		73015	22+22	6.82
	43011	9+9	4.44		73016	25+25	6.00
	43012	12+12	3.33		73017	30+30	5.00
	43013	15+15	2.66		73018	35+35	4.28
	43014	18+18	2.22		73026	40+40	3.75
	43015	22+22	1.81		73025	45+45	3.33
	43016	25+25	1.60		73033	50+50	3.00
	43017	30+30	1.33		73028	110	2.72
	43018	35+35	1.21		73029	220	1.36
	43019	40+40	1.09		73030	240	1.25
	43020	45+45	0.98	500VA £27.95	83016	25+25	10.0
	43021	50+50	0.89		83017	30+30	8.33
	43022	55+55	0.81		83018	35+35	7.14
	43023	60+60	0.74		83026	40+40	6.25
	43024	65+65	0.68		83025	45+45	5.55
	43025	70+70	0.62		83033	50+50	5.00
	43026	75+75	0.57		83042	55+55	4.54
	43027	80+80	0.52		83028	110	4.54
	43028	85+85	0.48		83029	220	2.27
	43029	90+90	0.44		83030	240	2.08
	43030	95+95	0.40	625VA £30.65	93017	30+30	10.41
	43031	100+100	0.37		93018	35+35	8.92
	43032	105+105	0.34		93026	40+40	7.81
	43033	110+110	0.31		93025	45+45	6.94
	43034	115+115	0.28		93033	50+50	6.25
	43035	120+120	0.26		93042	55+55	5.68
	43036	125+125	0.24		93028	110	5.68
	43037	130+130	0.22		93029	220	2.84
	43038	135+135	0.20		93030	240	2.60



Prices include VAT and carriage

Quantity prices available on request
Write or phone for free Data Pack

Jaytee Electronic Services

143 Reculver Road, Beltinge, Herne Bay, Kent CT6 6PL
Telephone: (0227) 375254 Fax: 0227 365104

SURVEILLANCE PROFESSIONAL QUALITY KITS EQUIPMENT

Whether your requirement for surveillance equipment is amateur, professional or you are just fascinated by this unique area of electronics **SUMA DESIGNS** has a kit to fit the bill. We have been designing electronic surveillance equipment for over 12 years and you can be sure that all of our kits are very well tried, tested and proven and come complete with full instructions, circuit diagrams, assembly details and all high quality components including fibreglass PCB. Unless otherwise stated all transmitters are tuneable and can be received on an ordinary VHF FM radio.

UTX Ultra-miniature room transmitter. Smallest room transmitter kit in the world! Incredible 10mm x 20mm including mic, 3-12V operation, 500m range.....**£15.95**

MTX Micro-miniature room transmitter. Best selling micro-miniature room transmitter. Just 17mm x 17mm including mic, 3-12V operation, 1000m range.....**£12.95**

STX High-performance room transmitter. High performance transmitter with a buffered output stage for greater stability and range. Measures 22mm x 22mm including mic. 6-12V operation, 1500m range.....**£14.95**

VT500 High-power room transmitter. Powerful 250mW output providing excellent range and performance. Size 20mm x 40mm, 9-12V operation. Range 3000m.....**£15.95**

VXT Voice activated room transmitter. Triggers only when sounds are detected. Very low standby current, variable sensitivity and delay with I.e.d. indicator. Size 20mm x 67mm, 9V operation, 1000m range.....**£18.95**

QTX180 Crystal controlled room transmitter. Narrow band FM transmitter for the ultimate in privacy. Operates on 180MHz and requires the use of a scanner receiver or our QRX180 kit (see catalogue). Size 20mm x 67mm, 9V operation, 1000m range.....**£39.95**

SCRX Subcarrier scrambled room transmitter. Scrambled output from this transmitter cannot be monitored without the SCDM decoder connected to receiver. Size 20mm x 67mm, 9V operation, 1000m range.....**£21.95**

SCDM Subcarrier decoder unit for SCRX. Connects to receiver earphone socket and provides decoded audio output to headphones. Size 32mm x 70mm, 9-12V operation.....**£21.95**

HVX400 Mains powered room transmitter. Connects directly to 240V a.c. supply for long term monitoring. Size 30mm x 35mm, 500m range.....**£18.95**

ATR2 Micro size telephone recording interface. Connects between telephone line (anywhere) and cassette recorder. Switches tape automatically as phone is used. All conversations recorded. Size 16mm x 32mm. Powered from line.....**£12.95**

UTLX Ultra-miniature telephone transmitter. Smallest telephone transmitter kit available. Incredible size of 10mm x 20mm. Connects to line (anywhere) and switches on and off with phone use. All conversations transmitted. Powered from line, 500m range.....**£14.95**

TLX700 Micro-miniature telephone transmitter. Best selling telephone transmitter. Being 20mm x 20mm it is easier to assemble than UTLX. Connects to line (anywhere) and switches on and off with phone use. All conversations transmitted. Powered from line, 1000m range.....**£12.95**

STLX High-performance telephone transmitter. High power telephone transmitter with buffered output stage providing excellent stability and performance. Connects to line (anywhere) and switches automatically with phone use. All conversations transmitted. Powered from line. Size 22mm x 22mm, 1500m range.....**£15.95**

TKX900 Signalling/tracking transmitter. Transmits a continuous stream of audio pulses with variable tone and rate. Ideal for signalling or tracking purposes. High power output gives range up to 3000m. Size 25mm x 63mm, 9V operation.....**£21.95**

CD600 Professional bug detector/locator. Multicolour bargraph readout of signal strength with variable rate bleeper and variable sensitivity used to detect and locate hidden transmitters. Switch to AUDIO CONFIRM mode to distinguish between localised bug transmission and normal legitimate signals such as pagers, cellular, taxis etc. Size 70mm x 100mm, 9V operation.....**£49.95**

★ ★ ★ SPECIAL ★ ★ ★

DLTX/DLRX Radio control switch. Remote control anything around your home or garden, outside lights, alarms, paging system etc. System consists of a small VHF transmitter with digital encoder and receiver unit with decoder and relay output, momentary or alternate. 8-way d.i.l. switches on both boards set your unique security code. TX size 45mm x 45mm, RX size 35mm x 90mm. Both 9V operation. Range up to 200m.....**Complete system (2 kits) £49.95**
Individual transmitter DLTX.....£18.95
Individual receiver DLRX.....£36.95

A build-up service is available on all of our kits if required.
UK customers please send cheques, PO's or registered cash. Please add £1.50 per order for P&P. Goods despatched ASAP allowing for cheque clearance. Overseas customers send sterling bank draft and add £5.00 per order for shipment. Credit card orders welcome on 0827 714476.

OUR LATEST CATALOGUE CONTAINING MANY MORE NEW SURVEILLANCE KITS NOW AVAILABLE. SEND TWO 20p STAMPS OR OVERSEAS SEND TWO IRC's.

SUMA DESIGNS
THE WORKSHOPS
95 MAIN ROAD
BAXTERLEY, Nr ATHERSTONE
WARWICKSHIRE CV9 2LE

**0827
714476**

INTERFACING THE RML NIMBUS

ANDREW CHANNERLEY

Part 2

The Nimbus is replacing the BBC micros in many schools, we take a look at it and its BBC-type parallel card.

THE Nimbus I/O bus interface consists of a multiplexed address and data bus, very much like the 80186 itself, except that the data bus-bandwidth is only 8-bits. The pin allocation is given in Table 1 (shown at the end of the article) and physically the bus is distributed by a 40-way ribbon cable inside the Nimbus casing, with IDC-type headers. Four card slots are available inside the casing, for four peripheral boards connecting to the bus.

We have already discussed the **chip-select unit**, the address allocations of the chip-selects are given below. These chip-selects

are brought out of the I/O bus connector via a 74LS244 buffer, as five, I/O mapped, selects designated BUS CS0, BUS CS1, BUS CS2, BUS CS3 and BUS CS4. The bi-directional data bus comprises AD0-AD7 and is buffered through a 74LS245, it is 8-bit wide and therefore all port addresses are **even**, this is illustrated on Fig. 9. The usual control signals are also available.

The bus signals include an 8MHz clock, as well as an asynchronous **ready** input to insert **wait** states, though it should be pointed out that all I/O cycles have two-wait states automatically inserted. The bus operates at TTL levels, driven by the line driver devices.

The allocation of chip selects is as follows:

Address range	chip select card
600-67Fh	4 Tape controller
580-5FFh	3
500-57Fh	2 I/O research
480-4FFh	1 BBC printer/user port
400-47Fh	0 DBC
0F8-0FFh	reserved
00-F7h	reserved

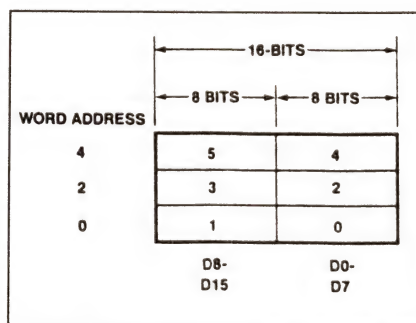
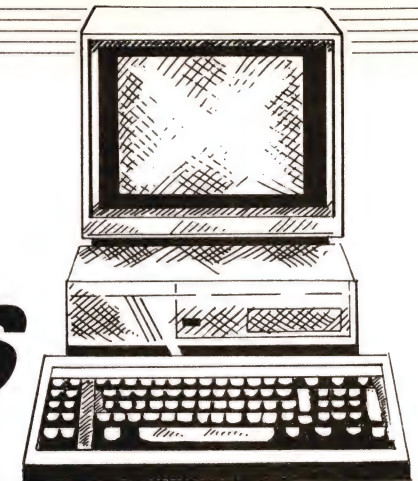


Fig. 9. Relation of word/byte to address space allocation.

Interrupt vectors and priority allocation:

Channel	Request	Vector	Priority
0	BINT0	80h	6.7
1	BINT1	82h	6.6
2	BINT2	0Fh	9(programmable)


The BBC printer/user port vector is 0Fh.

At this point, it's probably time to examine the **BBC printer/user port parallel card**, designed for continuity and ease in interfacing equipment/circuitry previously applied to the BBC. This is important, in particular in schools, where lots of interface equipment has been obtained at quite a high cost.

BBC-Type Printer and User Port

The BBC-type interface card slots into the Nimbus case and clips on to the I/O bus cable previously described (see photos). To the user, the card appears at the back of the Nimbus as two IDC sockets. One is a pin compatible, BBC type, 26-way IDC socket which is the parallel printer port. The other is a pin compatible, BBC-type, 20-way IDC socket which is the user port. The card is obtainable from RML, the manufacturers of the Nimbus PC.

In hardware terms, this card provides an identical BBC printer and user port environment. The original BBC printer and user ports are defined by a customized chip, the 6522 VIA (Versatile Interface Adapter). The Nimbus card has an identical 6522 VIA, a block diagram is shown in Fig. 10. Furthermore, it has a substantial software-support base. There is Richard Russell's version of BBC Basic for the Nimbus called BBCBasic(86), available from RML, with an interactive 80186/8086

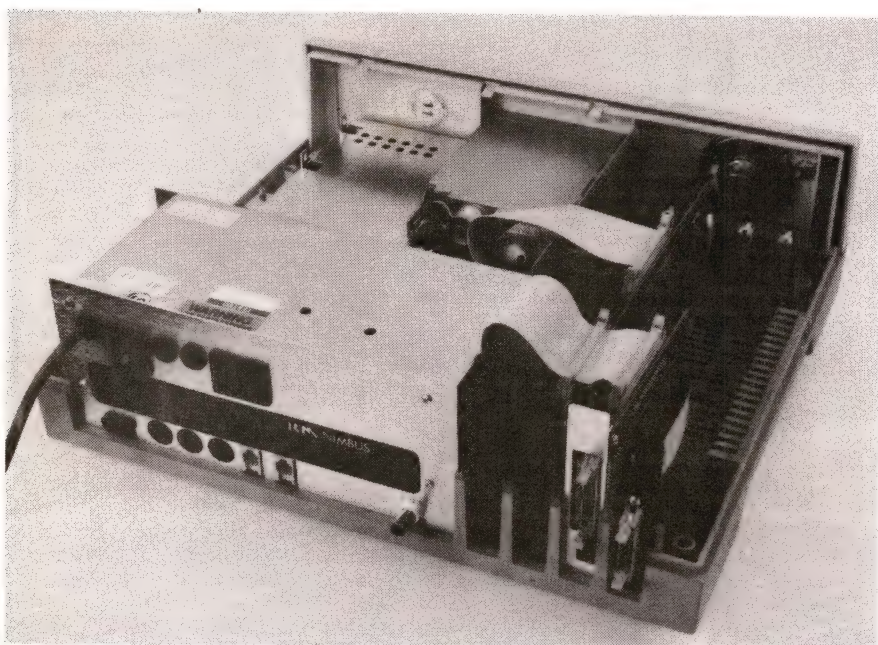

The RML Nimbus PC with the BBC-type interface card inserted.

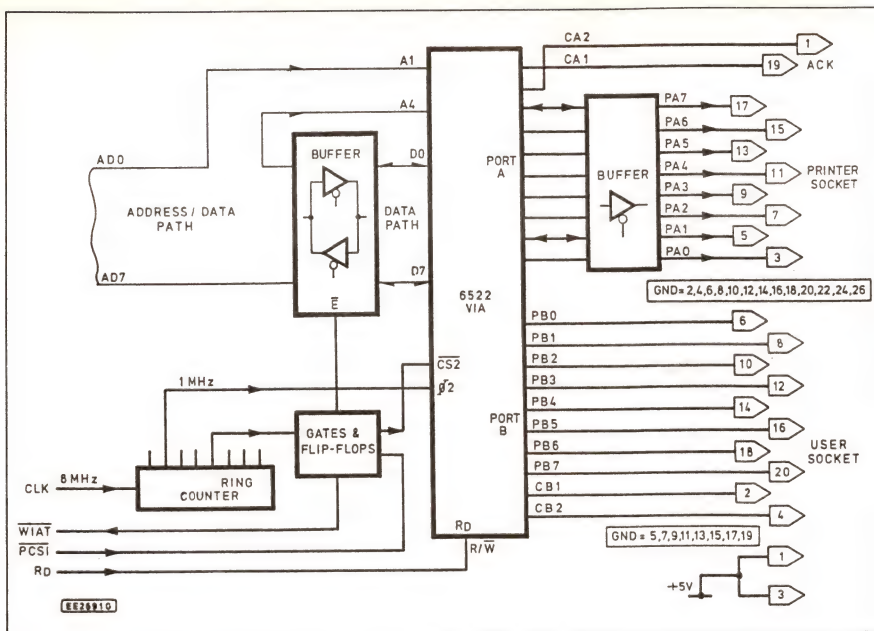


Fig. 10. Block diagram of the BBC Printer/User Port card for the RML Nimbus PC.

PROGRAMMERS MODEL OF 6522 VIA ADDRESS ASSIGNMENT		
BASE ADDRESS = 0480 HEX	HEX OFFSET ADDRESS	
Input/Output Port B (User)	00	↓
Input/Output Port A (Printer)	02	
DDRB (Data Direction B)	04	
DDRA (Data Direction A)	06	
Timer 1/Counter Low Byte	08	
Timer 1/Counter High Byte	0A	
Timer 1 Low Latch	0C	
Timer 1 High Latch	0E	
Timer 2/Counter Low Byte	10	
Timer 2/Counter High Byte	12	
Shift Register (SR)	14	
Auxiliary Control (ACR)	16	
Peripheral Control (PCR)	18	
Interrupt Flag (IFR)	1A	
Interrupt Enable (IER)	1C	
Input/Output Port A (No Handshake)	1E	
← BYTE WIDE →		

Fig. 11. Programmers model of 6522 VIA address assignment.

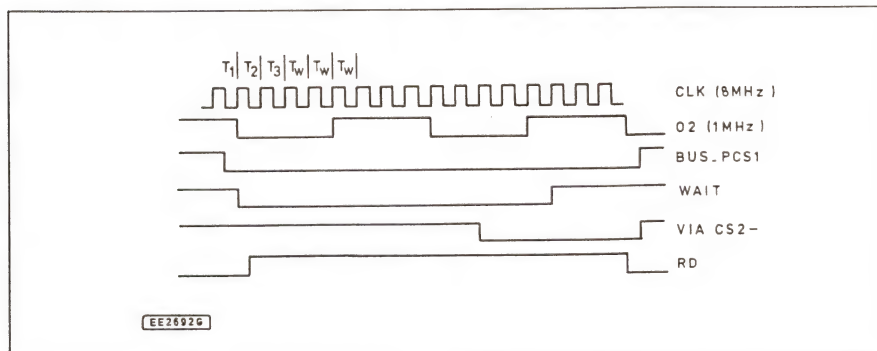


Fig. 12. Timing frame for a VIA read cycle.

T-states to complete, but with extra wait-states, T_w , can be extended to 18 or more T-states. The 1MHz clock simulates the operating frequency of a 1MHz 6502 CPU, data transfer occurs during VIA CS2 active (VIA chip-select active low) and the falling edge of the phi-2 clock. The RD (read) signal is active when high on the I/O bus. Frequency division is provided by a standard ring counter. Once wait is de-asserted, the cycle terminates 3T states later.

Software Support for the BBC Card

RML provides two main versions of Basic with which to access the Parallel I/O card. These versions are:

RML Basic2 : for user familiar with RML's 380Z/480Z

RML BBC Basic(86) : for users familiar with Acorn's BBC Basic

RML BBC Basic(86) is a version of **BBC Basic**. Users may know that the processor driving the Beeb is the 6502 and the Acorn Basic has an interactive assembler which is directly accessible from BBC Basic. The RML version of BBC Basic has an interactive 8086/80186 assembler, since the Nimbus is driven by the 80186 CPU, which too is accessible from Basic, hence the name **BBC Basic(86)**. It's worthwhile, though not essential, creating an AUTOEXEC.BAT file such that when booting the system MS-DOS automatically loads BBC Basic(86), or else just type **BBCload** at the MS-DOS prompt.

In communicating with the parallel printer/user card it's necessary to invoke PROC's and CALL's to assembled routines from within BBC Basic(86). Users have to code the CALL's themselves.

In addition, RML sends a parallel printer/user driver, PN 19140, on disk, called PARALLEL.SYS. This file you should transfer to your main boot/BBCload disk, such that when booting up the system, the default setting on the parallel card will be: **printer port as output** and **user port as input** (as on the Beeb). Otherwise it means writing additional code to set up the 6522 VIA.

RML Basic2

RML also produce their own Basic, RML Basic2, which has some configuration files appended to it and which facilitate access to the BBC parallel printer/user ports, without the necessity of preparing special purpose code. These configuration files are designated **!EXT.LCPP** and occur under **EXTNS.BCF** so that when loading Basic, the command is:

> **BASIC EXTNS.BCF**

Typical commands are:

userport send data byte x, for output to the user port

y:=userport receive byte(), for input to the user port

Examples of uses in both Basic's are given in the listings for the A-to-D applications.

Interfacing an A-to-D

Let's look now at an application which will interface with the BBC parallel card user port. The circuit diagram is shown in Fig. 13. The A-to-D converter used is an 8-bit device which, in addition, has eight separate, software selectable

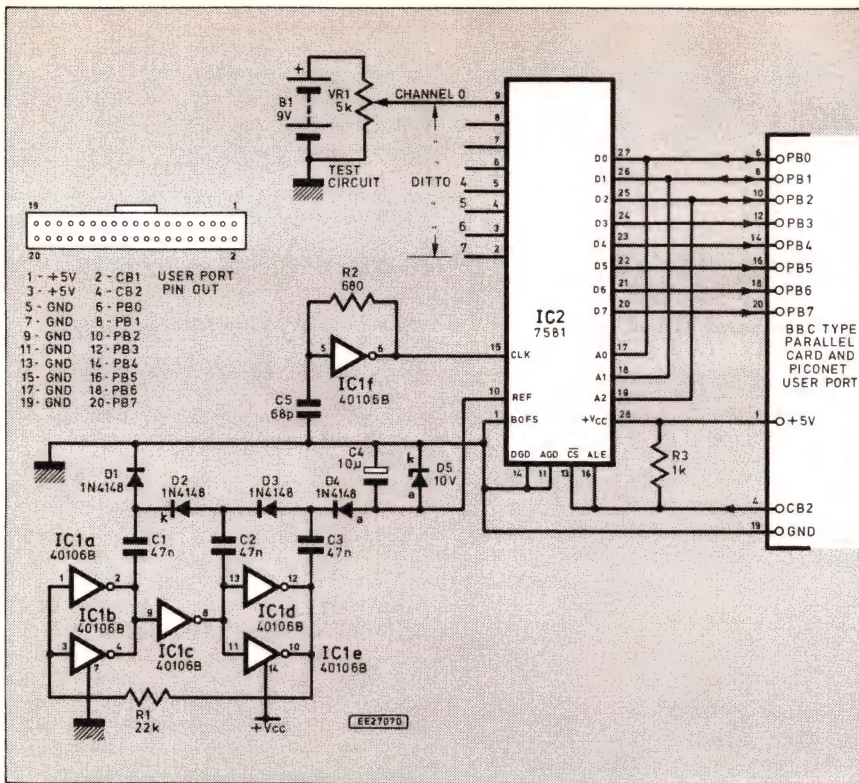


Fig. 13. Analogue to digital converter for the RML Nimbus BBC compatible user ports at the parallel card and the Piconet parallel interface.

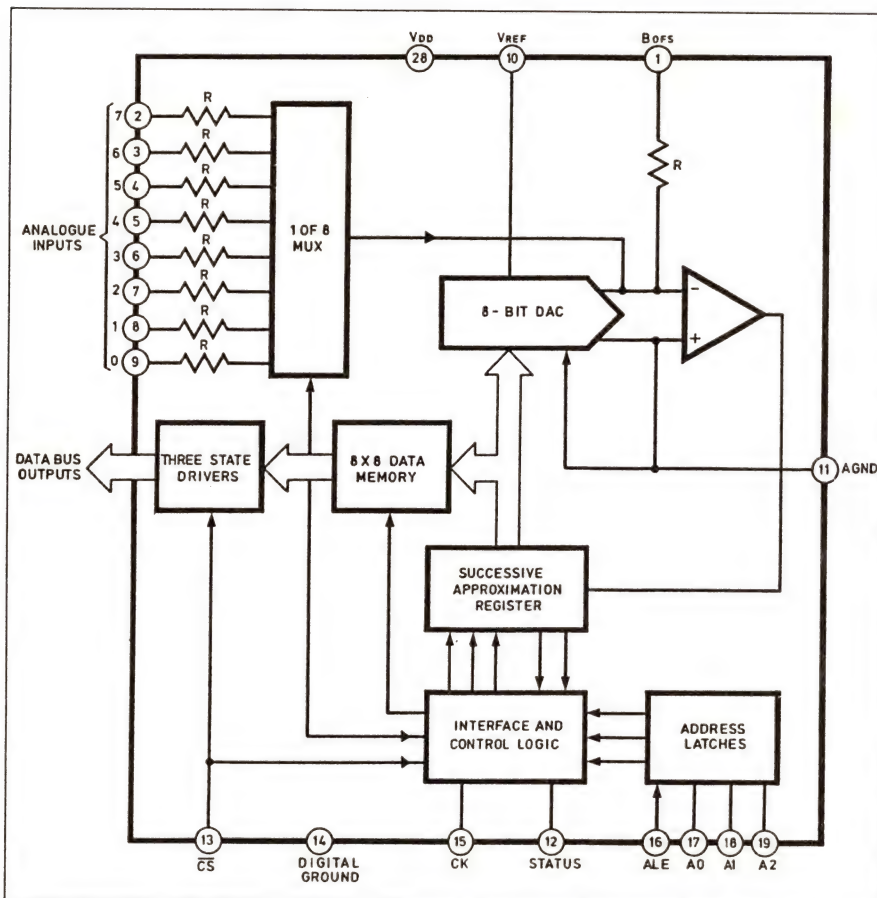


Fig. 14. Block diagram of the 7581 analogue to digital converter.

analogue channels. The voltage range at each analogue channel is between 0V to 10V.

The device digitizes using the technique of successive approximation. Conversion is

continuous and the digitized byte from each channel is loaded into one of 8-memory locations, these locations are in fact addressable and, under programme control, select the required data cell from

which to read the current, digitized byte. Fig. 14, is a block diagram of the device showing the salient features. The 8-bit DAC turns on/off the SAR bits in response to the comparator output. This output (0 or 1) depending on the DAC voltage being greater or less than the analog input voltage.

After eight successive trials, the digitised byte is transferred from the SAR to one of the memory cells and output to the data bus when the tri-state drivers are enabled at pin 13.

A single channel takes 80 clock cycles to convert, therefore for all eight channels taking 640 clock cycles. The address pins A0, A1, A2 select the required memory cell and are connected to data pins PB0, PB1, PB2 of the user port. Pin CB2 provides a latching signal for the addressable 8 byte memory, as well as a disable during channel selection and an enable during data output.

The synchronizing clock input is provided by the 40106B package of hex Schmitts (inverters) one of which provides a 1MHz conversion clock and the other five derive the necessary -10V reference voltage using a diode pump arrangement.

This particular A-to-D converter was also used on the 380Z/480Z, the Oric Atmos, Spectrum and BBC and interfaced to a large number of school science experiments.

Operational Software

The operational software comes in two listings:

(a) the listing of Fig. 15, is in RML BBC Basic(86). This Basic has an in-built 8086/80186 assembler. Communication with the 6522 VIA on the Parallel card is in 8086/80186 code.

(b) the listing of Fig. 16, is in RML Basic2 and uses the procedures provided by the extensions. It is user friendlier since all the VIA registers are accessible from high-level Basic. But... once a machine coder always a machine coder.

Construction

The complete A-to-D converter can be prototyped on a Euroboard, see Fig. 17, and the photograph. The only soldering required for this approach is in connecting the 20-way ribbon cable to 2 x 10-way headers which fit into the breadboard slots as shown in Fig. 17. The other end of the ribbon cable is attached to an IDC 20-way plug. This has a set of shearing pins which cut into the ribbon insulation, when pressed against the pins, and make a connection.

Of the 20-ribbon strands, only 12 are in fact required for actual soldering to the 10-way header. These are given below, with the ribbon number underneath:

GND	PB7	PB6	PB5	PB4	PB3
19	20	18	16	14	12
PB2	PB1	PB0	CB2	CB1	5V
10	8	6	4	2	1

The pin designation on the actual board is shown in Fig. 17, and on the circuit diagram of Fig. 13. The pin out of the IDC socket at the Nimbus BBC card is also given. These form the physical link between the A-to-D converter circuit and the Nimbus BBC user port.

The Euroboard comprises a central channel, on either side of which are 40 rows of five inserts, each row is at right angles to

Fig. 15. RML BBC Basic(86) operational software.

```

10 REM This listing uses the 80186/8086 assembler from
20 REM BBCBasic(86) in a procedure which sets up the User
30 REM port as output to select the analog channel on the
40 REM 7581, 8xchannel, Analog-to-Digital converter.
50 REM The handshake line CB2 is used to latch the channel
60 REM address and to enable/disable the 7581 ADC.
70 REM The remainder of the software plots the bytes.

```

80 PROC ASSEMBLE:REM assemble code

```

90 MOVE 0,0
90 MODE 4
100 V=0
110 REPEAT
120 V=V+1
130 CALL read:REM read data byte to G
140 Y=?G:REM read G
150 DRAW V,Y*4:REM plot it
160 PRINT TAB(35,2):STR$(Y)+ " ":REM also display onscreen
170 FOR T=0 TO 10:NEXT T:REM wait
180 UNTIL V>1200
190 GOTO 90
200 END

```

210 DEFPROC ASSEMBLE

```

220 HIMEM=&4000
230 FOR Z=0 TO 2 STEP 2
240 P%=&4000
250 [OPT Z
260 .G DB 0\reserve data byte
270 .read
280 MOV AL,&FF:LEA DX,&0480[04]:OUT DX,AL\User port output
290 MOV AL,&E0:LEA DX,&0480[18]:OUT DX,AL\CB2 high
300 MOV AL,0:LEA DX,&0480[0]:OUT DX,AL\select channel 0
310 MOV AL,&C0:LEA DX,&0480[18]:OUT DX,AL\CB2 low
320 MOV AL,0:LEA DX,&0480[04]:OUT DX,AL\User port input
330 LEA DX,&0480[0]:IN AL,DX:MOV [G],AL\read byte
340 .end RETF
350 ]
360 NEXT Z
370 ENDPROC

```

Fig. 16. RML Basic2 operational software.

```

10 REM This listing is in RMLBASIC2 with EXTNS.BCF which
20 REM contains !EXT LCPP.EXT. It works just like the
30 REM listing in BBCBasic(86), with CB2 latching the
40 REM channel address and turning the ADC on/off.
45 REM Communication is through the Parallel Card
48 REM User port socket.

```

```

50 SET MODE 80
60 SET ORIGIN 0,0
70 CLS
80 X:=0
90 SET USERPORT_DDR 255:REM User port output
100 SET LCPP_REGISTER 12,224:REM make CB2 high
110 USERPORT_SEND_DATA_BYTE 0:REM select channel 0
120 SET LCPP_REGISTER 12,192:REM make CB2 low
130 SET USERPORT_DDR 0:REM User port input
140 REPEAT
150 X:=X+1:REM dummy time axis
160 Y:=USERPORT_RECEIVE_BYTE ():REM read user port
170 LINE X,Y:X,Y
180 UNTIL X>638
190 GOTO 60

```

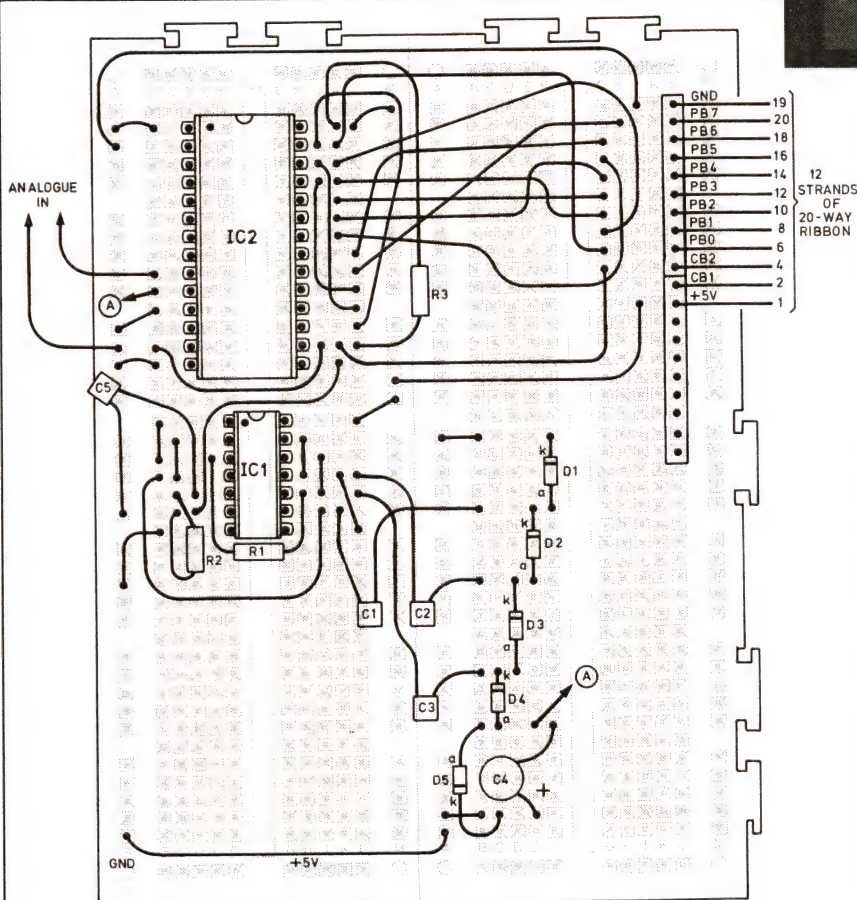
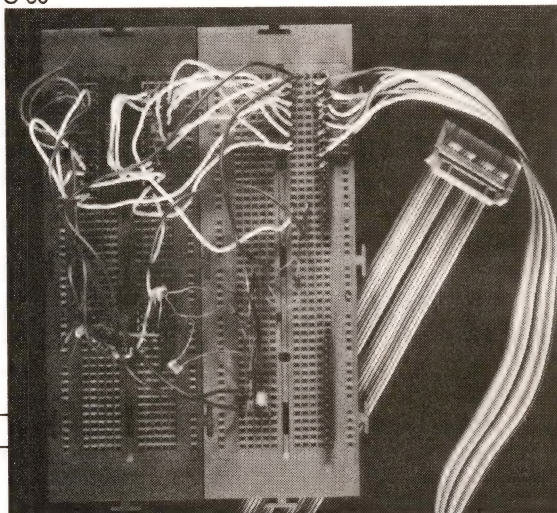


Fig. 17. Construction of the A to D converter.

COMPONENTS

Resistors

R1 22k
R2 680
R3 1k

All ¼W ± 5% carbon

Potentiometer

VR1 5k linear

Capacitors

C1, C2, C3 47nF ceramic (3 off)
C4 10µ tantalum 10V
C5 68p silvered mica

Semiconductors

D1 to D4 1N4148 or 1N4001 diodes (4 off)
D5 10V Zener diode 1.3W
IC1 40106 Hex Schmitt
IC2 7581JN ADC

Miscellaneous

0.1 inch pitch, 10-way p.c.b. header (2 off); 20-way IDC plug; plug in breadboards (2 off); ribbon cable; 9V PP3 battery; connecting wire.

Approx cost
guidance only

£25

plus breadboards

TABLE 1
RML NIMBUS BUS SPECIFICATION

Pin Name	Pin No.	Pin Type	Signal Description
12V	1, 2	O	+ 12V Power distribution connections
5V	3, 4, 5, 6	O	+ 5V Power distribution connections
GND	7, 12, 17, 19, 26, 32, 38	O	System ground. The 0V return for 5V, 12V and signal ground current
I/O GND	39, 40	O	I/O Ground. Noise free ground for peripherals, connected directly to the system star ground point. Must not be used to carry signal or power return currents.
$\overline{\text{RESET}}$	25	O	Reset indicates that the BCU is being reset at power up, or that the reset output of the System GA has been activated under program control. Reset is active low.
$\overline{\text{CLK}}$	18	O	The buffered, inverted '186 clock output 8MHz with 50 per cent duty cycle.
$\overline{\text{DMA REQ}}$	33	I	$\overline{\text{DMA REQ}}$ is driven low by a peripheral board to initiate a DMA transfer.
$\overline{\text{BINT0}}$	34	I	Bus interrupt request lines are driven low to request an interrupt.
$\overline{\text{BINT1}}$	35	I	
$\overline{\text{BINT2}}$	36	I	
AD7	16	B	Address/data bus. This time multiplexed I/O address and data bus is used exclusively for I/O byte wide transfers between mainboard and peripheral boards on the I/O bus. The AD bus is true (active high).
AD6	15	B	
AD5	14	B	
AD4	13	B	
AD3	11	B	
AD2	10	B	
AD1	9	B	
AD0	8	B	
$\overline{\text{ALE}}$	20	O	Address latch enable. Addresses are guaranteed to be valid on the AD bus for the low to high transition of $\overline{\text{ALE}}$. This signal may be used to demultiplex the AD bus.
RD	21	O	Read strobe indicates that the current bus activity is a read cycle. RD is active high.
WR	22	O	Write strobe indicates that the current bus activity is a write cycle. WR is active high.
I/O REQ	23	O	I/O request strobe indicates that the current bus cycle is an access of I/O space. I/O REQ is active high
$\overline{\text{WAIT}}$	24	I	$\overline{\text{WAIT}}$ informs the '186 that the device accessed by the current I/O bus cycle is not ready to complete the cycle. Wait states are added between T3 and T4, and the cycle extended. The cycle terminates 3 T states following the first positive transition of $\overline{\text{CLK}}$ after $\overline{\text{WAIT}}$ is de-asserted. Two wait states are automatically inserted in all I/O bus cycles, so $\overline{\text{WAIT}}$ must be inactive before the end of T3 if further wait states are not to be inserted. $\overline{\text{WAIT}}$ is active low.
BUF DIR	37	O	Buffer Direction indicates the driving status of the AD bus buffers on the BCU mainboard. When high, the AD bus is being driven by the mainboard drivers. When low, the mainboard drivers are in a high impedance state and peripheral boards have control of the AD bus.
$\overline{\text{CS4}}$	31	O	Buffered peripheral chip select outputs of '186. Chip select is made active when the current I/O bus cycle accesses an I/O address in a pre-defined range. Each chip select is decoded for a block of 128 I/O addresses. Chip selects are active low.
$\overline{\text{CS3}}$	30	O	
$\overline{\text{CS2}}$	29	O	
$\overline{\text{CS1}}$	28	O	
$\overline{\text{CS0}}$	27	O	

the length of the board. Each insert in a row of five is connected with the other four, but each row is not connected to any other row on the board. In addition, there are two columns of inserts which run the length of the board, close to the board edges. Each insert along such a column is connected with the other inserts, but each column is not connected with the other, nor with any rows. These columns usually form the power and ground rails.

Clip two such boards together as shown in the diagram. The two chips forming the A-to-D converter are inserted across the central channel of the prototype board, see the wiring diagram of Fig. 17. Note that the main A-to-D chip, the 7581LN, is inserted at the top end, the same as the ribbon cable and the 40106B hex-Schmitt's further down. Pin 1, of the 7581LN, is at the top left and pin 28 is at the top right. The data pins from the chip are then facing the corresponding pins of the 10-way headers.


Initially, choose two of the column inserts to act as supply rails and using a piece of insulated wire, bared at both ends, connect the appropriate pins together as shown on the circuit diagram. Some examples are given on the wiring diagram. Be methodical in your wiring, tick-off each connection on the circuit diagram which then becomes a record of connections in place. The circuit may look like a spaghetti junction, but that does not matter. The advantages of this method over immediate soldering is that mistakes can be easily rectified.

Testing

Once all connections are in place, key-in the software, either in BBC Basic(86) or RML Basic2 and connect the 20-way IDC plug to the user port. Using a 9V PP3 or PP9 and a 5k potentiometer, set up the test circuit as shown on the circuit diagram, using channel 0 at pin 9 of the 7581LN.


Run the software and twiddle the potentiometer, if all works well a changing plot should appear on the screen as you turn. If not, then depending on the error, check either software or hardware.

A software error is relatively straightforward to determine, usually the dummy time base fails to appear. A hardware error will mean making sure that your connections are in place, but that is not too much of a problem since all it entails is changing a wire link, or adding one if left-out, but with the board unplugged. Debugging sessions should not take more than a few minutes. In the last analysis you can always pull the wires out and start again!! □

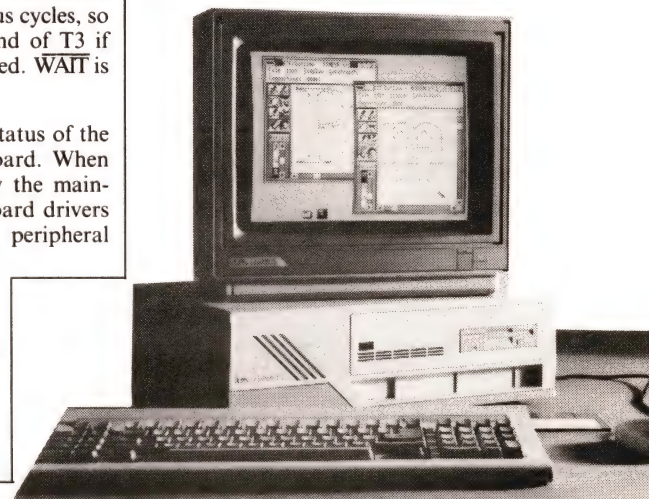

EASY-PC, SCHEMATIC and PCB CAD


NEW VERSION!
NOW DRAWS EVEN FASTER!

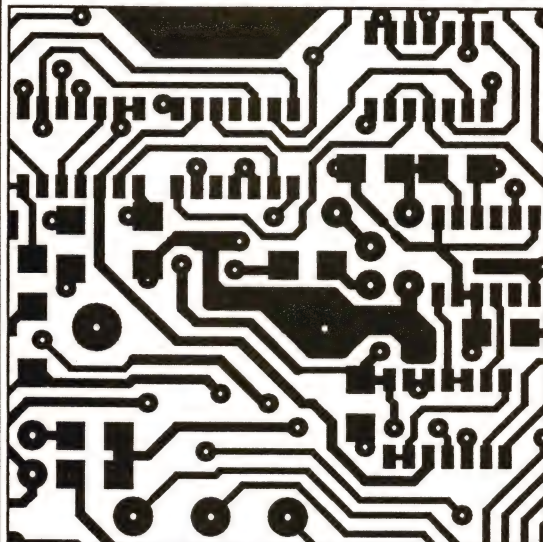

- Runs on:- PC/XT/AT/386 CGA EGA VGA.
- Design:- Single-sided, Double sided and Multilayer boards.
- Provides Surface Mount support.
- Standard output includes Dot Matrix printer, Pen Plotter, Photo-plotter and N.C. Drill.

**Still Only
£98.00!**

**BRITISH
DESIGN
AWARD
1989**

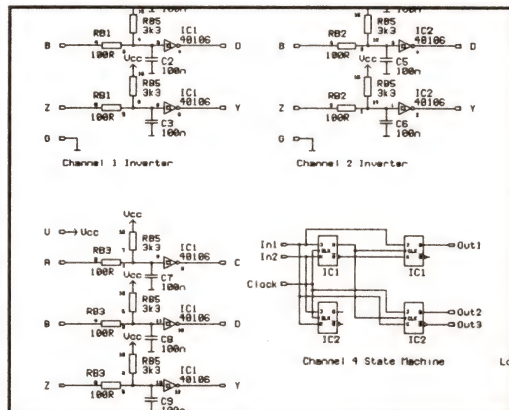

Fast Professional Quality Output at an Affordable Price

Write, 'Phone or Fax for full details:-

Number One Systems Ltd. 1

The CAD Specialists

REF: EVD, HARDING WAY, SOMERSHAM ROAD, ST. IVES, HUNTINGDON, CAMBS, PE17 4WR, ENGLAND.

Telephone: 0480 61778 (6 lines) Fax: 0480 494042

ACCESS, AMEX, MASTERCARD, VISA Welcome.

Remember
The Cricklewood
Service is Fast
and Efficient

**CRICKLEWOOD
ELECTRONICS**

**BIGGER
AND BETTER**

**1990 COMPONENTS
CATALOGUE**

- ONE OF THE LARGEST RANGES OF COMPONENTS IN THE UK
- FAST AND EFFICIENT SAME DAY PERSONAL SERVICE
- VERY COMPETITIVE PRICES; QUANTITY DISCOUNTS AVAILABLE
- DISCOUNT VOUCHERS INCLUDED
- NO MINIMUM ORDER

JUST LIKE A NEW CAR! YOU CAN ONLY JUDGE THE 1990 CATALOGUE BY LOOKING UNDER THE COVER. WITH OVER 13,000 STOCK LINES, CRICKLEWOOD ARE ABLE TO SUPPLY MOST OF THE COMPONENTS NEEDED FOR E.E. PROJECTS.

PHONE US FOR YOUR SPECIAL NEEDS.

FILL IN THE COUPON AND POST IT WITH YOUR CHEQUE, PO ETC FOR £1.50 TO RECEIVE YOUR 1990 CRICKLEWOOD ELECTRONICS CATALOGUE AND VOUCHERS WHICH YOU CAN USE AGAINST YOUR NEXT PURCHASE

Cricklewood Electronics Ltd
40 CRICKLEWOOD BROADWAY, LONDON, NW2 3ET
Tel: 081-450 0995/452 0161
Fax: 081-208 1441 Telex: 914977



TELEPHONE ORDERS OUR SPECIALITY

CRICKLEWOOD ELECTRONICS 1990 COMPONENTS CATALOGUE

PLEASE SEND COPIES OF THE 1990
CRICKLEWOOD ELECTRONICS CATALOGUE AT
£1.50 TO:

NAME

ADDRESS

.....

.....

.....

Remittance enclosed £..... **E**

CAR HEATER THERMOSTAT

T. R. de VAUX-BALBIRNIE

Luxury control for in-car comfort



ON A COLD morning, we want to get the car heater working as quickly as possible. Trying the booster fan results in icy blasts until the water in the cooling system is hot enough. Once the heater is working, the car interior soon becomes too hot and a juggling act with the heater controls is needed to keep the temperature steady and comfortable.

The present circuit puts the heater under thermostatic control. This it does by preventing the booster fan from operating until the water is hot. It then switches on until the interior reaches the required temperature and cycles as necessary to maintain this.

The circuit is housed in a plastic box mounted on the dashboard with air temperature control, i.e.d. indicators and a terminal block to which external connections are made. An on-off switch and auto/manual switch are also provided (see photograph).

The i.e.d.'s show the status of the system thus, when the ignition is switched on, a green one lights and goes off when the radiator water is hot and a red one operates when the car interior has reached the required temperature. Two sensors are used — one is attached to the engine block to monitor water temperature while an air sensor is housed in a small plastic box situated in the rear of the car.

CIRCUIT DESCRIPTION

The circuit diagram for the Car Heater Thermostat is shown in Fig. 1. The design centres around IC1, a dual operational amplifier integrated circuit. One section of this, IC1a, monitors the cooling system water temperature while IC1b is responsible for the air temperature inside the car.

Thermistors, R1 and R2 sense "air" and "water" temperatures respectively. These are negative temperature coefficient devices, on a rise of temperature, their resistance falls. Costs have been reduced here by using miniature rod thermistors instead of the more expensive bead type.

Consider thermistor R2 which forms a potential divider with resistor R4 and preset VR2. As the water temperature rises, its resistance falls resulting in a decreasing voltage being applied to the non-inverting input (pin 2) of IC1a. The inverting input (pin 1) meanwhile receives a fixed voltage of 4V approximately by the potential divider action of resistors R7 and R8 in conjunction with Zener diode, D4 and its series resistor, R11.

With the water temperature low, therefore, the voltage at the non-inverting input exceeds that at the inverting one and the op-amp is on with pin 12 high (positive supply voltage). This operates the green

light-emitting diode D2 (WATER COOL), through resistors R12 and R13.

When the water reaches some higher temperature dependent on the adjustment of preset VR2, (ADJ. WATER TEMP) the voltage at the non-inverting input will fall below that at the inverting one and the op-amp will switch off with pin 12 going low (negative supply voltage). Light-emitting diode D2 then goes off.


A similar situation occurs with R1 and IC1b but operates in the opposite sense. Note that R1 forms a potential divider with resistor R3 and control VR1. Thus, with air cool, R1 has a high resistance and hence a high voltage across it.

This voltage is applied to IC1b inverting input (pin 7). The non-inverting input (pin 6) voltage is set to 4V approximately by the potential divider action of R5 and R6 together with Zener diode, D4.

With low air temperature, therefore, the non-inverting input voltage exceeds the inverting one and IC1b is off, with pin 10 low. As the air temperature rises, the voltage at IC1b pin 7 falls and at some point determined by the setting of VR1 (ADJ. AIR TEMP), becomes less than that at the non-inverting one. IC1b then switches on with pin 10 high. Red light-emitting diode, D3, (AIR HOT) then comes on operating through R12 and R13.

In conditions of low water temperature or high air temperature the corresponding op-amp is therefore on. Current is then directed from either, or both, op-amp outputs through light-emitting diode, D2 or

Fig. 1. Complete circuit diagram for the Car Heater Thermostat.

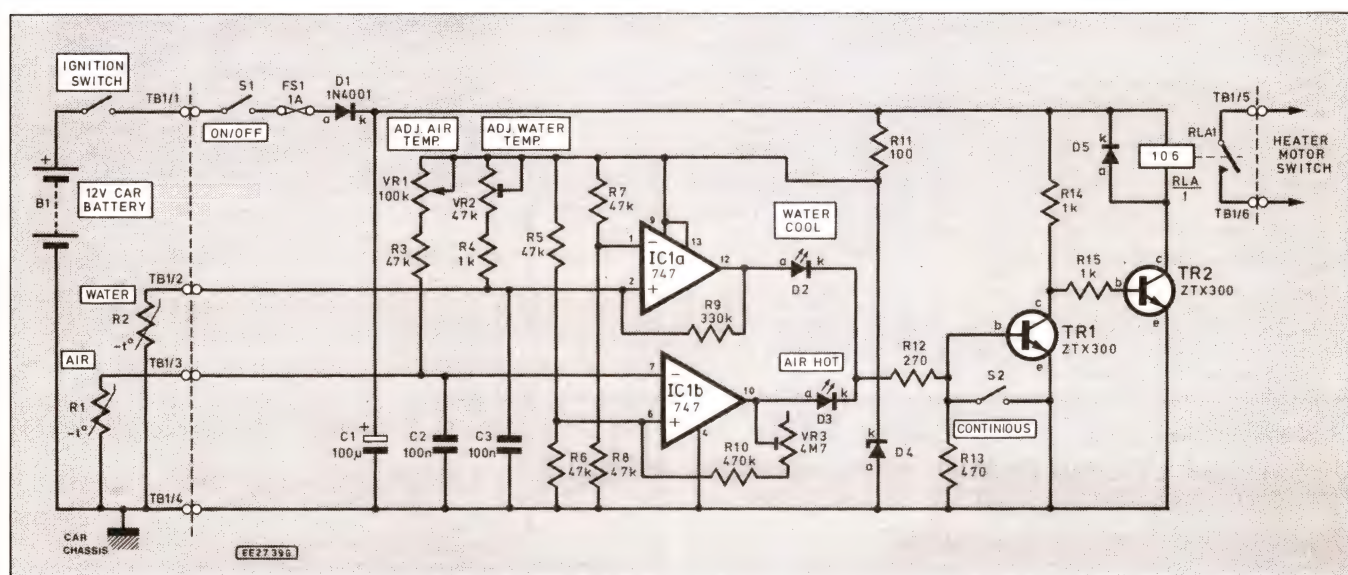

D3 as appropriate and resistor R12, to the base of transistor TR1 which, providing switch S2 is off, switches on with its collector low.

This low state is applied to TR2 base via R15 which therefore remains off. The relay coil RLA/1 thus receives no current and the normally-open contacts, RLA1, remain open. No current therefore reaches the heater motor.

In conditions of both hot water and cool air, both the op-amp outputs will be off so no current reaches transistor TR1 base and the collector remains high. This turns on TR2 and operates RLA/1 coil. The normally-open contacts therefore close and operate the heater fan motor.

Capacitors C2 and C3 allow any a.c. pickup arriving at the op-amp inputs through the thermistor connecting wires to be bypassed, this could otherwise cause faulty operation.

FEEDBACK

Resistor R10 and preset VR3 apply a small amount of positive feedback from IC1b output (pin 10) to the non-inverting

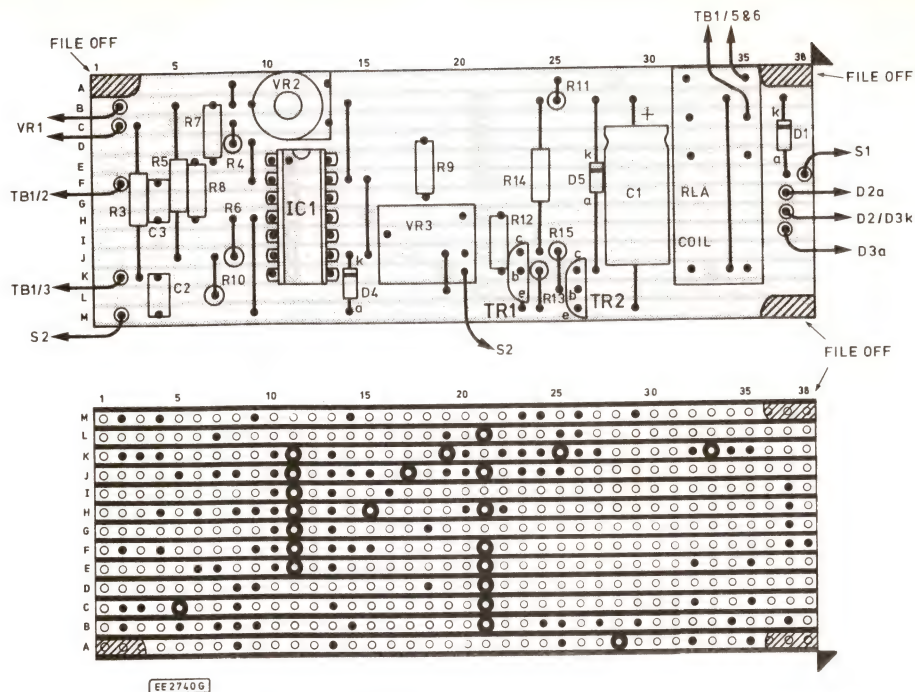


Fig. 2. Stripboard component layout and details of breaks required in the underside copper tracks. Note the wire links under VR3 and the relay.

input (pin 6). This has the effect of introducing a little backlash into the system making the "on" temperature slightly higher than the "off" one.

This makes for "clean" operation and avoids rapid on-off switching (relay chatter) which could occur close to the operating temperature. Preset VR3 allows some adjustment here and will be set for best results at the end of construction. In the water temperature section, positive feedback is similarly applied to IC1a pin 2 through resistor R9 and this is not adjustable since the operating temperature difference is not thought to be particularly critical.

Diode D1, in conjunction with capacitor C1, produces a smooth supply from the car charging circuit. Zener diode, D4, in combination with R11, stabilises the supply and this helps in providing precise operating temperatures. Diode D5 bypasses the high-voltage "spike" which appears when the relay switches off, this could otherwise damage semiconductor components.

Switch S2 (CONTINUOUS), turns off transistor TR1 whatever the states of the op-amp outputs. This it does by connecting the base to the negative line. This has the effect of switching on TR2 hence RLA/1 and operating the heater motor continuously. S1 is the on-off switch and fuse, FS1, provides protection in the event of overload or short-circuit.

CONSTRUCTION

The circuit panel for the Car Heater Thermostat is made from 0.1in. matrix stripboard, size 13 strips x 38 holes. The component layout and details of breaks required in the underside copper tracks are shown in Fig. 2.

Begin construction by cutting the board slightly too large then filing it to fit the slots of the plastic box securely. File off the small sections at the three corners as indicated.

Follow with all track breaks and inter-strip links as indicated. Check particularly that the link beneath RLA/1 position has been made.



COMPONENTS

Resistors

- R1, R2 VA1067S rod thermistors (2 off)
R3, R5, R6
R7, R8 47k (5 off)
R4, R14,
R15 1k (3 off)
R9 330k
R10 470k
R11 100
R12 270
R13 470
All 0.6W metal film.

See
SHOP
TALK
Page

Potentiometers

- VR1 100k rotary carbon, lin.
VR2 47k sub-min. preset, horiz.
VR3 4M7 sub-min. preset, horiz.

Capacitors

- C1 100μ axial elec. 16V
C2, C3 100n polyester layer (2 off)

Semiconductors

- D1, D5 1N4001 1A 50V rec. diode (2 off)
D2 5mm green l.e.d.
D3 5mm red l.e.d.
D4 BZY88C 7V5 Zener
TR1, TR2 ZTX300 npn silicon
IC1 747 dual op.amp


Miscellaneous

- RLA 12V 106ohm coil min. relay, with 16A changeover or make contacts
S1 Min. s.p.s.t. rocker switch
S2 Min. s.p.s.t. rocker switch
FS1 1A 20mm fuse, with chassis fuseholder

Stripboard 0.1in matrix, size 13 strips x 38 holes; plastic case, size 100mm x 76mm x 41mm (MB2); small plastic box for air sensor thermistor; 14-pin d.i.l. socket; 5A 8-way screw terminal block (TB1 6-way, TB2 2-way); thin sheet copper or aluminium for water temp. sensor, size 25mm x 50mm approx; light-duty twin stranded wire; 5A auto-type wire; auto-type connectors (Scotchlok); solder etc.

Approx cost
guidance only

£19

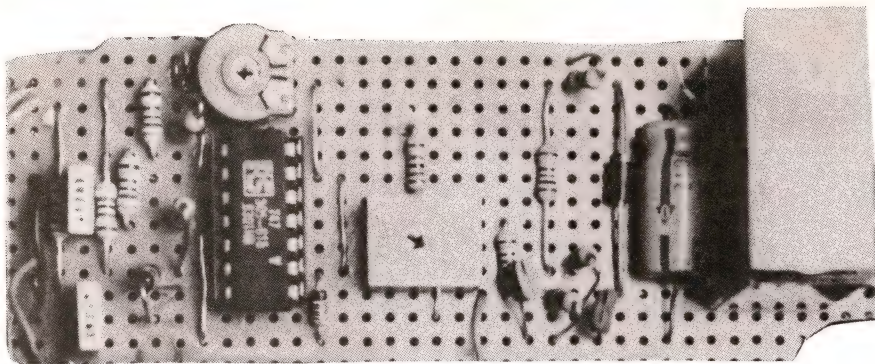

Layout of components on the completed circuit board.

Solder the on-board components into position paying particular attention to the polarities of all diodes and of capacitor C1. Make a careful check for errors, especially for adjacent copper strips which may have become accidentally "bridged" with solder.


Solder 15cm pieces of auto-type wire of **5A rating minimum** direct to the normally-open contacts of RLA/1 – **do NOT make these connections via the copper strips**. Solder 15cm pieces of light-duty stranded connecting wire to copper strips B, C, F, K and M along the left-hand side of the circuit panel and to F, G, H and I along the right-hand side. Adjust the sliding contacts of VR2 and VR3 to approximately mid-track position.

BASE

Prepare the box to receive the circuit panel by drilling holes in the lid for VR1 (SET TEMP), S1 (ON-OFF), S2 (CONTINUOUS), i.e.d. indicators D2 and D3 also for fuse, FS1. Drill holes in the side of the box for the 6-way screw terminal block TB1 mounting and secure all remaining components. Drill two 5mm holes nearby for the wires passing through from the circuit panel.

Refer to Fig. 3 and complete all internal wiring. "Rainbow" ribbon cable was used for some of the wiring in the prototype unit. This keeps the wires neat and the colours help to avoid mistakes.

Fig. 3. Wiring from the circuit board to off-board components.

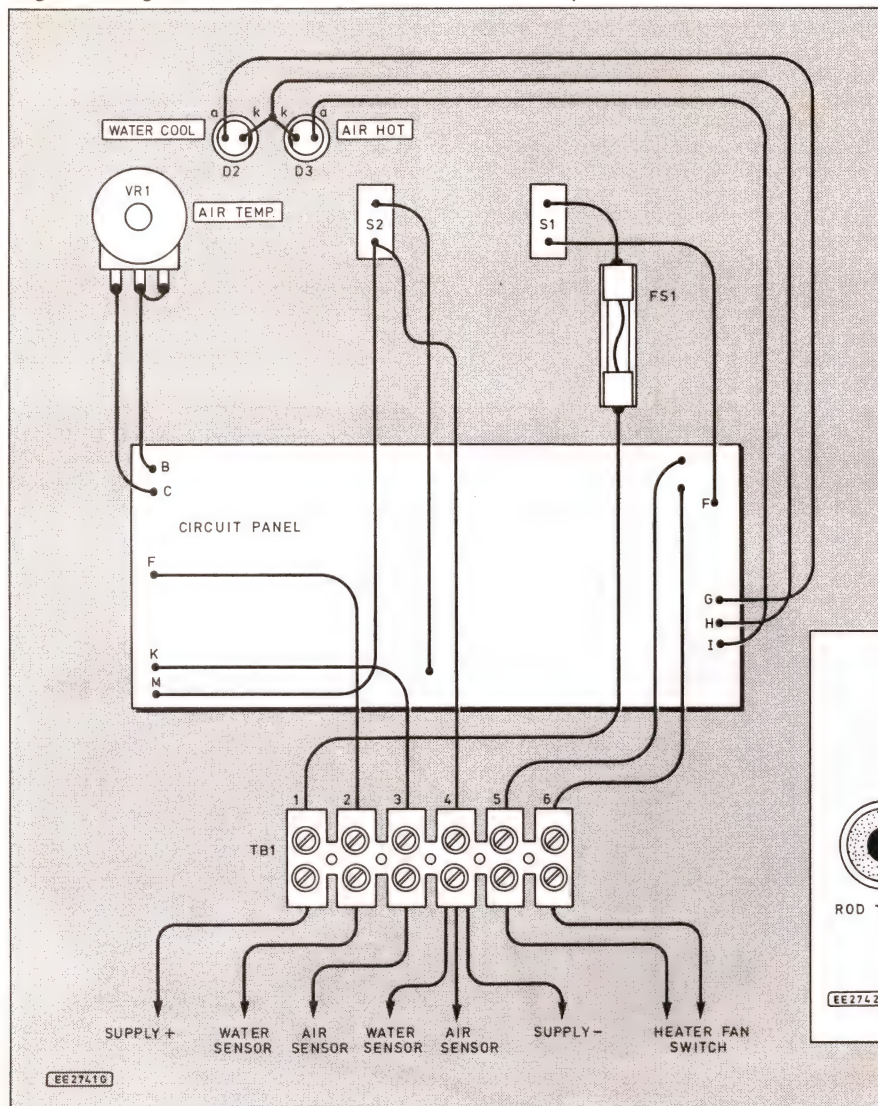

Connections to D2 and D3 should be soldered quickly since i.e.d.'s are easily damaged by excessive heat. Note also that they are polarized, the shorter wires are the cathode.

With the circuit panel in position route the wires leading from relay RLA/1 normally open contacts underneath and through the section filed off for this purpose. Slowly move the lid into position and check carefully that no components, especially FS1, cause short circuits at the copper tracks or elsewhere.

TEMPERATURE SENSORS

Referring to Fig. 4, make the water temperature sensor. The prototype used a piece of thin copper size 25mm x 50mm approximately. Aluminium would probably work just as well.

Cut this to size and bend it around a 5mm twist drill to provide a cavity for the rod thermistor. Sleeve the wire ends of the thermistor and secure it in position using quick-setting epoxy resin adhesive. Make sure that device is centrally-placed in the cavity and insulated from the metalwork with adhesive.

Measure a piece of light-duty twin stranded wire long enough to reach the sensor from the main unit position. Attach this wire to the sensor as shown.

Carefully clean and roughen an area of the vehicle engine block which becomes hot in operation and attach the thermistor sensor using epoxy-resin adhesive. The site must be clear of all moving parts and shielded from draughts as will occur when the car is moving.

Route the connecting wire to the main unit and connect it to TB1/2 and TB1/4 (polarity unimportant). Where the wire passes through a hole in metal, a rubber grommet must be used.

AIR SENSOR

Next make up the air sensor unit as outlined in Fig. 5. Attach the 2-way screw terminal block TB2 using a single fixing. Sleeve the wire ends of the thermistor and attach them to the terminal block as shown (see photograph).

Drill a matrix of holes in the lid so that air can circulate freely and allow the thermistor to respond quickly to changes in temperature. Drill a small hole in the box for the connecting wires to pass through.

Site the air sensor in some part of the car out of the main heater airflow. Somewhere in the rear of the car is probably best, perhaps on the parcel shelf.

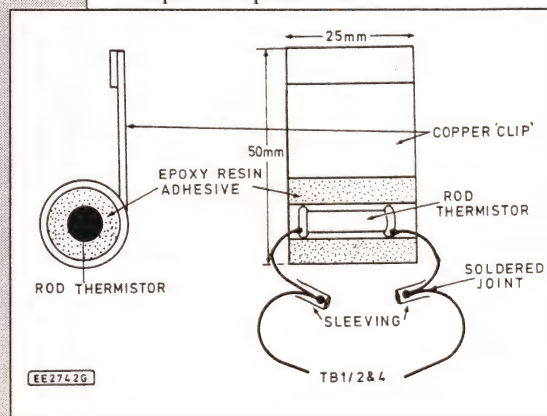


Fig. 4. Suggested method for making up the temperature sensor using copper or aluminium strips.

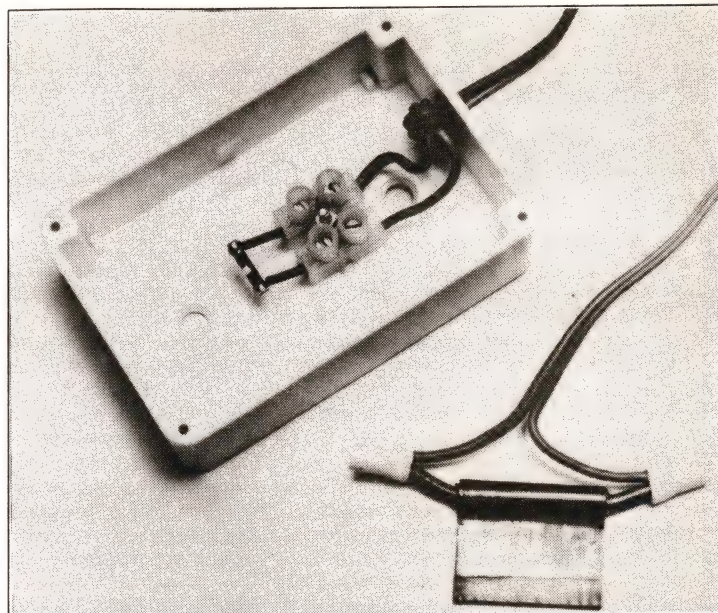
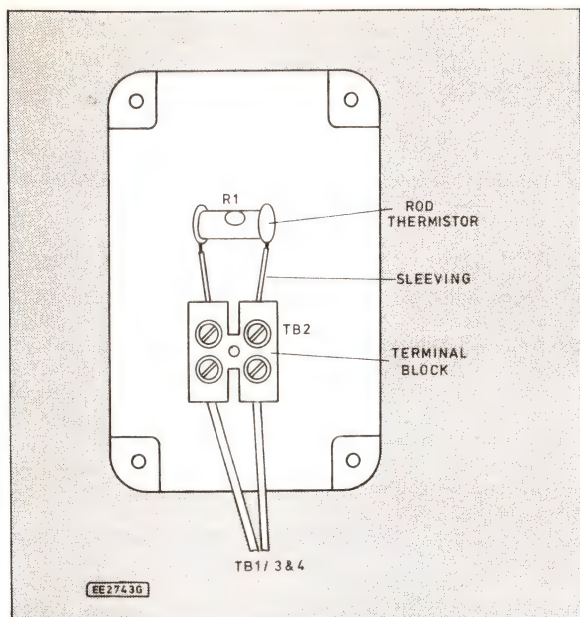


Fig. 5. Method of mounting the "air sensor" thermistor in a small case. A matrix of holes should be drilled in the case lid so that air can circulate freely. The photograph shows the two completed sensors illustrating the use of insulated sleeving covering the leads from the thermistors.

Using light-duty twin wire, connect it to TB1/3 and TB1/4 (polarity unimportant). Fix a strain relief clip or grommet inside the sensor box to provide strain relief. Secure the "air" sensor unit in position using an adhesive fixing pad.

ADJUSTMENT

Auto-type wire of 5A minimum rating **MUST** be used for the remaining TB1 connections. Connect TB1/5 and TB1/6 to the heater motor switch (polarity unimportant) *leaving existing connections intact*. "Scotchlok" connectors are best for this job, these can make connections to existing

wires without actually breaking them. In any case, proper connectors **MUST** be used – not taped joints.

It is probably better to use the low speed (less noisy) position if the heater has a twin speed motor. However, a final decision on this as well as the optimum positions of the other controls can be made later.

Connect TB1/1 to a fuse which is live only when the vehicle ignition is switched on and TB1/4 to a nearby "earth" point (car chassis). Note that TB1/4 now carries three external wires.

It now remains to adjust VR1, VR2 and VR3 for correct operation. When the lid of


the unit is removed for adjustment to VR2 and VR3, the ignition **MUST** be switched OFF and only switched ON when the screwdriver has been removed.

Run the car until the engine is warm enough for the heater to operate and adjust VR2 (WATER TEMP) until the green l.e.d. just goes off. With VR2 adjusted fully clockwise the operating temperature will be 40°C and when fully anti-clockwise, 100°C approximately.

Switch S2 to manual so that the heater fan is heard to operate. Run the car until the air has reached a comfortable temperature and adjust VR1 until the red l.e.d. just goes off. Switch S2 to automatic, the fan motor should continue to operate. Note that it is normal for the l.e.d.s to dim slightly when they are both on, this is a consequence of them both sharing the same current-limiting resistors, R12 and R13.


The thermostat should now operate correctly and it only remains to mount the unit securely on the dashboard. Over a trial period, preset VR3 may be adjusted to increase or reduce the backlash in the air temperature control, anti-clockwise rotation will increase the separation of the on and off temperatures. When fully clockwise this will be approximately 1°C. A scale may be made for VR1 control calibrated in °C but this was not thought worthwhile in the prototype unit. □

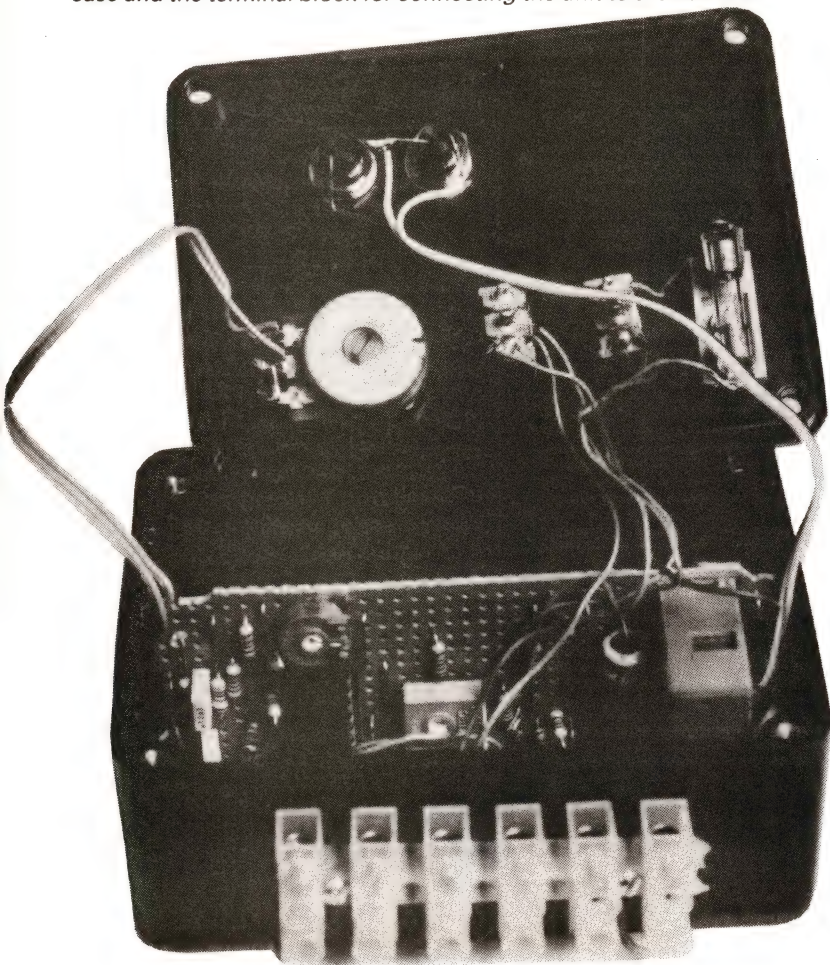The completed unit, with lid removed, showing the circuit board slotted into the case and the terminal block for connecting the unit to the vehicle.



ROBOT ROUNDUP

Nigel Clark

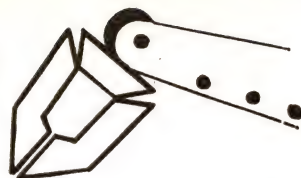

THIS year's annual round-up of what is available in the educational robot market shows a number of changes on this time last year. Every effort is made to ensure that the information is accurate but the prices (quoted ex-VAT) are approximate and most companies offer discounts for education so it is best to check with suppliers for exact prices.

ARMS

Alpha II (UMI) 5-axis plus variety of grippers, stepper motor drive with steel cable transmission, lift 1.36kg, reach 467mm. Control by on-board processor using teach pendant or computer through RS232 port. £10,800

Armndroid HS 1B (Hasfield Systems) 5-axis gripper, bi-polar stepper motor drive with steel-reinforced belt transmission. Lift 1kg, reach 480mm. Control by BBCs, Commodores, IBM and Nimbus. £1,500

Atlas II (LJ Technical Systems) 5-axis plus gripper, stepper driven with toothed belts. Lift 1kg. On-board micro and teach pendant for stand-alone systems. Wide range of operating software. Controllable from BBC and IBM-compatible machines. Work cell available. Arm costs £3,000, IBM Interface £350.

Beasty Plus (Commotion) 3-axis plus gripper, servo-driven, lift 75gms. Supplied in kit with instructions on how to build four different configurations and comprehensive user guide. Kit costs £120, Interface £35 extra.

Cyber 310 (Computer Voice) 5-axis plus gripper, stepper driven with belt and cable transmission. Lift 250gms. Software for all usual micros and has work cell. Robot £700.

EMU (LJ Technical Systems) 4-axis plus gripper, servo-driven with direct mechanical linkages, lift 100gms, software for BBC and LJ's Emma. £350, work cell extra.

Gamma (Hasfield Systems) 5-axis plus gripper, stepper motor drive with toothed belt transmission. Lift 1kg, reach 560mm. Pneumatic gripper optional. £10,000.

HRA 934 (Feedback Instruments) 5-axis plus gripper, hydraulically-powered (oil). Lift 2.5kgs. On-board processor and can be controlled by BBC, Apple, C64. Made only to order. Price on quotation in region of £3,300.

MA 2000 (TQ Intl) 6-axis plus gripper, servo-driven with toothed belt transmission, pneumatic gripper. Lift 1kg. Software for BBC, IBM and Open University's Hektor, was developed for Open University courses.

Gripper is fitted to take pneumatic tools and wired for sensors. Can be linked with MA 3000. Sells at £5,500 for export including basic software, discounts available for UK.

MA 3000 (TecQuipment) 5-axis arm plus gripper. Larger but simpler version of MA 2000. Can be linked with MA 2000 as part of system. £11,400.

Mentor (Cybernetic Applications) 5-axis plus gripper. Servo-driven can lift 1kg. Can be controlled by small-scale model simulator. Software for BBC, IBM and Apple. Can be networked with up to three other Cybernetic machines and work cell. £1,030.

Naiad (Cybernetic Applications) 5-axis plus gripper, lift 500gms, powered by water hydraulics. All axes driven by different kinds of hydraulic piston, all cylinders made of see-through plastic. Gripper can be powered by hydraulic system or pneumatic piston for which compressed air supply provided at extra cost.

As with Mentor it can be controlled by simulator and networked with up to three other Cybernetic machines and work cell. Software for BBC, IBM and Apple. £1,800.

Neptune I (Cybernetic Applications) 5-axis arm plus gripper. Electro-hydraulically powered (water). Lift 2.5kgs. Software for BBC, IBM and Apple and on-board processor. As with Mentor can be controlled by simulator and networked with up to three other Cybernetic machines and work cell. £4,280.

Neptune II (Cybernetic Applications) 6-axis plus gripper. Rest of specifications same as for Neptune I with addition that it can be controlled by touch sensors on all axes. £5,600.

TeachMover (UMI) 5-axis plus gripper, stepper motor drive with steel cable transmission. Lift 454gm, reach 444mm. On-board processor with teach pendant. £2,650.

SCARA ARMS

IVAX 901 (Feedback Instruments) 4-axis plus pneumatic gripper, servo-driven, lift 500gms, software for on-

board processor, IBM, BBC and Apple. Work cell available. £3,950.

PW801 (Feedback Instruments) 4-axis plus gripper, servos on all axes except end rotation which has a stepper motor. Lift 2kgs. Software for IBM and Apricot. Work cell available, interchangeable gripper jaws. Only made specially to order £8,000 with IBM pack £350.

RTX (UMI) 6-axis plus gripper, servo-driven, lift 4kgs, software for IBM. £8,200.

RT 100 (UMI) More robust version of RTX, intended for light industry £9,800.

Serpent I (Cybernetic Applications) 4-axis plus gripper, servo-driven with pneumatic power for vertical movement of gripper, height of arm set manually, software for BBC, IBM and Apple. Can be networked with up to three other Cybernetic machines and work cell. £2,865.


Serpent II (Cybernetic Applications) Same as Serpent I except that it has a longer reach. £2,900.

OTHERS

Kestrel (Cybernetic Applications) Gantry supported arm with 4 axes plus gripper, stepper driven, works in x, y and z co-ordinates, lift 2kgs, vacuum or two-fingered pneumatic gripper. Software for IBM can network with up to three other Cybernetic machines and work cell. £4,550.

PERCI (Proops Distributors) Simple arm controlled by microswitches and relays. Runs a routine using a magnet on the end of arm to pick up a ball bearing and placing it in a chute, down which it rolls to its initial position to be picked up again. Developed by Reading University's Department of Cybernetics to show what can be done with simple technology. In kit £60.

Fischertechnik spot welder simulation.

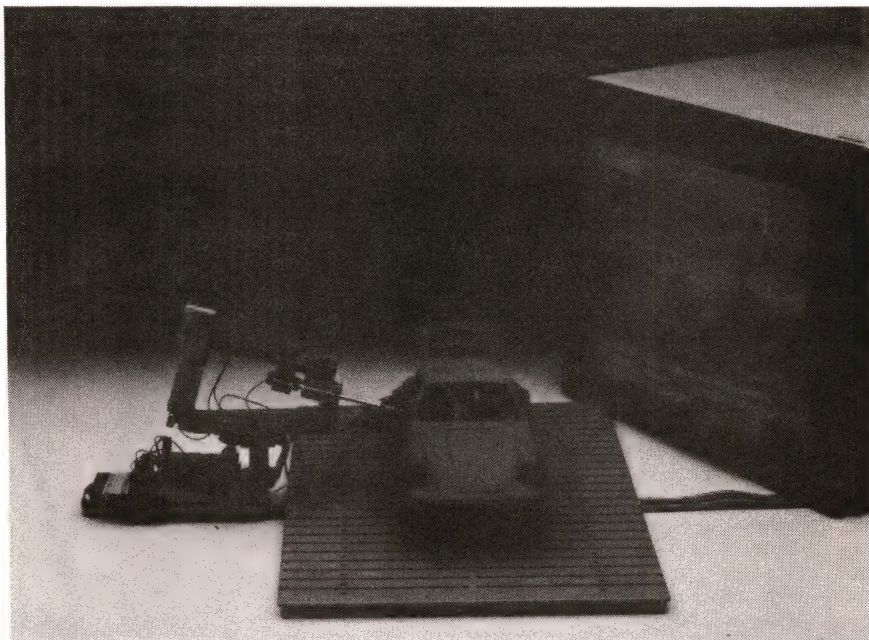

Petra (LJ Technical systems) pneumatic/electronic training systems: collection of conveyors, pick and place arm with pneumatic gripper component dispenser and sensors. Introduced as introduction to hybrid electronic/pneumatic devices. £2,800.

MOBILES

Jessop Turtle (Jessop Microelectronics) also known as the Edinburgh Turtle, it looks like an upturned mixing bowl, one of the earliest turtles controlled by a version of Logo. Powered by servos with optical encoders, includes pen.

Linked to computer by umbilical cord. Software for BBC, Apple, RML Nimbus and IBM. Developed 'Turtle Trails'. £200, Turtle Trails £20.

Lego Buggy (Lego and Resource) Two-wheeled servo-driven, built from Lego kit with Resource control board attached. Maze following, detecting obstacles, speed control and bar code reading can be done. Software in Buggy Basic. Control and Control IT. Kit and board £80, board £50.

PIP (Swallow Systems) Battery-powered stand-alone mobile uses Logo-like language. Two-wheeled driven by stepper motors.

Can store 39 program steps which can be extended by REPEAT function. Plays simple music. BBC and Nimbus leads for saving and downloading programs. Can be "dressed up", pencil holder included. £170.

Roamer (Valiant Technology) Two-wheeled, servo-driven stand-alone mobile, uses Logo-like language with instructions entered by a keypad on top of the Smartie-shaped machine. Pen holder. Appearances can be customized with kits, control box supplied extra. £70.

Trekker (Clwyd Technics) Two-wheeled servo-driven with pen, remote controlled via infra-red link, designed to resemble a turtle. Uses version of Logo and software for BBC, Apple and IBM. Microworlds being created in which it can be used. £260.

CONTROLLERS

Ezi-Dunn Controller (Commotion) One input and six outputs which can control up to three motors with simple on-off and reverse switches. L.E.D.S. on all channels. No memory.

SEQ (ProCom) Battery-powered with power supply alternative. Logo-like instructions entered by keypad, up to 40 instructions can be stored. All outputs and inputs have indicators. £90, power supply extra.

KITS

There are many types of modelling materials from which robotic devices can be built, for example Meccano and Plawcotech and even old cardboard boxes but most need the addition of electronic parts to allow them to be controlled. The manufacturers mentioned here all supply kits with their own controllers designed for robotic projects.

The most well known are **Lego**, with its Lego Technic series and **Fischertechnik**. Lego provides a variety of kits covering a range of complexity. Control can be provided by a simple hand held controller with no memory as well as computer control from a BBC.

It has also developed kits for all levels

ADDRESSES

Clwyd Technics, Antelope Industrial Estate, Rhydynwyn, near Mold, Clwyd.

Commotion, Redbourn House, Stockingswater Lane, Enfield EN3 7TD.

Computer Voice, Cherry Trees, Milwich, Stafford ST18 0EG.

Cybernetic Applications, West Portway Industrial Estate, Andover, Hampshire S10 3LF.

Economatics, Epic House, Dar-nall Road, Attercliffe, Sheffield S9 5AA.

Ezi-Dunn, 56 Malvern Drive, Hilltops, Stoney Stratford, Milton Keynes, MK11 2AE.

Feedback Instruments, Park Road, Crowborough, East Sussex TN6 2QR.

Hasfield Systems, The Old Rectory Stables, Hasfield, Gloucester GL19 4LG.

Jessop Microelectronics, Unit 6A, 3 Long Steet, London E2 8HJ.

LJ Technical Systems, Francis Way, Bowthorpe Industrial Estate, Norwich.

ProCom, 5 Churchill Road, Tavistock, Devon PL19 9BU.

Proops Distributors, Heybridge Estate, Castle Road, London NW1 8TD.

Resource, Exeter Road, off Coventry Grove, Doncaster DN2 4PY.

Stevenage Adventure Workpack, 29 Lytton Fields, Knebworth, Herts SG3 6BA.

Swallow Systems, 32 High Street, High Wycombe HP11 2AQ.

Testbed Technology, The Science Park, Hutton Street, Blackburn BB1 3BY.

TQ International, Bonsall Street, Long Eaton, Nottingham NG10 2AN.

UMI, UMI House, 9-16 St James Road, Surbiton, Surrey.

Valiant Technology, Gulf House, 370 York Road, Wandsworth, London SW18 1SP.

of schooling complete with teacher packs and worksheets. The models which can be built include arms, an x-y plotter and a buggy.

Fischertechnik was one of the first to develop kits for computer-controlled models. Including collections developed on behalf of **Economatics**, its main UK distributor, it offers a large range with some special kits to be used for the teaching of the "Craft and Design Technology National Curriculum".

There is also Nimbus and BBC software for the designing of control systems on screen. The kits include d.c. motors, potentiometers and switches to make a number of devices including arms, a buggy and an ingenious simulation of a spot welder.

Testbed Technology is a new name


which provides a similar array of components and a BBC Interface in its Polymek range. Course materials have been developed with pupil texts and teacher guides. The models can be controlled using Control Logo, Control IT as well as Testbed's own Micro Control Language, available on ROM chip for the BBC.

Stevenage Adventure Workpacks offers collections of motors, gears and switches along with plans for building devices and a circuit diagram for a BBC Interface. The kits are intended as introductions to control technology.

Ezi-Dunn (Commotion) has a basic kit of electronic and mechanical components and a special board which allows components to be connected without soldering.

PIP from Swallow Systems in action.



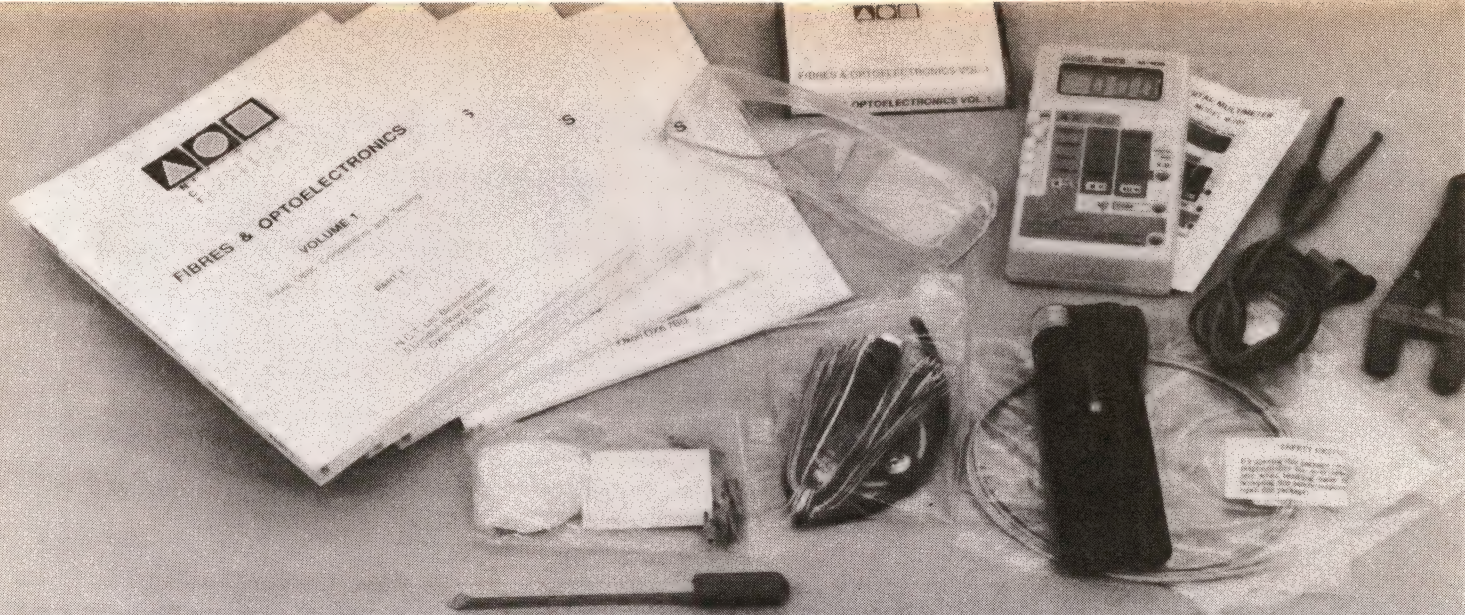

FIBRES AND OPTOELECTRONICS

REVIEWED BY
Mike Tooley B.A.

SOME time ago, I was lucky enough to be asked to review two Open Learning packages published by the National College of Technology (NCT Ltd). These packages (entitled *Digital Electronics – Volume 1* and *Electronic Circuits – Volume 1*) proved both to be of excellent quality and thus I was very pleased to be asked to take a look at another package from the same stable. This latest offering is entitled *Fibres and Optoelectronics – Volume 1*.

Like its predecessors, *Fibres and Optoelectronics* aims to provide students with approximately 45 hours of study. The learning process is again based upon a number of student centred practical assignments. The approach adopted by NCT is ideal for those who may prefer to learn from "hands on" experience. For those (like me) who may have left the classroom behind many years ago, this is a most effective method of learning. It places particular emphasis on real-world practical applications and can be put to use wherever and whenever necessary.

Open Learning

For those who may be new to the concept of Open Learning, the aim is simply to provide an independent student with sufficient learning support to complete a programme of study without having to attend a conventional instructional class. With today's acute shortages of skilled personnel in most areas of technology, this technique is becoming increasingly important as a means of updating engineers and technicians in several specialist areas. Typical of these specialisms is optoelectronic transmission where fibres are being increasingly used to replace the conventional coaxial and multi-core cables of yesteryear.

As with any Open Learning venture, success depends primarily on two factors; commitment on the part of the student and the overall quality of the Open Learning package. The first of these is a matter for the individual student whilst the second depends upon the provider of the Open Learning package and, more particularly, on the extent of the back-up offered to the student. In this respect, NCT courses score very highly as they are not only well thought out but they are very well presented and fully supported with tutorial assistance, assessment and certification. The NCT tutorial support (via a telephone "hotline") is available at a small additional charge.

In order that students can check their understanding, the course contains three "open-book" assessments which students can use to check their progress. For those who wish to gain a recognised qualification, students who successfully complete the programme (including assessments and workbook assignments) are eligible for the award of a Business and Technical Education Council (BTEC) Certificate of Achievement.

Since Open Learning courses require a good deal of self-discipline on the part of the student, a regular study plan makes a good starting point. To emphasise this point, Sylvia Merrett (one of the two audio tutors) advises that: "Your very first task is to sit down and work out your weekly timetable."

Course content

Fibres and Optoelectronics – provides a comprehensive introduction to electronic circuits and assumes no previous knowledge of the subject on the part of the student. The course is pitched at about BEC Level II/City and Guilds part 2 levels and covers the following topics; electromagnetic spectrum, wavelength/frequency relationship, transmission windows, safety with fibre, fibre handling, primary buffer, cladding and core details, PCS fibre, AS fibre, HCS fibre, TIR, refraction and reflection, refractive index, critical angles, Snell's law, numerical aperture, acceptance angle, use of stripping tool, use of microscope, stepped index multimode fibre, stepped index single mode fibre, graded index fibre, transmission delay times, working with 50/125µm fibre, working with 200µm fibre, working with 1mm fibre, stripping, connector fitting, use of epoxy, cable assembly, lapping and polishing, cable design, inspection of fibre samples, loose buffered cable, tight buffered cable, twin zip cable, manufacturers' specifications, a photodiode, irradiation, losses in fibres, connector losses, microbending losses, and practical tests on fibres.

As with other NCT programmes, *Fibres and Optoelectronics* moves backwards and forwards between the workbooks and audio cassette and this provides some useful variety in the study programme. Self-test questions are provided within the workbooks and students are encouraged to attempt these before referring to the answers provided. Such questions are designed so that students can evaluate their own progress through the course and assess their comprehension of each of the major topics.

It should, perhaps, be mentioned that the course contains some mathematics. This, however, is dealt with sympathetically such that the faint hearted need not worry. Formulae are only used when they are essential to understanding. As an example, the student gets to grips with some basic trigonometry in Part 1 as Snell's Law is introduced. Part 2, logarithms are used when decibels first appear.

Learning kit

The package supplied with the *Fibres and Optoelectronics* course comprises three spiral-bound workbooks, a spiral bound book containing solutions to the self test questions (STQ's) and student centred assignments (SCA's), a prototype breadboard, a pack of links and components, a sealed bag containing optical fibre, lapping and polishing equipment, safety glasses, an illuminated microscope, a cleaving tool and cable strippers, a digital multimeter, and an audio cassette. The only additional items required are a 9V PP9 battery, a light source (torch or Anglepoise lamp), a small quantity of epoxy resin based adhesive, and an audio cassette recorder.

Several of the items supplied within the *Fibres and Optoelectronics* package (notably the multimeter and microscope) should be regarded as something of an investment since they will

undoubtedly be useful when the course has been completed. An optional video which illustrates some of the visual concept of optical transmission is also available for free short-term loan to students who have registered for the NCT tutor service.

As the *Fibres and Optoelectronics* course progresses, students are involved with making measurements on a number of simple electronic circuits. There is no better way of doing this than with a modern digital multimeter and NCT provide such an instrument as part of the package. The meter employs a 3½ digit I.C.D. display and offers d.c. voltage, d.c. current, a.c. voltage, and resistance ranges. Accuracy on the d.c. ranges is $\pm 0.5\%$ with a maximum resolution of 1mV and 1µA on the d.c. voltage and current ranges respectively. The multimeter will undoubtedly prove to be extremely useful to students long after successful completion of the NCT study programme!

Workbooks

The three workbooks incorporate text regularly interspersed with details of the student-centred assignments. Each workbook should be regarded more as a personal reference of progress through the course rather than as a conventional textbook. Furthermore, since the course is highly structured, the workbooks should be followed in exact sequence. Each workbook contains between 83 and 101 pages and the workbook for Part 3 contains an index of topic references for all three parts of the course.

The standard of the workbooks is generally good, with "chatty" text and neatly presented computer-generated diagrams. The division of the course into three separate modules (each with its own text) is both logical and helps to make the material a little more manageable than if it had all been presented in one book.


The satisfactory completion of each of the workbooks represents a goal in its own right. Students can, therefore, build on their successes and steadily gain in confidence as they progress through the *Fibres and Optoelectronics* course.

The numerous "student centred assignments" present students with a series of tasks to carry out. Representative tasks include measuring the forward and reverse resistance of several light emitting diodes, constructing a CMOS astable oscillator which drives a pair of light emitting diodes, cutting and stripping optical fibres, transmitting the signal produced by the astable oscillator via a fibre, cleaving and inspecting fibres, fitting connectors, investigating lapping and polishing techniques. The final assignment (Assignment 17) should provide readers with some idea of the practical skills which are developed within the course. Students are informed that:

This assignment should take you about 6 hours to complete and you should then be able to:

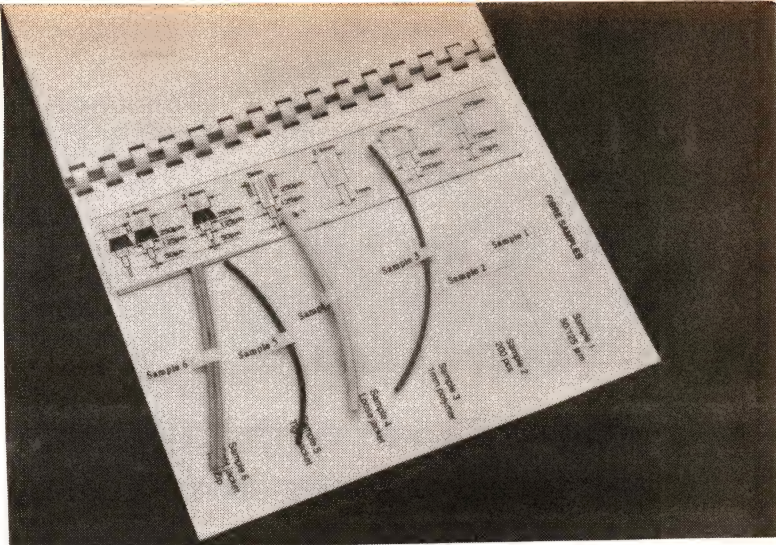1. Determine from test the numerical aperture (NA) of a fibre.
2. Observe losses due to connectors.
3. Record the effect of microbending.
4. Test and plot the results of linear coupling displacement, separation loss.
5. Test and record the effect due to losses due to angular displacements.
6. Test and plot the transmission losses due to lateral displacement.

For those who may run into difficulties, each student centred



A range of fibre samples is attached to the inside back cover of one of the workbooks.

assignment is supplied with a solution which is described in a separate booklet. Students are thus not left completely in the dark when things don't work out as planned!

Cost

Fibres and Optoelectronics - Volume 1 is priced at £199 (excluding VAT). Two levels of tutorial support are offered and both require a supplementary fee. In order to gain an NCT Certificate, students have to pay a further £17.50 whilst support to gain a BTEC Certificate of Achievement (including BTEC Registration) is priced at an additional £32 (both excluding VAT).

If the initial cost of the package is beyond your budget, many company training departments and Further Education Colleges are investing in Open Learning and it would be well worth contacting your Training Officer or the Open Learning Co-ordinator of your local college to see whether this package is available, or if it will soon be available.

In conclusion

Fibres and Optoelectronics meets a very definite need. Anyone wishing to get to grips with this new area of technology should find this package extremely useful. The course is both well structured and well supported and exemplifies the best of today's Open Learning offerings.

Having taught the principles of fibre optics to groups of electronics and computing students over the past five years, I feel that NCT have produced a most worthwhile package which completely de-mystifies a subject which is often felt to be rather "difficult". The package is comprehensive and very professionally presented, and ideally suited to those with no previous knowledge of the subject.

NCT Ltd are at Bicester Hall, 5 London Road, Bicester, Oxon OX6 7BU. Telephone: (0296) 613067.

Teach-In No 4

INTRODUCING DIGITAL ELECTRONICS

By Michael J. Cockcroft


Training Manager, Peterborough ITeC

This Teach-In No 4 Book has been designed as a complete course for the City and Guilds Introductory Digital Electronics syllabus (726/301). This open learning course was first published in monthly parts in EE. It was so popular that we are now republishing it in book form. The series starts at a level suitable for beginners and covers a vast amount of general electronics information. It is therefore suitable for everyone interested in the subject, including those taking GCSE Technology courses, and not just those wishing to achieve a City and Guilds certificate.

**Available from your newsagent
from Sept. 21st - Order Now**

EVERYDAY ELECTRONICS BINDERS

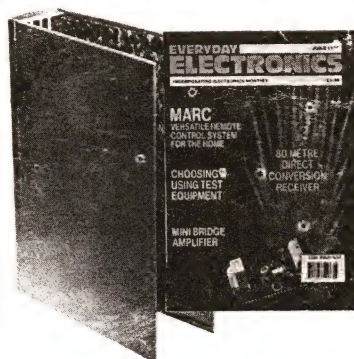Don't let your valuable issues of EE get binned, burned or bitten (by the dog!). Get one of our exquisite orange hard-back binders, slip each issue into it as you get them and you will always know where they are - we hope!



Binders to hold one volume (12 issues) are available from Everyday Electronics, 6 Church Street, Wimborne, Dorset BH21 1JH for £4.95 (£6.95 to European countries and £9.00 to other countries, surface mail) inclusive of postage and packing. **Payment in £ sterling only please.**

Binders are normally sent within seven days of receipt of your order but please allow up to 28 days for UK delivery - more overseas.

DIRECT BOOK SERVICE

The books listed have been selected as being of special interest to everyone involved in electronics and computing. They are supplied by mail order direct to your door. Full details are given on the last book page.

For another selection of books see next month's issue.

MORE BOOKS NEXT MONTH — MORE BOOKS NEXT MONTH

PROJECT CONSTRUCTION

HOW TO GET YOUR ELECTRONIC PROJECTS WORKING

R. A. Penfold

We have all built projects only to find that they did not work correctly, or at all, when first switched on. The aim of this book is to help the reader overcome just these problems by indicating how and where to start looking for many of the common faults that can occur when building up projects.

96 pages Order code BP110 £2.50

HOW TO DESIGN AND MAKE YOUR OWN P.C.B.s

R. A. Penfold

Deals with the simple methods of copying printed circuit board designs from magazines and books and covers all aspects of simple p.c.b. construction including photographic methods and designing your own p.c.b.s.

80 pages Order code BP121 £2.50

BEGINNER'S GUIDE TO BUILDING ELECTRONIC PROJECTS

R. A. Penfold

Shows the complete beginner how to tackle the practical side of electronics, so that he or she can confidently build the electronic projects that are regularly featured in magazines and books. Also includes examples in the form of simple projects.

112 pages Order code No. 227 £1.95

ELECTRONIC SCIENCE PROJECTS

O. Bishop

These projects range in complexity from a simple colour temperature meter to an infra-red laser. There are novelties such as an electronic clock regulated by a resonating spring, and an oscilloscope with solid-state display. There are scientific measuring instruments such as a pH meter and an electro-cardiometer. All projects have a strong scientific flavour. The way they work, and how to build and use them are fully explained.

144 pages Order code BP104 £2.95

CIRCUITS & DESIGN

PRACTICAL ELECTRONIC BUILDING BLOCKS—BOOK 1

PRACTICAL ELECTRONIC BUILDING BLOCKS—BOOK 2

R. A. Penfold

These books are designed to aid electronic enthusiasts who like to experiment with circuits and produce their own projects, rather than simply following published project designs.

BOOK 1 contains: Oscillators—sinewave, triangular, squarewave, sawtooth, and pulse waveform generators operating at audio frequencies. Timers—simple monostable circuits using i.c.s, the 555 and 7555 devices, etc. Miscellaneous—noise generators, rectifiers, comparators and triggers, etc.

BOOK 2 contains: Amplifiers—low level discrete and op-amp circuits, voltage and buffer amplifiers including d.c. types. Also low-noise audio and voltage controlled amplifiers. Filters—high-pass, low-pass, 6, 12, and 24dB per octave types. Miscellaneous—i.c. power amplifiers, mixers, voltage and current regulators, etc.

BOOK 1 128 pages Order code BP117 £1.95
BOOK 2 112 pages Order code BP118 £1.95

ELECTRONIC ALARM CIRCUITS MANUAL

R. M. Marston

One hundred and forty useful alarm circuits, of a variety of types, are shown in this volume. The operating principle of each one is explained in concise but comprehensive terms, and brief construction notes are given where necessary.

Aimed at the practical design engineer, technician and experimenter, as well as the electronics student and amateur.

124 pages Order code NE11 £10.95

DESIGNING DC POWER SUPPLIES

G. C. Loveday C.Eng MIERE

Covers all aspects of the design of regulated power units, using discrete, i.c. regulators and switched units. It also covers protection circuits and reference supplies. Many design examples and exercises all with fully worked solutions are given.

131 pages Order code BM2 £6.95



ELECTRONIC POWER SUPPLY HANDBOOK **NEW**

Ian R. Sinclair

This book covers the often neglected topic of electronic power supplies. All types of supplies that are used for electronics purposes are covered in detail, starting with cells and batteries and extending by way of rectified supplies and linear stabilisers to modern switch-mode systems, IC switch-mode regulators, DC-DC converters and inverters.

The devices, their operating principles and typical circuits are all dealt with in detail. The action of rectifiers and the reservoir capacitor is emphasised, and the subject of stabilisation is covered. The book includes some useful formulae for assessing the likely hum level of a conventional rectifier reservoir supply.

136 pages Order code PC108 £7.95

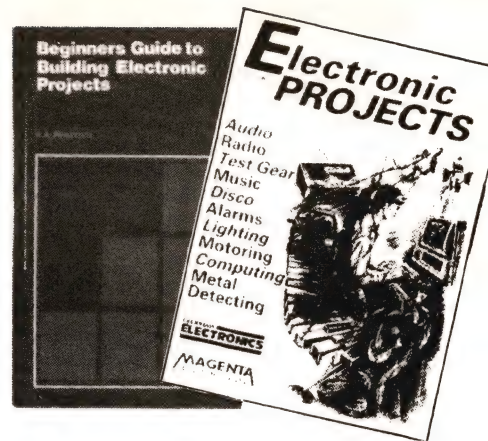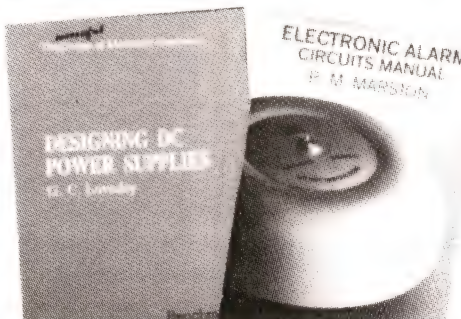

ELECTRONIC PROJECTS — BOOK 1

Published by *Everyday Electronics* in association with *Magenta Electronics*.

Contains twenty of the best projects from previous issues of *EE* each backed with a kit of components. The projects are: Seashell Sea Synthesiser, EE Treasure Hunter, Mini Strobe, Digital Capacitance Meter, Three Channel Sound to Light, BBC 16K Sideways Ram, Simple Short Wave Radio, Insulation Tester, Stepper Motor interface, Eprom Eraser, 200MHz Digital Frequency Meter, Infra Red Alarm, EE Equaliser Ioniser, Bat Detector, Acoustic Probe, Mainstester and Fuse Finder, Light Rider—(Lapel Badge, Disco Lights, Chaser Light), Musical Doorbell, Function Generator, Tilt Alarm, 10W Audio Amplifier, EE Buccaneer Induction Balance Metal Detector, BBC Midi Interface, Variable Bench Power Supply, Pet Scarer, Audio Signal Generator.

128 pages (A4 size) Order code EP1 £2.45

MICRO INTERFACING CIRCUITS—BOOK 1 MICRO INTERFACING CIRCUITS—BOOK 2

R. A. Penfold

Both books include practical circuits together with details of the circuit operation and useful background information. Any special constructional points are covered but p.c.b. layouts and other detailed constructional information are not included.

Book 1 is mainly concerned with getting signals in and out of the computer. Book 2 deals primarily with circuits for practical applications.

Book 1 112 pages Order code BP130 £2.25
Book 2 112 pages Order code BP131 £2.75

SENSORS AND TRANSDUCERS

Keith Brindley

There are a considerable number of transducers. Look through any electronic components catalogue and you'll find a wide variety of types, and each type has many versions. It's not easy to choose a transducer correctly for a particular function. In many specifications, terms and procedures are referred to which might deter you from using one that is, in fact, the best for the job. Yet, opting to use a transducer merely because it is easier to interface into the measuring system is not the answer. A greater knowledge of all types of transducers capable of doing the task is the ideal, and only then can a totally satisfactory decision be made to use one in particular.

176 pages Order code NE17 £12.95

ELECTRONIC CIRCUITS FOR THE COMPUTER CONTROL OF ROBOTS

Robert Penfold

Robots and robotics offer one of the most interesting areas for the electronics hobbyist to experiment in. Today the mechanical side of robots is not too difficult, as there are robotics kits and a wide range of mechanical components available. The micro controller is not too much of a problem either, since the software need not be terribly complex and many inexpensive home computers are well suited to the task.

The main stumbling block for most would-be robot builders is the electronics to interface the computer to the motors, and the sensors which provide feedback from the robot to the computer. The purpose of this book is to explain and provide some relatively simple electronic circuits which bridge this gap.

92 pages Order code BP179 £2.95

50 SIMPLE LED CIRCUITS

R. N. Soar

Contains 50 interesting and useful circuits and applications, covering many different branches of electronics, using one of the most inexpensive and freely available components—the light-emitting diode (LED). Also includes circuits for the 707 common anode display.

64 pages Order code BP42 £1.95

BOOK 2 50 more l.e.d. circuits Order code BP87 £1.95


ELECTRONICS SIMPLIFIED

—CRYSTAL SET CONSTRUCTION

F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.

Especially written for those who wish to participate in the intricacies of electronics more through practical construction than by theoretical study. It is designed for all ages upwards from the day one can read intelligently and handle simple tools.

80 pages Order Code BP92 £1.75

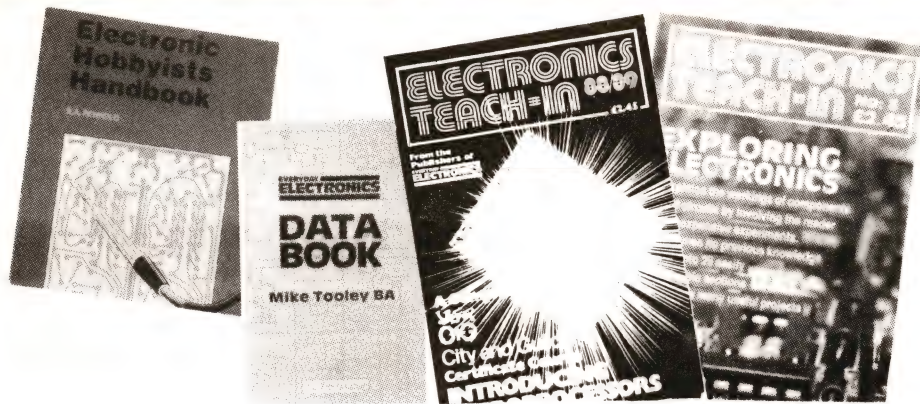

**ELECTRONICS TEACH-IN 88/89—
INTRODUCING MICROPROCESSORS**

Mike Tooley BA (published by *Everyday Electronics*)
A complete course that can lead successful readers to the award of a City and Guilds Certificate in Introductory Microprocessors (726/303). The book contains everything you need to know including full details on registering for assessment, etc.

80 pages (A4 size) Order code TI-88/89 £2.45

FROM ATOMS TO AMPERES

F. A. Wilson
Explains in crystal clear terms the absolute fundamentals behind electricity and electronics. Really helps you to discover and understand the subject, perhaps for the first time ever.

Have you ever: Wondered about the true link between electricity and magnetism? Felt you could never understand the work of Einstein, Newton, Boltzmann, Planck and other early scientists? Just accepted that an electron is like a little black ball? Got mixed up with e.m.f. and p.d.? Thought the idea of holes in semiconductors is a bit much?

Then help is at hand with this inexpensive book, in as simple a way as possible and without too much complex mathematics and formulae.

244 pages Order code BP254 £3.50

BEGINNERS GUIDE TO MICROPROCESSORS

E. A. Parr
An excellent grounding in microprocessors, this book is broadly relevant to the whole of our Introducing Microprocessors course. It is easy to read and well illustrated.

224 pages Temporarily out of print

ELECTRONICS—A "MADE SIMPLE" BOOK

G. H. Olsen
This book provides excellent background reading for our *Introducing Digital Electronics* series and will be of interest to everyone studying electronics. The subject is simply explained and well illustrated and the book assumes only a very basic knowledge of electricity.

330 pages Order code NE10 £4.95

**ELECTRONICS TEACH-IN No. 3 — EXPLORING
ELECTRONICS** (published by *Everyday Electronics*)

Owen Bishop
Another EE value for money publication aimed at students of electronics. The course is designed to explain the workings of electronic components and circuits by involving the reader in experimenting with them. The book does not contain masses of theory or formulae but straightforward explanations and circuits to build and experiment with.


Exploring Electronics contains more than 25 useful projects, assumes no previous knowledge of electronics and is split into 28 easily digestible sections.

88 pages (A4 size) Order code TI3 £2.45

**NEWNES ELECTRONICS
POCKET BOOK**

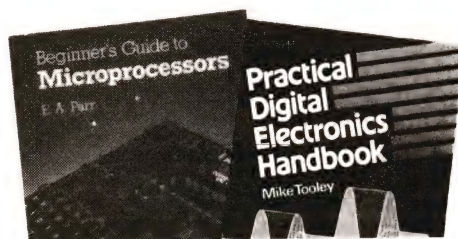E. A. Parr
Newnes Electronics Pocket Book has been in print for over twenty years and has covered the development of electronics from valve to semiconductor technology and from transistors to LSI integrated circuits and microprocessors. To keep up to date with the rapidly changing world of electronics, continuous revision has been necessary. This new Fifth Edition takes account of recent changes and includes material suggested by readers of previous editions. New descriptions of op amp. applications and the design of digital circuits have been added, along with a totally new chapter on computing, plus other revisions throughout.

315 pages (hard cover) Order Code NE02 £9.95



COMPUTING

**NEWNES COMPUTER ENGINEER'S
POCKETBOOK (Second Edition)**

Michael Tooley
An invaluable compendium of facts, figures, circuits and data, indispensable to the designer, student, service engineer and all those interested in computer and microcomputer systems. It will appeal equally to the hardware or software specialist and to the new band of "software engineers". This first edition covers a vast range of subjects at a practical level, with the necessary explanatory text. The data is presented in a succinct and rapidly accessible form so that the book can become part of an everyday toolkit.

205 pages (hard cover) Order code NE01 £9.95

AN INTRODUCTION TO Z80 MACHINE CODE

R. A. & J. W. Penfold
Takes the reader through the basics of microprocessors and machine code programming with no previous knowledge of these being assumed. The Z80 is used in many popular home computers and simple programming examples are given for Z80-based machines including the Sinclair ZX-81 and Spectrum, Memotech and the Amstrad CPC 464. Also applicable to the Amstrad CPC 664 and 6128.

144 pages Order code BP152 £2.75

A Z80 WORKSHOP MANUAL

E. A. Parr, B.Sc., C.Eng., M.I.E.E.
This book is intended for people who wish to progress beyond the stage of BASIC programming to topics such as machine code and assembly language programming, or need hardware details of a Z80 based computer.

192 pages Order Code BP112 £3.50

COMPUTERS AND MUSIC — AN INTRODUCTION

R. A. Penfold
Computers are playing an increasingly important part in the world of music, and the days when computerised music was strictly for the fanatical few are long gone. Computer-based music systems in the past have tended to be either horrendously expensive, very crude, or both! These days, prices are much more modest and the potential of the equipment is much greater. Consequently a lot of musicians are being tempted into the unfamiliar territory of computer music systems.

If you are more used to the black and white keys of a synth keyboard than the QWERTY keyboard of a computer, you may be understandably confused by the jargon and terminology bandied about by computer buffs. But fear not, setting up and using a computer-based music making system is not as difficult as you might think.

This book will help you learn the basics of computing, running applications programs, wiring up a MIDI system and using the system to good effect, in fact just about everything you need to know about hardware and the programs, with no previous knowledge of computing needed or assumed. This book will help you to choose the right components for a system to suit your personal needs, and equip you to exploit that system fully.

174 pages Order code PC107 £7.95

GETTING THE MOST FROM YOUR PRINTER

J. W. Penfold
Details how to use all the features provided on most dot-matrix printers from programs and popular word processor packages like Wordwise, Visawrite and Quill, etc. Shows exactly what must be typed in to achieve a given effect.

96 pages Order Code BP181 £2.95

EVERYDAY ELECTRONICS DATA BOOK

Mike Tooley BA
(published by EE in association with PC Publishing)

This book is an invaluable source of information of everyday relevance in the world of electronics. It contains not only sections which deal with the essential theory of electronic circuits, but it also deals with a wide range of practical electronic applications.

It is ideal for the hobbyist, student, technician and engineer. The information is presented in the form of a basic electronic recipe book with numerous examples showing how theory can be put into practice using a range of commonly available "industry standard" components and devices.

A must for everyone involved in electronics!
256 pages Order code DATA £8.95

ELECTRONIC HOBBYISTS HANDBOOK

R. A. Penfold
Provides an inexpensive single source of easily located information that the amateur electronics enthusiast is likely to need for the day-to-day pursuance of this fascinating hobby. Covers common component colour codes. Details the characteristics and pinouts of many popular semiconductor devices, including various types of logic ICs, operational amplifiers, transistors, FETs, unijunctions, diodes, rectifiers, SCRs, diacs, triacs, regulators and SMDs, etc. Illustrates many useful types of circuits, such as timers and oscillators, audio amplifiers and filters, as well as including a separate section on power supplies. Also contains a multitude of other useful data.

88 pages Order code BP233 £4.95

**ESSENTIAL THEORY FOR THE
ELECTRONICS HOBBYIST**

G. T. Rubaroo, T. Eng (C.E.I.), Assoc. I.E.R.E.

The object of this book is to supply the hobbyist with a background knowledge tailored to meet his or her specific requirements and the author has brought together the relevant material and presented it in a readable manner with minimum recourse to mathematics.

128 pages Order Code 228 £2.50

PRACTICAL DIGITAL ELECTRONICS HANDBOOK

Mike Tooley (Published in association with *Everyday Electronics*)

The vast majority of modern electronic systems rely heavily on the application of digital electronics, and the *Practical Digital Electronics Handbook* aims to provide readers with a practically based introduction to this subject. The book will prove invaluable to anyone involved with the design, manufacture or servicing of digital circuitry, as well as to those wishing to update their knowledge of modern digital devices and techniques. Contents: Introduction to integrated circuits; basic logic gates; monostable and bistable devices; timers; microprocessors; memories; input and output devices; interfaces; microprocessor buses. Appendix 1: Data. Appendix 2: Digital test gear projects; tools and test equipment; regulated bench power supply; logic probe; logic pulser; versatile pulse generator; digital IC tester; current tracer; audio logic tracer; RS-232C breakout box; versatile digital counter/frequency meter. Appendix 3: The oscilloscope. Appendix 4: Suggested reading. Appendix 5: Further study.

208 pages Order code PC100 £8.95

A CONCISE INTRODUCTION TO MS-DOS

N. Kantaris
This guide is written with the non-expert, busy person in mind and, as such, it has an underlying structure based on "what you need to know first, appears first". Nonetheless, the guide is also designed to be circular, which means that you don't have to start at the beginning and go to the end. The more experienced user can start from any section.

The guide covers versions 3.0, 3.1 and 3.2 of both PC-DOS and MS-DOS as implemented by IBM and other manufacturers of "compatible" microcomputers, including the AMSTRAD PC's. It covers both floppy disc-based systems and hard disc-based systems.

64 pages Order code BP232 £2.95

**AN INTRODUCTION TO 68000 ASSEMBLY
LANGUAGE**

R. A. & J. W. Penfold
Obtain a vast increase in running speed by writing programs for 68000 based micros such as the Commodore Amiga, Atari ST range or Apple Macintosh range etc., in assembly language. It is not as difficult as one might think and this book covers the fundamentals.

112 pages Order code BP184 £2.95

**THE ART OF PROGRAMMING THE ZX
SPECTRUM**

M. James, B.Sc., M.B.C.S.
It is one thing to have learnt how to use all the Spectrum's commands and functions, but a very different one to be able to combine them into programs that do exactly what you want them to. This is just what this book is all about—teaching you the art of effective programming with your Spectrum.

144 pages Order code BP119 £2.50

BEGINNER'S GUIDE TO HI-FI

Ian Sinclair

The *Beginner's Guide to Hi-Fi* will appeal to the audio enthusiast, whether newly won over by advances in technology or well established and wondering whether to update equipment. The book deals with the sound from its sources in the studio to its ultimate end in your ears, and shows what sound is, how it is recorded and how it is reproduced.

Every aspect of Hi-Fi, from pickup cartridges to loudspeakers, has been covered, and the emphasis has been on explaining design aims. Cassette systems have been given considerable prominence, including the more modern Dolby C and dbx noise reduction systems. The CD record has been covered in detail so that you can find out just why this system of sound reproduction is so superior.

194 pages

Temporarily out of print.

DATA & COMPONENT IDENTIFICATION

HOW TO IDENTIFY UNMARKED ICs

K. H. Recorr

Shows the reader how, with just a test-meter, to go about recording the particular signature of an unmarked i.c. which should enable the i.c. to then be identified with reference to manufacturers' or other data. An i.c. signature is a specially plotted chart produced by measuring the resistances between all terminal pairs of an i.c. Chart

Order code BP101

£0.95

INTERNATIONAL DIODE EQUIVALENTS GUIDE

A. Michaels

Designed to help the user in finding possible substitutes for a large selection of the many different types of diodes that are available. Besides simple rectifier diodes, also included are Zener diodes, i.e. d.s. diacs, triacs, thyristors, OCIs, photo and display diodes.

144 pages

Temporarily out of print

LINEAR IC EQUIVALENTS AND PIN CONNECTIONS

A. Michaels

Shows equivalents and pin connections of a popular selection of European, American and Japanese linear i.c.s. Also includes details of functions, manufacturer and country of origin.

320 pages

Temporarily out of print

RADIO AND ELECTRONIC COLOUR CODES AND DATA CHART

B. B. Babani

Although this chart was first published in 1971 it provides basic information on many colour codes in use throughout the world, for most radio and electronic components. Includes resistors, capacitors, transformers, field coils, fuses, battery leads, speakers, etc. It is particularly useful for finding the values of old components.

Chart

Order code BP7

£0.95

RADIO, TV, SATELLITE

AN INTRODUCTION TO AMATEUR RADIO

I.D. Poole

Amateur radio is a unique and fascinating hobby which has attracted thousands of people since it began at the turn of the century.

This book gives the newcomer a comprehensive and easy to understand guide through the subject so that the reader can gain the most from the hobby. It then remains an essential reference volume to be used time and again. Topics covered include the basic aspects of the hobby, such as operating procedures, jargon and setting up a station. Technical topics covered include propagation, receivers, transmitters and aerials etc.

150 pages

Order code BP257

£3.50

INTERNATIONAL RADIO STATIONS GUIDE

P. Shore

Provides the casual listener, amateur radio DXer and the professional radio monitor with an essential reference work designed to guide him or her around the ever more complex radio bands. This new edition has been completely revised and rewritten and incorporates much more information which is divided into the following sections:

Listening to Short Wave Radio; ITU Country Codes; World-wide Short Wave Radio Stations; European, Middle East and North African Long Wave Radio Stations; European, Near East and North African Medium Wave Radio Stations; Canadian Medium Wave Radio Stations; USA Medium Wave Radio Stations; Broadcasts in English; Programmes for DXers and Short Wave Listeners; UK FM Radio Stations; Time differences from GMT; Abbreviations; Wavelength/Frequency Conversion.

320 pages

Order code BP255

£4.95

AERIAL PROJECTS

R. A. Penfold

The subject of aerials is vast but in this book the author has considered practical aerial designs, including active, loop and ferrite aerials which give good performances and are relatively simple and inexpensive to build. The complex theory and mathematics of aerial design have been avoided.

Also included are constructional details of a number of aerial accessories including a pre-selector, attenuator, filters and tuning unit.

96 pages

Order code BP105

£2.50

AN INTRODUCTION TO LOUDSPEAKERS AND ENCLOSURE DESIGN

V. Capel

This book explores the various features, good points and snags of speaker designs. It examines the whys and wherefores so that the reader can understand the principles involved and so make an informed choice of design, or even design loudspeaker enclosures for him or herself. Crossover units are also explained, the various types, how they work, the distortions they produce and how to avoid them. Finally there is a step-by-step description of the construction of the *Kapellmeister* loudspeaker enclosure.

148 pages

Order Code BP256

£2.95

MUSICAL APPLICATIONS OF THE ATARI ST's

R. A. Penfold

The Atari ST's are now firmly established as the computers to use for electronic music applications. The range and sophistication of these applications are much greater than most people may realise, but there are still a lot of misconceptions about just what can and cannot be achieved. This book will help you sort out the fact from the fallacy and to get the most musically from the ST's.

A wide selection of topics are covered, including the internal sound chip; MIDI; applications programs such as sequencing and score writing, etc; simple but useful add-on projects and MIDI programming.

90 pages

Order code BP246

£5.95

TESTING & TEST GEAR

TRANSISTOR RADIO FAULT-FINDING CHART

C. E. Miller

Used properly, should enable the reader to trace most common faults reasonably quickly. Across the top of the chart will be found four rectangles containing brief description of these faults, viz—sound weak but undistorted, set dead, sound low or distorted and background noises. One then selects the most appropriate of these and following the arrows, carries out the suggested checks in sequence until the fault is cleared.

Chart

Order code BP70

£0.95

HOW TO USE OSCILLOSCOPES AND OTHER TEST EQUIPMENT

R. A. Penfold

This book explains the basic function of an oscilloscope, gives a detailed explanation of all the standard controls, and provides advice on buying. A separate chapter deals with using an oscilloscope for fault finding on linear and logic circuits. Plenty of example waveforms help to illustrate the control functions and the effects of various fault conditions. The function and use of various other pieces of test equipment are also covered, including signal generators, logic probes, logic pulser, and crystal calibrators.

104 pages

Order code BP267

£3.50

AN INTRODUCTION TO SATELLITE TELEVISION

F.A. Wilson

As a definitive introduction to the subject this book is presented on two levels. For the absolute beginner or anyone thinking about purchasing or hiring a satellite TV system, the story is told as simply as such a complex one can be in the main text.

For the professional engineer, electronics enthusiast, student or others with technical backgrounds, there are numerous appendices backing up the main text with additional technical and scientific detail formulae, calculations, tables etc.

There is also plenty for the DIY enthusiast with practical advice on choosing and installing the most problematic part of the system—the dish antenna.

104 pages

Order Code BP195

£5.95

COMMUNICATION

F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.

A look at the electronic fundamentals over the whole of the communication scene. This book aims to teach the important elements of each branch of the subject in a style as interesting and practical as possible. While not getting involved in the more complicated theory and mathematics, most of the modern transmission system techniques are examined including line, microwave, submarine, satellite and digital multiplex systems, radio and telegraphy. To assist in understanding these more thoroughly, chapters on signal processing, the electromagnetic wave, networks and transmissions assessment are included, finally a short chapter on optical transmission.

256 pages

Order Code BP89

£2.95

AN INTRODUCTION TO VHF/UHF FOR RADIO AMATEURS

I. D. Poole

This book covers the essentials required to gain the most from using the VHF and UHF bands. As such it will be of use to both the newcomer and more experienced operator alike.

Topics included in this book include propagation, descriptions of the bands with outlines of the bandplans and channels, aerials, receivers, transmitters and a special chapter on scanners. In addition to this repeater and mobile operation are included as well as DXing and data modes together with a section on packet radio.

102 pages

Order Code BP281

£3.50

PRACTICAL MIDI HANDBOOK

R.A. Penfold

The Musical Instrument Digital Interface (MIDI) is surrounded by a great deal of misunderstanding, and many of the user manuals that accompany MIDI equipment are quite incomprehensible to the reader.

The Practical MIDI Handbook is aimed primarily at musicians, enthusiasts and technicians who want to exploit the vast capabilities of MIDI, but who have no previous knowledge of electronics or computing. The majority of the book is devoted to an explanation of what MIDI can do and how to exploit it to the full, with practical advice on connecting up a MIDI system and getting it to work, as well as deciphering the technical information in those equipment manuals.

128 pages Order code PC101

£5.95

COMPUTERS AND MUSIC

— see computer section

DIRECT BOOK SERVICE

(A Division of Wimborne Publishing Ltd.)

TO ORDER

Please state the title and order code clearly, print your name and address and add the required postage to the total order.

Add 75p to your total order for postage and packing (overseas readers add £1.50 for countries in Europe, or add £2.00 for all countries outside Europe, surface mail postage) and send a PO, cheque or international money order (£ sterling only) made payable to **Direct Book Service** quoting your name and address, the order code and quantities required to **DIRECT BOOK SERVICE, 33 GRAVEL HILL, MERLEY, WIMBORNE, DORSET, BH21 1RW** (mail order only).

See next month's issue for another three page selection of books.

Although books are normally sent within seven days of receipt of your order, please allow a maximum of 28 days for delivery. Overseas readers allow extra time for surface mail post.

Please check price and availability (see latest issue of *Everyday Electronics*) before ordering from old lists.

Note—our postage charge is the same for one book or one hundred books!



MORE BOOKS NEXT MONTH

THE DREAM MACHINE ▷

Adjust the controls to suit your mood and let the gentle, relaxing sound drift over you. At first you might hear soft rain, sea surf, or the wind through distant trees. Almost hypnotic, the sound draws you irresistibly into a deep, refreshing sleep.

For many the thought of waking refreshed and alert from perhaps the first truly restful sleep in years is exciting enough in itself. For more adventurous souls there are strange and mysterious dream experiences waiting. Take lucid dreams, for instance. Imagine being in control of your dreams and able to act out your most secret wishes and fantasies. With the Dream Machine anything is possible.

DREAM MACHINE PARTS SET **£22.77**

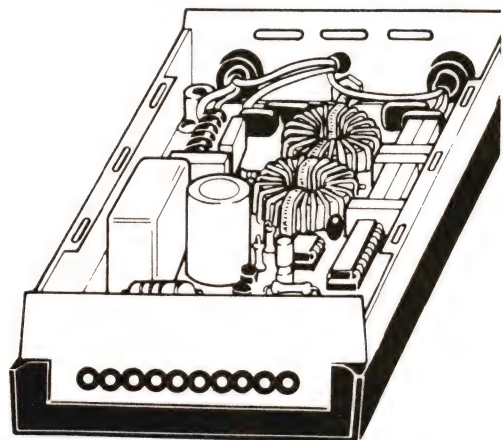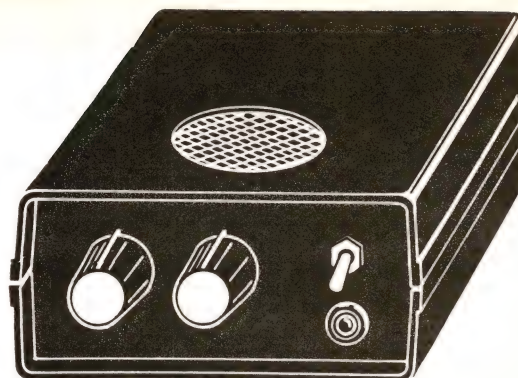

▷ POWER CONDITIONER

You don't have to be a hi-fi nut to notice the huge improvement in sound quality when you run your music system from a clean mains supply. How do you describe the difference? It's as if all this time your favourite artists have been playing and singing inside a wardrobe . . . and someone just opened the door and let them out. You could spend twenty times as much on special cables, plugs, mats and stuff without achieving a tenth of the difference. But don't take my word for it. Try it for yourself.

The sophisticated circuitry of the Power Conditioner begins with a bank of six VDRs to eliminate impulsive spikes. Then comes a massive filter with thirteen capacitors and two current-balanced inductors to smooth away every trace of noise and interference. A ten LED logarithmic display flicks up and down as each spike is eliminated, and gives a second by second account of the interference removed. Maximum load 1.5kW.



POWER CONDITIONER PARTS SET **£34.27**

MAINS CONDITIONER ▷

A general purpose workhorse for cleaning up the mains supply to computers, hi-fi, television sets, and any other electronic equipment that might be disturbed by mains interference. The solid, no-nonsense circuit will handle loads up to 1kW, and the PCB can be built into the equipment to be protected or housed in the optional case.

MAINS CONDITIONER PARTS SET (no case) **£6.21**

RUGGED CASE (optional) **£2.07**

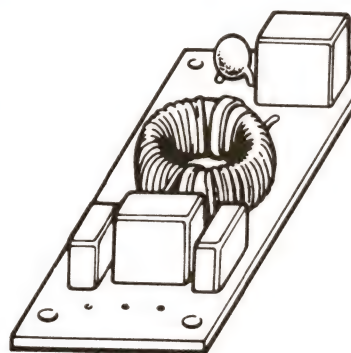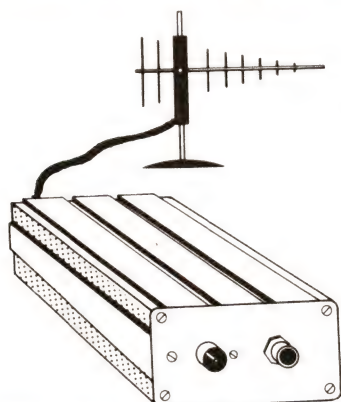

▷ AERIAL BOOSTER

Good TV pictures from an indoor aerial, from a caravan aerial, or in areas of poor reception. This booster ranks with the very best, giving wideband operation from 10MHz to 1.4GHz (it will boost FM radio signals too), mid-band gain of up to 26dB, and a wide supply voltage range of 9V to 26V. It will run from car batteries for caravanners, dry batteries for campers, or a battery eliminator for use in the home.

There are two parts sets for the project. AA1 gives you the PCB, hybrid amplifier, components and instructions. AA2 is the optional case set: rugged screened box, front and rear panels, waterproofing gaskets, feet, sockets and hardware.

AA1 PARTS SET **£14.72** AA2 PARTS SET **£5.52**

KNIGHT RAIDER ▷

The ultimate lighting effect for your car. Picture this: eight powerful lights in line along the front and eight along the rear. You flick a switch on the dashboard control box and a point of light moves lazily from left to right leaving a comet's tail behind it. Flip another switch and the point becomes a bar, bouncing backwards and forwards along the row. Now try one of the other six patterns. An LED display on the console lets you see what the main lights are doing.

The Knight Raider parts set contains the case and all components for the control box. The pattern generator and lamp driver is supplied as a PCB with all components for you to mount anywhere convenient. We supply the electronics, you supply the lamps (from any car accessories shop).

KNIGHT RAIDER PARTS SET **£28.52**



Specialist
SEMICONDUCTORS

Tel: (0600) 3715

LIMITED

SALES DEPT., ROOM 111, FOUNDERS HOUSE, REDBROOK, MONMOUTH, GWENT.

ORDERING

All prices include VAT

UK orders: please add £1.15 postage and packing.

Eire and overseas: please deduct VAT and add £5.00 carriage and insurance.



ACCESS

Phone 0600 3715 for immediate attention to your Access order.

PCB SERVICE

Printed circuit boards for certain constructional projects are available from the PCB Service, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for overseas airmail. Remittances should be sent to **The PCB Service, Everyday Electronics, 6 Church Street, Wimborne, Dorset BH21 1JH**. Cheques should be crossed and made payable to **Everyday Electronics (Payment in £ sterling only)**.

Boards for some older projects – not listed here – can often be obtained from Magenta Electronics, 135 Hunter St., Burton-on-Trent, Staffs DE14 2ST. Tel: 0283 65435 or Lake Electronics, 7 Middleton Close, Nuthall, Nottingham NG16 1BX. Tel: 0602 382509.

NOTE: While 90% of our boards are now held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery – overseas readers allow extra if ordered by surface mail. Please check price and availability in the latest issue before ordering. We can only supply boards listed in the latest issue. Boards can only be supplied on a payment with order basis.

PROJECT TITLE	Order Code	Cost
Noise Gate SEP'87	577	£4.41
Transtest OCT'87	580	£3.32
BBC Sideways RAM/ROM NOV'87	585	£4.10
Stereo Noise Gate APR'88	597	£6.65
Pipe & Cable Locator	598	£3.00
Inductive Proximity Detector	574	£3.00
Multi-Channel Remote Light Dim MAY'88		
Transmitter	599	£3.00
Receiver	600	£3.07
Door Sentinel	605	£3.00
Multi-Chan Remote Light Dim JUN'88		
Relay/Decoder	601	£4.86
Dimmer Board	602	£3.07
Power Supply	603	£3.00
Headlight Reminder	611	£3.00
Video Wiper JUL'88	612	£6.75
Isolink	613	£4.21
Tea Tune AUG'88	609	£3.00
Time Switch	614	£4.84
Suntan Timer	610	£3.07
Car Alarm	615	£3.12
Breaking Glass Alarm SEP'88	617	£4.27
Amstrad PIO	618	£6.77
EPROM Eraser OCT'88	620	£4.07
Doorbell Delay NOV'88	616	£3.56
Micro Alarm	621	£3.12
Infra-Red Object Counter Trans	622	£4.61
Receiver	623	£3.23
Display	624	£3.05
Seashell Sea Synthesiser	625	£4.84
Reaction Timer Main Board DEC'88	626	£3.46
Display Board	627	£3.00
Downbeat Metronome	629	£4.84
EPROM Programmer (On Spec) DEC'88	630	£8.29
Phasor	631	£5.64
Monkey/Hunter Game JAN'89	634	£3.36
Continuity Tester FEB'89	619	£2.67
4-Channel Light Dimmer	635	£7.67
Mini PSU	636	£3.23
Sound-to-Light Interface MAR'89	637	£6.24
Midi Pedal	639	£7.00
Midi Merge	640	£3.00
Audio Lead Tester	641	£5.77
Light Sentinel APR'89		
Main Control Board	632	£9.20
Remote Interface (4 boards)	633	£4.59
Electron User Port	638	£6.64
4-Channel Auto-Fade Interface	642	£6.80
Pet Scarer MAY'89	644	£3.00
Electron A/D Interface	645	£4.84
Spectrum EPROM Programmer JUN'89	628	£7.87
Bat Detector	647	£4.95
Programmable Pocket Timer JUL'89	648	£3.82
Electronic Spirit Level AUG'89	649	£3.85
Distance Recorder	651	£5.23
Treasure Hunter	652	£3.73

PROJECT TITLE	Order Code	Cost
Xenon Beacon SEP'89	650	£4.13
Probe Pocket Treasure Finder	653	£4.12
Power Supplies – Fixed Voltage	654	£4.08
Variable Voltage	655	£4.48
Music on Hold OCT'89	646	£3.85
Power Supplies – 25V 700mA	656	£4.35
30V 1A	657	£4.55
EE Seismograph – Control	658	£4.08
Detector	659	£4.22
Lego/Logo & Spectrum	660	£6.49
Wash Pro NOV'89	643	£3.83
Biofeedback Monitor – Front End	661	£4.52
Processor	662	£4.56
Power Supplies – 1.5V-25V 2A	663	£4.78
Logo/Logo & Spectrum Interface	664	£5.60
EE Electrode Impedance Meter DEC'89	665	£3.98
Biofeedback Signal Generator JAN'90	666	£4.08
Four-Channel Light Chaser	667	£6.70
Quick Cap Tester FEB'90	668	£3.92
Weather Station		
Anemometer – Freq./Volt Board	670	£3.94
Optional Display	669	£3.73
Wind Direction	673/674	£4.22
System Power Supply	675	£3.59
Prophet In-Car Ioniser	676	£3.18
EE Weather Station MAR'90		
Display Driver	672 & 678	£4.22
Display and Sensor	671	£4.47
Fermostat Mk2	677	£4.28
Superhet Broadcast Receiver-Tuner/Amp	679/680	£4.22
Stereo Noise Generator APR'90	681	£4.24
Digital Experimenter's Unit – Pulse Generator	682	£4.46
Power Supply	683	£3.66
Enlarger Timer	684	£4.28
EE Weather Station		
Rainfall/Sunlight Display	685	£4.27
Rainfall Sen and Sunlight Sen	686/687	£4.16
Amstrad Speech Synthesiser	689	£4.68
Quizmaster	690	£4.74
80 Metre Direct Conversion Radio JUN'90	691	£4.95
Mains Appliance Remote Control		
Infra-Red Transmitter	692/693	£4.75
Mains Appliance Remote Control JUL'90		
Encoder Board A	694	£6.61
Encoder Board B	695	£4.78
The Tester	696	£4.15
Mains Appliance Remote Control AUG'90		
Mains ON/OFF Decoder	697	£4.55
(5 or more 697's ordered together £3.25 each)		
Simple Metronome	698	£3.94
Hand Tally SEP'90		
Main Board (double-sided)		
Display	699, 700	£10.95
Alarm Bell Time-Out	701	£4.10
Mains Appliance Remote Control		
Temperature Controller (p.c.b. only)	702	£5.20
Ghost Waker Oct'90	703	£4.32
Frequency Meter	704	£5.25

Please note it is important to give project title as well as order code.

EE PRINTED CIRCUIT BOARD SERVICE

Please send me the following p.c.b.s.

Order Code Project Quantity Price

.....

.....

I enclose cheque/PO for £.....

Name.....

Address.....

Please allow 28 days for delivery (see note above)


BLOCK CAPITALS PLEASE

JOIN UP WITH LITESOLD

Professional Soldering Equipment at Special Mail-Order Prices.

SK18 Soldering Kit. £19.75

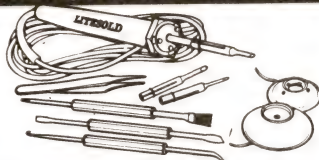Build or repair any electronic project. LC18 240v 18w iron with 3.2, 2.4, and 1.6mm bits. Pack of 18 swg flux-cored 60/40 solder. Tweezers. 3 soldering aids. Reel of De-Solder braid. In PVC presentation wallet.



ADAMIN Miniature Iron £8.60

Possibly smallest mains iron in the world. Ideal for fine work. Slim

nylon handle with finger grip. Interchangeable bits available 1.2, 1.6, 2.4, 3.4 and 4.7mm. Fitted with 2.4mm. 240v 12w (12v available). Presentation wallet.

'L' Series Lightweight Irons. 12w £9.20

High efficiency irons for all electronic hobby work. Non-roll handles with finger guards. Stainless steel element shafts. Screw-connected elements. Slip-on bits available from 1.6 to 4.7mm. LA12

model, 12w, 2.4mm bit. LC 18 Model, 18w, 3.2mm bit. 240v Std - 12v available. Presentation wallet.

Soldering Iron Stands 3&4 £7.33



Designed specially for LITESOLD irons. Heavy, solid-plastic base with non-slip pads. Won't tip over, holds iron safely. With wiping sponge and location for spare (hot) bits. No 5 stand for EC50 iron No 4 stand for ADAMIN miniature iron No 3 stand for LA12 and LC18 Irons.

De-Solder Pumps £8.65

High Quality version of increasingly popular type of tool. Precision made anodised aluminium body, plunger guard and high-seal piston. Easy

thumb operation. Automatic solder ejection. Conductive PTFE nozzle - no static problems.

Prices include p&p and VAT. Send order with Cheque/PO. Ring for Access/Visa sales



LIGHT SOLDERING DEVELOPMENTS LTD. DEPT. EE
97-99 GLOUCESTER ROAD, CROYDON CR0 2DN. 081 689 0574

MICRO-PRESSURE CAR ALARM

Most people now realise that the locks fitted to the majority of cars are hopelessly inadequate to stop even the school age joy-rider and some form of electronic anti-theft system is essential. Even our politicians have begun to say such systems should be fitted as standard! Even so, most cars are still not equipped with an alarm system. There are three main reasons for this, the high cost of an effective alarm, the time and cost of installing a complex system and the inconvenience of operating the alarm every time the car is used. Recognising these problems, the **electronize MICRO-PRESSURE ALARM** has been designed to give the best possible performance at a price everyone can afford, to provide extremely simple fitting and the easiest possible operation.

MICRO-PRESSURE is a unique system that senses the changes in air pressure inside the car. As a door catch is released air is drawn out, causing a minute drop in pressure which sets off the alarm. The alarm protects all doors and the tailgate without the need for additional sensors or switches and the alarm is so sensitive that it can still operate with a window partly open. A handpass filter makes the alarm immune to loud noises and most sensitive to the frequencies produced by door opening.

There are only three wires to connect, two into the horn circuit and one to the ignition switch. A Power MOSFET transistor is used, instead of the traditional output relay, reducing the operating current to only a few milliamperes, so low that the alarm can be powered from the horn circuit without any supply connections. The alarm is small and light and can be secured with nylon ties. No holes to drill in awkward places.

Once fitted the alarm operates its self! When you switch off the ignition and close the door there is a 1 minute delay before the alarm arms its self. When you return there is a 10 second delay and audible warning before the alarm begins to blast the horn intermittently for about a minute. All you have to do is switch on the ignition, or a hidden switch if you prefer, to cancel the alarm.

You can buy the **MICRO-PRESSURE ALARM** as a complete parts kit at £15.75 or ready assembled and tested at £21.75

VOLT DROP ALARM

This alarm has all the above features except **MICRO-PRESSURE** sensing. It has the same simple fitting and operation but is triggered by the volt drop principle, relying on the existing door switches and light. Available as a complete parts kit at £14.55 or assembled and tested at £20.55

TOTAL ENERGY DISCHARGE ELECTRONIC IGNITION

Our long established extended CDI system uses the existing contacts to allow easy fitting whilst the electronics removes the adverse effects and boosts the spark. CDI is no longer fitted as standard because of its high cost and complexity but its unsurpassed fire power is still used for racing, including formula one. Give your car the best spark available at £20.95 for the parts kit or £26.25 for the assembled and tested unit.

Please note, our kits are not just a bag of components and a PCB. They include everything, detailed instructions, case and even solder. Likewise assembled units come complete with instructions, wire, connectors etc.

All prices now include VAT and post & packing. Add £3 for delivery outside Europe. Order direct (quote ref. C0A) or send for more information from:-

ELECTRONIZE DESIGN

tel. 021 308 5877

2 Hillside Road, Four Oaks, Sutton Coldfield, B74 4DQ

A HANDY NEW ADDITION TO OUR VERSATILE MULTIMETER RANGE

DIGITAL CAPACITANCE METER


An extremely useful hand-held capacitance meter measuring from 1pF to 20,000µF in nine ranges.

Features include:

- 13mm, 3.5 digit LCD
- Zero adjustment
- Low battery indicator
- One year warranty
- Supplied with battery (PP3), manual and test leads
- Just one of our many low cost Digital Multimeters - send for full details

£38.⁹⁸

inc. VAT
please add £1.00
for p + p

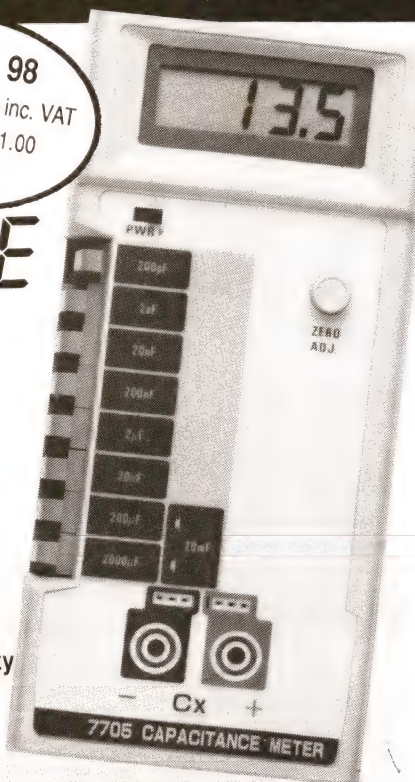

Specification

ranges	res.	accuracy
200pF	0.1pF	+ (0.5% + 1 digit + 0.5pF)
2nF	1.0pF	+ (0.5% + 1 digit)
20nF	10pF	+ (0.5% + 1 digit)
200nF	100pF	+ (0.5% + 1 digit)
2µF	1.0nF	+ (0.5% + 1 digit)
20µF	10nF	+ (0.5% + 1 digit)
200µF	100nF	+ (0.5% + 1 digit)
2000µF	1µF	± (1.0% + 1 digit)
20,000µF	10µF	+ (2.0% + 1 digit)

Overload protection	0.25A 250V fuse
Excitation voltage	3.2V, all ranges
Dimensions	180 x 85 x 38mm

OUT NOW!

- The new Cirket Catalogue
- 184 pages
 - Discount vouchers
 - 1,000's of products



Cirket

£1.60 inc.

SAME DAY DESPATCH - 0992 444111

Cirket Distribution Ltd.

Park Lane, Broxbourne, Herts. EN10 7NQ

Tel. Enquiries (0992) 441306 Fax. (0992) 464457

EVERYDAY ELECTRONICS

CLASSIFIED

Reach effectively and economically today's enthusiasts anxious to know of your products and services through our semi-display and classified pages. The prepaid rate for semi-display spaces is £8.00 (plus VAT) per single column centimetre (minimum 2.5 cm). The prepaid rate for classified advertisements is 30 pence (plus VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday Electronics. VAT must be added. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Everyday Electronics, 6 Church Street, Wimborne, Dorset BH21 1JH. Tel: (0202) 881749.

RCS VARIABLE VOLTAGE D.C. BENCH POWER SUPPLY

1 to 24 volts up to 1/2 amp. 1 to 20 volts up to 1 amp. 1 to 16 volts up to 1 1/2 amps A.C. Fully stabilised. Twin panel meters for instant voltage and current readings. Overload protection.

Fully variable.
Operates from
240V A.C.
Compact Unit.
size 9 x 5 1/2 x 3in.



£42 inc. VAT
+ Post £2

RADIO COMPONENT SPECIALISTS



337 WHITEHORSE ROAD, CROYDON
SURREY, U.K. Tel: 081-6841665



List, Large SAE. Delivery 7 days. Callers welcome. Closed Wednesday

ELECTRONIC COMPONENTS

SEND FOR OUR 1991 CATALOGUE
CONTAINS 000's OF PRODUCT LINES
INCLUDING SMD COMPONENTS

SEND CHEQUE OR P.O. FOR
£1.80 TO:

SARM DIGITAL

13 Pearle Street, Macclesfield
Cheshire SK10 2AL

Mail Order Only. Prop N. Farrar

ELECTRONIC COMPONENTS

EVERYTHING FOR YOUR NEXT PROJECT

THE BIGGEST DISPLAY IN THE SOUTH
IS AT

FRASER ELECTRONICS

42 ELM GROVE * SOUTHSEA *
HANTS

Telephone 0705-815584

N. R. BARDWELL LTD

10	-4p 3w MBB Rotary Switches.....	£1.00
200	-Signal Diodes 1N4148.....	£1.00
100	-Rectifier Diodes 1N4001.....	£1.00
100	-Zener Diodes 6V8 400mW.....	£1.00
30	-Assorted diode sockets up to 40 pin.....	£1.00
30	-Assorted sockets/conn's DII, Edge, IDC, Header etc.....	£1.00
30	-Transistors BC478.....	£1.00
25	-Assorted High Brightness Leds.....	£1.00
20	-Miniature SP/CO Slide Switches.....	£1.00
20	-Magnetic ear pips plus lead and plug.....	£1.00
75	-Electrolytics 4.7uF 63V.....	£1.00
1	-Peltier effect Heat Pump.....	£1.95
1	-10 watt Stereo Amplifier. 4 Controls plus data.....	£2.95

Prices include VAT, postage 85p. All items new. Many more lines in stock. Lists free. Shop open Mon/Sat 9.30-5.30

288 Abbeydale Road, Sheffield S7 1FL
Tel (0742) 552886. Fax (0742) 500689

Manufacturers Original Spares

AMSTRAD * SINCLAIR * COMMODORE Computer Spares	
AMSTRAD	{ CPC 464 SERVICE MANUAL.....£8.49
	{ PCW8256/8512 SERVICE MANUAL.....£13.59
SINCLAIR	{ ULA6C001E (48K + 1).....£15.99
SPECTRUM	{ ULA7K010E/40056 (128K + 2).....£16.36
	{ KEYBOARD MEMBRANE (48K).....£4.50
	{ MODULATOR UM1233.....£4.75
COMMODORE	{ 6510 CPU (C64/C).....£9.87
CUSTOM	{ 6526 CIA (C64/C).....£10.86
CHIPS	{ 6581 SID (C64/C).....£14.94
	{ 8701 CLK. GEN. (C64/128).....£7.56
	{ 906114 PLA (C64/C).....£5.73

Many ATARI Spares NOW AVAILABLE. WE CAN ALSO SUPPLY A RANGE OF SPECIFIC SPARES for many makes of TV, VCR, Audio Equipment. Write (S.A.E. Please) or Tel: 0452 26883 for a price and availability on your requirements.

For Catalogue/Lists, please send 45p stamps/cheque etc.
MAIL ORDER ONLY. Please add 95p (UK) P&P to above orders.
MARAPET (EEK), 1 Hornbeam Mews, Gloucester GL2 0UE

NEW VHF MICROTRANSMITTER KIT

Tuneable 80-135MHz, 500 metre range, sensitive electret microphone, high quality PCB.
SPECIAL OFFER complete kit ONLY £5.95
Assembled and ready to use £9.95 post free.

Access/Visa orders telephone 021 411 1821
S.A.E. for details of this and other kits. Cheques/P.O.s payable to:

QUANTEK ELECTRONICS LTD
Kits Dept. (EE), 45a Station Road
Northfield, Birmingham B31 3TE

BARGAIN OFFER

Tektronic C1001 Scope Video Camera
Video out 9 pin D-fitting - BNC STNC Signal out 12V
Price new £3700. For Sale Unused **£2,700**

Merich Holdings.

Guernsey House, 1 Rue Maurepas
St Peter Port, Guernsey CI
Phone 0481 21190

PLEASE MENTION
EVERYDAY ELECTRONICS
WHEN REPLYING TO
ADVERTISEMENTS

G.C.S.E. ELECTRONIC KITS. Ten different, £10.50 (+ 70p p&p) or SAE for details. SirKit Electronics, 70 Oxford Rd, Clacton CO15 3TE.

KITS. Microtransmitter with free mic, £3.99. Telephone transmitter £4.99. Automatic telephone recording switch, £8.99. Plans for protection devices, surveillance, etc. Sae list. P.O. Box 55, Cannock, Staffs. (05438 71902, 24 hrs).

T.M. ELECTRONIC kits transmitters, receivers plus many more. Sae plus 50p (A4) New 1990 Catalogue. Under New Management, 39 Mayeswood Road, Grove Park, London SE12 9RR.

CHEMILUMINESCENT LIGHTSTICKS from USA-fascinating effect. Four mixed, £5 (includes p&p). Literature free. Lilco Ltd, 23 Middlewood Park, Livingston EH54 8AZ.

MOSFET AMPLIFIER RACKS-240 volts-£15.95!! 1 Regent Road, Ilkley. 40 New components plus illustrated catalogue £1.

EPROM SERVICE

Erasing and Copying service. Any eprom erased (inc. Psion Datapaks) for 2p per K. e.g. 2732 eprom or 32k datapak = 64p.

Copying from your own supplied master also 2p per K. Editing service also available, details on request. Please include 50p postage on orders under £10.

CHASE ELECTRONIC SERVICES
7 The Willows, Brereton, Staffs WS15 1EP

TEST EQUIPMENT MAINTENANCE

Spare Parts, Service Manuals and a comprehensive Repair Service now available for all makes of Electronic Test Equipment (Scopes, Generators, PSU's, Counters, DMM's, AVO's etc, etc)

We support equipment manufactured by over 100 different companies.

New and secondhand Test equipment also supplied.

Building a Project? Contact us with all your component requirements.

Trade enquiries welcome.

Hesing Technology

41 Bushmead Road, Eaton Socon,
St. Neots, Cambs PE19 3BT

Tel: (0480) 214488/216870

FM Transmitter Kits also a Telephone Bug Detector Kit

Ready built FM transmitter £6.50 including P&P

These are commercial kits.

We also stock a selection of Scanning receivers so Telephone for latest stock or ask for a free catalogue

HOTLINE ELECTRONICS

97 LEIGH RD, ATHERTON, GT MANCHESTER

Tel: (0942) 891140

Mail Order Only

TECHNICAL INFO SERVICES (EE)

76 Church St, Larkhall, Lanarkshire ML9 1HE

Phone 0698-884585 Mon-Fri, 9-5.

any other time 0698-883334, FOR FAST QUOTES

WORLD'S LARGEST COLLECTION SERVICE MANUALS - Most obtainable elsewhere. Prices range from only £4.50 - large s.a.e. any quotation, no obligation to buy.

WORLD'S SOLE Suppliers of TV & Video Repair manuals, etc. from TV TECHNIC, also such publishers as Heinemann, Newnes, TV Technic, Thorn etc. Every published service sheet in stock, supplied full size, not bits & pieces. CTV's or any combination £3.50 plus Lsae, any other single item £2.50 plus Lsae. Complete Circuit Sets for most Videorecorders only £7 set (no serv sheets made)

LSAE for QUOTATIONS plus GIANT CATALOGUE - NEWSLETTERS

BARGAINS - FREE S/Ht as available.

Comprehensive TV Repair Manual £9.50. Complete Radio Service and Repair Course £9.50. Complete Repair & Service Manuals - Mono TV £12.50. CTV £17.00. Video £19.50. Complete Repair Data with circuit - Mono TV £9.50. CTV £12.50. Video £11.50.

£3.00 plus LSAE BRINGS THE ONLY COMPREHENSIVE SERVICE SHEETS & MANUALS, CATALOGUES plus FREE CHASSIS GUIDE and £4.00 OF VOUCHERS

LOUDSPEAKERS

Large selection of specialist and general purpose chassis speakers from subminiature through high-quality bass, midrange and high frequency units to large discos, P.A. and guitar types. Also cabinets, things grilles, etc.

MONACOR SP-90 70 Watt 8" full range \$15.99 + \$2 P&P. ALTAI 20 Watt 4" bass \$4.10 + \$2 P&P. 15 Watt 6 1/2" bass/mid cloth edge 1" coil \$7 + \$2 P&P. SOUNDLAB 60 Watt 6 1/2" full range \$14 + \$2 P&P. MONACOR SP-250 200 Watt 10" bass unit \$34.50 + \$2.50 P&P. MPI-1000 75 Watt piezo tweeter 40 kHz \$5.99 + \$4 P&P. DM-20 300 Watt 2 woy crossover 2,000Hz \$14.37 + \$1 P&P. DM-5 100 Watt 3 woy crossover 1,500/6,500Hz \$12 + \$4 P&P. HILLS 100 Watt 2 woy crossover 3,000Hz \$4.83 + \$4 P&P. MONACOR DT-90 60 Watt fluid filled tweeter \$7.80 + \$4 P&P. SP-250GI 70 watt 10" guitar speaker \$17.99 + \$2.50 P&P.

LARGE SAE FOR LISTS-FAST BY-RETURN SERVICE

STRACHAN ELECTRONICS (EE)

9 Croall Place, Leith Walk, Edinburgh EH7 4LT

BLACK FOX AUDIO SYSTEMS

18 Rugeley Road, Chase Terrace, Walsall
West Midlands WS7 8QA

MOSFET POWER AMPS SUITABLE FOR DIGITAL

SOUND PFD30 30W into 8 ohms 170/990mV.....£34.00

C/W regulated power supply, heatsinks PFD50 50W

into 8 ohms 353/1.4mV.....£28.00

PFD140 140W into 8 ohms 565/1.980mV.....£36.00

C/W heatsinks, voltage regulators on driver stage, if sound quality not to your satisfaction money refunded. Power supplies available.

5 YEAR GUARANTEE



NATIONAL
COLLEGE OF
TECHNOLOGY

PACKAGED SHORT COURSES

The National College of Technology (NCT Ltd) offers a range of packaged short courses in analogue electronics, digital electronics, fibres & optoelectronics and programmable logic controllers for study at home or at work. The advantages are that you may,

- commence at any time
- work at your own pace
- have a tutor (optional)

and there is no travelling involved. BTEC certificates are available subject to the conditions of the award. These highly popular packed courses contain workbooks, a cassette tape, circuit board and components necessary to provide both theoretical and practical training.

Whether you are a newcomer to electronics or have some experience and simply need updating, there is probably a packaged short course ready for you. Write or telephone for details, quoting Everyday Electronics, to:

**NCT Ltd, Bicester Hall,
5 London Road, Bicester
Oxon OX6 7BU**

or telephone (0296) 613067 Ext. 202.

SHERWOOD ELECTRONIC COMPONENTS 45 Rutland Street, Mansfield, Notts NG18 4AP

SPECIAL PACKS — All at £1.00 each

SP1	12x5mm Red LEDs	SP32	4xCmos 4077
SP2	12x5mm Green LEDs	SP33	4xCmos 4081
SP3	12x5mm Yellow LEDs	SP34	2xCmos 4510
SP4	10x5mm Amber LEDs	SP35	2xCmos 4511
SP5	36x5mm 1 part LED clips	SP36	20x10µF/25V Rad.Elect.Caps.
SP6	12x3mm Red LEDs	SP37	15x100µF/35V Rad.Elect.Caps.
SP7	12x3mm Green LEDs	SP38	20x47µF/25V Rad.Elect.Caps.
SP8	10x3mm Yellow LEDs	SP39	12x470µF/16V Rad.Elect.Caps.
SP9	40x3mm 1 part LED clips	SP40	15xBC237 Transistors
SP10	50x1N4148 signal diodes	SP41	25xmixed Transistors
SP11	25x1N4001 rectifier diodes	SP42	2xLM1458
SP12	25x1N4002 rectifier diodes	SP43	4xLM1458
SP13	25xRad.Elec.Caps. (1-1000µF)	SP44	12x5mm Leds-4 each, Red, Green Yellow
SP18	15xBC182 Transistors	SP45	25x1N4000 series rect. diodes
SP19	15xBC183 Transistors	SP46	15x400mW zeners—assorted values
SP20	15xBC184 Transistors	SP47	5xminiature push button switches
SP21	15xBC212 Transistors	SP101	15 metres of 22SWG 60-40 solder
SP22	15xBC214 Transistors	SP102	15x8 pin DIL sockets
SP23	15xBC549 Transistors	SP103	12x14 pin DIL sockets
SP24	5xCmos 4001	SP104	12x16 pin DIL sockets
SP25	5x555 Timer	SP105	5x74LS00 I.C.s
SP26	5x741 Op-Amp	SP106	5x74LS02 I.C.s
SP27	5xCmos 4002	SP107	20xmixed presets—Hor. +Vertical
SP28	5xCmos 4011	SP108	15xBC382 Transistors
SP29	3xCmos 4013	SP109	15xBC557 Transistors
SP30	5xCmos 4025	SP110	4x74LS13 I.C.s
SP31	4xCmos 4071		

1 pack of your choice FREE when you buy any 10 of the above £1.00 packs.

ADDITIONAL PACKS

SP50	25x5mm Red LEDs	£2.00
SP51	25x5mm Green LEDs	£2.00
SP52	50xRad. Elec. Caps.	£1.95
SP53	30xDIL sockets 8, 14, 16	£2.00
SP54	1xTIL38 + 1xTIL100	£1.80
SP57	100x1N4148 diodes	£1.75
SP65	60x3mm+5mm Leds	£4.80

RESISTOR PACKS

0.25W Carbon Film resistors 10R-10M	£2.75
5 each value — total 365	£2.75
10 each value — total 730	£4.50
1000 popular values	£6.00
Individual resistors	2p ea.
10+ one value	1p ea.
100 one value	75p

CMOS

4000	20p	4070	24p
4001	20p	4071	24p
4002	20p	4072	24p
4006	60p	4075	27p
4011	20p	4077	27p
4013	34p	4081	24p
4017	50p	4093	24p
4023	27p	4510	60p
4025	20p	4511	60p
4027	47p	4514	120p
4040	65p	4515	120p
4047	60p	4516	60p
4049	37p	4518	60p
4060	75p	4528	65p
4066	37p	4538	90p

LINEAR

555	20p
556	75p
741	21p
747	67p
CA3140E	45p
CA3240E	120p
LM339	50p
LM380	120p
LM723	55p
LM1458	50p
TL071	55p
TL072	75p
TL081	35p
TL082	50p

TRANSISTORS

BC182	10p
BC183	10p
BC184	10p
BC212	10p
BC214	10p
BC239	12p
BC337	12p
BC547	12p
BC549	10p
BC557	12p
BC559	12p
2N3702	11p
2N3703	11p
2N3705	11p
2N3706	11p

Cheques or P.O. to:

**SHERWOOD ELECTRONIC
COMPONENTS**

Please add £1 P&P to orders under £20.00

This only a small sample of components stocked, send 75p for new 1990 catalogue, contains vouchers redeemable against orders over £5.00. **NO VAT**

WATCH THIS SPACE ... MONTHLY ...

for just a few examples from our extensive and changing stocks of COMPONENTS, CAPACITORS, CONNECTORS, FUSES, HARDWARE, TEST EQUIPMENT, RELAYS, SWITCHES, SEMICONDUCTORS, MINI CIRCUITS, BAND FILTERS, etc. etc. etc.

Crystal Filters 21.4 megohm 15KT band width.....	£5.00	each
3 Pole Helical Filters 405 meg.....	£2.50	each
Siemens Intelligent displays DL3416 & DL2416T.....	£3.00	each
Siemens Intelligent displays DL461T.....	£2.00	each
Cooling fans		
12 & 24V	60mm sq x 20mm deep.....	£4.00 each
24 & 115V	80mm sq x 20mm & 38mm deep.....	£5.00 each
24 & 115V	92mm sq x 25.4mm deep.....	£6.00 each
12, 24 & 115V	119mm sq x 25.4 & 38mm deep.....	£6.00 each
Cooling Fans by Papst 119mm x 38mm deep 48 volts.....	£6.00	each
RF transistors MRF 137 8613.....	£7.50	each
RF transistors TPM 4040 9-0930.....	£25.00	each
RF transistors SRF 1818-2 8520.....	£7.50	each
RF transistors SRF 1818-2 8520 in matching pairs.....	£10.00	per pair
IRF 9240 rectifiers.....	£4.00	each
UHF Connector plug.....	£0.50	each
2N5038 90V.....	£0.50	each
DRG 1765 Option 104 Analogue device.....	£3.50	each
Spectrol multialid counters ref 15 built-in lock.....	£3.25	each
Power Products PM 5932 power supply 115V-240mA in 15V-150mA out.....	£5.00	each
Speakers 8" diameter twin cone 8 ohm.....	£1.75	each
Speakers 57mm diameter Mylar Tootone.....	£1.00	each
Transceiver fist microphone fitted filelead and 12 pin DIN plug.....	£2.25	each
Davall relays 25/2MS/185 ohm PCB mount.....	£0.50	each
Takamisawa relays 24V a.c. coil 27 x 21 x 35mm.....	£0.50	each
Aromat DX2 12V solid state relays.....	£3.50	each
Schaffner mains filters FN346-OT to BS613 110/250V 50/60Hz.....	£2.50	each
Memory DAC 9356-12.....	£1.25	each
MCM 6184C45 Static RAM.....	£1.35	each
CY7C 2452-35PC RAM.....	£2.50	each
CD 4044 BCN CMOS.....	£0.30	each
TMS 44C56 D RAM.....	£2.50	each
AD 8616 Analogue device.....	£3.00	each
AD574KD.....	£2.50	each
AD 625CA.....	£2.50	each

ALL PRICES INCLUDE VAT.

Add £2 postage/packing. Allow 14 days for delivery Payment. Cash/cheque/P.O. with order

A MONTHLY comprehensive list is available showing varying and changing stocks. More comprehensive stock lists will be sent with each order on despatch. Surplus stocks purchased for cash

K.B. COMPONENTS

21 Playle Chase, Gt. Totham, Maldon, Essex CM98UT

Tel: 0621 893204

Page Make-up for £185 plus VAT

IF YOU are looking for a superb, page make-up system complete with over 200 typefaces, that really works and won't cost you an arm and a leg, Typefit is the system for you.

Why? Because for only £185 you get:

- ☐ Access to over £60k hard/software, and over 200 genuine Monotype and ITC fonts from 1 - 1000 pt.
- ☐ Disc processing through our typesetting bureau from £2.50 for an A4 page.
- ☐ Page make-up, on screen. ☐ Clear, accurate WYSIWYG.
- ☐ A system that's easy to learn and simple to use.
- ☐ Full on-screen help, and telephone back-up.
- ☐ Software that runs on IBM PCs and compatibles.

Send us your discs or modem your files and your typesetting will be returned the same day.

**EVERYDAY
ELECTRONICS
is produced
entirely on
Typefit**

Typefit

Interested? Please 'phone
Terry or Paul for further
information or a
demonstration
disc. Please
state disc
size and
density.

THE TYPESETTING BUREAU LTD

6 Church Street, Wimborne, Dorset BH21 1JH. Tel: (0202) 882299.
Fax: 841692. Modem: 882270. DX: 45314 Wimborne. Datalinx: TYPBUR

B.C.E ELECTRONICS



4000 CMOS

4000	22p	4023	22p	4071	23p	4526	64p
4001	23p	4027	28p	4077	23p	4534	354p
4011	23p	4035	80p	4081	23p	4541	53p
4013	28p	4047	41p	40106	37p	4554	354p
4017	44p	4050	32p	4502	67p	4561	221p
4021	48p	4069	23p	4511	53p	4585	53p

LINEAR

CA3046	71p	LM387	192p	NE5534	80p	TL082	62p
CA 3240E	159p	LM393	39p	SL560C	268p	TL084	78p
ICM7555	71p	LM710	80p	SP8629	265p	UA709C	62p
ICM7556	124p	LM723	44p	TBA120S	95p	UA741	28p
LF351	48p	LM3914	336p	TBA810	103p	UA747C	78p
LF356	103p	LM3915	336p	TDA2030H	177p	UA748C	45p
LM311	39p	MC3302	133p	TDA7000	225p	ULN2003	71p
LM317T	85p	MC3340	203p	TL071	53p	ULN2004	71p
LM339	39p	NE555	28p	TL072	62p	ULN2803	118p
LM380	142p	NE556	53p	TL074	78p	XR2206CP	540p
LM381N	300p	NE565	159p	TL081	48p	ZN414	142p
						ZN1034E	295p

TRANSISTORS

AC127/128	58p	BFY50	35p	TIP42	150p
AD161/162	90p	BFY51	35p	TIP141	106p
BC107/8/9	19p	BFY52	35p	TIP142	150p
BC182/182L	13p	BU208/208A	177p	TIP2955	95p
BC184	13p	BU508	168p	TIP3055	95p
BC184L	13p	MJ2955	115p	ZTX300	21p
BC212/212L	13p	MJE2955	71p	ZTX500	21p
BC548	11p	MJE3055	71p	2N2222A	30p
BF194	32p	TIP29A	46p	2N3053	41p
BF196	32p	TIP29C	48p	2N3055	78p
BF198	25p	TIP41	106p	2N3703	14p

FULL RANGE OF CMOS, TTL & LINEAR I.C.S. LARGE RANGE OF TRANSISTORS, RESISTORS, CAPACITORS, BOXES, PLUGS, SOCKETS, SWITCHES, P.C.B. MATERIALS, SERVICE AIDS, TOOLS AND LOTS MORE FOR THE ELECTRONICS ENTHUSIAST.

Send 20p stamp for lists. All prices include VAT. Please add 60p p&p Mon., Tues., Wed., Fri., Sat. 10.00-6.00. CLOSED THURSDAYS



(0543) 277572



Unit 3, Chasewood Park Business Centre
Hednesford Road, Heath Hayes
Cannock, Staffs WS12 5HL

ADVERTISERS INDEX

ACTICON	651
A&G ELECTRONICS	696
B.C. ELECTRONICS	696
BK ELECTRONICS	Cover (iii)
BULL ELECTRICAL	Cover (ii)
CAMBRIDGE COMP.SCIENCE	648
CES	648
CIRKIT DISTRIBUTION	693
CRICKLEWOOD ELECTRONICS	679
CR SUPPLY COMPANY	696
ELECTRONIZE DESIGN	693
ELV FRANCE	628/629
GEM-TECH	648
GRANDATA	646
GREENWELD ELECTRONICS	626
HART ELECTRONIC KITS	645
HENRY'S AUDIO ELECTRONICS	649
HIGH-Q ELECTRONICS	672
HIGHGRADE COMPONENTS	630
HOBBYKIT	649
ICS	672
JAYTEE ELECTRONIC SERV'S	673
KB COMPONENTS	695
LITESOLD	693
LONDON ELECTRONICS COLLEGE	696
MAGENTA ELECTRONICS	632/633
MAPLIN ELECTRONICS	Cover (iv)
MARCO TRADING	651
NATIONAL COLLEGE OF TECH.	695
NUMBER ONE SYSTEMS	679
OMNI ELECTRONICS	649
QUILLER	658
RADIO & TV COMPONENTS	631
SERVICE TRADING CO	648
SHERWOOD ELEC. COMP.	695
SPECIALIST SEMICONDUCTORS	691
SUMA DESIGNS	673
TANDY	669
THE TYPESETTING BUREAU	695
TK ELECTRONICS	634

BTEC ELECTRONICS TECHNICIAN FULL-TIME TRAINING

2 YEAR
BTEC National Diploma (OND)
ELECTRONIC & COMMUNICATIONS ENGINEERING
(Electronics, Computing, Television, Video, Testing & Fault Diagnosis)

1 YEAR
BTEC National Certificate (ONC)
ELECTRONIC ENGINEERING

1—INFORMATION TECHNOLOGY
(Electronics, Satellite TV, Networks, Telecomms)

2—ELECTRONIC EQUIPMENT SERVICING
(Electronics, Television, Video Cassette Recorders, CCTV, Testing and Fault Diagnosis)

3—SOFTWARE ENGINEERING
(Electronics, Assembler, BASIC, Pascal, CAD/CAM)

4—COMPUTING TECHNOLOGY
(Electronics, Computing Software/Hardware, Microelectronics)

10 MONTHS
BTEC Higher National Certificate (HNC)
COMPUTING TECHNOLOGY & ROBOTICS
(Microprocessor Based Systems, Control, Robotics)

These courses include a high percentage of college based practical work to enhance future employment prospects
No additional fees for overseas students

Shortened courses of from 3 to 6 months can be arranged for applicants with previous electronics knowledge

THOSE ELIGIBLE CAN APPLY FOR E.T. GRANT SUPPORT
AN EQUAL OPPORTUNITIES PROGRAMME

O.N.C. and O.N.D.
Next Course Commences
Monday 17th September 1990
FULL PROSPECTUS FROM

LONDON ELECTRONICS COLLEGE
(Dept. EE) 20 PENYVERN ROAD
EARLS COURT, LONDON SW5 9SU
TEL 071-373 8721

AG & G ELECTRONICS

ELECTRONIC COMPONENTS MAIL ORDER COMPANY.

1990 COMPONENTS CATALOGUE IS AVAILABLE NOW.

FREE entry to win an ultraviolet exposure Unit Value £200.

Electronic Components at the right prices.

- FAST SERVICE
- LOW PRICES
- LARGE DISCOUNTS



Competition ends 31 Dec 1990.

0.5" ORANGE DUAL LED DISPLAY

Value £2.00 absolutely free !!!

Simply complete and return the order form below and we will send your free gift.

PLEASE SEND A COPY OF THE A & G ELECTRONICS CATALOGUE AT £1.00 (REFUNDABLE WITH MY FIRST ORDER) AND MY FREE GIFT TO:

NAME
ADDRESS

I HAVE ENCLOSED £ Tick box to enter the competition. ☐

A & G ELECTRONICS LTD.
Free Post, 100 Park Avenue,
London E 6 2BR. (No Stamp Required)
TEL: 081-552 2386 Fax: 081-519 3419.

Carbon Film resistors 1/4W 5% E24 series 0.51R to 10MΩ	1p
100 off per value—75p, even hundreds per value totalling 1000	£6.00p
Metal Film resistors 1/4W 10R to 1MΩ 5% E12 series—2p, 1% E24 series	3p
Mixed metal/carbon film resistors 1/2W E24 series 1R0 to 10MΩ	1 1/2p
1 watt mixed metal/Carbon Film 5% E12 series 4R7 to 10 Megohms	5p
Linear Carbon pre-sets 100mW and 1/4W 100R to 4M7 E6 series	7p
Miniature polyester capacitors 250V working for vertical mounting	
.015, .022, .033, .047, .068-4p, 0.1-5p, 0.12, 0.15, 0.22-6p, 0.47-8p, 1.0-12p	
Mylar (polyester) capacitors 100V working E12 series vertical mounting	
1000p to 8200p - 3p, .01 to .068 - 4p, 0.1 - 5p, 0.12, 0.15, 0.22-6p, 0.47/50V-8p	
Submin ceramic plate capacitors 100V wkg vertical mountings. E12 series	
2% 1.8pf to 47pf - 3p, 2% 56 pf to 330pf - 4p, 10% 390p - 4700p	4p
Disc/plate ceramics 50V E12 series 1P0 to 1000P, E6 Series 1500P to 47000P	2p
Polystyrene capacitors 63V working E12 series long axial wires	
10pf to 820pf - 3p, 1000 pf to 10,000pf - 4p, 12,000 pf	5p
741 Op Amp - 20p, 555 Timer	22p
cmos 4001 - 20p, 4011 - 22p, 4017	40p
ALUMINIUM ELECTROLYTICS (Mfids/Volts)	
1/50, 2/250, 4/750, 10/25, 10/50	5p
22/16, 22/25, 22/50, 47/16, 47/25, 47/50	6p
100/16, 100/25 7p; 100/50 12p; 100/100	14p
220/16 8p; 220/25, 220/50 10p; 470/16, 470/25	11p
1000/25 25p; 1000/35, 2200/25 35p; 4700/25	70p
Submin. tantalum bead electrolytics (Mfids/Volts)	
0.1/35, 0.22/35, 0.47/35, 1.0/35, 3.3/16, 4.7/16	14p
2.2/35, 4.7/25, 4.7/35, 6.8/16 15p; 10/16, 22/6	20p
33/10, 47/6, 22/16 30p; 47/10 35p; 47/16 60p; 47/35	80p
VOLTAGE REGULATORS	
1A + or - 5V, 8V, 12V, 15V, 18V & 24V	55p
DIODES (piv/amps)	
75/25mA 1N4148 2p, 800/1A 1N4006 6p, 400/3A 1N5404 14p, 115/15mA OA91	6p
100/1A 1N4002 4p, 1000/1A 1N4007 7p, 60/1.5A S1M1 5p, 100/1A bridge	25p
400/1A 1N 4004 5p, 1250/1A BY127 10p, 30/1.5A OA47	8p
Zener diodes E24 series 3V3 to 33V 400 mW - 8p, 1 watt	12p
Battery snaps for PP3 - 6p for PP9	12p
L.E.D.'s 3mm, & 5mm. Red, Green, Yellow - 10p. Grommets 3mm - 2p, 5mm	2p
Red flashing L.E.D.'s require 5V supply only	50p
Mains indicator neons with 220k resistor	10p
20mm fuses 100mA to 5A. G blow 5p. A/surge 8p. Holders, chassis mounting	5p
High speed pc drill 0.8, 1.0, 1.3, 1.5, 2.0mm - 30p. Machines 12V dc	£7.00
HELPING HANDS 6 ball joints and 2 croc clips to hold awkward jobs	£3.50p
AA/HP7 Nicad rechargeable cells 80p each. Universal charger unit	£6.50p
Glass reed switches with single pole make contacts - 8p. Magnets	12p
0.1" Stripboard 2 1/2" x 1" 9 rows 25 holes - 20p, 3 3/4" x 2 1/2" 24 rows 37 holes	60p
TRANSISTORS	
BC107/8-12p, BC547/8-9p, BC557/8-9p, BC182, 182L, BC183, 183L, BC184, 184L, BC212, 212L-10p, BC327, 337, 337L-12p, BC727, 737-12p, BD135/6/7/8-25p, BCY70-15p, BFY50/51/52-20p, BFX88-15p, 2N3055-50p, TIP31, 32-30p, TIP41, 42-40p, BU208A-E1.20, BF195, 197-12p	

THE CR SUPPLY CO
127 Chesterfield Rd., Sheffield S8 0RN
Tel: 0742 557771 Return posting


OMP POWER AMPLIFIER MODULES-TURNABLES-DIMMERS-LOUDSPEAKERS-19 INCH STEREO RACK AMPLIFIERS

OMP POWER AMPLIFIER MODULES

Supplied ready built and tested.

OMP POWER AMPLIFIER MODULES Now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models available to suit the needs of the professional and hobby market, i.e., Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE all models include Toroidal power supply, Integral heat sink, Glass fibre P.C.B., and Drive circuits to power compatible Vu meter. Open and short circuit proof.

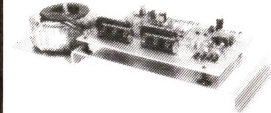THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



OMP100 Mk 11 Bi-Polar Output power 110 watts R.M.S. into 4 ohms, Frequency Response 15Hz - 30KHz - 3dB, T.H.D. 0.01%, S.N.R. -118dB, Sens. for Max. output 500mV at 10K, Size 355 x 115x65mm. **PRICE £33.99 + £3.00 P&P.**

NEW SERIES II MOS-FET MODULES

OMP/MF 100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor, >300, Slew Rate 45V/uS, T.H.D. Typical 0.002%, Input Sensitivity 500mV, S.N.R. -125dB, Size 300 x 123 x 60mm. **PRICE £39.99 + £3.00 P&P.**

OMP/MF200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D. Typical 0.001%, Input Sensitivity 500mV, S.N.R. -130dB, Size 300 x 155 x 100mm. **PRICE £62.99 + £3.50 P&P.**

OMP/MF300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D. Typical 0.0008%, Input Sensitivity 500mV, S.N.R. -130dB, Size 330 x 175 x 100mm. **PRICE £79.99 + £4.50 P&P.**

NOTE:— MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS, STANDARD — INPUT SENS. 500mV BAND WIDTH 100KHz, PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) — INPUT SENS. 775mV, BAND WIDTH 50KHz, ORDER STANDARD OR PEC



Vu METER Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 L.E.D. diodes (7 green, 4 red) plus an additional on/off indicator. Sophisticated logic control circuits for very fast rise and decay times. Tough moulded plastic case, with tinted acrylic front. Size 84 x 27 x 45mm. **PRICE £8.50 + 50p P&P.**

LOUDSPEAKERS



LARGE SELECTION OF SPECIALIST LOUDSPEAKERS AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER GRILLES, CROSS-OVERS AND HIGH POWER, HIGH FREQUENCY BULLETS AND HORNS, LARGE S.A.E. (30p STAMPED) FOR COMPLETE LIST.

McKENZIE:— INSTRUMENTS, P.A., DISCO, ETC.

ALL McKENZIE UNITS 8 OHMS IMPEDANCE

8" 100 WATT C8100GPM GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID, DISCO, RES. FREQ. 80Hz, FREQ. RESP. TO 14KHz, SENS. 99dB. **PRICE £29.30 + £2.00 P&P**
10" 100 WATT C10100GP GUITAR, VOICE, ORGAN, KEYBOARD, DISCO, EXCELLENT MID, RES. FREQ. 70Hz, FREQ. RESP. TO 6KHz, SENS. 100dB. **PRICE £35.58 + £2.50 P&P**
10" 200 WATT C10200GP GUITAR, KEYBOARD, DISCO, EXCELLENT HIGH POWER MID, RES. FREQ. 45Hz, FREQ. RESP. TO 7KHz, SENS. 103dB. **PRICE £48.67 + £2.50 P&P**
12" 100 WATT C12100GP HIGH POWER GEN. PURPOSE, LEAD GUITAR, DISCO, RES. FREQ. 45Hz, FREQ. RESP. TO 7KHz, SENS. 98dB. **PRICE £37.59 + £3.50 P&P**
12" 100 WATT C12100TC TWIN CONE, HIGH POWER WIDE RESPONSE, P.A., VOICE, DISCO, RES. FREQ. 45Hz, FREQ. RESP. TO 14KHz, SENS. 100dB. **PRICE £38.58 + £3.50 P&P**
12" 200 WATT C12200B HIGH POWER BASS, KEYBOARDS, DISCO, P.A. RES. FREQ. 40Hz, FREQ. RESP. TO 7KHz, SENS. 100dB. **PRICE £65.79 + £3.50 P&P**
12" 300 WATT C12300GP HIGH POWER BASS, LEAD GUITAR, KEYBOARDS, DISCO, ETC. RES. FREQ. 45Hz, FREQ. RESP. TO 5KHz, SENS. 100dB. **PRICE £87.51 + £3.50 P&P**
15" 100 WATT C15100BS BASS GUITAR, LOW FREQUENCY, P.A., DISCO, RES. FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS. 98dB. **PRICE £55.05 + £4.00 P&P**
15" 200 WATT C15200BS VERY HIGH POWER BASS, RES. FREQ. 40Hz, FREQ. RESP. TO 4KHz, SENS. 99dB. **PRICE £75.10 + £4.00 P&P**
15" 250 WATT C15250BS VERY HIGH POWER BASS, RES. FREQ. 40Hz, FREQ. RESP. TO 4KHz, SENS. 99dB. **PRICE £82.54 + £4.50 P&P**
15" 400 WATT C15400BS VERY HIGH POWER, LOW FREQUENCY BASS, RES. FREQ. 40Hz, FREQ. RESP. TO 4KHz, SENS. 102dB. **PRICE £96.47 + £4.50 P&P**
18" 400 WATT C18404BS EXTREMELY HIGH POWER, LOW FREQUENCY BASS, RES. FREQ. 27Hz, FREQ. RESP. TO 3KHz, SENS. 99dB. **PRICE £172.06 + £5.00 P&P**

EARBENDERS:— HI-FI, STUDIO, IN-CAR, ETC.

ALL EARBENDER UNITS 8 OHMS (Except EB8-50 & EB10-50 which are dual impedance tapped (at 4 & 8 ohm))


BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED FOAM SURROUND
8" 50 WATT EB8-50 DUAL IMPEDANCE, TAPPED 4 & 8 OHM BASS, HI-FI, IN-CAR, RES. FREQ. 40Hz, FREQ. RESP. TO 7KHz, SENS. 97dB. **PRICE £8.90 + £2.00 P&P**
10" 50 WATT EB10-50 DUAL IMPEDANCE, TAPPED 4 & 8 OHM BASS, HI-FI, IN-CAR, RES. FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS. 99dB. **PRICE £12.00 + £2.50 P&P**
10" 100 WATT EB10-100 BASS, HI-FI, STUDIO, RES. FREQ. 35Hz, FREQ. RESP. TO 3KHz, SENS. 96dB. **PRICE £27.76 + £3.50 P&P**
12" 60 WATT EB12-60 BASS, HI-FI, STUDIO, RES. FREQ. 28Hz, FREQ. RESP. TO 3KHz, SENS. 92dB. **PRICE £21.00 + £3.00 P&P**
12" 100 WATT EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO, RES. FREQ. 26Hz, FREQ. RESP. TO 3KHz, SENS. 93dB. **PRICE £38.75 + £3.50 P&P**
FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND
5 1/2" 60 WATT EB5-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 63Hz, FREQ. RESP. TO 20KHz, SENS. 92dB. **PRICE £9.99 + £1.50 P&P**
6 1/2" 60 WATT EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 38Hz, FREQ. RESP. TO 20KHz, SENS. 94dB. **PRICE £10.99 + £1.50 P&P**
8" 60 WATT EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 40Hz, FREQ. RESP. TO 18KHz, SENS. 89dB. **PRICE £12.99 + £1.50 P&P**
10" 60 WATT EB10-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 35Hz, FREQ. RESP. TO 12KHz, SENS. 86dB. **PRICE £16.49 + £2.00 P&P**

TRANSMITTER HOBBY KITS

PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT AND INSTRUCTIONS

3W FM TRANSMITTER 80-108MHz, VARICAP CONTROLLED PROFESSIONAL PERFORMANCE, RANGE UP TO 3 MILES, SIZE 38 x 123mm, SUPPLY 12V @ 0.5AMP. **PRICE £14.49 + £1.00 P&P**

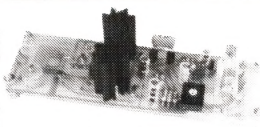FM MICRO TRANSMITTER (BUG) 100-108MHz VARICAP TUNED COMPLETE WITH VERY SENS FET MIC, RANGE 100-300m, SIZE 56 x 46mm, SUPPLY 9V BATT. **PRICE £8.62 + £1.00 P&P**



3 watt FM Transmitter

* PRICES INCLUDE V.A.T. * PROMPT DELIVERIES * FRIENDLY SERVICE * LARGE S.A.E., 30p STAMPED FOR CURRENT LIST.

OMP VARISPEED TURNABLE CHASSIS.



★ MANUAL ARM ★ STEEL CHASSIS ★ ELECTRONIC SPEED CONTROL 33 & 45 ★ VARI PITCH CONTROL ★ HIGH TORQUE SERVO DRIVEN DC MOTOR ★ TRANSIT SCREWS ★ 12" DIE CAST PLATTER ★ NEON STROBE ★ CALIBRATED BAL WEIGHT ★ REMOVABLE HEAD SHELL ★ 1/2" CARTRIDGE FIXINGS ★ CUE LEVER ★ POWER 220-240V 50-60Hz ★ 390x305mm ★ SUPPLIED WITH MOUNTING CUT-OUT TEMPLATE

PRICE £59.99 + £3.50 P&P.


OPTIONAL MAGNETIC CARTRIDGES

STANTON AL500
PRICE £16.99 + 50p P&P

GOLDRING G850
PRICE £6.99 + 50p P&P

OMP MOS-FET POWER AMPLIFIERS, HIGH POWER, TWO CHANNEL 19 INCH RACK

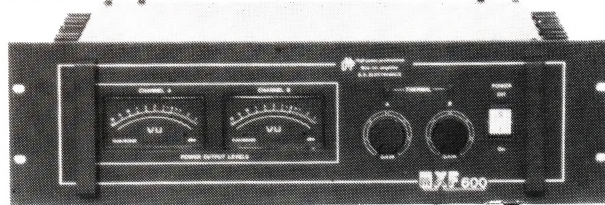THOUSANDS PURCHASED BY PROFESSIONAL USERS



NEW MXF SERIES OF POWER AMPLIFIERS

THREE MODELS:— **MXF200** (100w + 100w)

MXF400 (200w + 200w) **MXF600** (300w + 300w)

All power ratings R.M.S. into 4 ohms.

FEATURES: ★ Independent power supplies with two Toroidal Transformers ★ Twin L.E.D. Vu meters ★ Rotary indexed level controls ★ Illuminated on/off switch ★ XLR connectors ★ Standard 775mV inputs ★ Open and short circuit proof ★ Latest Mos-Fets for stress free power delivery into virtually any load ★ High slew rate ★ Very low distortion ★ Aluminium cases ★ MXF600 Fan Cooled with D.C. Loudspeaker and Thermal Protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.


SIZES:— MXF 200 W19" x H3 1/2" (2U) x D11"
 MXF 400 W19" x H5 1/4" (3U) x D12"
 MXF 600 W19" x H5 1/4" (3U) x D13"

MXF200 £171.35

PRICES: MXF400 £228.80

MXF600 £322.00

SECURICOR DELIVERY £12.00 EACH

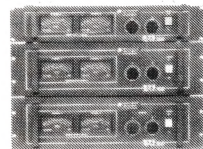

OMP LINNET LOUDSPEAKERS

THE VERY BEST IN QUALITY AND VALUE



MADE ESPECIALLY TO SUIT TODAY'S NEED FOR COMPACTNESS WITH HIGH OUTPUT SOUND LEVELS, FINISHED IN HARDWEARING BLACK VYNIDE WITH PROTECTIVE CORNERS, GRILLE AND CARRYING HANDLE INCORPORATES 12" DRIVER PLUS HIGH FREQ. HORN FOR FULL FREQ. RANGE: 45Hz-20KHz BOTH MODELS 8 OHM, SIZE H18" x W15" x D12"

CHOICE OF TWO MODELS


POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET

OMP 12-100 (100W 100dB) PRICE £159.99 PER PAIR

OMP 12-200 (200W 102dB) PRICE £209.99 PER PAIR

SECURICOR DEL.:— £12.00 PER PAIR

IN CAR STEREO BOOSTER AMPLIFIER

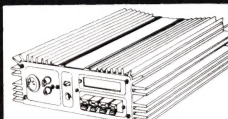

TWO SUPERB HIGH POWER CAR STEREO BOOSTER AMPLIFIERS


150 WATTS (75+75) INTO 4 OHMS
 300 WATTS (150+150) INTO 4 OHMS

FEATURES: ★ HIGH & LOW INPUT IMPEDANCES ★ HIGH & LOW INPUT SENSITIVITIES ★ VARIABLE INPUT GAIN CONTROL ★ SHORT CIRCUIT OUTPUT PROTECTION ★ POWER REQUIREMENT 12V. D.C. **PRICES: 150 WATT £43.00 300 WATT £95.00 + £3.00 P&P EACH**

PIEZO ELECTRIC TWEETERS-MOTOROLA

PIEZO ELECTRIC TWEETERS — MOTOROLA

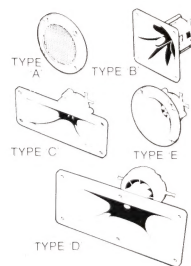Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is **not** required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**



TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-fi speakers. **Price £4.90 each + 50p P&P**

TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. **Price £5.99 each + 50p P&P**

TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-fi systems and quality discos etc. **Price £6.99 each + 50p P&P**


TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-fi systems and quality discos. **Price £9.99 each + 50p P&P**

TYPE 'E' (KSN1038A) 3 3/4" horn tweeter with attractive silver finish trim. Suitable for Hi-fi monitor systems etc. **Price £5.99 each + 50p P&P**

LEVEL CONTROL Combines on a recessed mounting plate, level control and cabinet input jack socket. 85x85mm. **Price £3.99 + 50p P&P.**

STEREO DISCO MIXER

STEREO DISCO MIXER with 2 x 5 band L & R graphic equalisers and twin 10 segment L.E.D. Vu Meters. **Many outstanding features** 5 inputs with individual faders providing a useful combination of the following:—
 3 Turntables (Mag). 3 Mics. 4 Line including CD plus Mic with talk over switch Headphone Monitor. Pan Pot L & R. Master Output controls. Output 775mV. Size 360x280x90mm. Supply 220-240V. **Price £134.99 — £4.00 P&P**

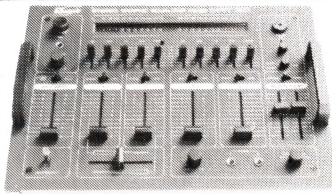

B. K. ELECTRONICS Dept EE

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX. SS2 6TR

TEL: 0702-527572 FAX: 0702-420243



POSTAL CHARGES PER ORDER £1.00 MINIMUM OFFICIAL ORDERS WELCOME FROM SCHOOLS, COLLEGES, GOVT. BODIES, ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER, VISA ACCESS ACCEPTED BY POST, PHONE OR FAX.



1991 BUYER'S GUIDE TO ELECTRONIC COMPONENTS

Maplin

FEATURING:
AN ELECTRONICS
CAST OF
THOUSANDS!

POWER-PACKED
WITH OVER
600 PAGES!!

STARRING
HUNDREDS OF
NEW PRODUCTS
AT SUPER
LOW PRICES!

**SHOWING
NOW!**
at your local
WHSMITH

PERFORMANCES DAILY
At your local branch
of WHSMITH
ONLY £2.45

Order you copy of the New MAPLIN Catalogue on sale NOW
Pick up a copy from any WHSMITH for just £2.45 or post this coupon now to receive your
copy for just £2.45 + 50p p&p. If you live outside the U.K. send £4.95 or
20 International Reply Coupons. I enclose £2.95.

Name _____
Address _____
Post Code _____
Send to Maplin Electronics,
P.O. Box 3, Rayleigh,
Essex SS6 8LR.